



Video Solution on Website:-

<https://physicsaholics.com/home/courseDetails/55>

Video Solution on YouTube:-

<https://youtu.be/2tVzRIWForY>

Written Solution on Website:-

<https://physicsaholics.com/note/notesDetailis/52>

Q 1. An electric wire is connected across a cell of e.m.f. E . The current I is measured by an ammeter of resistance R . According to ohm's law:

(a) $E = I^2 R$

(b) $E = IR$

(c) $E = \frac{I}{R}$

(d) $E = \frac{R}{I}$

Q 2. In Ohm's law experiment, potential drop across a resistance was measured as $v = 5 \text{ Volt}$ and current was measured as $i = 2 \text{ amp}$. If least count of the (voltage measuring device) and ammeter (current measuring device) are $0.1V$ and $0.01A$ respectively then find the maximum permissible error in measuring resistance:


(a) 1.5%

(b) 2.5%

(c) 1%

(d) 5%

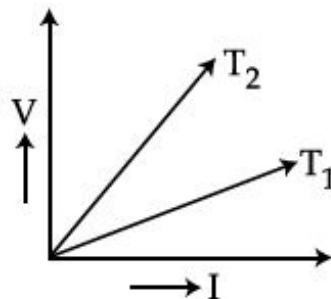Q 3. The voltage-current ($V-I$) graph of a metallic circuit at two different temperature T_1 and T_2 is shown, then:



(a) $T_1 < T_2$

(b) $T_1 > T_2$

(c) $T_1 = T_2$

(d) cant say anything

Q 4. By a cell a current of 0.9 A flows through 2 ohm resistor and 0.3 A through 7 ohm resistor. The internal resistance of the cell is:

(a) 0.5Ω

(b) 1.0Ω

(c) 1.2Ω

(d) 2.0Ω


Q 5. A cell of e.m.f. E is connected with an external resistance R , then potential difference across cell is V . The internal resistance of cell will be:

(a) $\frac{(E-V)}{E} R$

(b) $\frac{(E-V)}{V} R$

(c) $\frac{(V-E)}{V} R$

(d) $\frac{(V-E)}{E} R$

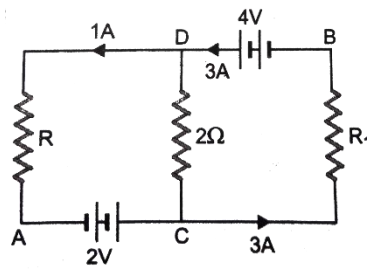


- (a) 2 V (b) 4 V
(c) 8 V (d) 10 V

Q 12. If E is the emf of a cell of internal resistance r and external resistance R , then potential difference (V) across R is given as:


- (a) $V = \frac{E}{R+r}$ (b) $V = E$
(c) $V = \frac{E}{1+\frac{r}{R}}$ (d) $V = \frac{E}{1+\frac{R}{r}}$

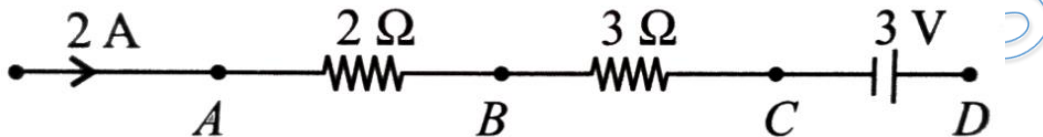Q 13. In the given circuit the potential at point B is zero, the magnitude of potential at points A and D will be:



- (a) $V_A = 4 V, V_D = 9 V$ (b) $V_A = 3 V, V_D = 4 V$
(c) $V_A = 9 V, V_D = 3 V$ (d) $V_A = 4 V, V_D = 3 V$

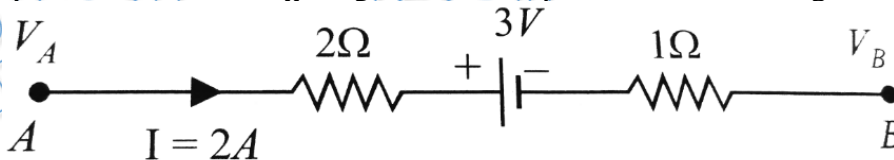Q 14. The potential difference $V_A - V_B$ between the point A and B in the given figure is:



- (a) 6 V (b) 9 V
(c) -3 V (d) 3 V



PRATEEK JAIN
PHYSICSAHOLICS

Answer Key

Q.1 b	Q.2 b	Q.3 a	Q.4 a
Q.5 b	Q.6 d	Q.7 d	Q.8 a
Q.9 c	Q.10 b	Q.11 a	Q.12 c
Q.13 d	Q.14 b		