

DPP – 5 (Current Electricity)

Video Solution on Website:-

<https://physicsaholics.com/home/courseDetails/55>


Video Solution on YouTube:-

<https://youtu.be/Mj1GqNdb4CQ>

Written Solution on Website:-


<https://physicsaholics.com/note/notesDetalis/52>

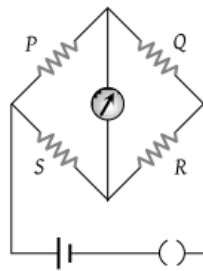- Q 1. In a Wheatstone bridge circuit $P = 2\ \Omega$, $Q = 3\ \Omega$, $R = 6\ \Omega$ and $S = 8\ \Omega$. In order to obtain balance, shunt resistance across S must be:




- (a) $2\ \Omega$ (b) $3\ \Omega$
 (c) $6\ \Omega$ (d) $8\ \Omega$

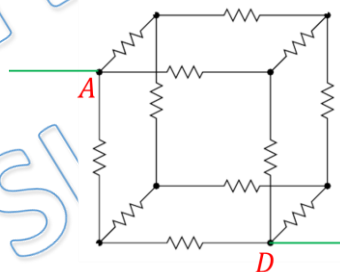- Q 2. If all the resistors are identical having resistance $R\ \Omega$. Find equivalent resistance between A and D?




- (a) $\frac{7R}{12}$ (b) $\frac{4R}{3}$
 (c) $\frac{3R}{4}$ (d) $\frac{12R}{7}$

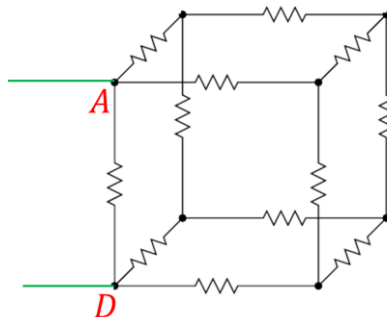- Q 3. If all the resistors are identical having resistance $R\ \Omega$. Find equivalent resistance between A and D?




- (a) $\frac{7R}{12}$ (b) $\frac{4R}{3}$
 (c) $\frac{3R}{4}$ (d) $\frac{12R}{7}$

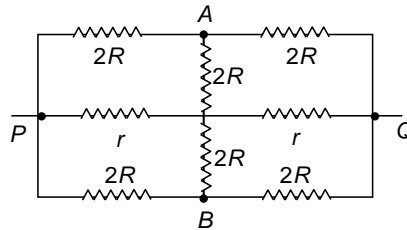Q 4. The effective resistance between point P and Q of the electrical circuit shown in the figure is




- (a) $2Rr / (R + r)$
 (b) $8R(R + r) / (3R + r)$
 (c) $2r + 4R$
 (d) $5R / 2R + 2r$

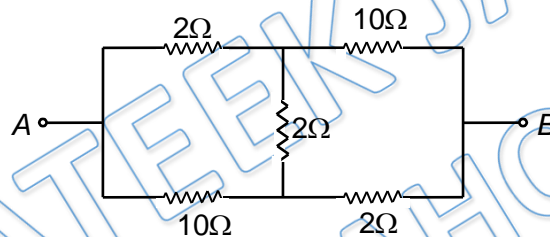Q 5. Find the effective resistance (in ohm) between the points A and B of the following network.




- (a) 4 (b) 8
 (c) 13 (d) 10

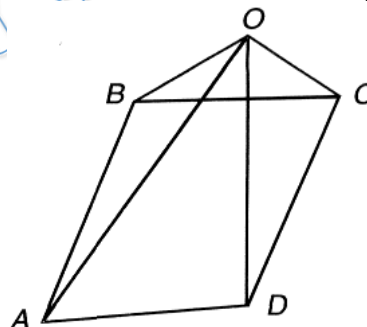Q 6. Eight identical resistance r each are connected as shown. If equivalent resistance between AD is R_1 and that between AC is R_2 then $\frac{R_1}{R_2}$




- (a) 4 : 5
 (b) 2 : 3
 (c) 3 : 5
 (d) 1 : 3

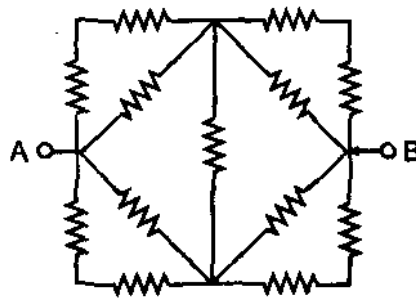Q 7. Thirteen resistors each of resistance H are connected in the circuit as shown in figure. Net resistance between A and B is:




- (a) $2R$ (b) $4R/3$
 (c) $2R/3$ (d) R

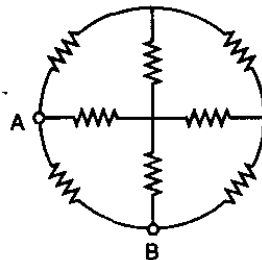Q 8. Eight resistances each of resistance 50Ω are connected in the circuit as shown in figure. The equivalent resistance between A and B is:




- (a) $\frac{80}{3}\Omega$ (b) $\frac{16}{3}\Omega$
 (c) $\frac{150}{7}\Omega$ (d) $\frac{19}{2}\Omega$

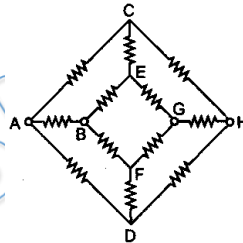Q 9. Twelve resistors each of resistance 1Ω are connected in the circuit shown in figure. Net resistance between points A and H would be




- (a) $\frac{5}{3}\Omega$
 (b) 1Ω
 (c) $\frac{3}{4}\Omega$
 (d) $\frac{7}{6}\Omega$

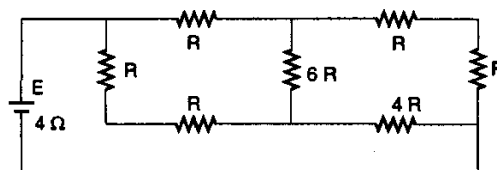Q 10. A battery of internal resistance 4Ω is connected to the network of resistances as shown. In order that the maximum power can be delivered to the network the value of R in Ω should be




- (a) $\frac{4}{9}$
- (b) 2
- (c) $\frac{8}{3}$
- (d) 18

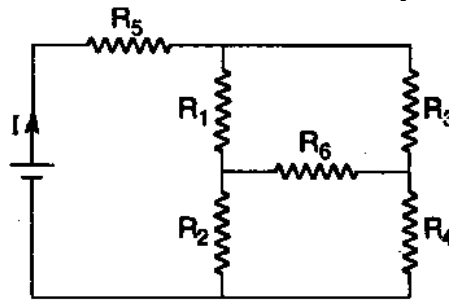Q 11. In the given circuit, it is observed that the current I is independent of the value of the resistance R_6 . Then, the resistance values must satisfy




- (a) $R_1 R_2 R_5 = R_3 R_4 R_6$
- (b) $\frac{1}{R_5} = \frac{1}{R_6} = \frac{1}{R_1 + R_2} + \frac{1}{R_3 + R_4}$
- (c) $R_1 R_4 = R_2 R_3$
- (d) $R_1 R_3 = R_2 R_4$

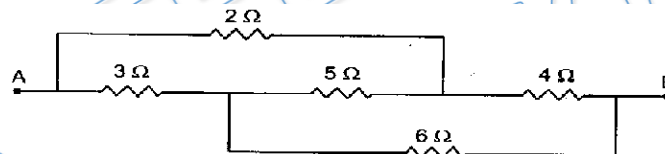Q 12. In the circuit shown, some potential difference is applied between A and B. The equivalent resistance between A and B is R .




- (a) No current flows through the 5-Ω resistor.
- (b) $R = 15\Omega$
- (c) $R = 12.5\Omega$
- (d) $R = \frac{18}{5}\Omega$

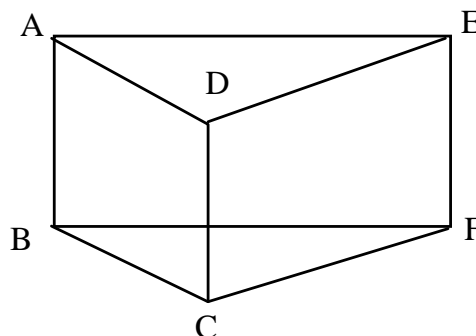Q 13. Find effective resistance between A and B, if all sides of prism have equal resistance R .




- (a) $3R/5$ (b) $2R/5$
 (c) $R/5$ (d) $2R$

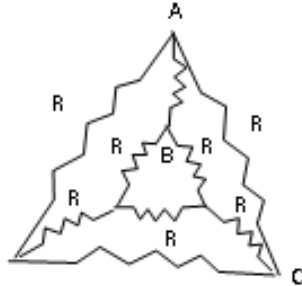Q 14. Find effective resistance between A and B, if all sides of prism have equal resistance R.



- (a) $3R/5$ (b) $2R/5$
 (c) $R/8$ (d) $2R$

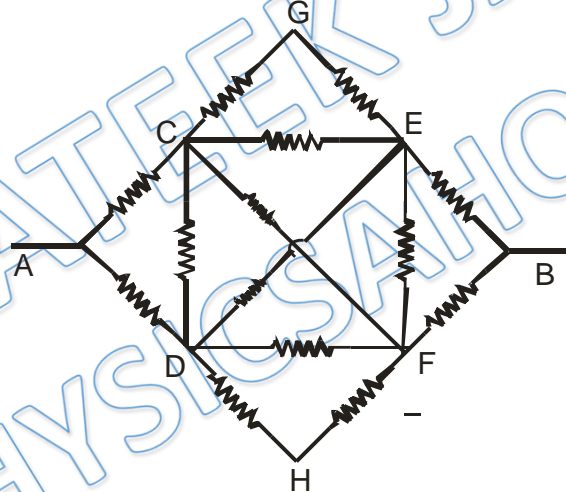Q 15. Fourteen identical resistors each of resistance r are connected as shown. The equivalent resistance between the points A and B is



- (a) r
 (b) $14r$
 (c) $r/14$
 (d) $1.2r$



PRATEEK JAIN
PHYSICSAHOLICS

Answer Key

Q.1 d	Q.2 c	Q.3 a	Q.4 a	Q.5 a
Q.6 a	Q.7 c	Q.8 a	Q.9 c	Q.10 b
Q.11 c	Q.12 a, d	Q.13 a	Q.14 a	Q.15 d