

## DPP – 8 (Current Electricity)

Video Solution on Website:-

<https://physicsaholics.com/home/courseDetails/55>


Video Solution on YouTube:-

<https://youtu.be/Tdv9nluQq2w>

Written Solution on Website:-


<https://physicsaholics.com/note/notesDetailis/52>

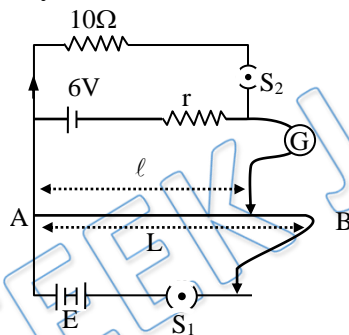- Q 1. In the arrangement shown in figure when the switch  $S_2$  is open, the galvanometer shows no deflection for  $l = L/2$ . When the switch  $S_2$  is closed, the galvanometer shows no deflection for  $l = 5L/12$ . The internal resistance ( $r$ ) of 6 V cell, and the emf  $E$  of the other battery are respectively-



- (A) 3ohm, 8V      (B) 2ohm, 12V  
(C) 2ohm, 24V    (D) 3ohm, 12V

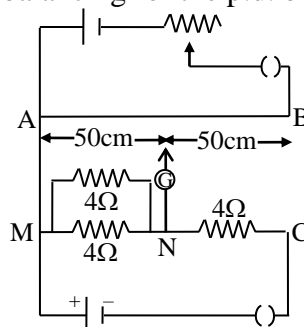
- Q 2. In the following figure, the p.d. between the points M and N is balanced at 50 cms length. The length in cms, balancing for the p.d. between points N and C will be –



- (A) 40      (B) 100  
(C) 75      (D) 25



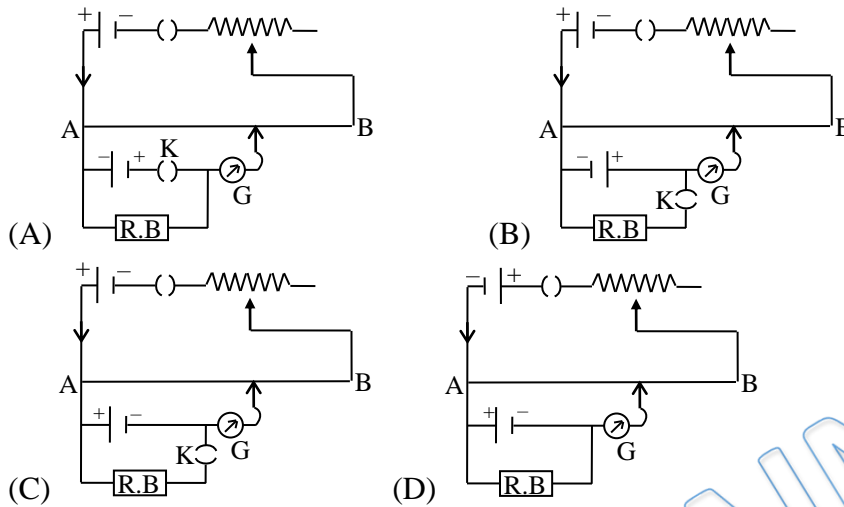Q 3. Correct diagram for the determination of internal resistance of a primary cell by potentiometer




Q 4. With two resistance  $R_1$  and  $R_2$  ( $>R_1$ ) in the two gaps of a metre bridge the balance was found to be  $1/3$  m from the zero end. When a  $6 \Omega$  resistance is connected in series with the smaller of the two resistance, the point is shifted to  $2/3$  m from the same end, then  $R_1$  and  $R_2$  are -

- (A)  $2 \Omega, 4 \Omega$                       (B)  $3 \Omega, 6 \Omega$   
 (C)  $4 \Omega, 8 \Omega$                       (D)  $4 \Omega, 2 \Omega$

Q 5. A wire connected in the left gap of a metre bridge balances a  $10 \text{ohm}$  resistances in the right gap at a point which divides the bridge wire in the ratio  $3:2$ . Then the resistance of the wire will be -

- (A)  $5 \text{ohm}$                                   (B)  $10 \text{ohm}$   
 (C)  $15 \text{ohm}$                                 (D)  $20 \text{ohm}$

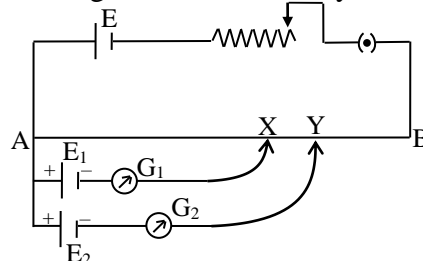Q 6. A potentiometer experiment is setup as shown in fig. If both the galvanometer shows null deflections for the sliding contacts at x and y as shown then -




- (A)  $E_1 = E_2$                               (B)  $E_1 > E_2$   
 (C)  $E_1 < E_2$                               (D) none of the above



Q 7. A cell of emf ( $E$ ) and internal resistance ( $r$ ) is balanced across ( $l$ ) length of potentiometer wire. If another cell of emf  $2E$  and internal resistance ( $2r$ ) is connected in parallel to the first cell, then the balancing length will be

- (A)  $l/3$                       (B)  $2l/3$   
 (C)  $4l/3$                       (D)  $2l$

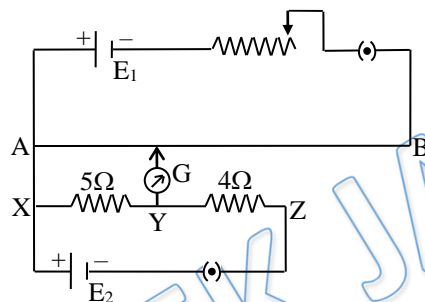Q 8. In a potentiometer arrangement shown in fig. The balancing length for p.d. across  $xy$  points is found to be  $45.5\text{cm}$ . Then the balancing length for p.d. across ( $Y$ ) and ( $Z$ ) would be



- (A)  $45.50\text{ cm}$                       (C)  $36.40\text{ cm}$   
 (B)  $56.87\text{ cm}$                       (D) none of the above


Q 9. A 6 volt battery is connected to the terminals of a three metre long wire of uniform thickness and resistance of  $100\text{ ohm}$ . The difference of potential between two points on the wire separated by a distance of  $50\text{ cm}$  will be -

- (A) 2 volt                      (B) 3 volt  
 (C) 1 volt                      (D) 1.5 volt

Q 10. In an experiment on measurements of emf of a cell by a potentiometer, the balancing length for a cell of emf  $E$  and internal resistance  $r$  is found to be  $l$ . Now if another cell of emf  $E$  and internal resistance  $2r$  is connected in parallel to the first cell and balancing length determined, then the balancing length will be-

- (A)  $l$                                   (B)  $2l$   
 (C)  $2l/3$                               (D) none

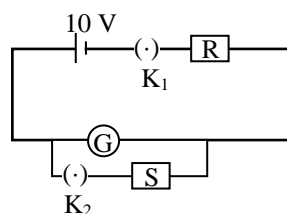Q 11. If galvanometer has  $500\text{ ohm}$  resistance and  $R = 5000\text{ ohm}$ , then what should be the resistance connected to galvanometer in parallel to it so that its deflection reduces to half -




- (A) 544 ohm                      (B) 500 ohm  
(C) 455 ohm                      (D) None

Q 12. A meter bridge with resistance  $R_1$  and  $R_2$  connected in two gaps is balanced at 0.4 m from zero end. If smaller resistance is connected in series with 10 ohm resistance, the balance point is shifted to 0.4 m from other end. The value of smaller resistance is -

- (A) 40 ohm                                      (B) 60 ohm  
(C) 20 ohm                                      (D) 8 ohm

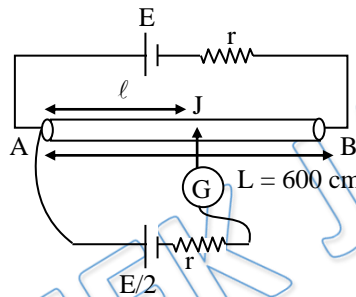Q 13. If resistance of potentiometer wire =  $15r$  then calculate the balance length  $l$  :




- (A) 320 cm                      (B) 200 cm  
(C) 400 cm                      (D) 100 cm

Q 14. A 10 m long wire of resistance 20 ohm is connected in series with a battery of emf 3V (negligible internal resistance) and a resistance of 10 ohm. Find the potential gradient along the wire -

- (A) 3 V/m                                      (B) 0.2 V/m  
(C) 0.1 V/m                                      (D) 0.3 V/m

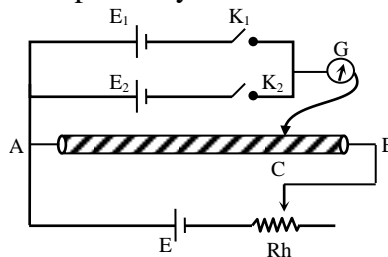Q 15. Figure shows the potentiometer arrangement to compare the emf of cells  $E_1$  and  $E_2$ . Length of the resistance wire AB is 100 cm. If null point obtained for  $E_1$  and  $E_2$  are at distance 20 cm and 40 cm respectively from B then  $E_1/E_2$  is -



- (A) 1 : 2                      (B) 4 : 5  
(C) 3 : 2                      (D) 4 : 3



## Answer Key

Q.1 b	Q.2 b	Q.3 c	Q.4 a	Q.5 c
Q.6 c	Q.7 c	Q.8 c	Q.9 c	Q.10 a
Q.11 c	Q.12 d	Q.13 a	Q.14 b	Q.15 d