



DPP – 4 (Current Electricity)

Video Solution on Website :-

<https://physicsaholics.com/home/courseDetails/98>


Video Solution on YouTube:-

<https://youtu.be/VQ1Y7ZGz3W4>

Written Solution on Website:-


<https://physicsaholics.com/note/notesDetails/53>

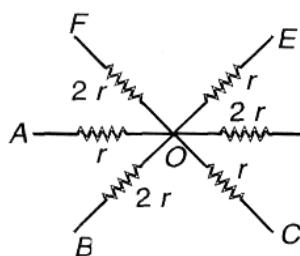- Q 1. The terminal network shown in the figure consists of 6 resistors. The points A, C and E all are at potential 20 V while points B, D and F are at potential -10 volt then potential of junction O will be




- (a) Zero (b) 10 V (c) 15 V (d) -5V

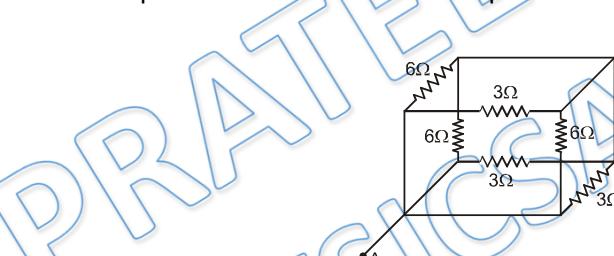- Q 2. Find the equivalent resistance between points A and B :




- (a) 2Ω (b) $\frac{2}{3}\Omega$ (c) $\frac{3}{2}\Omega$ (d) $\frac{1}{2}\Omega$

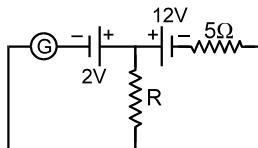- Q 3. In the circuit shown, the galvanometer shows zero current. The value of resistance R is :




- (a) 1Ω (b) 2Ω (c) 4Ω (d) 9Ω

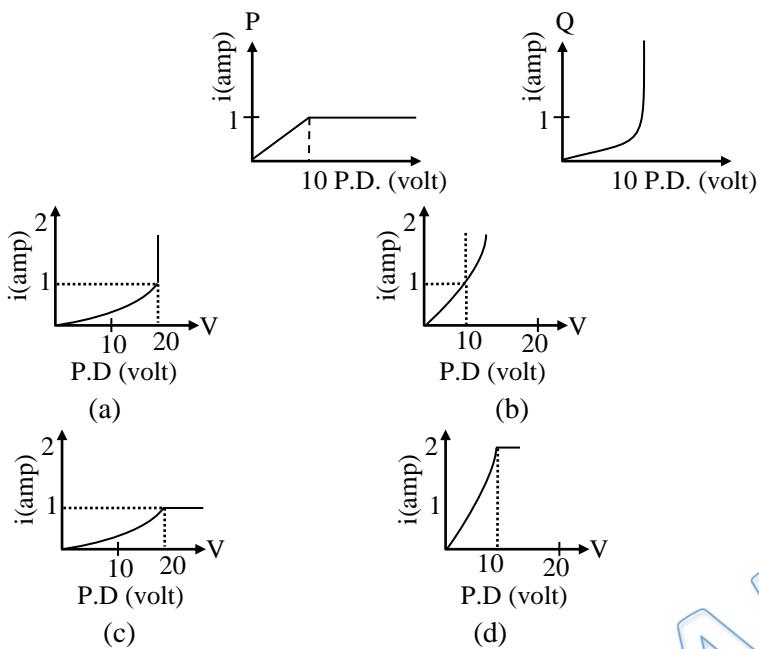- Q 4. Two current elements P and Q have current voltage characteristics as shown below; Which of the graphs given below represents current voltage characteristics when P and Q are in series




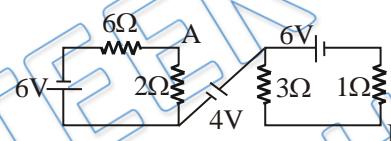- Q 5. In the network shown in the figure below, calculate the potential difference between A and B ? ($V_B - V_A$) =




- (a) 1V
 (b) -1V
 (c) 2V
 (d) -2V

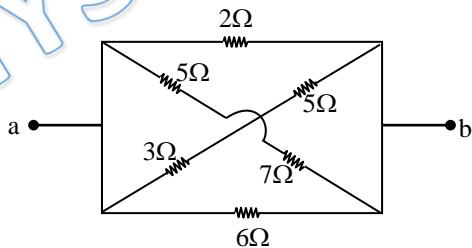- Q 6. Find the equivalent resistance between a & b




- (a) $\frac{7}{8}\Omega$
 (b) $\frac{8}{7}\Omega$
 (c) $\frac{6}{7}\Omega$
 (d) $\frac{7}{6}\Omega$

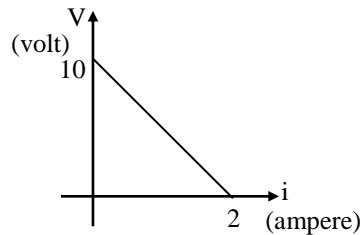- Q 7. A battery of emf E and internal resistance r is connected across a resistance R. Resistance R can be adjusted to any value greater than or equal to zero. A graph is plotted between the current (i) passing through the resistance and potential difference (V) across it. Select the correct alternative(s) –




- (a) internal resistance of battery is 5ohm
- (b) emf of the battery is 20V
- (c) maximum current which can be taken from the battery is 4A
- (d) V-i graph can never be a straight line as shown in figure

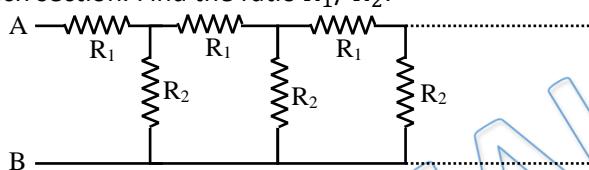Q 8. Consider an infinite ladder network. A voltage is applied between points A & B. If the voltage is halved after each section. Find the ratio R_1 / R_2 .




- (a) 1/2
- (b) 1/3
- (c) 2
- (d) None of these

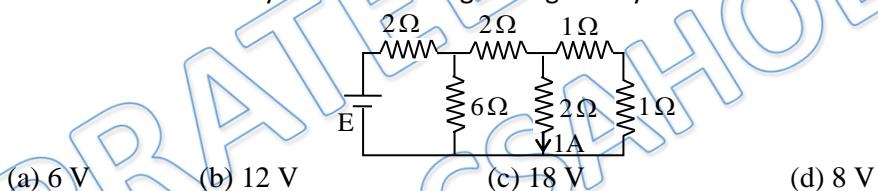Q 9. The emf of the battery shown in the figure is given by –



- (a) 6 V
- (b) 12 V
- (c) 18 V
- (d) 8 V

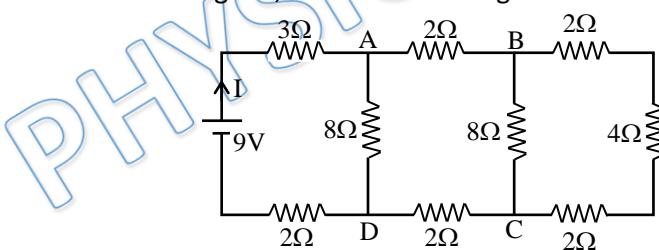Q 10. In the circuit shown in figure , the current through –



- (a) the 3ohm resistor is 0.50 A
- (b) the 3ohm resistor is 0.25 A
- (c) the 4ohm resistor is 0.50 A
- (d) the 4ohm resistor is 0.25 A


Q 11. There are two concentric spheres of radius a and b respectively. If the space between them is filled with medium of resistivity ρ , then the resistance of the inter gap between the two spheres will be

- | | |
|--|--|
| (a) $\frac{\rho}{4\pi(b+a)}$ | (b) $\frac{\rho}{4\pi} \left(\frac{1}{b} + \frac{1}{a} \right)$ |
| (c) $\frac{\rho}{4\pi} \left(\frac{1}{a^2} - \frac{1}{b^2} \right)$ | (d) $\frac{\rho}{4\pi} \left(\frac{1}{a} - \frac{1}{b} \right)$ |




Physicsaholics

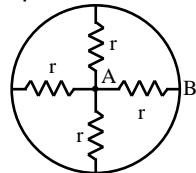Q 12. The equivalent resistance between point A and B is -



- (a) $4r$
- (b) $2r$
- (c) r
- (d) $r/4$

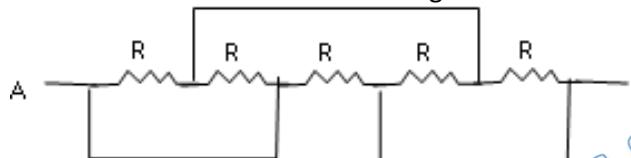Q 13. The equivalent resistance between A and B in the given circuit




- (a) R
- (b) $R/2$
- (c) $R/3$
- (d) $2R/3$

Q 14. A 10 V car battery with negligible internal resistance is connected to a series combination of a 4Ω resistor that obeys Ohm's law and a thermistor that does not obey Ohm's law, but instead has a current – voltage relation $V = \alpha I + \beta I^2$ with $\alpha = 2\Omega$ and $\beta = 4\Omega/A$. The current through the 4Ω resistor is

- (a) 1 A
- (b) 2 A
- (c) $2/5$ A
- (d) 5 A

Q 15 Find current in wire AB ?

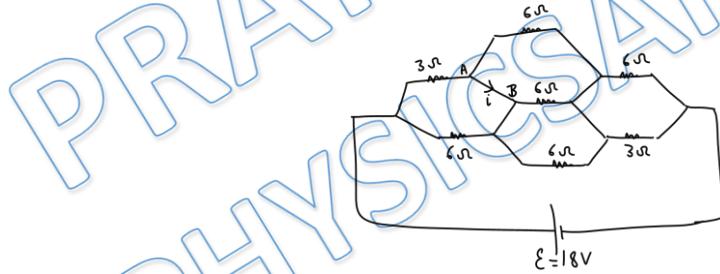

- (a) 1A
- (b) 2A
- (c) 3A
- (d) 4A



PRATEEK JAIN PHYSICSAHOLICS

Answer Key

Q.1 b	Q.2 b	Q.3 a	Q.4 c	Q.5 a
Q.6 b	Q.7 a	Q.8 a	Q.9 b	Q.10 d
Q.11 d	Q.12 d	Q.13 b	Q.14 a	Q.15 a