



Video Solution on Website:-

<https://physicsaholics.com/home/courseDetails/79>

Video Solution on YouTube:-

<https://youtu.be/cBIWLGP3oyI>


Written Solution on Website:-

<https://physicsaholics.com/note/notesDetails/61>

- Q 1. Two inductors of 10mH respectively are connected together in a series combination so that their magnetic fields aid each other giving cumulative coupling. Their mutual inductance is given as 5mH. Calculate the total inductance of the series combination  
(a) 15 mH (b) 20 mH  
(c) 25 mH (d) 30 mH
- Q 2. Three inductors of 10mH, 40mH and 50mH are connected together in a series combination with no mutual inductance between them. Calculate the total inductance of the series combination.  
(a) 100 mH (b) 6.89 mH  
(c) 50 mH (d) 10 mH
- Q 3. Three pure inductors each of 2H are connected as shown in the figure. The equivalent inductance of the circuit between A & B is



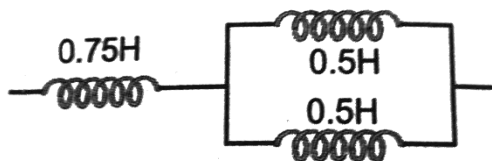- (a)  $\frac{8}{6}$  H (b) 6H  
(c) 2H (d) none of these
- Q 4. The equivalent inductance of two inductors is  $2.4\text{ H}$  when connected in parallel and  $10\text{ H}$  when connected inductors in series. Then find inductance of inductors ?  
(a) 6H, 4H (b) 3H, 6H  
(c) 6H, 3H (d) 12.4H, 7.6H
- Q 5. Three inductances are connected as shown below. Assuming no coupling, the resultant inductance will be-




- (a) 0.25 H (b) 0.5 H



- (c) 0.75 H (d) 1 H

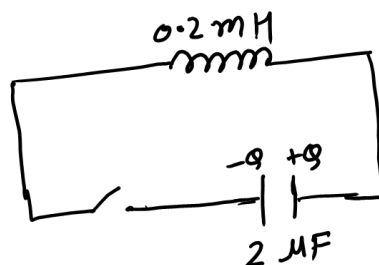- Q 6. A capacitor of capacity  $2 \mu\text{F}$  is charged to a potential difference of 12V. It is then connected across an inductor of inductance  $6 \mu\text{H}$ . What is the current (in A) in the circuit at a time when the potential difference across the capacitor is 6V  
(a) 2 (b) 4  
(c) 6 (d) 8
- Q 7. In an LC circuit the capacitor has maximum charge  $q_0$ . The value of  $\left(\frac{dI}{dt}\right)_{\max}$  is:  
(a)  $\frac{q_0}{LC}$  (b)  $\frac{q_0}{\sqrt{LC}}$   
(c)  $\frac{q_0}{LC} - 1$  (d)  $\frac{q_0}{LC} + 1$
- Q 8. A  $16 \mu\text{F}$  capacitor is charged to a 20 Volt potential. Battery is then disconnected and inductor of inductance 40 mH is connected across the capacitor, So that LC oscillations are step-up. Maximum current in the coil is  
(a) 0.4 A (b) 2 A  
(c) 0.8 A (d) 0.2 A
- Q 9. A charged  $30 \mu\text{F}$  capacitor is connected to a 27 mH inductor. What is the angular frequency of free oscillations of the circuit ?  
(a)  $1.1 \times 10^3 \text{ rad/s}$  (b)  $10^4 \text{ rad/s}$   
(c)  $2.1 \times 10^2 \text{ rad/s}$  (d)  $11 \times 10^3 \text{ rad/s}$
- Q 10. A 1.5 mH inductor in an LC circuit stores a maximum energy of  $30 \mu\text{J}$ . What is the maximum current in the circuit ?  
(a) 2 A (b) 4.4 A  
(c) 1.2 A (d) 0.2 A
- Q 11. Fig. shows LC circuit with initial charge on capacitor  $200 \mu\text{C}$ . If at  $t = 0$ , switch is closed, find the first instant when energy stored in inductor becomes one third that of capacitor:



- (a) 8  $\mu\text{sec}$  (b) 10.5  $\mu\text{sec}$   
(c) 2.5  $\mu\text{sec}$  (d) 1  $\mu\text{sec}$



## Answer Key

<b>Q.1 d</b>	<b>Q.2 a</b>	<b>Q.3 a</b>	<b>Q.4 a</b>	<b>Q.5 d</b>
<b>Q.6 c</b>	<b>Q.7 b</b>	<b>Q.8 a</b>	<b>Q.9 a</b>	<b>Q.10 d</b>
<b>Q.11 b</b>				

PRATEEK JAIN  
PHYSICSAHOLICS