

DPP – 4 (Capacitor)

Video Solution on Website:-

<https://physicsaholics.com/home/courseDetails/65>


Video Solution on YouTube:-

<https://youtu.be/yhpVIY6IjvQ>

Written Solution on Website:-

<https://physicsaholics.com/note/notesDetailis/62>

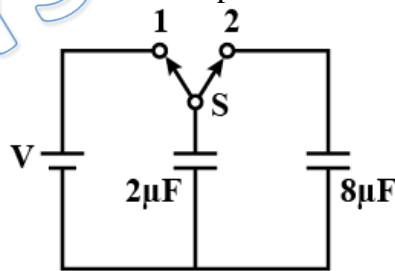
- Q 1. Two capacitors of capacitances $1\mu\text{F}$ and $3\mu\text{F}$ are charged to the same voltages 5V . They are connected in parallel with oppositely charged plates connected together. Then
- Final common voltage will be 5V
 - Final common voltage will be 2V
 - Heat produced in the circuit will be zero
 - Heat produced in the circuit will be $37.5\mu\text{J}$
- Q 2. A capacitor of $5\mu\text{F}$ is charged to a potential of 100V . Now, this charged capacitor is connected to a battery of 100V with the positive terminal of the battery connected to the negative plate of the capacitor. For the given situation, mark the correct statement.
- The charge flowing through the 100V battery is $500\mu\text{C}$
 - The charge flowing through the 100V battery is $2000\mu\text{C}$
 - Work done by the battery is 0.1J
 - Work done on the battery is 0.1J
- Q 3. A 12pF capacitor is connected to a 50V battery. How much of electrostatic energy is stored in the capacitor?
- $15 \times 10^{-9}\text{J}$
 - $5 \times 10^{-10}\text{J}$
 - $1.5 \times 10^{-10}\text{J}$
 - $1 \times 10^{-8}\text{J}$
- Q 4. A $2\mu\text{F}$ capacitor is charged as shown in figure. The percentage of its stored energy dissipated after the switch S is turned to position 2 is



- 0%
 - 20%
 - 75%
 - 80%
- Q 5. A capacitor of capacitance $100\mu\text{F}$ is connected across a battery of emf 6.0V through a resistance of $20\text{k}\Omega$ for 4.0s . The battery is then replaced by a thick wire. What will be the charge on the capacitor 4.0s after the battery is disconnected? (Given $e^{-2} = .15$)
- $76.5\mu\text{C}$
 - $30\mu\text{C}$
 - $85\mu\text{C}$
 - $58\mu\text{C}$




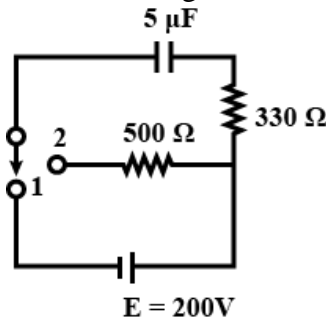- Q 6. The amount of heat generated in 500Ω resistance, when the key is thrown over from contact 1 to 2, as shown in figure is?



- (a) $40 \times 10^{-3} \text{ J}$ (b) $50 \times 10^{-3} \text{ J}$
 (c) $60 \times 10^{-3} \text{ J}$ (d) $30 \times 10^{-3} \text{ J}$

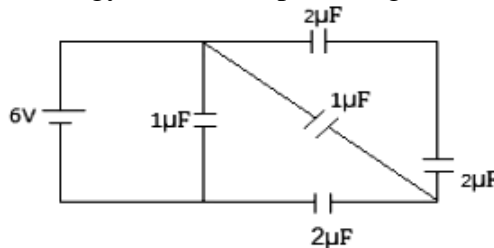- Q 7. Find total energy stored in capacitors given in the circuit



- (a) $36 \times 10^{-6} \text{ J}$ (b) $3.6 \times 10^{-7} \text{ J}$
 (c) $45 \times 10^{-5} \text{ J}$ (d) $25 \times 10^{-6} \text{ J}$


- Q 8. The two parallel plates of a condenser have been connected to a battery of 300 V and the magnitude of charge collected at each plates is $1\mu\text{C}$. The energy supplied by the battery is:

- (a) $6 \times 10^{-4} \text{ J}$ (b) $3 \times 10^{-4} \text{ J}$
 (c) $1.5 \times 10^{-4} \text{ J}$ (d) $4.5 \times 10^{-4} \text{ J}$

- Q 9. A parallel-plate capacitor with the plate area 100cm^2 and the separation between the plates 1.0cm is connected across a battery of emf 24 volts. Find the force of attraction between the plates.


- (a) $2 \times 10^{-6} \text{ N}$ (b) $3.45 \times 10^{-4} \text{ N}$
 (c) $1.32 \times 10^{-5} \text{ N}$ (d) $2.57 \times 10^{-7} \text{ N}$

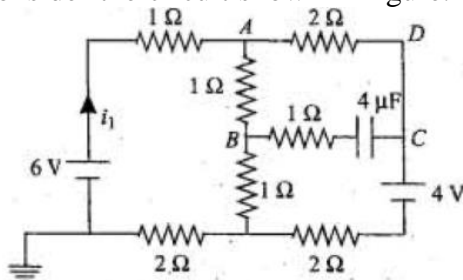- Q 10. Consider the circuit shown in figure. The circuit is in steady state. The value of i_1 is:




- (a) $\frac{7}{9}$ A (b) $\frac{14}{13}$ A
 (c) $\frac{14}{3}$ A (d) $\frac{13}{27}$ A

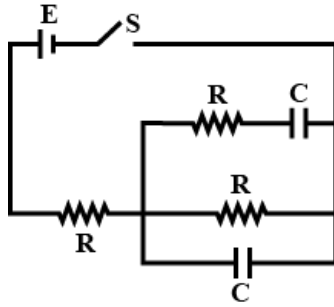Q 11. In the given circuit, if the current through cell is I , immediately after closing the switch and will become I' long after closing the switch, then $\frac{I}{I'}$




- (a) 2 (b) $\frac{2}{3}$
 (c) $\frac{3}{2}$ (d) 3

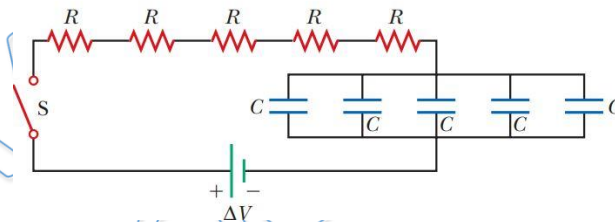Q 12. What is the time constant of the circuit shown in Figure? Each of the five resistors has resistance R , and each of the five capacitors has capacitance C . The internal resistance of the battery is negligible.




- (a) RC (b) $5 RC$
 (c) $10 RC$ (d) $25 RC$

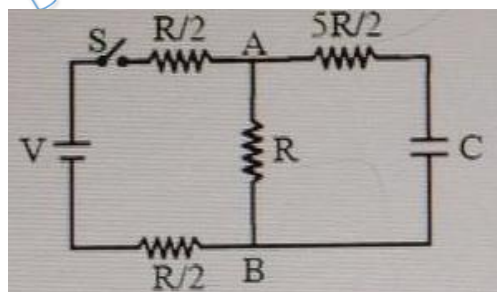Q 13. In the circuit shown in figure, the battery is an ideal one with emf V . The capacitor is initially uncharged. Switch S is closed at time $t = 0$. The final charge Q on the capacitor is:




- (a) $\frac{CV}{2}$ (b) $\frac{CV}{3}$
 (c) CV (d) $\frac{CV}{6}$

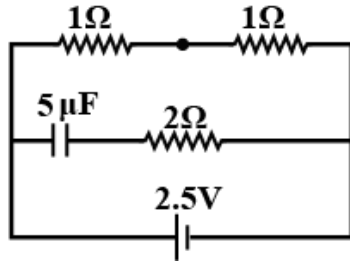- Q 14. A capacitor of capacitance $5\mu\text{F}$ is connected as shown in the figure. The internal resistance of the cell is 0.5Ω . The amount of charge on the capacitor plate is



- (a) $0\mu\text{C}$ (b) $5\mu\text{C}$
(c) $10\mu\text{C}$ (d) $25\mu\text{C}$

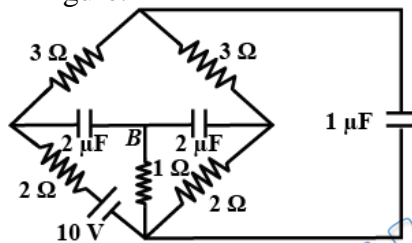
- Q 15. The circuit shown in Figure is in steady state. Find the energy stored in the capacitors shown in Figure.



- (a) $8\mu\text{J}$ (b) $80.5\mu\text{J}$
(c) $35\mu\text{J}$ (d) $17.5\mu\text{J}$

- Q 16. What is the energy stored per unit volume in vacuum, where the intensity of electric field is 10^3 V/m ? ($\epsilon_0 = 8.85 \times 10^{-12}\text{ C}^2/\text{N} - \text{m}^2$)
- (a) $8.85 \times 10^{-6}\text{ J/m}^3$ (b) $4.425 \times 10^{-6}\text{ J/m}^3$
(c) $4.425 \times 10^{-8}\text{ J/m}^3$ (d) $8.85 \times 10^{-5}\text{ J/m}^3$

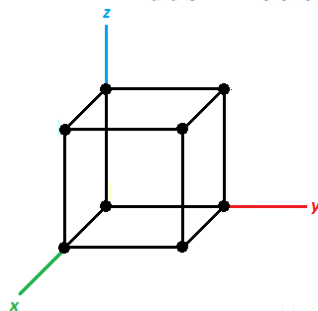- Q 17. Electric field in a region is found to be $\mathbf{E} = 3y\hat{j}$. The total energy stored in electric field inside the cube shown will be



- (a) $9a^5\epsilon_0$ (b) $3a^5\epsilon_0$
(c) $\frac{3}{2}a^5\epsilon_0$ (d) zero

- Q 18. Find out energy stored in the electric field of uniformly charged thin spherical shell of total charge Q and radius R .

- (a) $\frac{kQ^2}{2R}$ (b) $\frac{kQ^2}{3R}$
(c) $\frac{3kQ^2}{2R}$ (d) $\frac{2kQ^2}{R}$



- Q 19. A parallel plate capacitor has an electric field of 10^5 V/m between the plates. If the charge on the capacitor plate is $1\mu\text{C}$, then force on each capacitor plate is-
- (a) 0.1 N (b) 0.05 N
(c) 0.02 N (d) 0.01 N

Answer Key

Q.1 d	Q.2 c	Q.3 a	Q.4 d	Q.5 a
Q.6 c	Q.7 a	Q.8 c	Q.9 d	Q.10 b
Q.11 a	Q.12 d	Q.13 a	Q.14 c	Q.15 b
Q.16 b	Q.17 c	Q.18 a	Q.19 b	