

## DPP – 4 (Capacitor)

Video Solution on Website :-

<https://physicsaholics.com/home/courseDetails/103>


Video Solution on YouTube:-

<https://youtu.be/cq4Z-W7mCC8>

Written Solution on Website:-

<https://physicsaholics.com/note/notesDetailis/63>

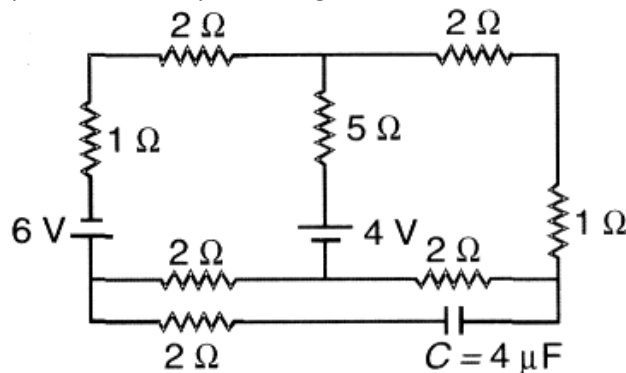
Q 1. Find charge on capacitor in steady state of given circuit



- (a)  $9.6 \mu\text{C}$   
(c)  $4.8 \mu\text{C}$



- (b)  $7.2 \mu\text{C}$   
(d)  $2.4 \mu\text{C}$

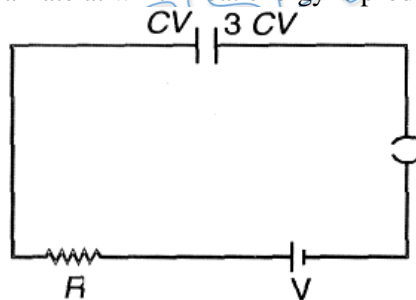Q 2. Plates of a parallel plate capacitor C have charges  $CV$  and  $3CV$  on its plate. If switch is closed at  $t = 0$ . Then initial rate at which heat energy is produced in resistance R is




- (a)  $\frac{V^2}{R}$   
(b)  $4 \frac{V^2}{R}$   
(c)  $9 \frac{V^2}{R}$   
(d)  $16 \frac{V^2}{R}$

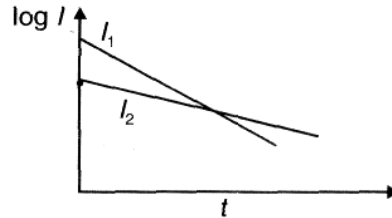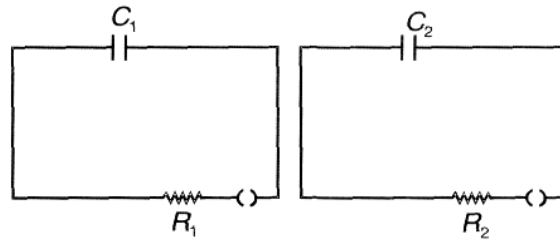Q 3. Two capacitors of capacitance  $C_1$  and  $C_2$  are charged to a potential difference  $V$  and connected in series with resistance  $R_1$  and  $R_2$  at  $t = 0$ . Both keys are closed. Graph of current  $I_1$  &  $I_2$  in two circuits are as shown here. Which of the following must be incorrect?




- (a)  $R_1 > R_2$       (b)  $R_1 < R_2$       (c)  $C_1 > C_2$       (d)  $C_1 < C_2$

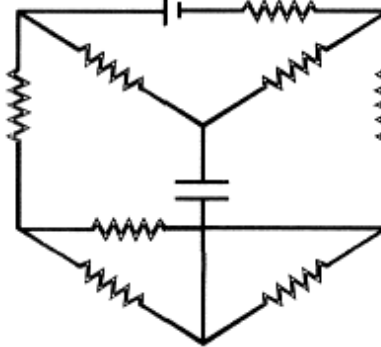Q 4. What is equivalent time constant of following RC circuit?



- (A)  $1.5 RC$   
 (B)  $3RC$   
 (C)  $2RC$   
 (D)  $RC/2$

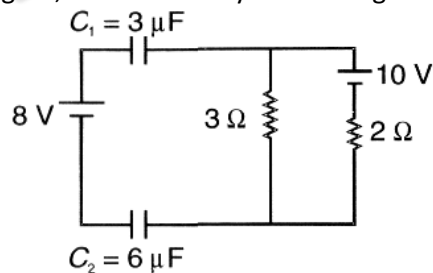
Q 5. In the circuit shown in figure, find the steady state charge on C, capacitor




- (a)  $2\mu C$   
 (b)  $3\mu C$   
 (c)  $4\mu C$   
 (d) Zero



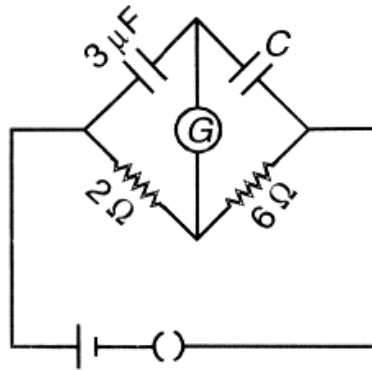
- Q 6. If key K, is closed in circuit shown in figure and galvanometer doesn't give deflection at any time, then value of C is



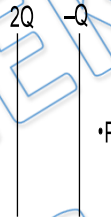
- (a)  $3\mu\text{F}$   
 (b)  $9\mu\text{F}$   
 (c)  $4\mu\text{F}$   
 (d)  $1\mu\text{F}$
- Q 7. In the figure shown the plates of a parallel plate capacitor have unequal charges. Its capacitance is 'C'. P is a point outside the capacitor and close to the plate of charge  $-Q$ . The distance between the plates is 'd'.



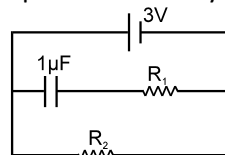- (A) A point charge at point 'P' will experience electric force due to capacitor  
 (B) The potential difference between the plates will be  $\frac{3Q}{2C}$   
 (C) The energy stored in the electric field in the region between the plates is  $\frac{9Q^2}{8C}$   
 (D) The force on one plate due to the other plate is  $\frac{Q^2}{2\pi\epsilon_0 d^2}$
- Q 8. A  $1\mu\text{F}$  capacitor is connected in the circuit shown below. The e.m.f. of the cell is 3 volts and internal resistance is 0.5 ohms. The resistors  $R_1$  and  $R_2$  have values 4 ohms and 1 ohm respectively. The charge on the capacitor in steady state must be :




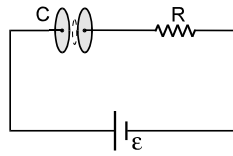- (A)  $2\mu\text{C}$   
 (B)  $1\mu\text{C}$   
 (C)  $1.33\mu\text{C}$   
 (D) zero
- Q 9. In the circuit shown the capacitor of capacitance C is initially uncharged. Now the capacitor is connected in the circuit as shown. The charge passed through an imaginary circular loop parallel to the plates (also circular) and having the area equal to half of the area of the plates, in one time constant is:




- (A)  $C\epsilon \left(1 - \frac{1}{e}\right)$
- (B)  $\frac{C\epsilon}{2} \left(1 - \frac{1}{e}\right)$
- (C)  $\frac{C\epsilon}{4}$
- (D) zero

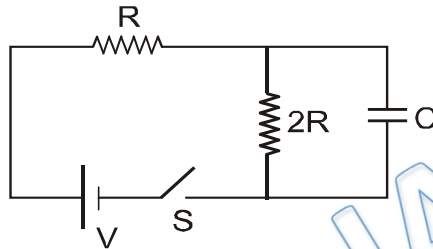Q 10. Consider the circuit shown, capacitor is uncharged initially. Switch is closed at  $t = 0$ , then select correct alternative/s :



- (A) charge on the capacitor as function of time is  $q = \frac{2CV}{3} \left(1 - e^{-\frac{3t}{2RC}}\right)$
- (B) current in the resistance  $2R$  on function of time will be  $i = \frac{V}{3R} \left(1 - e^{-\frac{3t}{2RC}}\right)$
- (C) current in the resistance  $2R$  on function of time will be  $i = \frac{V}{3R} \left(1 - e^{-\frac{3t}{2RC}}\right)$
- (D) charge on the capacitor on function of time will be  $q = \frac{2CV}{3} \left(1 - e^{-\frac{t}{2RC}}\right)$

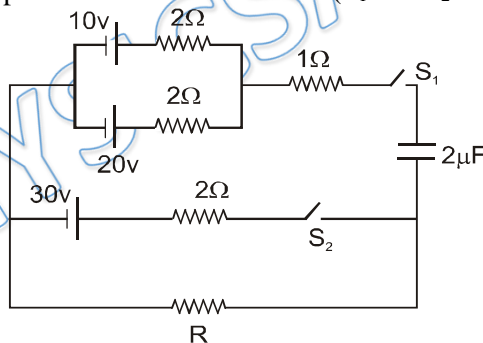
Q 11. Some ideal batteries and an unknown resistance are connected as shown in the circuit. At  $t = 0$ , current in  $R$  is 1 amp towards left. Calculate  $R$ . ( $S_1$  and  $S_2$  are closed at  $t = 0$ )



- (A)  $20.5 \Omega$
- (B)  $21.5 \Omega$
- (C)  $20 \Omega$
- (D) None of these
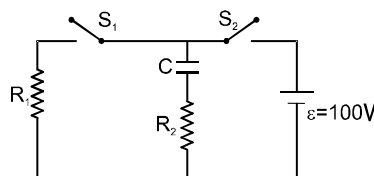
### Comprehension (Q.12 TO Q.14)

In the circuit shown in the figure the capacitor is initially uncharged





- Q 12.  $S_1$  and  $S_2$  are simultaneously closed at  $t = 0$ . Power dissipated in the resistor  $R_1$  is 0.2 W and initial current through  $R_2$  is 10 mA. Choose the correct option :
- (A)  $R_1 = 50\text{k}\Omega$  ,  $R_2 = 10\text{M}\Omega$  (B)  $R_1 = 50\text{k}\Omega$  ,  $R_2 = 10\text{k}\Omega$   
(C)  $R_1 = R_2 = 50\text{k}\Omega$  (D)  $R_1 = 10\text{k}\Omega$  ,  $R_2 = 50\text{k}\Omega$
- Q 13. When the capacitor gets fully charging switch  $S_2$  is opened. It is observed that after 5 sec, the current in  $R_1$  is 0.74 mA. [ $\ln(2.25) = 0.812$ ]. Choose the correct option :
- (A)  $C = 100\text{mF}$  approximately  
(B)  $C = 50\text{mF}$  approximately  
(C) The charge on the capacitor at the instant mentioned in the question is approximately equal to 2 mC  
(D) Both (A) and (C) are correct
- Q 14. At the instant mentioned in the previous question  $S_1$  is opened and  $S_2$  is closed simultaneously. Taking this instant is  $t = 0$ , the charge on the capacitor as a function of time is best represented by
- (A)  $q = (4.4 e^{-t})\text{mC}$  (B)  $q = (10 + 5.6 e^{-t})\text{mC}$   
(C)  $q = (10 - 5.6 e^{-t})\text{mC}$  (D)  $q = (5.6 e^{-t} - 1.2)\text{mC}$

PRATEEK JAIN  
PHYSICSAHOLICS

## Answer Key

Q.1 a	Q.2 b	Q.3 a	Q.4 a	Q.5 c
Q.6 d	Q.7 a, b, c	Q.8 a	Q.9 d	Q.10 a, b
Q.11 b	Q.12 b	Q.13 a	Q.14 c	