

DPP – 5 (Capacitor)

Video Solution on Website :-

<https://physicsaholics.com/home/courseDetails/103>


Video Solution on YouTube:-

<https://youtu.be/J5joY0NdvVM>


Written Solution on Website:-

<https://physicsaholics.com/note/notesDetails/63>

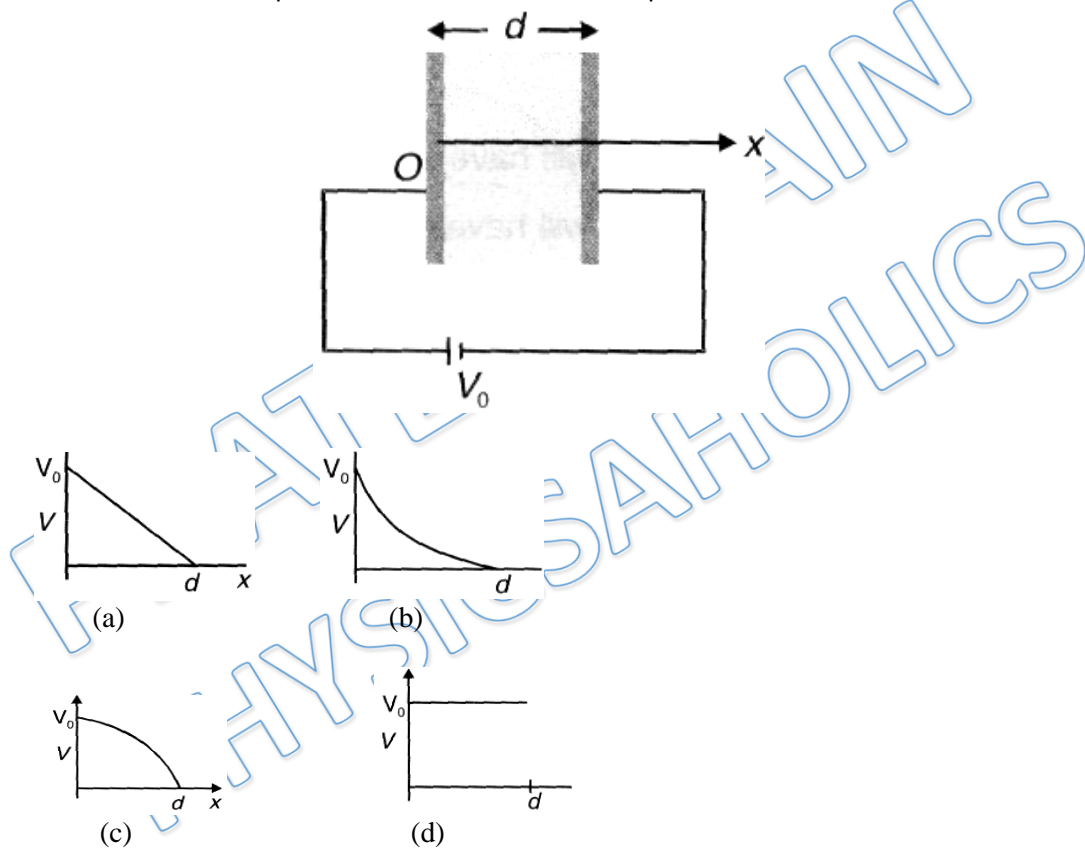- Q 1. The gap between plates of a parallel plate capacitor is filled with dielectric whose dielectric constant varies uniformly from K to $2K$ in a direction perpendicular to the plates. Potential difference between plates is V . Correct variation of potential with x is



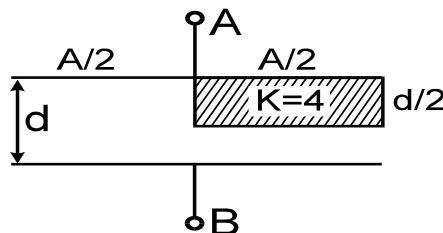- Q 2. Find the equivalent capacitance between terminals 'A' and 'B'. The letters have their usual meaning.



(a) $\frac{6 \epsilon_0 A}{5 d}$

(b) $\frac{13 \epsilon_0 A}{10 d}$



(c) $\frac{10 \epsilon_0 A}{7 d}$

(d) $\frac{5 \epsilon_0 A}{7 d}$


Q 3. Column-I gives certain situations in which capacitance of a capacitor is changed by different means. Column-II gives resulting effect under different conditions. Match the statements in column-I with the corresponding statements in column-II

- | Column-I | Column-II |
|--|--|
| (A) The plates of a plane parallel plate capacitor are slowly pulled apart. | (p) Increases if the capacitor is maintained at constant charge. |
| Then the magnitude of electric field intensity inside the capacitor | |
| (B) The plates of a plane parallel plate capacitor are slowly pulled apart. Then the potential energy stored in the capacitor | (q) Decreases if the capacitor is maintained at constant charge. |
| (C) The capacitance of an air filled plane parallel plate capacitor on insertion of dielectric. | (r) Increases if the capacitor is maintained at constant potential difference. |
| (D) A dielectric slab is inserted inside an air filled plane parallel plate capacitor. The potential energy stored in the capacitor. | (s) Decreases if the capacitor is maintained at constant potential difference. |

Q 4. The capacitance of a parallel plate capacitor is C_0 when the plates has air between them. This region is now filled with a dielectric slab of dielectric constant K and capacitor is connected with battery of EMF E and zero internal resistance. Now slab is taken out, then

- charge $EC_0(K - 1)$ flows through the cell
- energy $E^2 C_0(K - 1)$ is absorbed by the cell
- the energy stored in the capacitor is reduced by $E^2 C_0(K - 1)$
- the external agent has to do $E^2 C_0(K - 1)$ amount of work to take out the slab

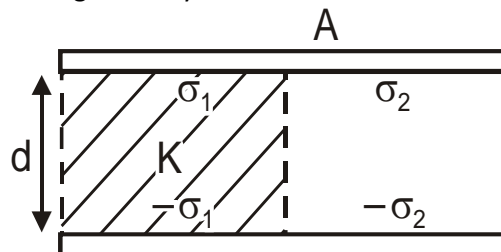Q 5. A parallel plate capacitor of area A and separation d is charged to potential difference V and removed from the charging source. A dielectric slab of constant $K = 2$, thickness d and area $\frac{A}{2}$ is inserted, as shown in the figure. Let σ_1 be free charge density at the conductor-dielectric surface and σ_2 be the charge density at the conductor-vacuum surface.




- The electric field have the same value inside the dielectric as in the free space between the plates.
- The ratio $\frac{\sigma_1}{\sigma_2}$ is equal to $\frac{2}{1}$.
- The new capacitance is $\frac{3\epsilon_0 A}{2d}$

(d) The new potential difference is $\frac{2}{3} V$

- Q 6. An uncharged parallel plate capacitor is connected to a battery. The electric field between the plates is 10 V/m . Now a dielectric of dielectric constant 2 is inserted between the plates filling the entire space. The electric field between the plates now is
- (a) 5 V/m (b) 20 V/m
 (c) 10 V/m (d) none of these



- Q 7. A parallel plate capacitor (without dielectric) is charged and disconnected from a battery. Now a dielectric is inserted between the plates. The electric force on a plate of the capacitor will:
- (a) decrease
 (b) increase
 (c) remain same
 (d) depends on the width of the dielectric

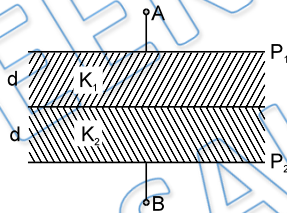- Q 8. In the figure shown P_1 and P_2 are two conducting plates having charges of equal magnitude and opposite sign. Two dielectrics of dielectric constant K_1 and K_2 fill the space between the plates as shown in the figure. The ratio of electrical energy in 1st dielectric to that in the 2nd dielectric is



- (a) $1 : 1$ (b) $K_1 : K_2$
 (c) $K_2 : K_1$ (d) $K_2^2 : K_1^2$

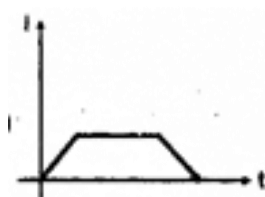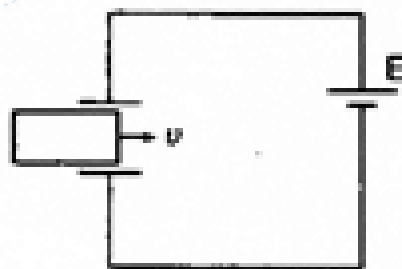
- Q 9. A dielectric slab of area A and thickness d is inserted between the plates of capacitor of area $2A$ and distance between plates d with a constant speed v as shown in figure. The capacitor is connected to a battery of emf E . The current in the circuit varies with time as




(a)



(b)

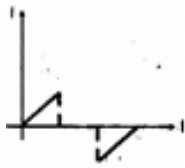


(c)

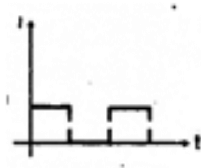


(d)

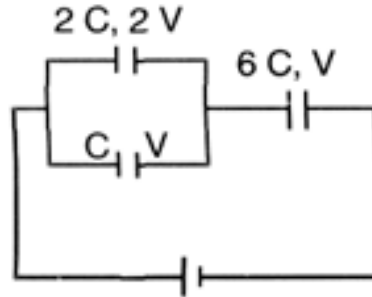- Q 10. Diagram shows three capacitors with capacitance and breakdown voltage mentioned. What should be maximum value of the external emf of source such that no capacitor breakdown?



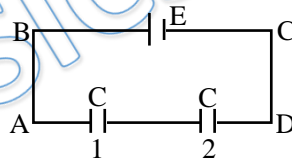- (a) V
 (b) 2 V
 (c) 1.5 V
 (d) 4 V
- Q 11. A dielectric of dielectric constant $K = 2$ is pasted on conductor sphere of radius 1 meter to make its radius 2 meter. Find capacitance of system ?
- (a) $\frac{4}{27}$ nF (b) $\frac{27}{4}$ nF (c) 4 nF (d) None of these
- Q 12. In the adjoining figure, capacitor (1) and (2) have a capacitance 'C' each. When the dielectric of dielectric constant K is inserted between the plates of one of the capacitor, the total charge flowing through battery is



- (a) $\frac{KCE}{K+1}$ from B to C
 (b) $\frac{KCE}{K+1}$ from C to B
 (c) $\frac{(K-1)CE}{2(K+1)}$ from B to C
 (d) $\frac{(K-1)CE}{2(K+1)}$ from C to B



Answer Key

Q.1 b	Q.2 b	Q.3	Q.4 a, b	Q.5 a, b, c, d
Q.6 c	Q.7 c	Q.8 c	Q.9 b	Q.10 c
Q.11 a	Q.12 d			

Q.3 (A) – s, ; (B) – p, s ; (C) – p, r ; (D) – q, r

PRATEEK JAIN
PHYSICSAHOLICS