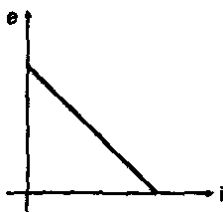


Video Solution on Website :- <https://physicsaholics.com/home/courseDetails/104>


Video Solution on YouTube:- <https://youtu.be/xAhvcTRPmxg>

Written Solution on Website:- <https://physicsaholics.com/note/notesDetails/65>


- Q 1. In an L-R circuit connected to a battery of constant emf E switch s is closed at time $t = 0$. If e denotes the induced emf across inductor and i the current in the circuit at any time t . Then which of the following graphs shows the variation of e with i ?




(a)

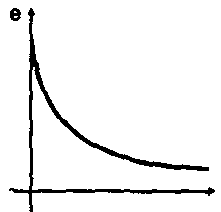

(b)

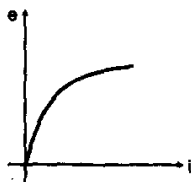


(c)

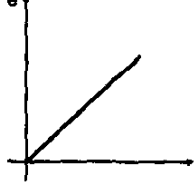


(d)

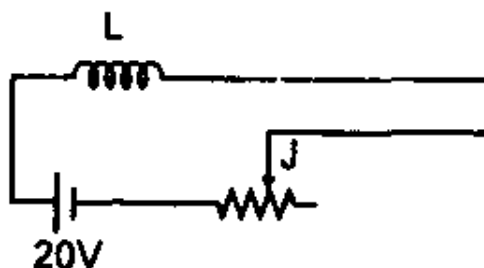- Q 2. In the circuit shown in figure the jockey J is being pulled towards right so that the resistance in the circuit is increasing. Its value at some instant is 5Ω . The current in the circuit at this instant will be:




- (a) 4 A
 (b) less than 4 A
 (c) more than 4 A
 (d) may be less than or more than 4 A depending on the value of L

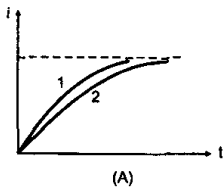
- Q 3. Current growth in two L-R circuits (B) and (C) is as shown in figure (A). Let L_1 , L_2 , R_1 and R_2 be the corresponding values in two circuits. Then:



(A) (a) $R_1 > R_2$

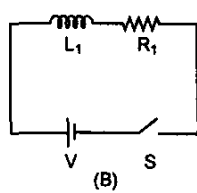


(B) (b) $R_1 = R_2$

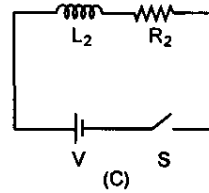

(C) (c) $L_1 > L_2$


(d) $L_1 < L_2$

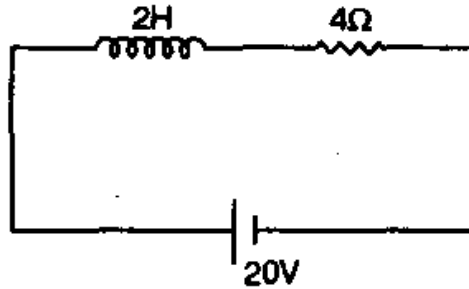- Q 4. In the L-R circuit shown in figure, potential difference across the resistance at some instant is 4 V. Then:




- (a) current is increasing at a rate of 8 A/s at this instant
 (b) power supplied by the battery at this instant is 20 W
 (c) power stored in the magnetic field at this instant is 16 W
 (d) current in the circuit at this instant is 1 A

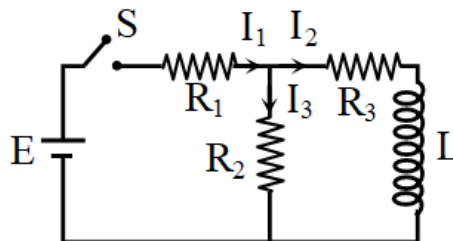- Q 5. In the figure circuit, if $E = 10V$, $R_1 = 2 \text{ ohm}$, $R_2 = 3 \text{ ohm}$, $R_3 = 6 \text{ ohm}$ and $L = 5 \text{ henry}$. The current I_1 just after pressing the switch S is



- (a) $(10/4)$ ampere
 (b) $(10/5)$ ampere
 (c) $(10/12)$ ampere
 (d) $(10/6)$ ampere

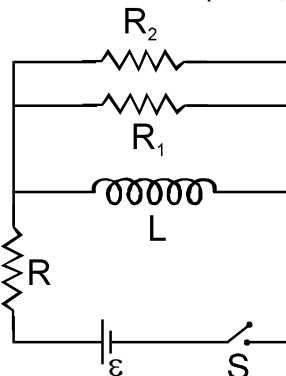
- Q 6. Switch S is closed for a long time . at $t = 0$ It is opened, then:





- (a) total heat produced in resistor R after opening the switch is $\frac{1}{2} \frac{L\varepsilon^2}{R^2}$
 (b) total heat produced in resistor R_2 after opening the switch is $\frac{1}{2} \frac{L\varepsilon^2}{R^2} \left(\frac{R_1}{R_1+R_2} \right)$
 (c) heat produced in resistor R_1 after opening the switch is $\frac{1}{2} \frac{R_2 L \varepsilon^2}{(R_1+R_2) R^2}$
 (d) Current through R_1 just after opening the switch is $\frac{\varepsilon}{R} \cdot \left(\frac{R_1}{R_1+R_2} \right)$

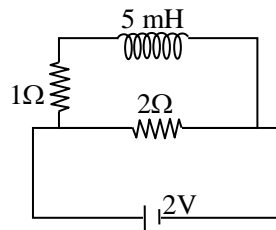
Q 7. When induced emf in inductor coil is 50% of its maximum value then stored energy in inductor coil in the given circuit will be-



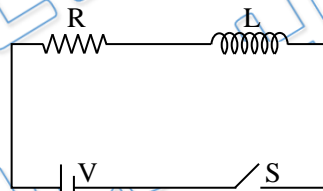
- (a) 2.5 mJ
 (b) 5 mJ
 (c) 15 mJ
 (d) 20 mJ

Passage (Q.8 to Q.10)

A resistor and inductor are connected in series through a battery. The switch S is closed at time $t = 0$.







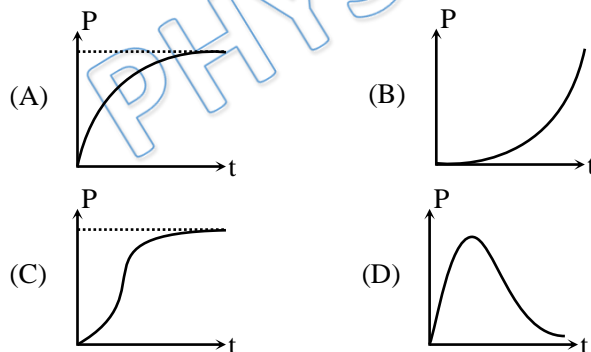Q 8. The rate of Joule heating (P) in resistor varies with the time 't' is best represented by the graph.




- Q 9. What is the magnitude of current flowing when the rate of increase of magnetic energy in the inductor is maximum –
 (a) $I = V/R$
 (b) $I = V/2R$
 (c) $I = V/4R$
 (d) $I = (V/R) \ln 2$

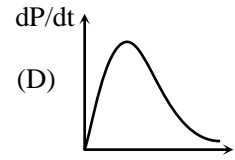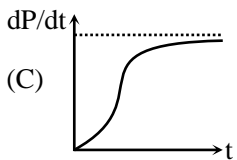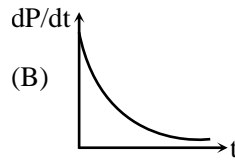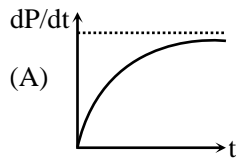Q 10. Which of the following graph best represent rate of change of power dissipated in resistor as a function of time -




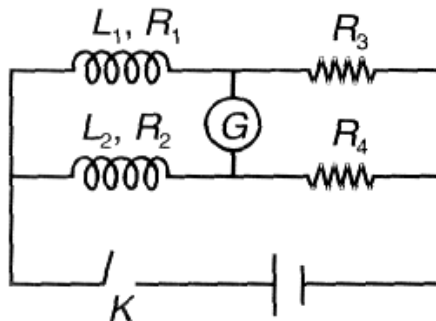Q 11. After the key k is closed, galvanometer in the shown arrangement shows zero deflection at all the times if (R_1 , and R_2 are resistances of inductors L_1 and L_2)



- (a) $\frac{R_1}{R_2} = \frac{R_3}{R_4} = \frac{L_1}{L_2}$
 (b) $\frac{R_2}{R_1} = \frac{R_3}{R_4} = \frac{L_1}{L_2}$
 (c) $\frac{L_1}{L_2} = \frac{R_1}{R_2} = \frac{R_3}{R_4}$
 (d) $\frac{L_1}{L_2} = \frac{R_3}{R_4}$

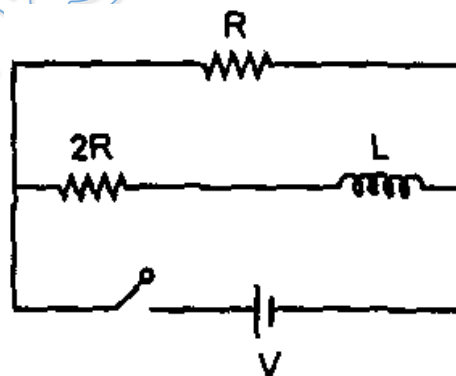Q 12. The ratio of time constants during current growth and current decay of the circuit shown in figure is:



- (a) 1 : 1 (b) 3 : 2 (c) 2 : 3 (d) 1 : 3



Answer Key

Q.1 a	Q.2 c	Q.3 b, d	Q.4 a, b, c, d	Q.5 b
Q.6 b, c	Q.7 a	Q.8 c	Q.9 b	Q.10 d
Q.11 a	Q.12 b			

PRATEEK JAIN
PHYSICSAHOLICS