

DPP – 4 (Semiconductor)

Video Solution on Website:-

<https://physicsaholics.com/home/courseDetails/63>


Video Solution on YouTube:-

<https://youtu.be/zyA86Uok2Ik>

Written Solution on Website:-


<https://physicsaholics.com/note/notesDetails/22>

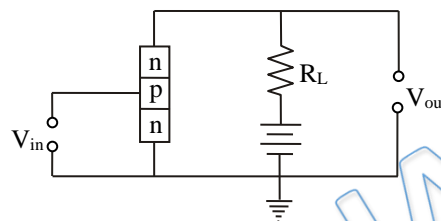Q 1. An n-p-n transistor circuit is arranged as shown in fig. It is –



- (a) a common-base amplifier circuit
- (b) a common-emitter amplifier circuit
- (c) a common-collector amplifier circuit
- (d) none of the above

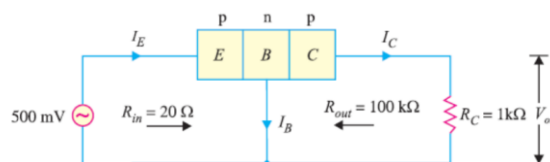Q 2. A common base transistor amplifier has an input resistance of $20\ \Omega$ and output resistance of $100\ \text{k}\Omega$. The collector load is $1\ \text{k}\Omega$. If a signal of $500\ \text{mV}$ is applied between emitter and base, find the voltage amplification. Assume α_{ac} to be nearly one.




- (a) 25
- (b) 50
- (c) 75
- (d) 100

Q 3. In a common base connection, current amplification factor is 0.9. If the emitter current is $1\ \text{mA}$, determine the value of base current.


- (a) $0.1\ \text{mA}$
- (b) $0.2\ \text{mA}$
- (c) $0.4\ \text{mA}$
- (d) $0.5\ \text{mA}$

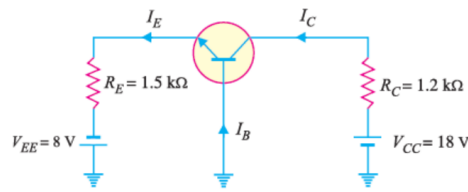Q 4. For the common base circuit shown in Figure, determine I_C and V_{CB} . Assume the transistor to be of silicon.



- (a) 4.87 mA ,12.16 V
- (b) 3.27 mA ,11.16 V
- (c) 4.87 mA ,11.16 V
- (d) 3.27 mA ,12.16 V

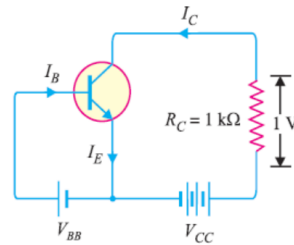Q 5. For a transistor, $\beta = 45$ and voltage drop across $1\text{k}\Omega$ which is connected in the collector circuit is 1 volt. Find the base current for common emitter connection.




- (a) 0.022 mA
- (b) 0.011 mA
- (c) 0.033 mA
- (d) 0.044 mA

Q 6. A transistor is connected in common emitter (CE) configuration in which collector supply is 8 V and the voltage drop across resistance R_C connected in the collector circuit is 0.5 V. The value of $R_C = 800 \Omega$. If $\alpha = 0.96$, determine base current


- (a) 0.026 mA
- (b) 0.011 mA
- (c) 0.033 mA
- (d) 0.044 mA

Q 7. Choose the correct option:

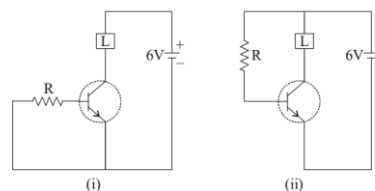


- (a) In circuit 1 lamp does not glow but in circuit 2 lamp glows
- (b) In circuit 1 as well as 2 lamp does not glow
- (c) In circuit 1 lamp glows but in 2 lamp does not glow
- (d) In both circuit lamp glows

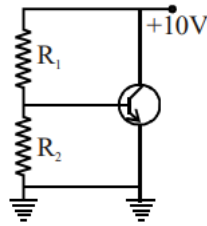Q 8. Figure shows an n-p-n transistor. Choose the correct statement out of the following :




- (a) Collector-base junction as well as emitter-base junction both are forward biased
- (b) Collector-base junction as well as emitter-base junction both are reverse biased
- (c) Collector-base junction is forward biased and emitter-base junction is reverse biased
- (d) Collector-base junction is reverse-biased and emitter-base junction is forward biased

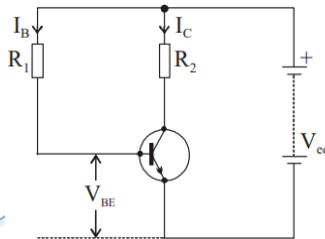Q 9. In the junction transistor voltage amplifier circuit of figure, if $R_1 = 100 \text{ k}\Omega$, $R_2 = 1 \text{ k}\Omega$, $V_{ec} = 6.0 \text{ V}$ and $V_{BE} = 0.6 \text{ V}$, current gain = 60



- (a) $I_B = 54 \mu\text{A}$
- (b) $I_C = 3.24 \text{ mA}$
- (c) the voltage across $R_2 = 3.24 \text{ V}$
- (d) the voltage across the collector-emitter = 3.24 V

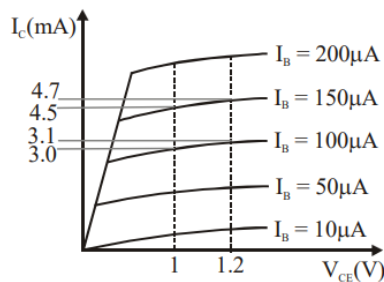Q 10. Output characteristic of n-p-n transistor in CE configuration is shown. From the characteristic curve determine the current gain at $V_{CE} = 1 \text{ V}$ –



- (a) 30
- (b) 32
- (c) 28
- (d) 40

Q 11. A transistor is connected in common emitter configuration. The collector emitter voltage is 8V and load resistance of 800Ω is connected in the collector circuit. The voltage drop across the load resistance is 0.5V. If α be 0.96, what is the base current

- (a) $5 \mu\text{A}$



- (b) $8 \mu A$
- (c) $9.6 \mu A$
- (d) $26 \mu A$

PRATEEK JAIN
PHYSICSAHOLICS

Answer Key

Q.1) b	Q.2) b	Q.3) a	Q.4) a	Q.5) a
Q.6) a	Q.7) a	Q.8) d	Q.9) a,b,c	Q.10) a
Q.11) d				