

Video Solution on Website:-

<https://physicsaholics.com/home/courseDetails/63>


Video Solution on YouTube:-

<https://youtu.be/BxSn5XyyhAc>

Written Solution on Website:-

<https://physicsaholics.com/note/notesDetailis/22>

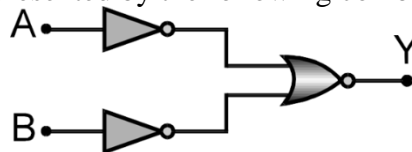Q 1. Which logic gate is represented by the following combination of logic gates –




- (a) OR  
(b) NAND  
(c) AND  
(d) NOR

Q 2. Add binary numbers  $101 + 110 = ?$

- (a) 1011  
(b) 1001  
(c) 0111  
(d) 111

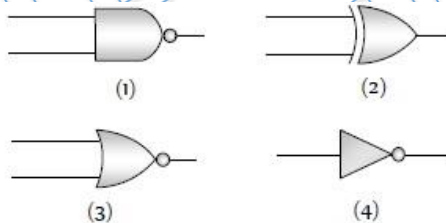Q 3. Given below are symbols for some logic gates. The XOR gate and NOR gate respectively are



- (a) 1 and 2  
(b) 2 and 3  
(c) 3 and 4  
(d) 1 and 4

Q 4. The following truth table corresponds to the logic gate

A	0	0	1	1
B	0	1	0	1
X	0	1	1	1

- (a) NAND  
(b) OR  
(c) AND  
(d) XOR

Q 5. What will be the input of A and B for the Boolean expression  $\overline{(A + B)} \cdot \overline{(A \cdot B)} = 1$

- (a) 0, 0  
(b) 0, 1  
(c) 1, 0  
(d) 1, 1



Q 6. Which of the following logic gate is an universal gate

- (a) OR  
(b) NOT

- (c) AND (d) NOR

- Q 7. Boolean algebra is essentially based on  
 (a) Truth  
 (b) Logic  
 (c) Symbol  
 (d) Numbers

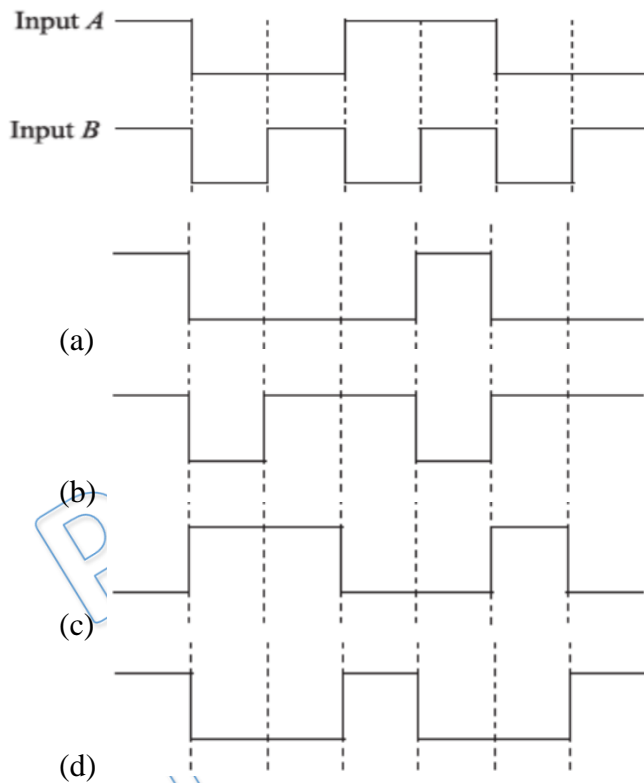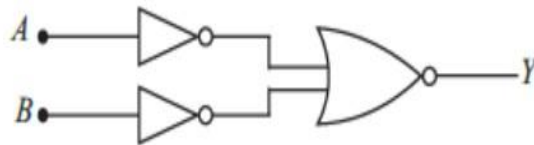- Q 8. The logic circuit shown below has the input waveforms 'A' and 'B' as shown. Pick out the correct output waveform




- Q 9. The truth table for NOT gate is

	Input	output		Input	output
	1	1		1	0
(a)	0	0	(b)	0	0
	Input	output		Input	output
	1	0		0	1
(c)	0	1	(d)	1	1

- Q 10. In the Boolean algebra, the following one is wrong


- (a)  $1.0 = 0$
- (b)  $0.1 = 0$
- (c)  $1.1 = 0$
- (d)  $1.1 = 1$

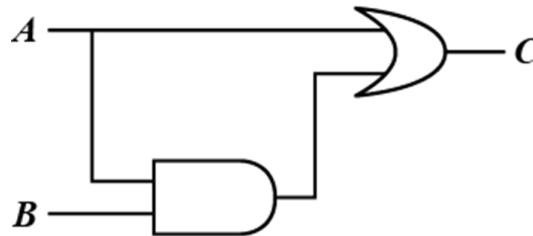Q 11. For the combination of gates shown here, which of the following truth table parts not true?



- (a)  $A = 0, B = 1, C = 1$
- (b)  $A = 0, B = 0, C = 0$
- (c)  $A = 1, B = 1, C = 1$
- (d)  $A = 1, B = 0, C = 1$

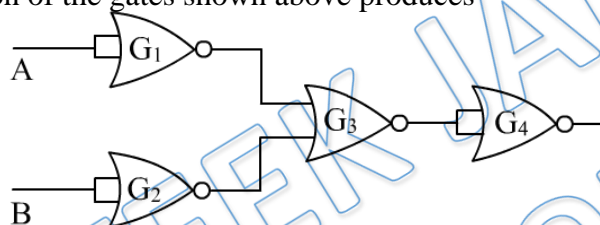Q 12. The combination of the gates shown above produces




- (a) AND gate
- (b) XOR gate
- (c) NOR gate
- (d) NAND gate

Q 13. The combination of gates shown below yields




- (a) NAND gate
- (b) OR gate
- (c) NOT gate
- (d) XOR gate

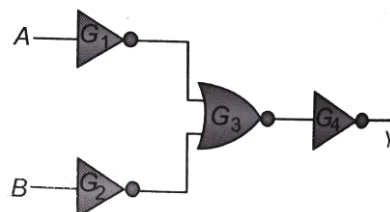Q 14. The combination of gates shown below produces




- (a) AND gate
- (b) XOR gate
- (c) NOR gate
- (d) NAND gate

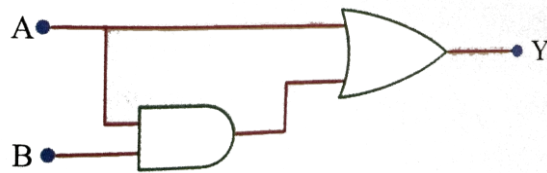Q 15. The output of the combination of the gates shown in the figure below is



- (a)  $A + (A \cdot B)$                       (b)  $(A+B) A + \bar{B}$   
 (c)  $(A \cdot B) + (\bar{A} \cdot \bar{B})$                 (d)  $(A+B) (\bar{A} \cdot \bar{B})$

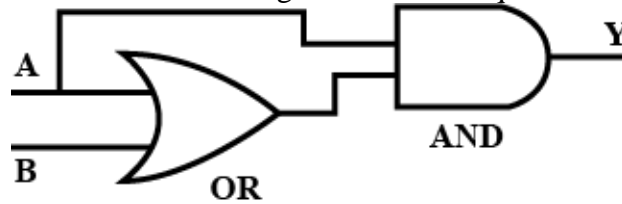Q 16. The output Y of the combination of gates shown in equal to:



- (a) A    (b)  $\bar{A}$   
 (c)  $A + B$                                       (d)  $A \cdot B$

PRATEEK JAIN  
PHYSICSAHOLICS

## Answer Key

Q.1 c	Q.2 a	Q.3 b	Q.4 b	Q.5 a
Q.6 d	Q.7 b	Q.8 a	Q.9 c	Q.10 c
Q.11 a	Q.12 d	Q.13 b	Q.14 d	Q.15 a
Q.16 a				


PLUS **ICONIC\*\***

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

24 months	₹2,333/mo	>
No cost EMI	₹56,000	
18 months	₹2,625/mo	>
No cost EMI	₹47,250	
12 months	₹3,208/mo	>
No cost EMI	₹38,500	
6 months	₹4,667/mo	>
No cost EMI	₹28,000	

To be paid as a one-time payment

[View all plans](#)

 Add a referral code APPLY

# PHYSICSLIVE


PLUS **ICONIC\*\***

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

24 months	₹2,100/mo	>
No cost EMI	+10% OFF ₹50,400	
18 months	₹2,363/mo	>
No cost EMI	+10% OFF ₹42,525	
12 months	₹2,888/mo	>
No cost EMI	+10% OFF ₹34,650	
6 months	₹4,200/mo	>
No cost EMI	+10% OFF ₹25,200	

To be paid as a one-time payment

[View all plans](#)

 Awesome! **PHYSICSLIVE** code applied ✗


Use code **PHYSICSLIVE** to get 10% OFF on Unacademy PLUS.

# **NEET & JEE Main Written Solution**

**DPP-3 Semi Conductors: Logic Gates & Digital  
Electronics**

**By Physicsaholics Team**

Solution: 1

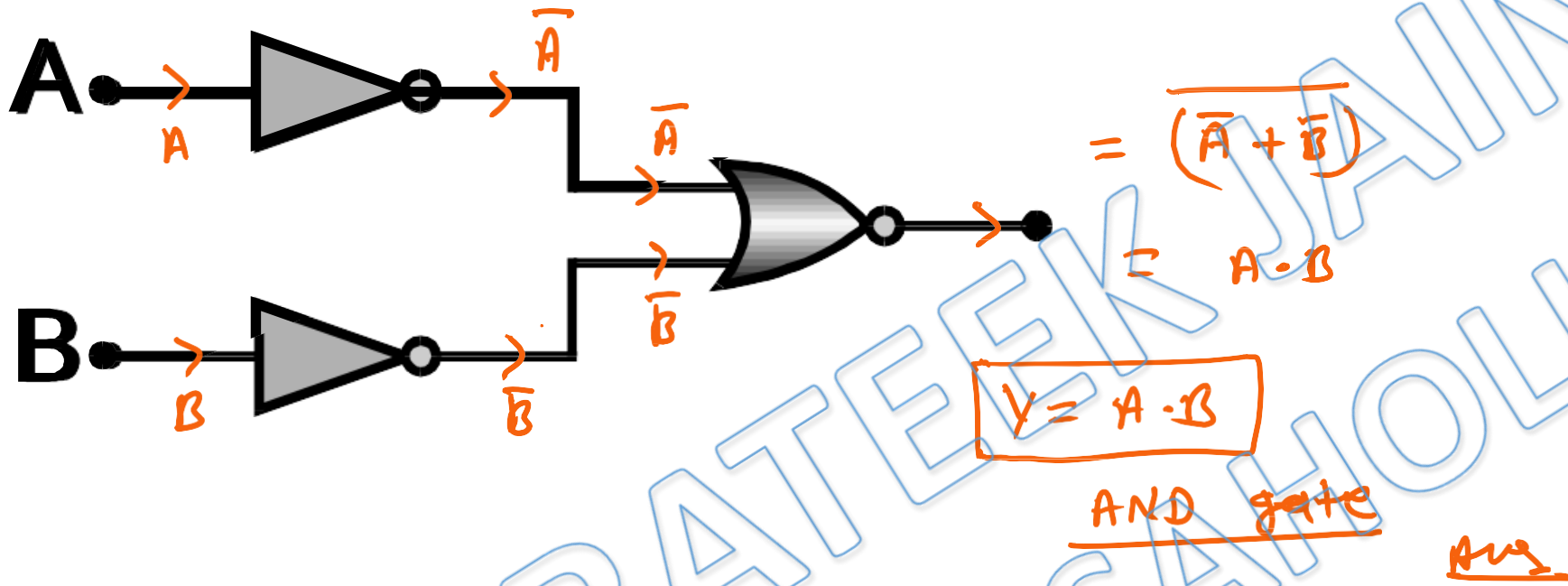

Ans. c

Solution: 2

$$\begin{array}{r} \text{+} \\ \begin{array}{|c|c|c|} \hline 1 & 0 & 1 \\ \hline 1 & 1 & 0 \\ \hline \end{array} \\ \hline 10 \quad 1 \quad 1 \end{array}$$


So,  $101 + 110 = 1011$  *Ans*

PRATEEK JAIN  
PHYSICSAHOLICS


Ans. a




Solution: 3

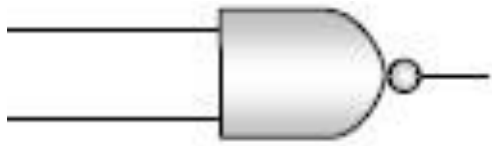


(1) NAND gate.

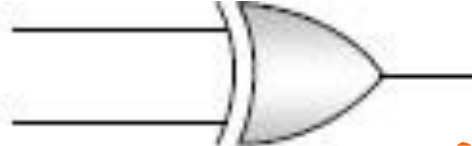

(2) XOR gate

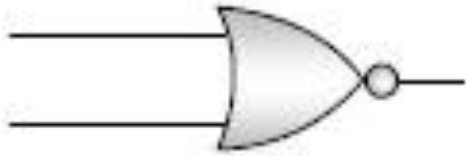

(3) NOR gate

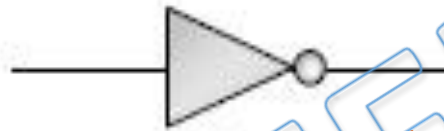

(4) NOT gate.

PRATEEK JAIN  
PHYSICSAHOLICS

Ans. b

Solution: 4

A	0	0	1	1
B	0	1	0	1
X	0	1	1	1

$$A + B = X$$

$$0 \ 0 \ 0$$

$$0 \ 1 \ 1$$

$$1 \ 0 \ 1$$

$$1 \ 1 \ 1$$

Correct truth table

so;

$$X = A + B$$

OR gate

Ans.

Ans. b

Solution: 5

$$\overline{(A+B)} \cdot \overline{(A \cdot B)} = 1$$

(D)

For output;

$$Y = \overline{(A+B)} \cdot \overline{(A \cdot B)}$$

$$= (\overline{A} \cdot \overline{B}) \cdot (\overline{A} + \overline{B})$$

$$= (\overline{A} \cdot \overline{B}) \cdot \overline{A} + (\overline{A} \cdot \overline{B}) \cdot \overline{B}$$

$$= \overline{A} \cdot \overline{B} + \overline{A} \cdot \overline{B}$$

$$= \overline{A} \cdot \overline{B}$$

$$Y = \overline{A+B}$$

so; (a) 0, 0

$$Y = \overline{(0+0)} = 1 \checkmark$$

Ans

Ans. a

Solution: 6

NOR gates are considered as universal gates, because all the gates like AND, OR, NOT can be obtained by using only NOR gates.

PRATEEK JAIN  
PHYSICSAHOLICS

Ans. d


Solution: 7

Boolean algebra is essentially based on logic. It is also known as logical algebra.

PRATEEK JAIN  
PHYSICSAHOLICS


Ans. b

Solution: 8

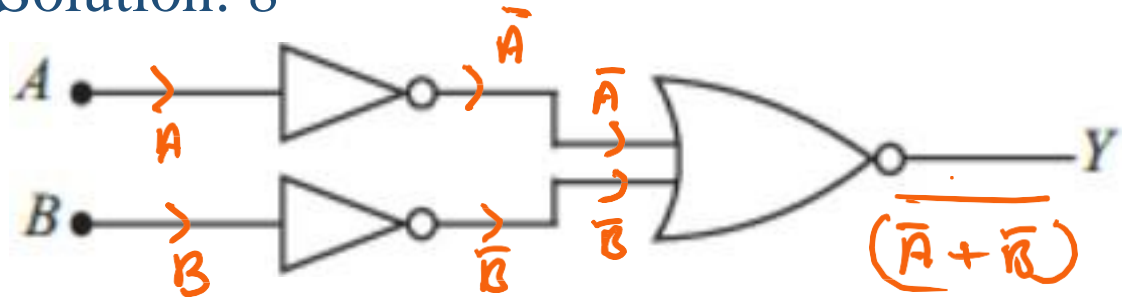

$$Y = \overline{(\bar{A} + \bar{B})}$$

$$Y = A \cdot B$$

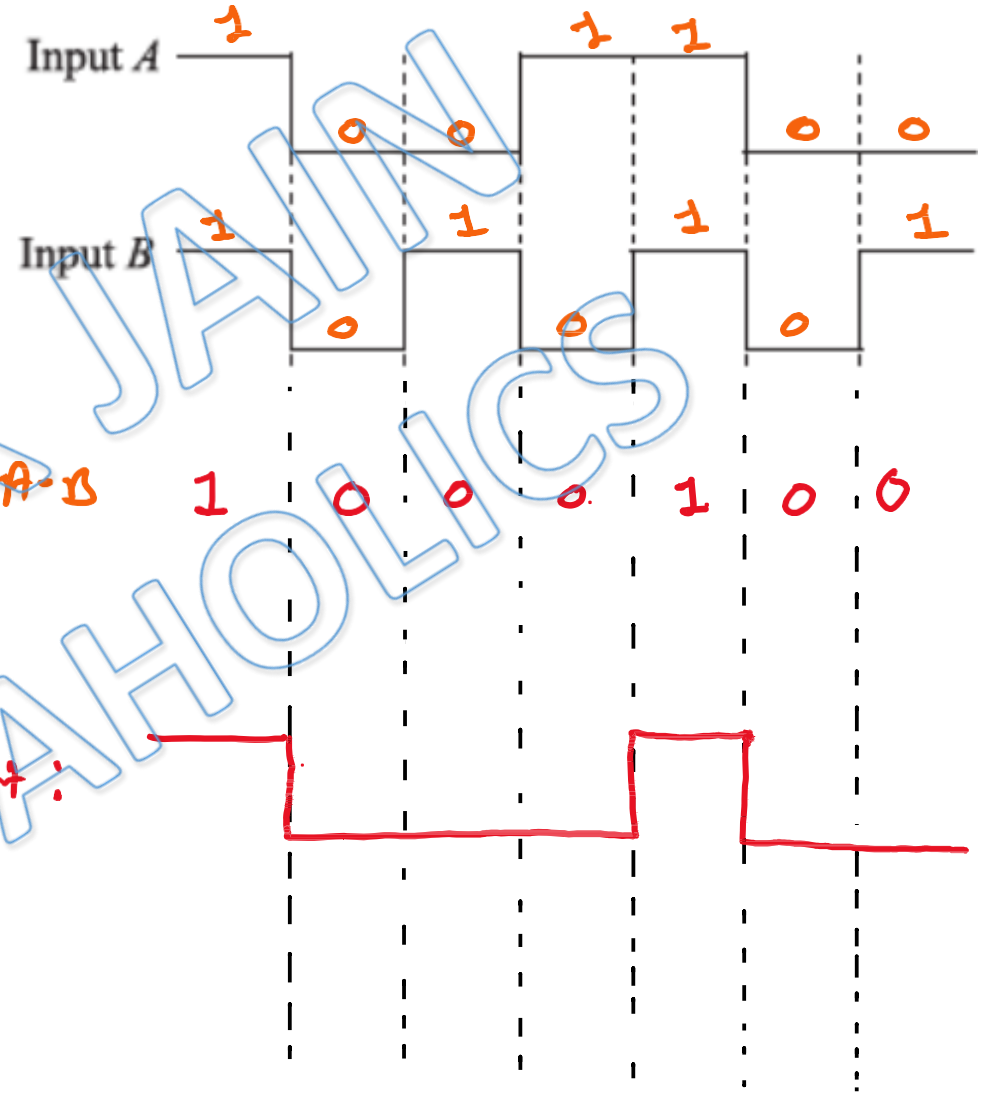

Ans. a

Solution: 9

NOT gate gives the reverse of the input as output. Truth table for NOT gate is:

Input	output
1	0
0	1

PRATEEK JAIN  
PHYSICSAHOLICS

Ans. c

Solution: 10

In the Boolean algebra,

$$1 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$


$$1 \cdot 1 = 1$$

PRATEEK JAIN  
PHYSICSAHOLICS

Ans. c



## Solution: 11

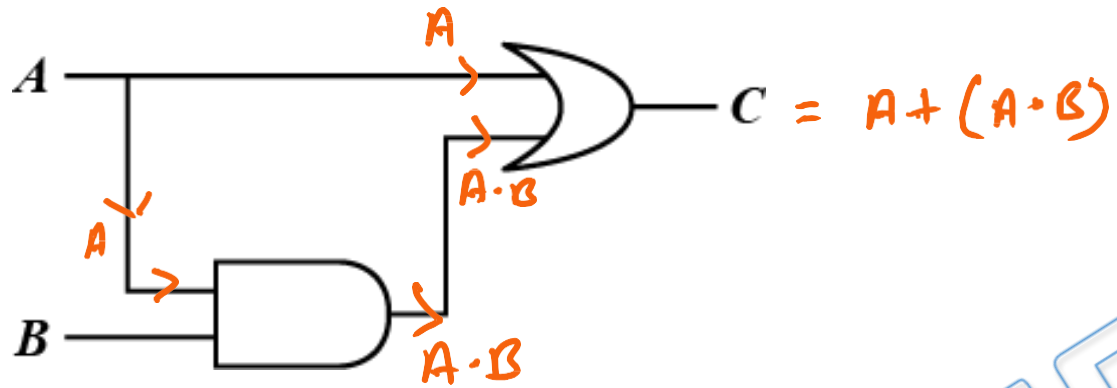

So,  $C = A + (A \cdot B)$

Ⓐ  $A=0; B=1$

$$C = 0 + (0 \cdot 1)$$

$$C = 0$$

Ⓑ  $A=0; B=0$

$$C = 0 + (0 \cdot 0)$$

$$C = 0$$

Ⓒ  $A=1; B=1$   
 $C = 1 + (1 \cdot 1)$

$$C = 1$$

Ⓓ  $A=1; B=0$


$$C = 1 + (1 \cdot 0)$$

$$C = 1$$

So, Ⓒ is not true

Ans. a

Solution: 12

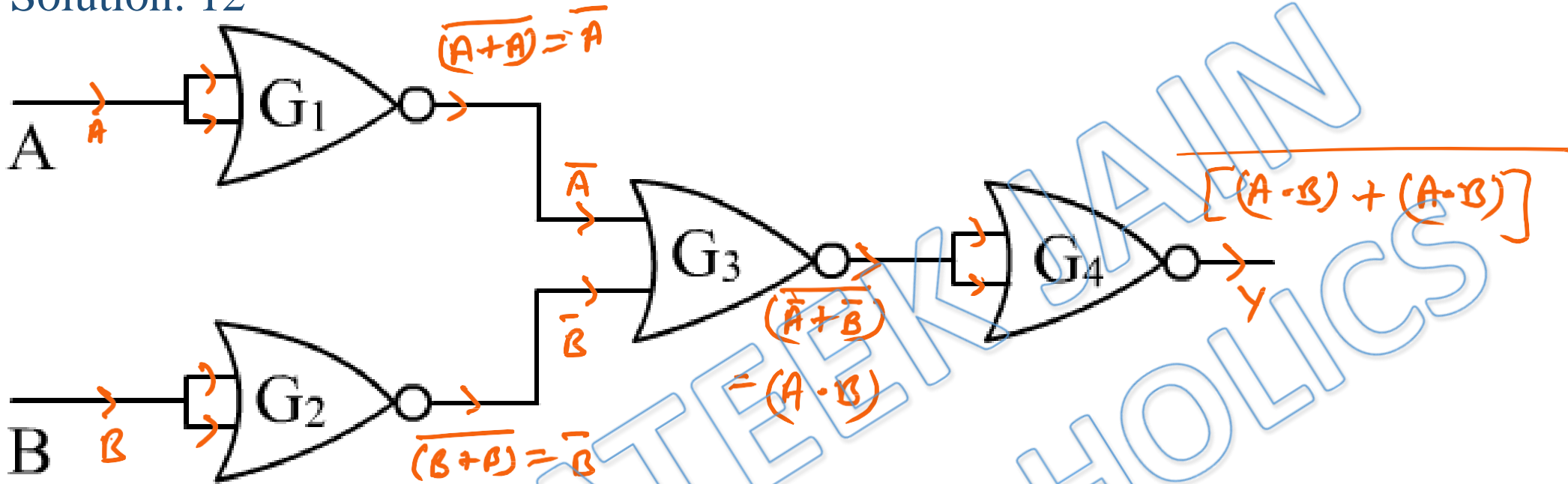

So, output ;  $Y = \overline{[(A \cdot B) + (A \cdot B)]} = \overline{(A \cdot B)}$


$$Y = \bar{A} \bar{B}$$

this output is for NAND gate.

Ans


Ans. d

Solution: 13

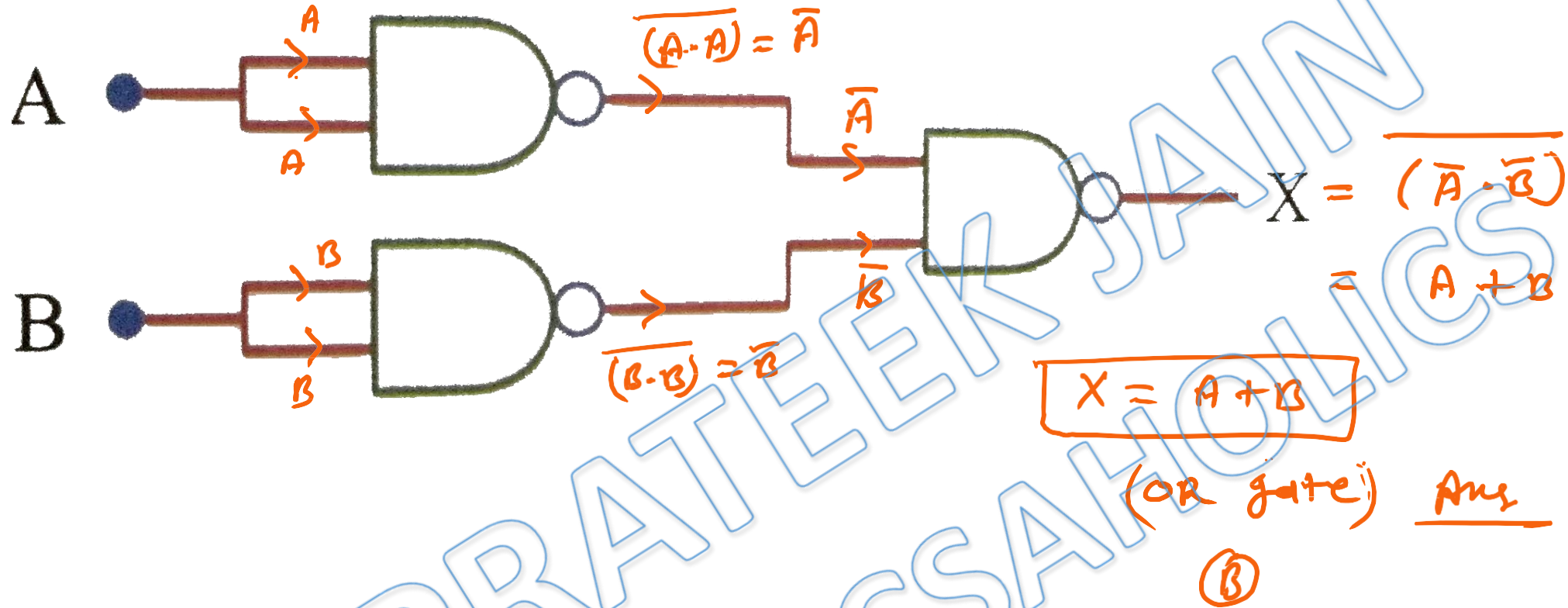

Ans. b

Solution: 14

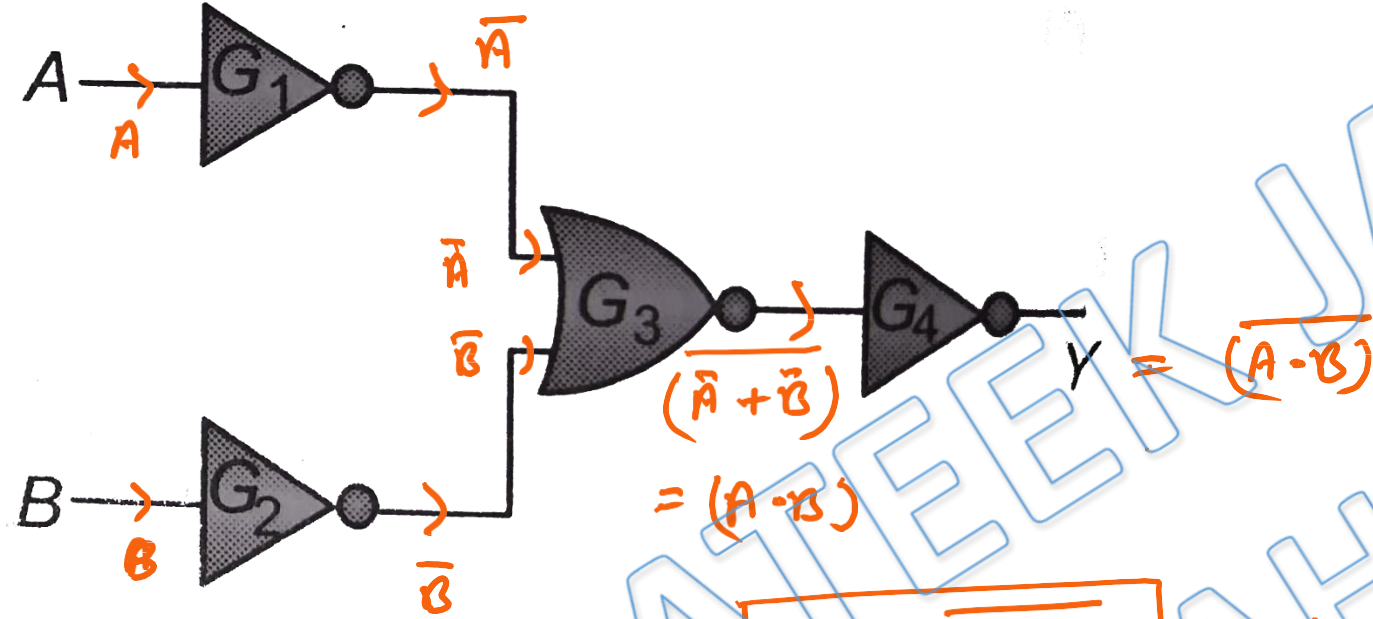


So,  $y = \overline{(\bar{A} + \bar{B})}$  output

NAND gate.

Ans


Ans. d

Solution: 15

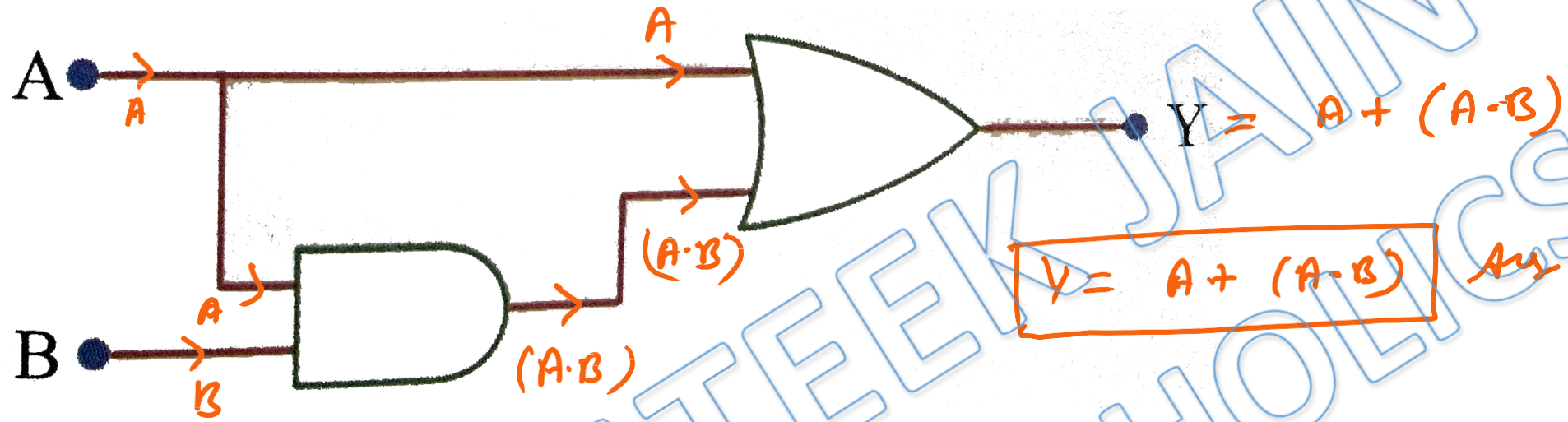

Ans. a

Solution: 16

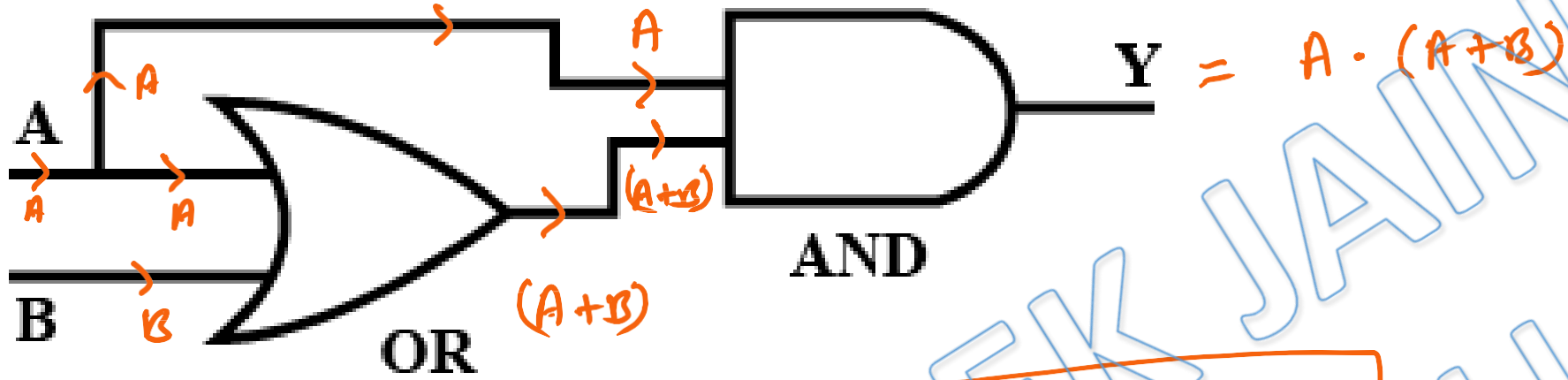

output;

$$Y = A \cdot (A+B)$$

$$Y = A \cdot A + A \cdot B$$

$$= A + A \cdot B$$

$$= A(1+B)$$

$$= A(1)$$

$$Y = A \quad \text{Ans}$$

Ans. a

For Video Solution of this DPP, Click on below link

Video Solution  
on Website:-

<https://physicsaholics.com/home/courseDetails/63>

Video Solution  
on YouTube:-

<https://youtu.be/BxSn5XyyhAc>

Written Solution  
on Website:-

<https://physicsaholics.com/note/notesDetails/22>

 **SUBSCRIBE**



[@Physicsaholics](#)

[@Physicsaholics\\_prateek](#)

[@NEET\\_Physics](#)  
[@IITJEE\\_Physics](#)

[physicsaholics.com](#)

[Unacademy](#)



**CLICK**



Chalo Niklo