



Video Solution on Website:-

<https://physicsaholics.com/home/courseDetails/55>

Video Solution on YouTube:-

<https://youtu.be/2tVzRIWForY>

Written Solution on Website:-

<https://physicsaholics.com/note/notesDetailis/52>

Q 1. An electric wire is connected across a cell of e.m.f.  $E$ . The current  $I$  is measured by an ammeter of resistance  $R$ . According to ohm's law:

(a)  $E = I^2 R$

(b)  $E = IR$

(c)  $E = \frac{I}{R}$

(d)  $E = \frac{R}{I}$

Q 2. In Ohm's law experiment, potential drop across a resistance was measured as  $v = 5 \text{ Volt}$  and current was measured as  $i = 2 \text{ amp}$ . If least count of the (voltage measuring device) and ammeter (current measuring device) are  $0.1V$  and  $0.01A$  respectively then find the maximum permissible error in measuring resistance:


(a) 1.5%

(b) 2.5%

(c) 1%

(d) 5%

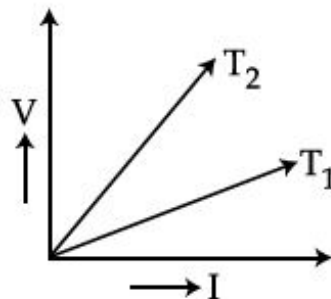Q 3. The voltage-current ( $V$ - $I$ ) graph of a metallic circuit at two different temperature  $T_1$  and  $T_2$  is shown, then:



(a)  $T_1 < T_2$

(b)  $T_1 > T_2$

(c)  $T_1 = T_2$

(d) cant say anything

Q 4. By a cell a current of  $0.9 \text{ A}$  flows through  $2 \text{ ohm}$  resistor and  $0.3 \text{ A}$  through  $7 \text{ ohm}$  resistor. The internal resistance of the cell is:

(a)  $0.5\Omega$

(b)  $1.0\Omega$

(c)  $1.2\Omega$

(d)  $2.0\Omega$

Q 5. A cell of e.m.f.  $E$  is connected with an external resistance  $R$ , then potential difference across cell is  $V$ . The internal resistance of cell will be:

(a)  $\frac{(E-V)}{E} R$

(b)  $\frac{(E-V)}{V} R$


(c)  $\frac{(V-E)}{V} R$

(d)  $\frac{(V-E)}{E} R$




- Q 6. The potential difference in open circuit for a cell is 2.2 volts. When a 4 ohm resistor is connected between its two electrodes the potential difference becomes 2 volts. The internal resistance of the cell will be:
- (a) 1 ohm (b) 0.2 ohm  
(c) 2.5 ohm (d) 0.4 ohm

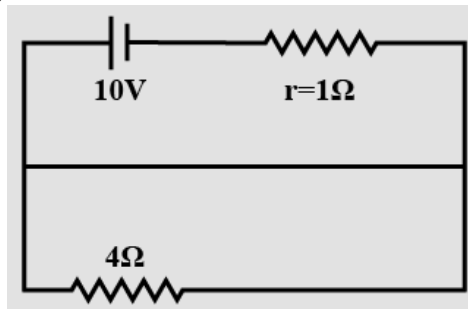- Q 7. Potential difference across the terminals of the battery shown in figure is - ( $r$ = internal resistance of battery)



- (a) 8 V (b) 10 V  
(c) 6 V (d) zero

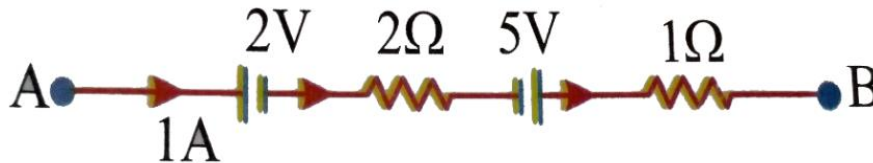- Q 8. The potential difference between points A and B is:




- (a) 0 V (b) 2 V  
(c) 1 V (d) 3 V

- Q 9. The potential difference across terminals of a battery is 9V, when a current of 3.5A flows through it from its negative terminal to the positive terminal. When a current of 2A flows through in the opposite direction, the terminal potential difference is 12V. Find the internal resistance and emf of the battery:
- (a)  $0.545\Omega$ , 8.1 V (b)  $1.54\Omega$ , 8.1 V  
(c)  $0.545\Omega$ , 10.91 V (d)  $1.345\Omega$ , 9.1 V

- Q 10. Kirchoff's current law represents a mathematical statement of fact that:
- (a) voltage cannot accumulate at node  
(b) charge cannot accumulate at node  
(c) charge at the node is infinite  
(d) none of the mentioned

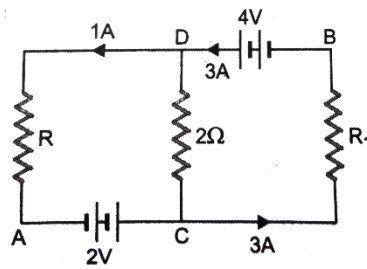- Q 11. In the given circuit assuming point A at zero potential use Kirchoff's rules to determine the potential at point B:




- (a) 2 V                      (b) 4 V  
(c) 8 V                      (d) 10 V

Q 12. If  $E$  is the emf of a cell of internal resistance  $r$  and external resistance  $R$ , then potential difference ( $V$ ) across  $R$  is given as:


- (a)  $V = \frac{E}{R+r}$                       (b)  $V = E$   
(c)  $V = \frac{E}{1+\frac{r}{R}}$                       (d)  $V = \frac{E}{1+\frac{R}{r}}$

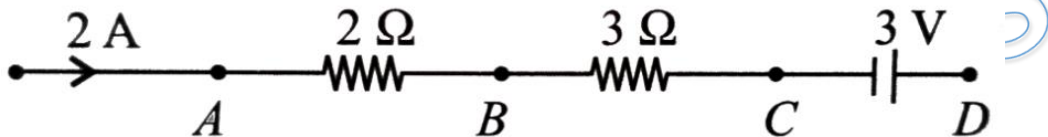Q 13. In the given circuit the potential at point B is zero, the magnitude of potential at points A and D will be:



- (a)  $V_A = 4 V, V_D = 9 V$                       (b)  $V_A = 3 V, V_D = 4 V$   
(c)  $V_A = 9 V, V_D = 3 V$                       (d)  $V_A = 4 V, V_D = 3 V$

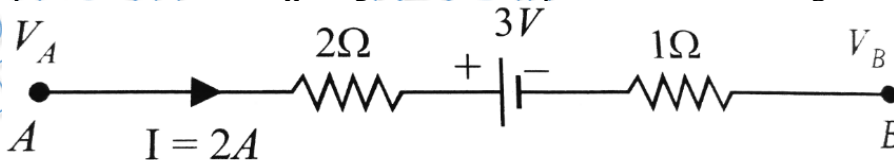Q 14. The potential difference  $V_A - V_B$  between the point A and B in the given figure is:



- (a) 6 V                      (b) 9 V  
(c) -3 V                      (d) 3 V



PRATEEK JAIN  
PHYSICSAHOLICS

## Answer Key

<b>Q.1 b</b>	<b>Q.2 b</b>	<b>Q.3 a</b>	<b>Q.4 a</b>
<b>Q.5 b</b>	<b>Q.6 d</b>	<b>Q.7 d</b>	<b>Q.8 a</b>
<b>Q.9 c</b>	<b>Q.10 b</b>	<b>Q.11 a</b>	<b>Q.12 c</b>
<b>Q.13 d</b>	<b>Q.14 b</b>		


PLUS **ICONIC\*\***

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

24 months	₹2,333/mo	>
No cost EMI	₹56,000	
18 months	₹2,625/mo	>
No cost EMI	₹47,250	
12 months	₹3,208/mo	>
No cost EMI	₹38,500	
6 months	₹4,667/mo	>
No cost EMI	₹28,000	

To be paid as a one-time payment

[View all plans](#)

 Add a referral code APPLY

# PHYSICSLIVE


PLUS **ICONIC\*\***

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

24 months	₹2,100/mo	>
No cost EMI	+10% OFF ₹50,400	
18 months	₹2,363/mo	>
No cost EMI	+10% OFF ₹42,525	
12 months	₹2,888/mo	>
No cost EMI	+10% OFF ₹34,650	
6 months	₹4,200/mo	>
No cost EMI	+10% OFF ₹25,200	

To be paid as a one-time payment

[View all plans](#)

 Awesome! **PHYSICSLIVE** code applied ✗

Use code **PHYSICSLIVE** to get 10% OFF on Unacademy PLUS.

# Written Solution

**DPP-3 Current Electricity: Ohm's Law,**

**Battery and Kirchhoff's current law**

**By Physicsaholics Team**

Solution: 1

By Ohm's Law

$$I \propto E$$

$$I = \frac{E}{R}$$

( $\frac{1}{R}$  - Proportional constant)

$R =$  Resistance

$$\therefore \boxed{E = IR}$$

Ans. b

Solution: 2

$$R = \frac{V}{I}$$

$$R = \frac{5}{2} \Omega = 2.5 \Omega$$

$$\frac{\Delta R}{R} \times 100 = \frac{\Delta V}{V} \times 100 + \frac{\Delta I}{I} \times 100$$

$$\% \Delta R = \frac{0.1}{5} \times 100 + \frac{0.01}{2} \times 100$$


$$= 2\% + 0.5\%$$

$$\% \Delta R = 2.5\%$$

Ans. b



Solution: 3

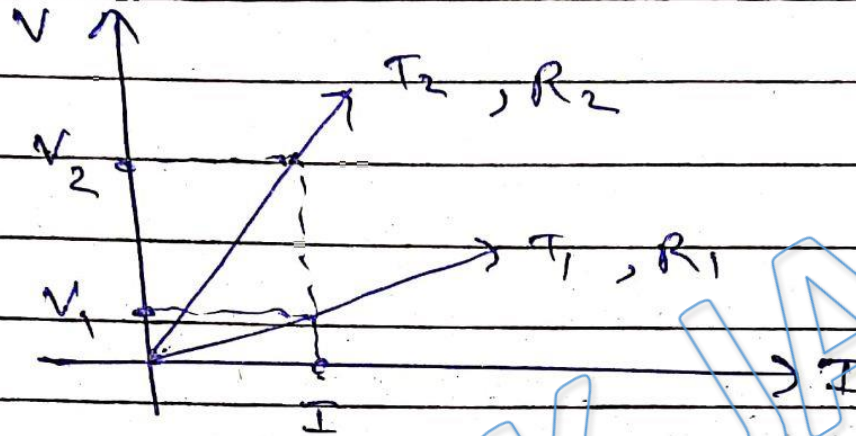

$$V = IR$$

when  $I = \text{constant or same}$

$$V \propto R$$

$$V_2 > V_1 \Rightarrow R_2 > R_1$$



when  $T \uparrow \Rightarrow R \uparrow$

$$\therefore \boxed{T_2 > T_1}$$

Ans. a

Solution: 4

Let internal resistance =  $r$

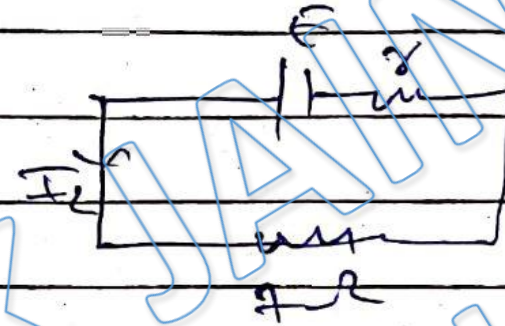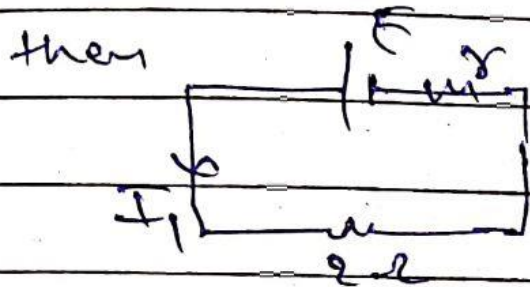

$$I_1 = \frac{\mathcal{E}}{r+2} = 0.9$$

$$I_2 = \frac{\mathcal{E}}{r+7} = 0.5$$

$$\mathcal{E} = 0.9(r+2) \quad \text{--- (1)}$$

$$\mathcal{E} = 0.5(r+7) \quad \text{--- (2)}$$

From eq<sup>n</sup> (1) & (2)


$$0.9(r+2) = 0.5(r+7)$$

$$r = 2r$$

$$r = 0.5r$$

Ans. a

Solution: 5

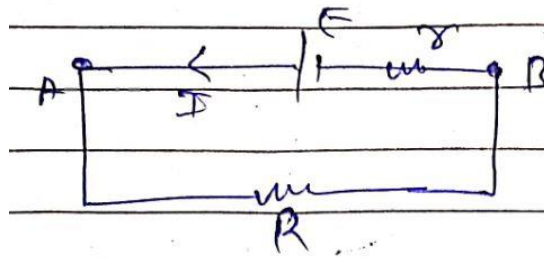

$$I = \frac{E}{R+r}$$

$$V_A - V_B = V = \mathcal{E}$$

$$V_A - E + Ir = V_B$$

$$V_A - V_B = V = E - Ir$$

$$V = E - \frac{E}{R+r} r$$

$$V = \frac{ER + Er - Er}{R+r}$$

$$V = \frac{ER}{R+r}$$

$$V(R+r) = ER$$

$$r = \frac{V(R)}{V - E}$$

$$r = \left( \frac{E - V}{V} \right) R$$

Ans. b

Solution: 6

$$\text{Emf}; E = 2.2 \text{ Volt}$$

$$R = 4 \Omega$$

$$\text{then}; V = 2 \text{ Volt}$$

$$\therefore r = \left( \frac{E - V}{V} \right) R$$


$$= \frac{2.2 - 2}{2} \times 4$$

$$r = \frac{0.2}{2} \times 4$$

$$r = 0.4 \Omega$$

Ans. d

Solution: 7

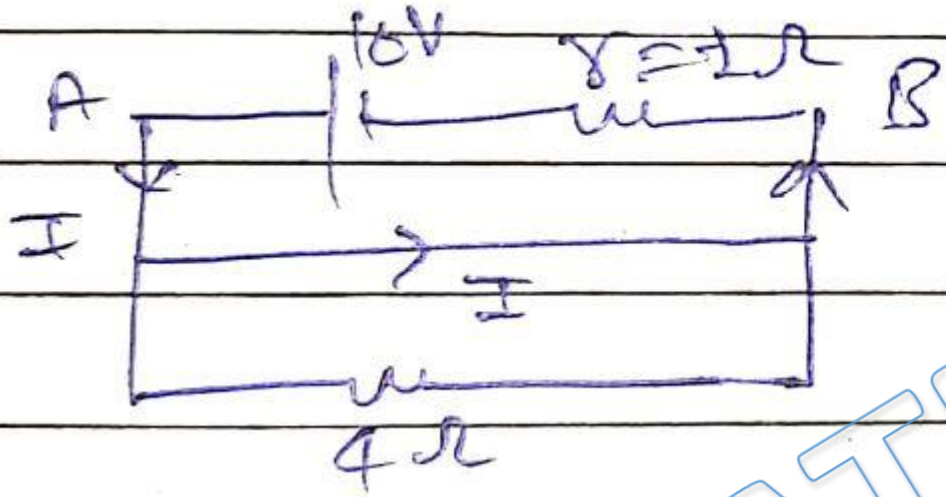

current will not flow

resistance


$$10 = 10 \text{ Amp}$$

$$V_A - V_B = 10 - 10 \times 1$$

$$V_A - V_B = 0$$

Ans. d

Solution: 8

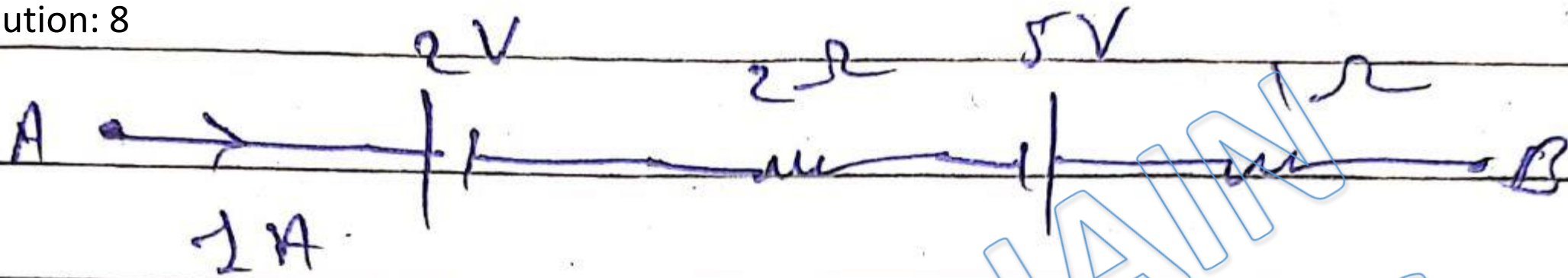


$$V_A - 2 - 1 \times 2 + 5 - 1 \times 1 = V_B$$

$$V_A - V_B = 2 + 2 - 5 + 1$$

$$V_A - V_B = \text{zero} \quad \text{ⓐ} \quad 0 \text{ Volt}$$

Ans. a


Solution: 9

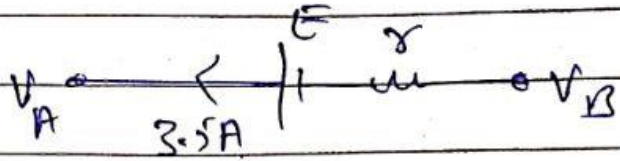

$$V_A - E + 3.5r = V_B$$

$$V_A - V_B = E - 3.5r$$

$$E - 3.5r = 9V \quad \text{--- (1)}$$

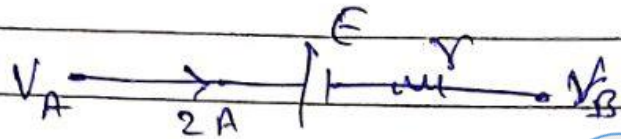

$$V_A - E - 2r = V_B$$

$$V_A - V_B = E + 2r$$

$$E + 2r = 12V \quad \text{--- (2)}$$

$$eq^n (2) - eq^n (1) \Rightarrow 5.5r = 3'$$

$$r = \frac{3}{5.5} = 0.545\Omega$$

Put value of  $r$  in eq^n (2)

$$E = 10.91V$$

$$r = 0.545\Omega \quad \& \quad E = 10.91V$$

Ans. c


Solution: 10

Charge cannot accumulate at the node, it can only flow in and out of the node

Ans. b



Solution: 11

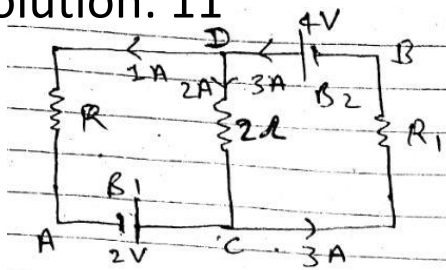

From Kirchhoff's current law at node D;  $\sum I = 0$

$\therefore$  Current in Branch DC  
 $I_{DC} = 2A$

Now for Battery B1

$$V_C - V_A = 2 \text{ Volt}$$

$$4V_A = 0 \text{ Volt (given)}$$

$$\therefore V_C = 2 \text{ Volt}$$

$$I_{DC} = \frac{V_D - V_C}{2} = 2$$

$$\Rightarrow V_D - V_C = 4 \Rightarrow V_D = 4 + V_C$$

$$\Rightarrow V_D = 6 \text{ Volt}$$


Now for Battery B2

$$V_D - V_B = 4 \text{ Volt}$$

$$V_B = V_D - 4 \text{ Volt}$$

$$V_B = 6 - 4$$

$$V_B = 2 \text{ Volt}$$

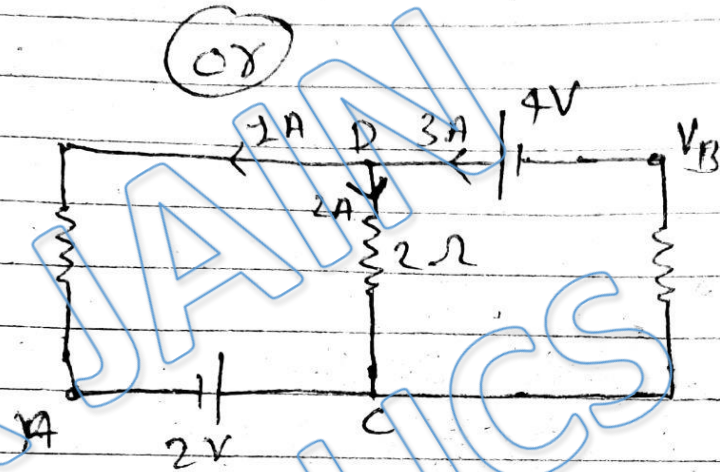

Current in DC wire

$$I_{DC} = 3 - 1 = 2 \text{ Amp}$$

for the path

$$A \rightarrow C \rightarrow D \rightarrow B$$


$$V_A + 2 + 2 \times 2 - 4 = V_B$$

$$V_B = 2 + 4 - 4 + V_A$$

$$V_B = 2 \text{ Volt}$$

Ans. a

Solution: 12

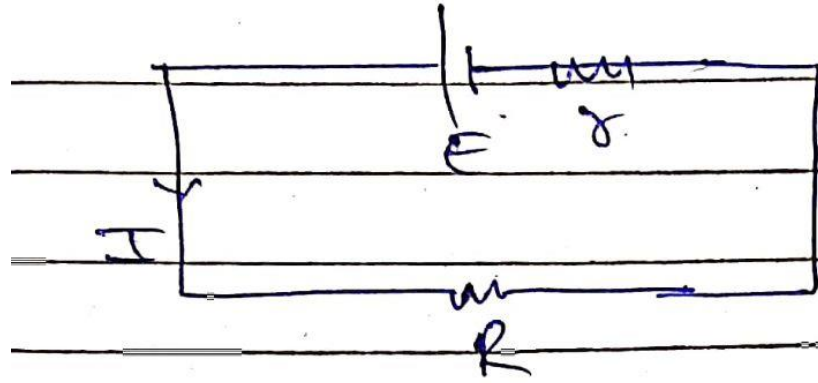

$$R_{eq} = r + R$$

$$\therefore I = \frac{E}{R + r}$$

$$V = IR$$

$$V = \frac{E}{R + r} \times R = \frac{E}{\left(\frac{R + r}{R}\right)}$$

$$V = \frac{E}{1 + \frac{r}{R}}$$

Ans. c

Solution: 13



$$V_B = 0$$

$$I_{AB} = 2 \text{ Amp} = \frac{V_A - V_B}{2}$$

$$V_A - V_B = 4$$

$$\boxed{V_A = 4 \text{ Volt}}$$

Now

from B to D

$$I = 2 \text{ A}$$

$$V_B - 2 \times 3 + 3 = V_D$$

$$V_D = V_B - 6 + 3$$


$$= 0 - 6 + 3$$

$$\boxed{V_D = -3 \text{ Volt}}$$

$$\boxed{|V_A| = 4 \text{ Volt}, |V_D| = 3 \text{ Volt}}$$

Ans. d

Solution: 14

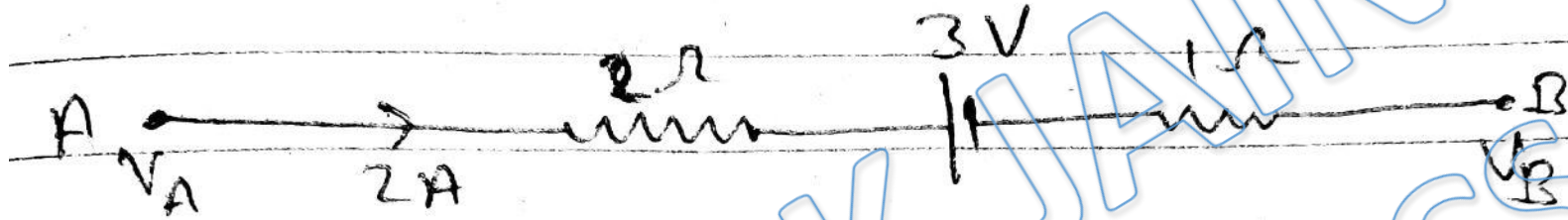

$$V_A - 2 \times 2 - 3 - 1 \times 2 = V_B$$

$$V_A - V_B = 2 \times 2 + 3 + 1 \times 2$$

$$V_A - V_B = 9 \text{ Volt}$$

Ans. b

For Video Solution of this DPP, Click on below link

Video Solution  
on Website:-

<https://physicsaholics.com/home/courseDetails/55>

Video Solution  
on YouTube:-

<https://youtu.be/2tVzRIWForY>

Written Solution  
on Website:-

<https://physicsaholics.com/note/notesDetails/52>



[@Physicsaholics](#)

[@Physicsaholics\\_prateek](#)

[@NEET Physics](#)

[@IITJEE Physics](#)

[physicsaholics.com](#)



**CLICK**

Chalo Niklo