



## DPP – 4 (Current Electricity)

Video Solution on Website:-

<https://physicsaholics.com/home/courseDetails/55>


Video Solution on YouTube:-

<https://youtu.be/BXhrsfhozQ0>

Written Solution on Website:-


<https://physicsaholics.com/note/notesDetais/52>

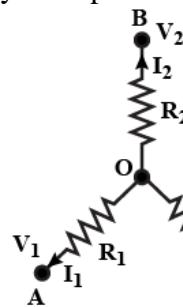Q 1. A circuit has a section ABC as shown in figure. If the potentials at points A, B and C are  $V_1$ ,  $V_2$  and  $V_3$  respectively. The potential at point O is?




- (a)  $V_1 + V_2 + V_3$
- (b)  $\left[ \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right] \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]^{-1}$
- (c)  $\left[ \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right]$
- (d) zero

Q 2. Find the current in wire AB:

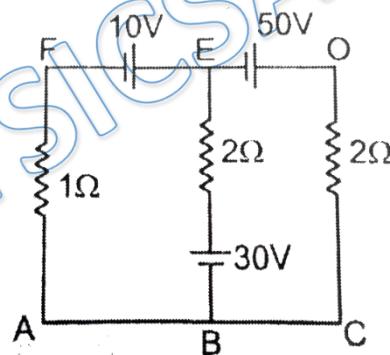


- (a) 10 amp
- (b) 12 amp
- (c) 7 amp
- (d) 4 amp

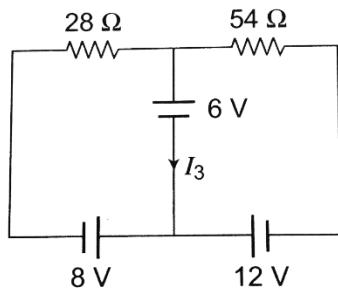Q 3. Consider the circuit shown in the figure. The magnitude of current  $I_3$  is equal to:




- (a) 5 amp      (b) 3 amp  
(c) 2 amp      (d)  $\frac{5}{6}$  amp

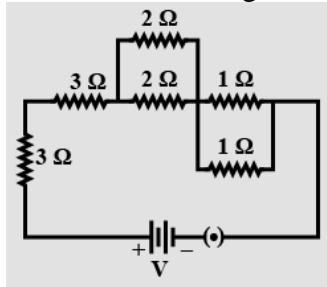Q 4. Find the equivalent resistance of the following circuit.




- (a)  $\frac{15}{2}$  Ω      (b)  $\frac{13}{2}$  Ω  
(c) 7 Ω      (d) 12 Ω

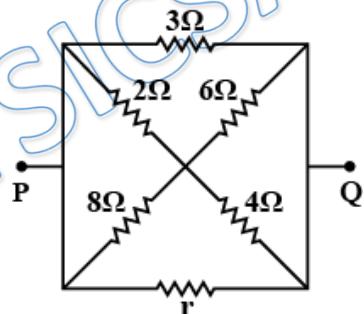Q 5. In the network shown, the equivalent resistance between P and Q is  $\frac{4}{3}$  Ω. Hence the value of r is:



- (a) 3 Ω      (b) 4 Ω  
(c) 5 Ω      (d) 6 Ω

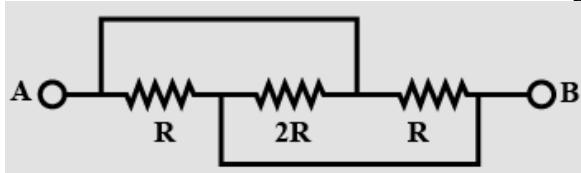
Q 6. The effective equivalent resistance between A and B in the figure, is?



- (a)  $\frac{3}{2}R$       (b)  $\frac{2}{3}R$   
(c)  $\frac{2}{5}R$       (d)  $2R$




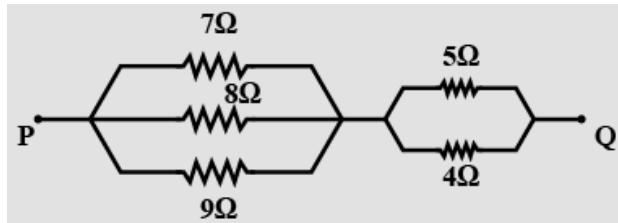Q 7. For the circuit given below, calculate the equivalent resistance between the points P and Q:



- (a)  $3.56 \Omega$   
(b)  $2.56 \Omega$   
(c)  $4.86 \Omega$   
(d)  $7.26 \Omega$

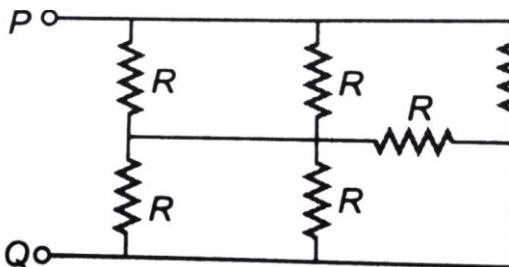Q 8. In the circuit shown in figure  $R = 55\Omega$  the equivalent resistance between the point P and Q is:




- (a)  $30 \Omega$   
(b)  $35 \Omega$   
(c)  $55 \Omega$   
(d)  $25 \Omega$

Q 9. A wire of resistance R is cut into n equal parts. These parts are then connected in parallel. The equivalent resistance of combination will be:

- (a)  $nR$   
(b)  $\frac{R}{n}$   
(c)  $\frac{n}{R}$   
(d)  $\frac{R}{n^2}$

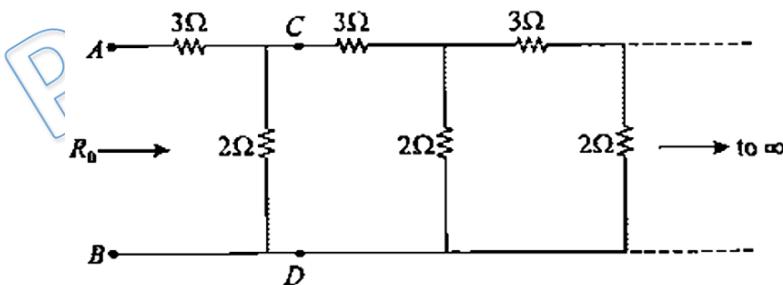Q 10. Find the equivalent resistance of the infinite ladder circuit shown in figure across terminals A and B :




- (a)  $\frac{3+\sqrt{33}}{2}$   
(b)  $\frac{3+\sqrt{35}}{2}$   
(c)  $\frac{2+\sqrt{35}}{3}$   
(d)  $\frac{2+\sqrt{33}}{3}$

Q 11. The equivalent resistance between A and B is:




# Physicsaholics

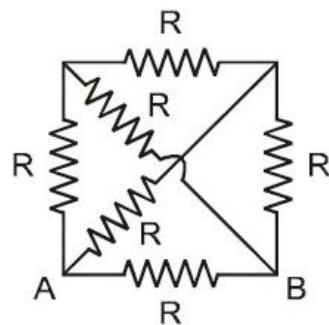




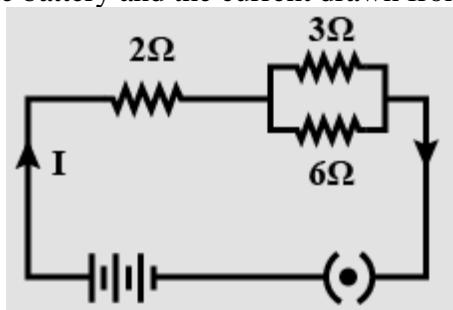
Q 12. In the given electric circuit, the current flowing through 3 ohm resistor is 1 ampere. Find the voltage of the battery and the current drawn from it:



- (a) 6 V, 1 amp      (b) 4 V, 1.5 amp  
(c) 6 V, 1.5 amp      (d) 4 V, 1 amp

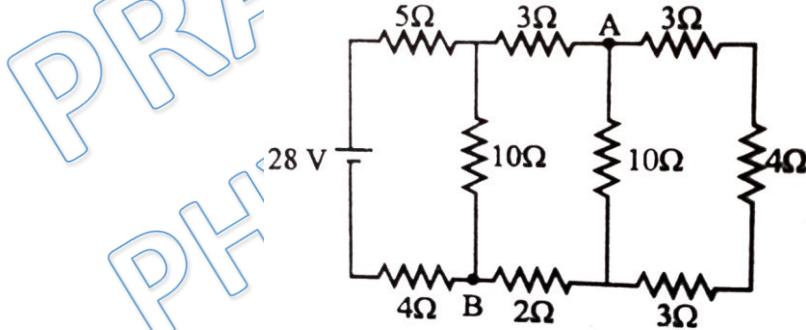**Q 13.** Consider the circuit shown in the figure:



- (a) the current in the  $5\Omega$  resistor is 2A
  - (b) the current in the  $5\Omega$  resistor is 1A
  - (c) the potential difference  $V_A - V_B$  is 10V
  - (d) the potential difference  $V_A - V_B$  is 5V



# PRATEEK JAIN

# PHYSICSAHOLICS

## Answer Key

<b>Q.1 b</b>	<b>Q.2 a</b>	<b>Q.3 d</b>	<b>Q.4 a</b>	<b>Q.5 d</b>
<b>Q.6 c</b>	<b>Q.7 c</b>	<b>Q.8 d</b>	<b>Q.9 d</b>	<b>Q.10 a</b>
<b>Q.11 b</b>	<b>Q.12 c</b>	<b>Q.13 a</b>		

PLUS

ICONIC \*

- India's Best Educators
- Interactive Live Classes
- Structured Courses & PDFs
- Live Tests & Quizzes
- Personal Coach
- Study Planner

24 months      ₹2,333/mo  
No cost EMI      ₹56,000 >

18 months      ₹2,625/mo  
No cost EMI      ₹47,250 >

12 months      ₹3,208/mo  
No cost EMI      ₹38,500 >

6 months      ₹4,667/mo  
No cost EMI      ₹28,000 >

To be paid as a one-time payment

[View all plans](#)



Add a referral code

APPLY

# PHYSICSLIVE

PLUS

ICONIC \*

- India's Best Educators
- Interactive Live Classes
- Structured Courses & PDFs
- Live Tests & Quizzes
- Personal Coach
- Study Planner

24 months      ₹2,100/mo  
No cost EMI      +10% OFF ₹50,400 >

18 months      ₹2,363/mo  
No cost EMI      +10% OFF ₹42,525 >

12 months      ₹2,888/mo  
No cost EMI      +10% OFF ₹34,650 >

6 months      ₹4,200/mo  
No cost EMI      +10% OFF ₹25,200 >

To be paid as a one-time payment

[View all plans](#)



Awesome! PHYSICSLIVE code applied




# **Written Solution**

**DPP-4 Current Electricity: Kirchhoff's Voltage Law, Series & Parallel combination of resistance and Wheatstone bridge**

**By Physicsaholics Team**

Solution: 1

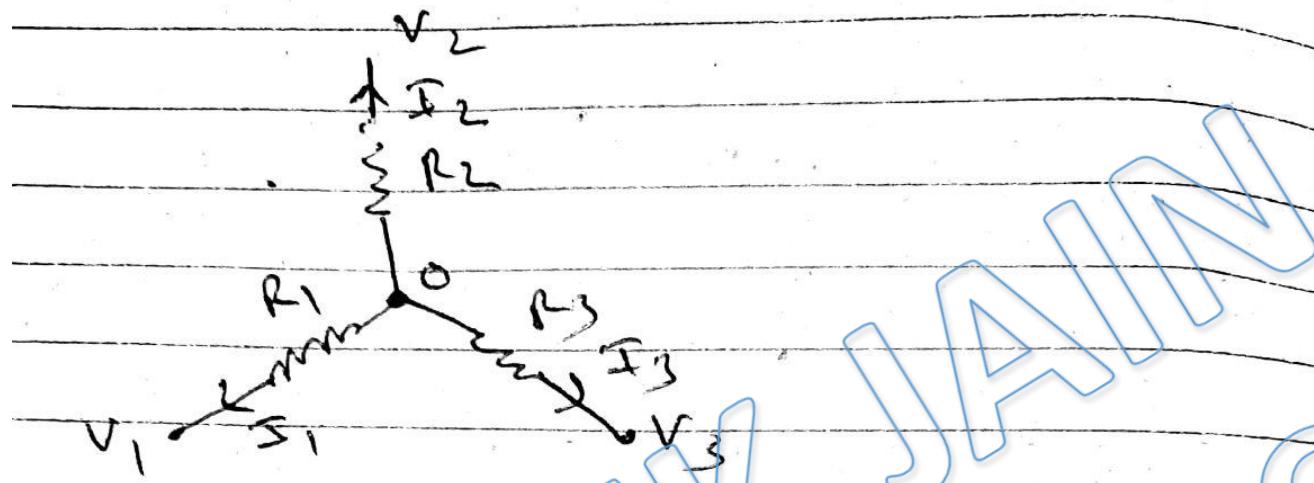

at node 'O'

$$I_1 + I_2 + I_3 = 0$$

$$\frac{V_0 - V_1}{R_1} + \frac{V_0 - V_2}{R_2} + \frac{V_0 - V_3}{R_3} = 0$$


$$\frac{V_0}{R_1} + \frac{V_0}{R_2} + \frac{V_0}{R_3} - \frac{V_1}{R_1} - \frac{V_2}{R_2} - \frac{V_3}{R_3} = 0$$

$$V_0 \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$

$$V_0 = \left[ \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right] \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]$$

Ans. b

Solution: 2

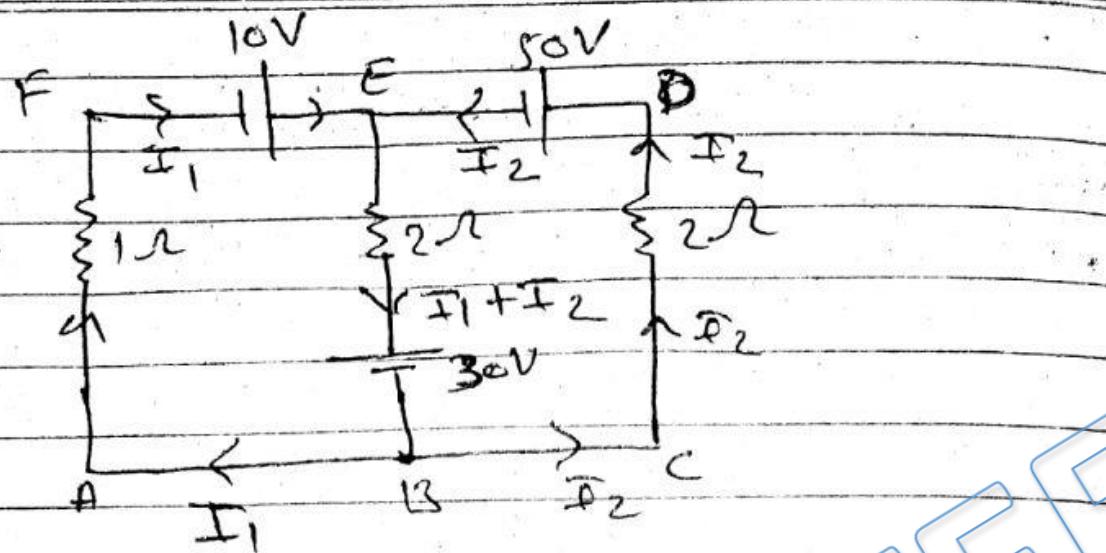

in loop AF $\subset$ B A

$$-I_1 \times 1 + 10 - (I_1 + I_2) \times 2 - 30 = 0$$

$$-I_1 - 2I_1 + 2I_2 = 20$$

$$2I_2 - 3I_1 = 20 \quad \text{--- (1)}$$

in loop BCD $\subset$ B

$$-I_2 \times 2 - 50 - (I_1 + I_2) \times 2 - 30 = 0$$

$$-2I_2 - 50 - 2I_1 - 2I_1 - 30 = 0$$

$$-4I_2 - 2I_1 = 80 \quad \text{--- (2)}$$

from eq ① & ②


$$I_1 = 10 \text{ amp}$$

current in wire AB =  $I_1$

$$\boxed{I_1 = 10 \text{ amp}}$$

Ans. a

Solution: 3

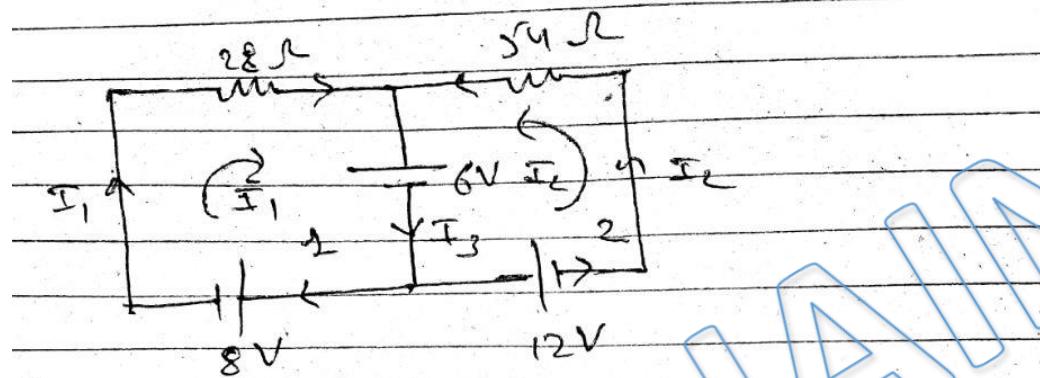

$$I_3 = I_1 + I_2$$

in Loop - 1

$$-8 - 28I_1 - 6 = 0$$

$$I_1 = -\frac{14}{28} = -\frac{1}{2} \text{ Amp.} \quad \textcircled{1}$$

in Loop - 2

$$-12 - 54I_2 - 6 = 0$$

$$I_2 = -\frac{18}{54} = -\frac{1}{3} \text{ Amp.} \quad \textcircled{2}$$



$$I_3 = I_1 + I_2 = -\frac{1}{2} - \frac{1}{3} = -\frac{5}{6} \text{ amp.}$$

$$|I_3| = \frac{5}{6} \text{ Amp}$$

-ve sign shows that the direction  
of current will be opposite to  
that is assumed.




Ans. d

Solution: 4

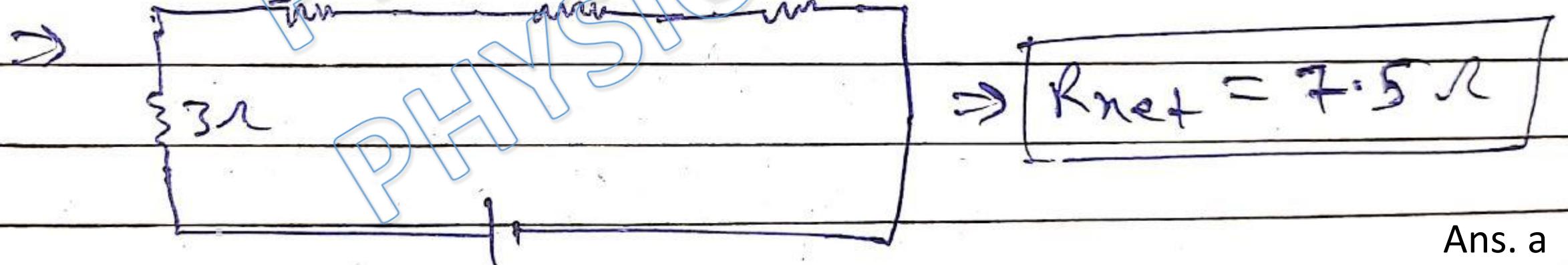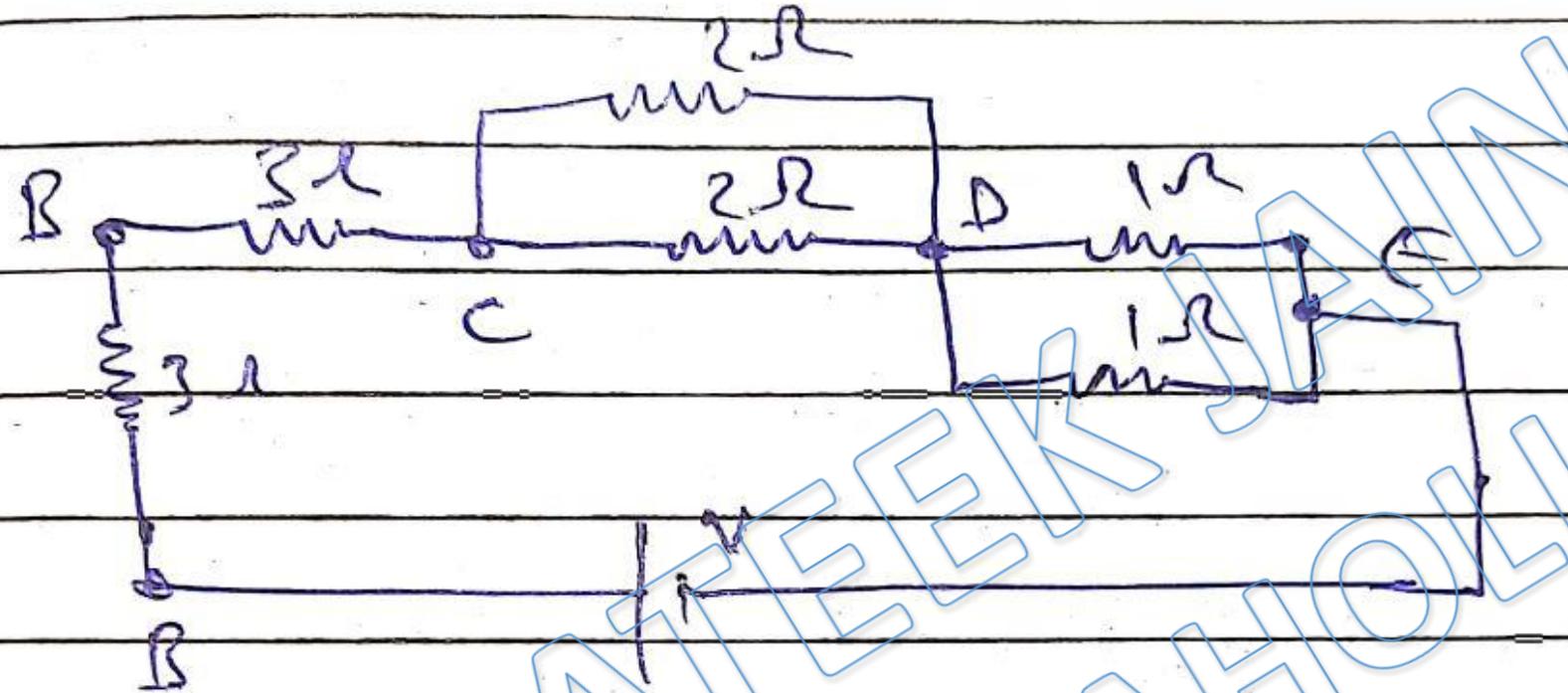

Ans. a

Solution: 5

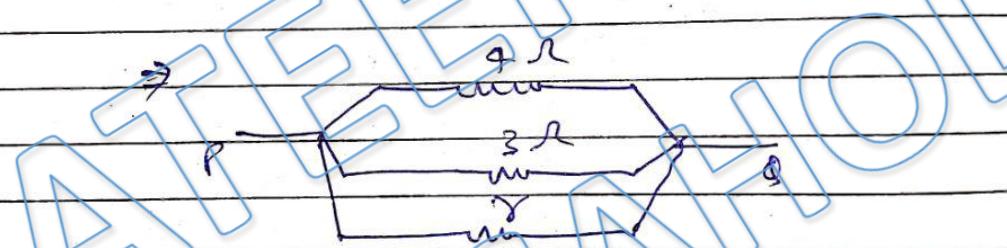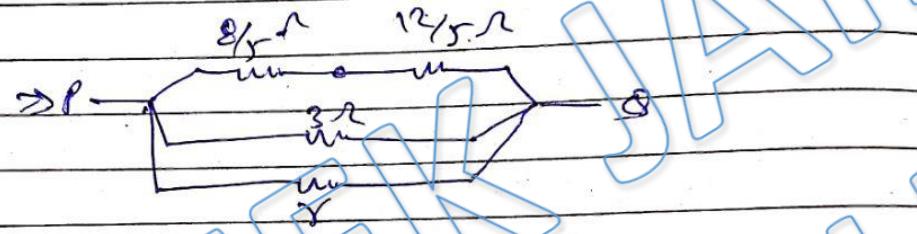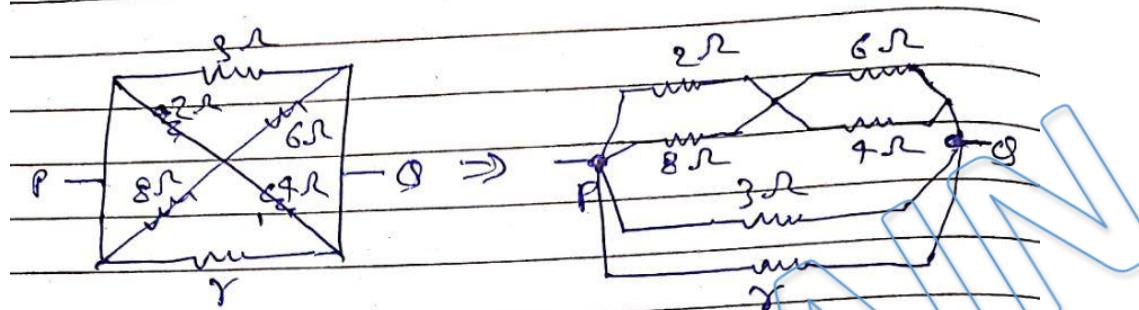

$$R_{net} = \frac{4}{3} \Omega$$

$$R_{net} = \frac{1}{a} + \frac{1}{3} + \frac{1}{d}$$

$$\frac{3}{4} = \frac{1}{a} + \frac{1}{3} + \frac{1}{d}$$


$$\frac{3}{4} = \frac{7}{12} + \frac{1}{d}$$

$$r = 6\Omega$$

PRACTICE PHYSICS  
PHYSICS


Ans. d

Solution: 6

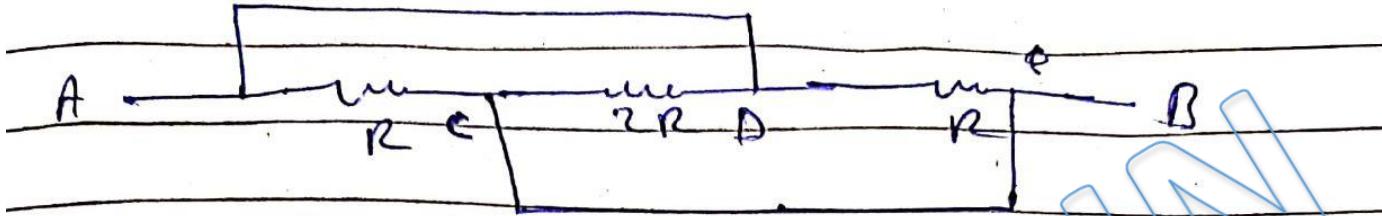

$$V_A = V_D$$

$$V_C = V_B$$

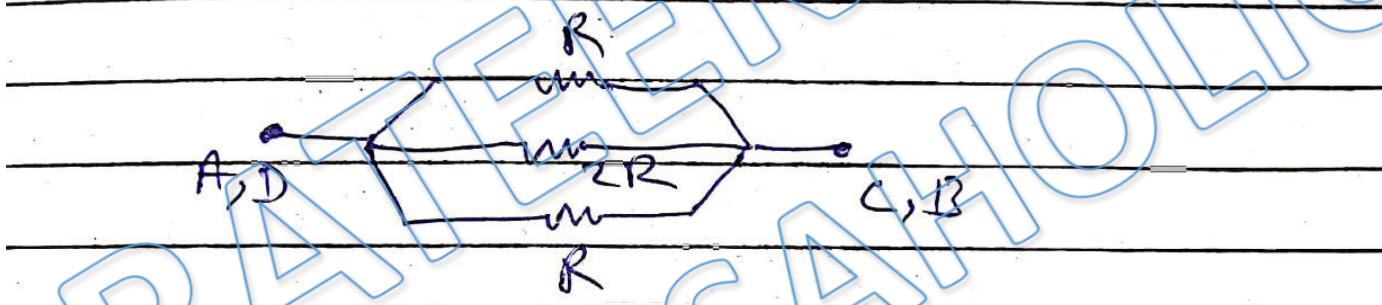


$$\frac{1}{R_{net}} = \frac{1}{R} + \frac{1}{2R} + \frac{1}{R}$$

$$= \frac{2}{2R} + \frac{1}{2R} + \frac{3}{2R}$$

$$R_{net} = \frac{2R}{5}$$

Ans. c

Solution: 7

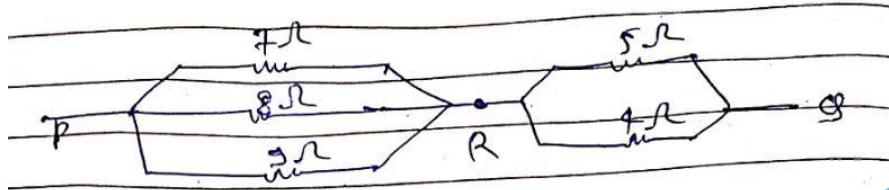

$$R_{PR} = ?$$

$$\frac{1}{R_{PR}} = \frac{1}{7} + \frac{1}{8} + \frac{1}{5}$$

$$R_{PR} = \frac{7 \times 8 \times 9}{8 \times 9 + 7 \times 9 + 7 \times 8}$$

$$R_{PR} = \frac{504}{191} \Omega$$

$$R_{RS} = \frac{4 \times 5}{4 + 5} = \frac{20}{9} \Omega$$

$$R = R_{PR} + R_{RS}$$
$$= \frac{504}{191} + \frac{20}{9}$$




$$R = \frac{3820 + 4536}{1719} \Omega$$

$$R = \frac{8356}{1719} \Omega$$

$$R = 4.86 \Omega$$

Ans. c

Solution: 8

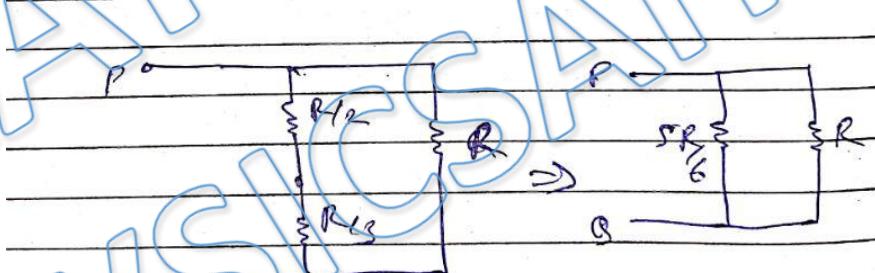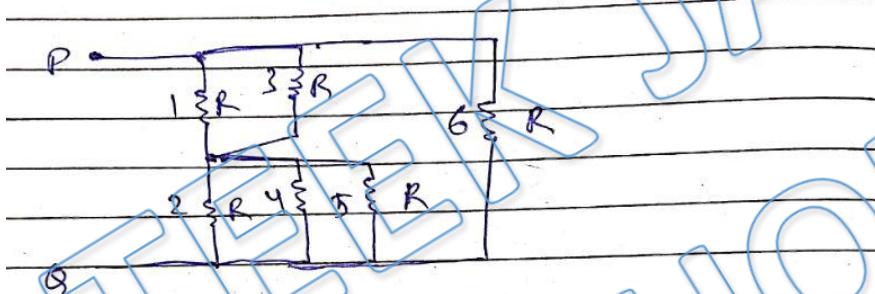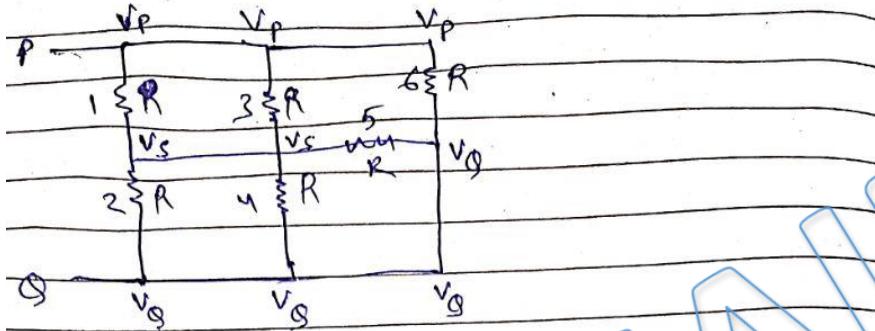

$$R_{eq} = \frac{R \times 5R/6}{R + 5R/6} = \frac{5}{11} R$$

$$R_{eq} = \frac{5 \times 55}{11}$$

$$\boxed{R_{eq} = 25 \Omega}$$

Ans. d

Solution: 9

$$R = \frac{\rho l}{A}$$

$$R \propto l$$

when wire is cutted in  $n$  parts  
then length of one part =  $\frac{l}{n}$   
 $\therefore$  resistance ( $r$ ) of one part  $r = ?$

$$\frac{R}{n} = \frac{l}{\frac{l}{n}} = n$$

$$r = \frac{R}{n}$$

Wire connected in parallel



$$R_{parallel} = \frac{1}{r} + \frac{1}{r} + \frac{1}{r} + \dots + n \text{ times}$$


$$= \frac{n}{r}$$

$$R_{parallel} = \frac{R}{n} = \frac{R/n}{n}$$

$$R_{parallel} = \frac{R}{n^2}$$


Ans. d

Solution: 10

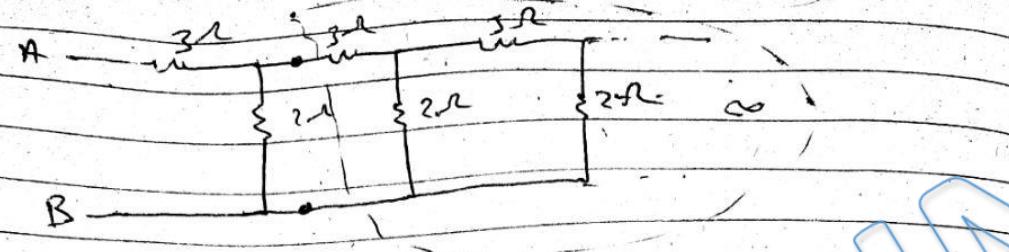

Let net resistance across  
AB is  $n$

then:

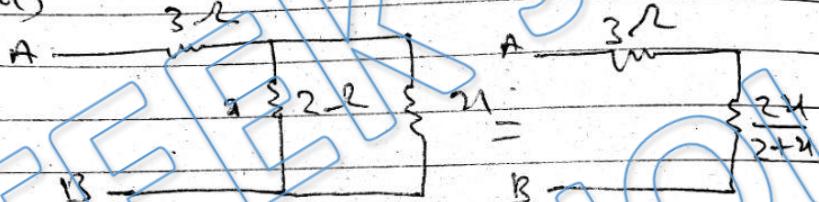

$$R_{AB} = n = \frac{3 + 2n}{2+n}$$

$$n = \frac{G + 5n}{2+n}$$

$$2n + n^2 = G + 5n$$

$$n^2 - 3n - G = 0$$




$$n = \frac{-(-3) \pm \sqrt{(-3)^2 - 4 \times 1 \times (-G)}}{2 \times 1}$$

$$= \frac{3 \pm \sqrt{9 + 2G}}{2}$$

$$\boxed{n = \frac{3 + \sqrt{33}}{2} \Omega}$$

Ans. a


Solution: 11

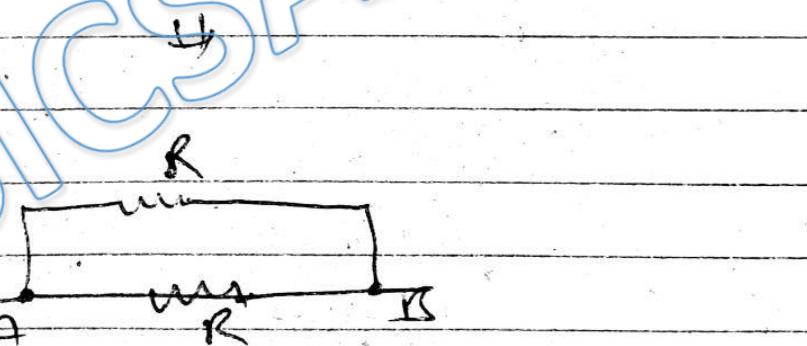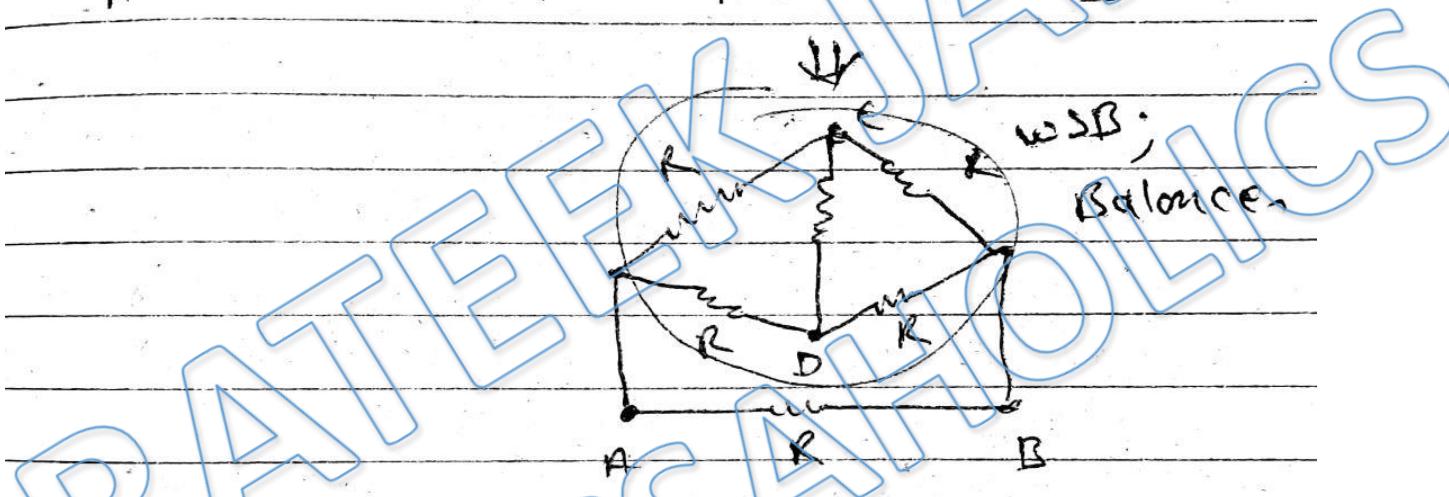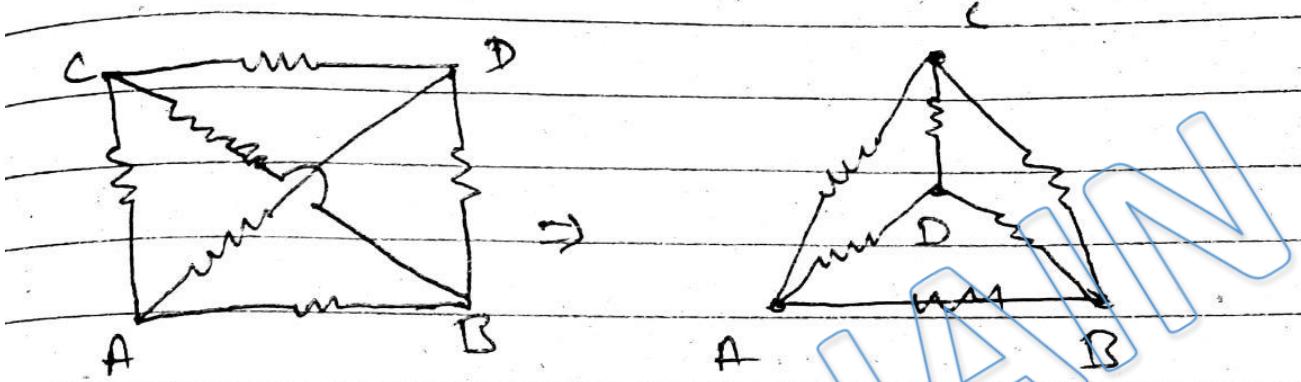

$$R_{AB} = R_{12}$$

Ans. b

Solution: 12

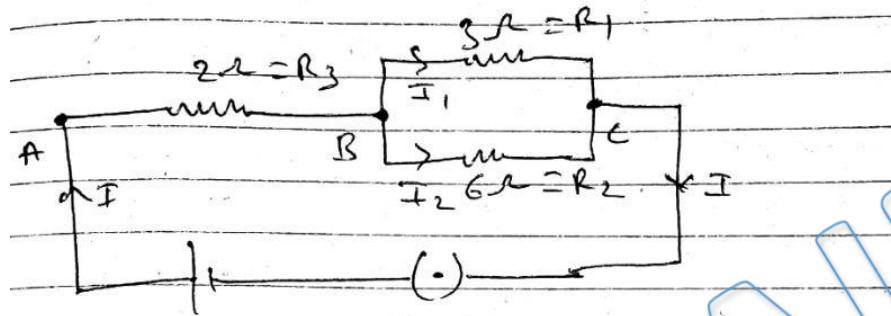

Voltage

Potential difference across  $R_1$  &  
 $R_2$  are same.

$$I_1 = 2 \text{ Amp}$$

$$V = I_1 R_1 = I_2 R_2$$

$$1 \times 3 = I_2 \times 6$$

$$I_2 = \frac{1}{6} \text{ Amp}$$

$$I = I_1 + I_2$$

$$I = 1 + \frac{1}{6} \Rightarrow I = \frac{7}{6} \text{ Amp}$$

$$R_{eq} = \frac{2 + \frac{1}{6}}{\frac{1}{3} + \frac{1}{6}}$$

$$R_{eq} = 2 + 2 = 4 \Omega$$


$$V = IR$$

$$V = \frac{3}{2} \times 4$$

$$V = 6 \text{ Volt}$$

Ans. c

Solution: 13

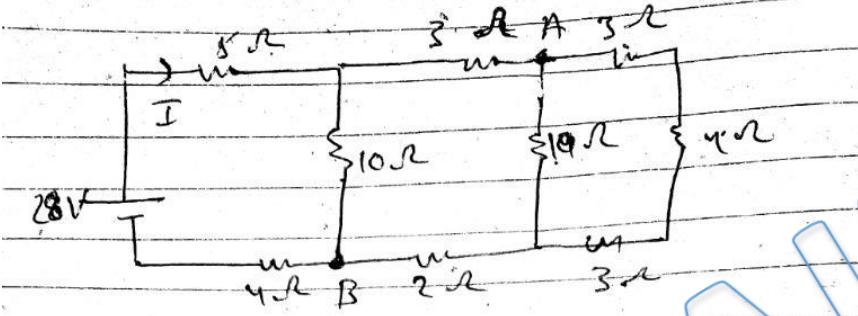

current in  $5\Omega$  resistor

$$i_s = I$$

$$I = \frac{28}{R_{eq}}$$

$$R_{eq} = 14\Omega$$

$$I = \frac{28}{14}$$

$$I = 2 \text{ Amp}$$



~~A → C → B~~

$$V_A + 1 \times 3 - 1 \times 10 = V_B$$

$$V_A - V_B = 10 - 3$$

$$\boxed{V_A - V_B = 7 \text{ volt}}$$

Ans. a

**For Video Solution of this DPP, Click on below link**

**Video Solution  
on Website:-**

<https://physicsaholics.com/home/courseDetails/55>

**Video Solution  
on YouTube:-**

<https://youtu.be/BXhrsfhozQ0>

**Written Solution  
on Website:-**

<https://physicsaholics.com/note/notesDetails/52>



SUBSCRIBE



[@Physicsaholics](#)

[@Physicsaholics\\_prateek](#)

[@NEET\\_Physics](#)  
[@IITJEE\\_Physics](#)

[physicsaholics.com](#)



**CLICK**

chalon Niklo