

## DPP – 5 (Current Electricity)

Video Solution on Website:-

<https://physicsaholics.com/home/courseDetails/55>


Video Solution on YouTube:-

<https://youtu.be/Mj1GqNdb4CQ>

Written Solution on Website:-


<https://physicsaholics.com/note/notesDetails/52>

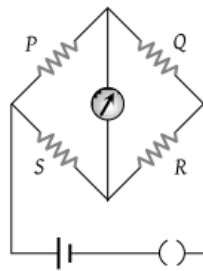- Q 1. In a Wheatstone bridge circuit  $P = 2\ \Omega$ ,  $Q = 3\ \Omega$ ,  $R = 6\ \Omega$  and  $S = 8\ \Omega$ . In order to obtain balance, shunt resistance across  $S$  must be:




- (a)  $2\ \Omega$             (b)  $3\ \Omega$   
 (c)  $6\ \Omega$             (d)  $8\ \Omega$

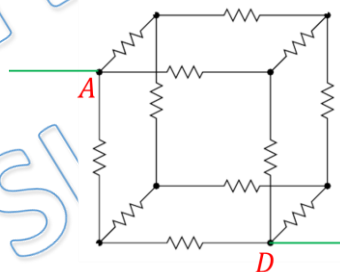- Q 2. If all the resistors are identical having resistance  $R\ \Omega$ . Find equivalent resistance between A and D?




- (a)  $\frac{7R}{12}$             (b)  $\frac{4R}{3}$   
 (c)  $\frac{3R}{4}$             (d)  $\frac{12R}{7}$

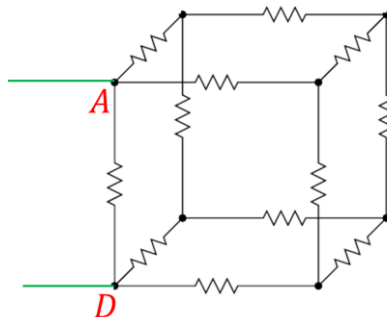- Q 3. If all the resistors are identical having resistance  $R\ \Omega$ . Find equivalent resistance between A and D?




- (a)  $\frac{7R}{12}$                       (b)  $\frac{4R}{3}$   
 (c)  $\frac{3R}{4}$                         (d)  $\frac{12R}{7}$

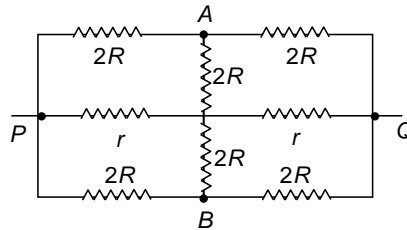Q 4. The effective resistance between point  $P$  and  $Q$  of the electrical circuit shown in the figure is




- (a)  $2Rr / (R + r)$   
 (b)  $8R(R + r) / (3R + r)$   
 (c)  $2r + 4R$   
 (d)  $5R / 2R + 2r$

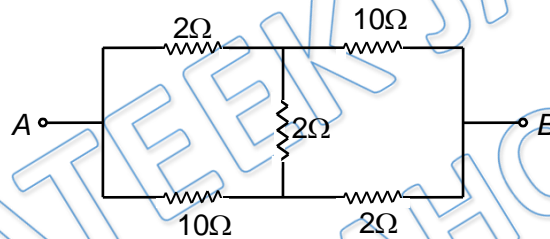Q 5. Find the effective resistance (in ohm) between the points  $A$  and  $B$  of the following network.




- (a) 4                              (b) 8  
 (c) 13                            (d) 10

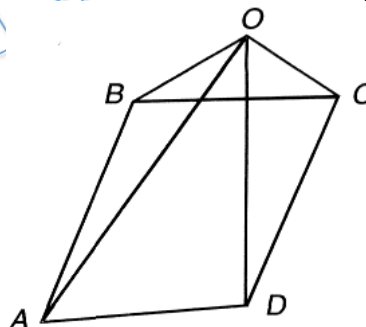Q 6. Eight identical resistance  $r$  each are connected as shown. If equivalent resistance between  $AD$  is  $R_1$  and that between  $AC$  is  $R_2$  then  $\frac{R_1}{R_2}$




- (a) 4 : 5  
 (b) 2 : 3  
 (c) 3 : 5  
 (d) 1 : 3

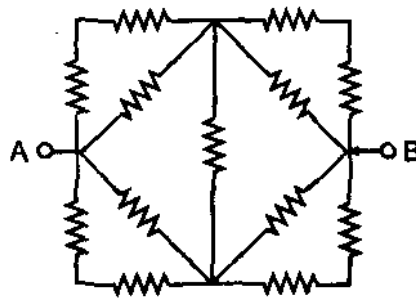Q 7. Thirteen resistors each of resistance  $H$  are connected in the circuit as shown in figure. Net resistance between  $A$  and  $B$  is:




- (a)  $2R$                       (b)  $4R/3$   
 (c)  $2R/3$                     (d)  $R$

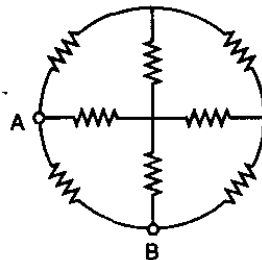Q 8. Eight resistances each of resistance  $50\Omega$  are connected in the circuit as shown in figure. The equivalent resistance between A and B is:




- (a)  $\frac{80}{3}\Omega$                       (b)  $\frac{16}{3}\Omega$   
 (c)  $\frac{150}{7}\Omega$                     (d)  $\frac{19}{2}\Omega$

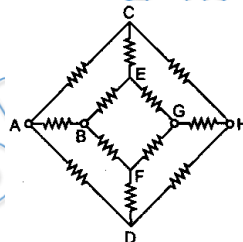Q 9. Twelve resistors each of resistance  $1\Omega$  are connected in the circuit shown in figure. Net resistance between points A and H would be




- (a)  $\frac{5}{3}\Omega$   
 (b)  $1\Omega$   
 (c)  $\frac{3}{4}\Omega$   
 (d)  $\frac{7}{6}\Omega$

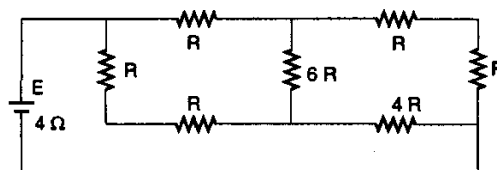Q 10. A battery of internal resistance  $4\Omega$  is connected to the network of resistances as shown. In order that the maximum power can be delivered to the network the value of  $R$  in  $\Omega$  should be




- (a)  $\frac{4}{9}$
- (b) 2
- (c)  $\frac{8}{3}$
- (d) 18

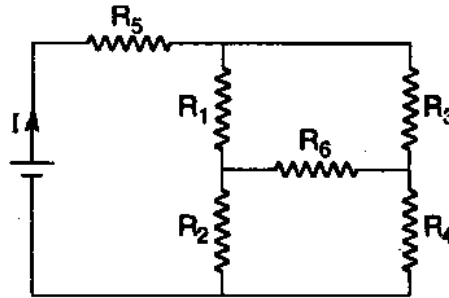Q 11. In the given circuit, it is observed that the current  $I$  is independent of the value of the resistance  $R_6$ . Then, the resistance values must satisfy




- (a)  $R_1 R_2 R_5 = R_3 R_4 R_6$
- (b)  $\frac{1}{R_5} = \frac{1}{R_6} = \frac{1}{R_1 + R_2} + \frac{1}{R_3 + R_4}$
- (c)  $R_1 R_4 = R_2 R_3$
- (d)  $R_1 R_3 = R_2 R_4$

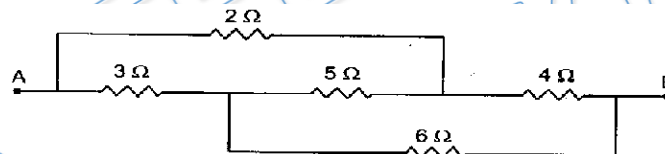Q 12. In the circuit shown, some potential difference is applied between A and B. The equivalent resistance between A and B is  $R$ .




- (a) No current flows through the 5-Ω resistor.
- (b)  $R = 15\Omega$
- (c)  $R = 12.5\Omega$
- (d)  $R = \frac{18}{5}\Omega$

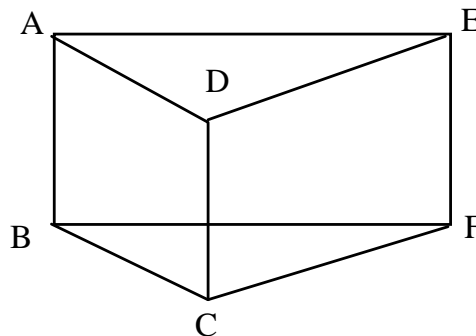Q 13. Find effective resistance between A and B, if all sides of prism have equal resistance  $R$ .




- (a)  $3R/5$                       (b)  $2R/5$   
 (c)  $R/5$                          (d)  $2R$

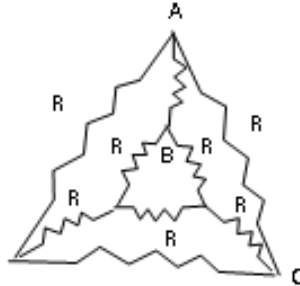Q 14. Find effective resistance between A and B, if all sides of prism have equal resistance R.



- (a)  $3R/5$                       (b)  $2R/5$   
 (c)  $R/8$                         (d)  $2R$

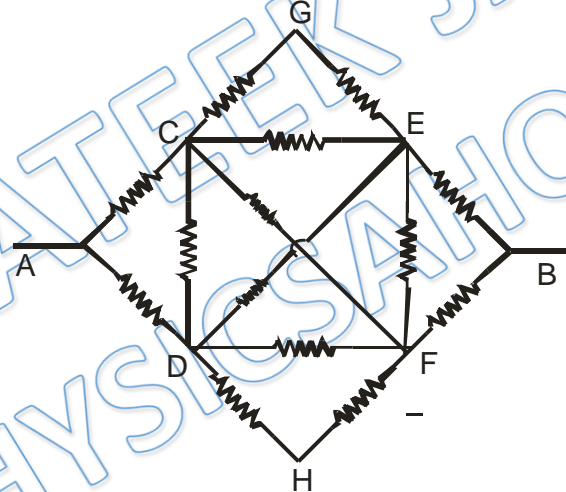Q 15. Fourteen identical resistors each of resistance  $r$  are connected as shown. The equivalent resistance between the points A and B is



- (a)  $r$   
 (b)  $14r$   
 (c)  $r/14$   
 (d)  $1.2r$



PRATEEK JAIN  
PHYSICSAHOLICS

## Answer Key

|               |                  |               |               |               |
|---------------|------------------|---------------|---------------|---------------|
| <b>Q.1 d</b>  | <b>Q.2 c</b>     | <b>Q.3 a</b>  | <b>Q.4 a</b>  | <b>Q.5 a</b>  |
| <b>Q.6 a</b>  | <b>Q.7 c</b>     | <b>Q.8 a</b>  | <b>Q.9 c</b>  | <b>Q.10 b</b> |
| <b>Q.11 c</b> | <b>Q.12 a, d</b> | <b>Q.13 a</b> | <b>Q.14 a</b> | <b>Q.15 d</b> |


PLUS **ICONIC\*\***

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

|             |           |   |
|-------------|-----------|---|
| 24 months   | ₹2,333/mo | > |
| No cost EMI | ₹56,000   |   |
| 18 months   | ₹2,625/mo | > |
| No cost EMI | ₹47,250   |   |
| 12 months   | ₹3,208/mo | > |
| No cost EMI | ₹38,500   |   |
| 6 months    | ₹4,667/mo | > |
| No cost EMI | ₹28,000   |   |

To be paid as a one-time payment

[View all plans](#)

 Add a referral code APPLY

# PHYSICSLIVE


PLUS **ICONIC\*\***

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

|             |                  |   |
|-------------|------------------|---|
| 24 months   | ₹2,100/mo        | > |
| No cost EMI | +10% OFF ₹50,400 |   |
| 18 months   | ₹2,363/mo        | > |
| No cost EMI | +10% OFF ₹42,525 |   |
| 12 months   | ₹2,888/mo        | > |
| No cost EMI | +10% OFF ₹34,650 |   |
| 6 months    | ₹4,200/mo        | > |
| No cost EMI | +10% OFF ₹25,200 |   |

To be paid as a one-time payment

[View all plans](#)

 Awesome! **PHYSICSLIVE** code applied ✗

Use code **PHYSICSLIVE** to get 10% OFF on Unacademy PLUS.

# Written Solution

**DPP-5 Current Electricity: Wheat Stone bridge,  
Symmetric circuit, Cube problems**

**By Physicsaholics Team**



Solution: 1

To balance wheat-stone bridge —


$$\frac{P}{Q} = \frac{S'}{R} \quad \text{where } S' \text{ is effective of } S \text{ \& } Y$$

$$\Rightarrow S' = \frac{PR}{Q} = \frac{2 \times 6}{3} = 4 \Omega$$

$$\Rightarrow \frac{8Y}{Y+8} = 4$$

$$\Rightarrow Y + 8 = 2Y$$

$$\Rightarrow Y = 8 \Omega$$

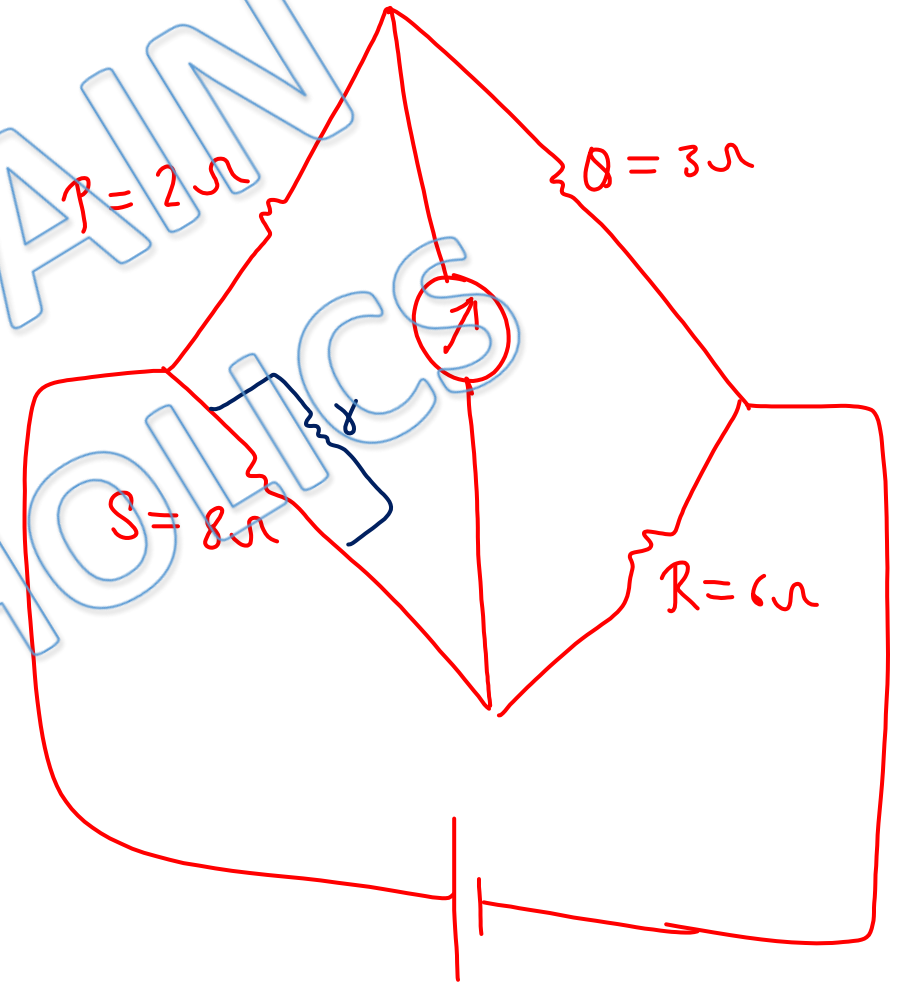

Ans. d

Solution: 2

AB & BD are reverse symmetric wires



⇒ They have equal current  $I_1$ .

⇒ Current in wire BP = 0


Similarly AC & CD are reverse

symmetric ⇒ equal current  $I_2$

AC & CD ⇒ Current in CP' = 0

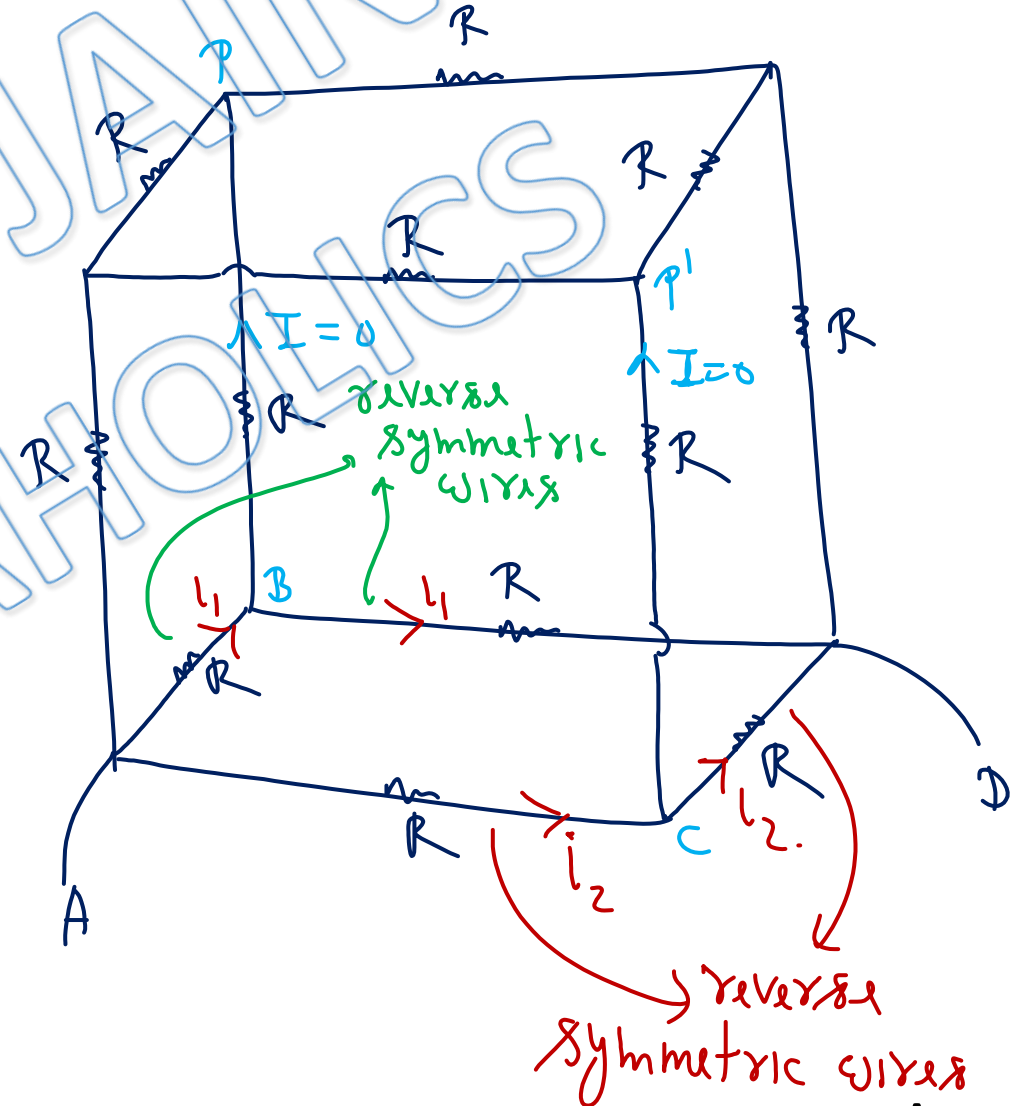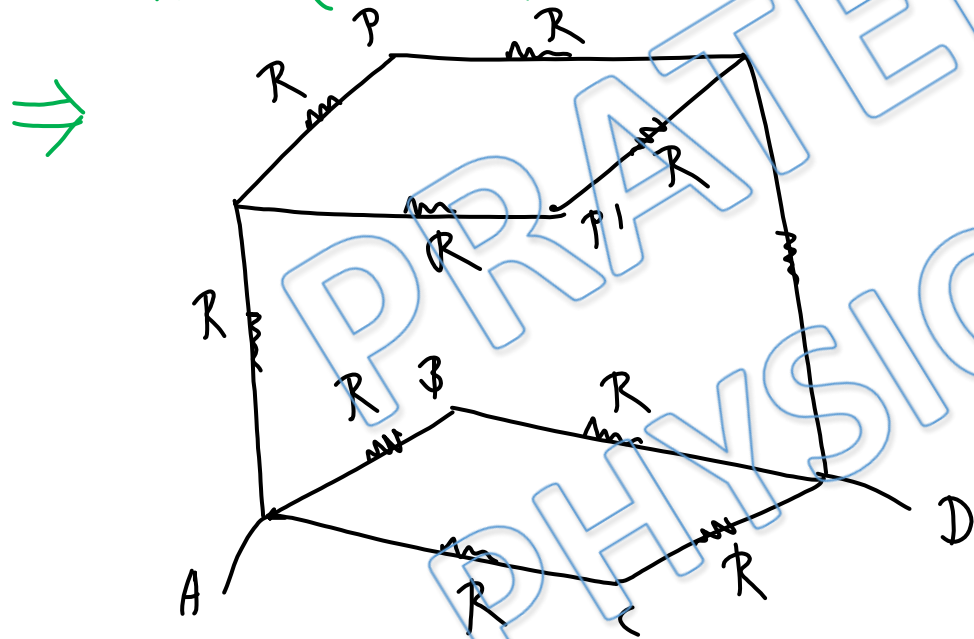

Ans. c

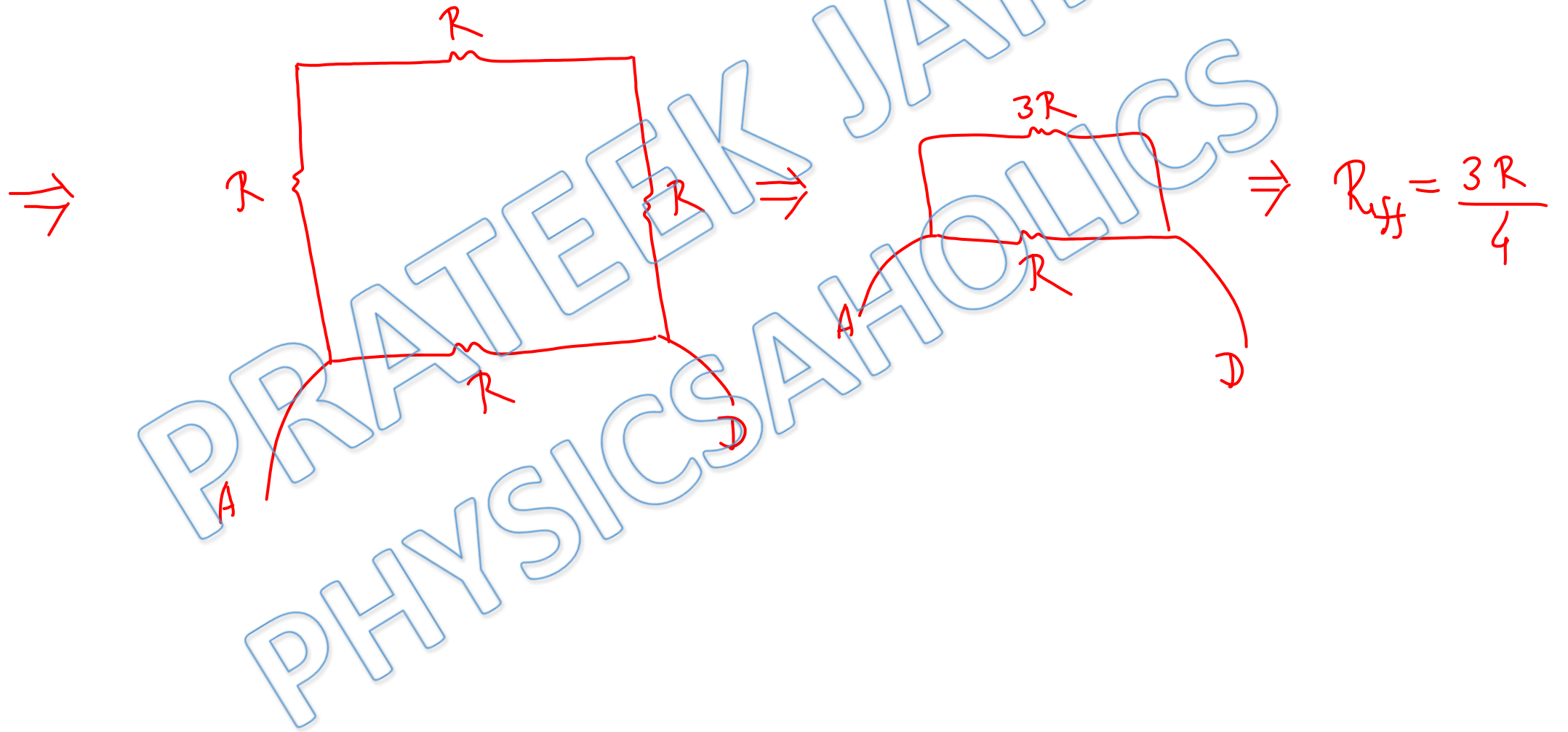



Ans. c

Solution: 3


In circuit  $P$  &  $P'$  are symmetric points  
" "  $Q$  &  $Q'$  " " " "  
symmetric points have same potential

⇒ Connect  $P$  to  $P'$ ,  $Q$  to  $Q'$  as  
shown by green wires

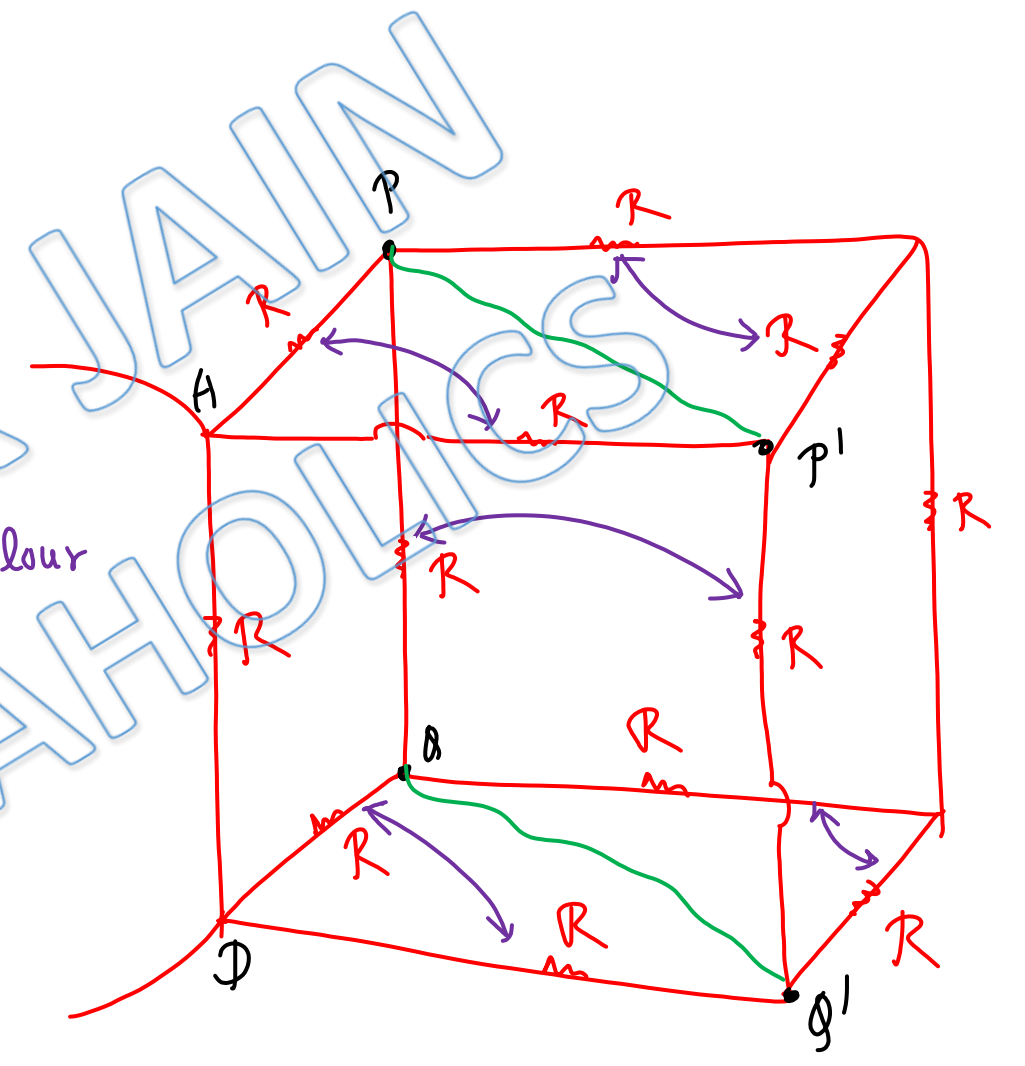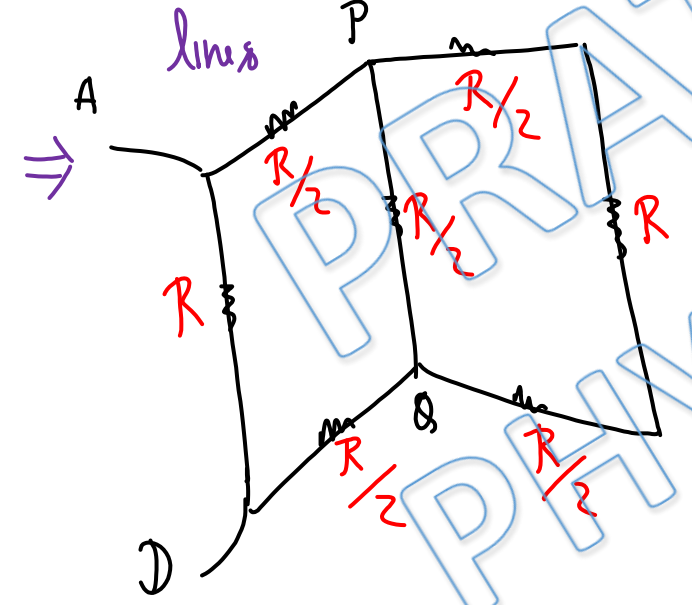⇒ Parallel wires are shown by violet colour  
lines



Ans. a


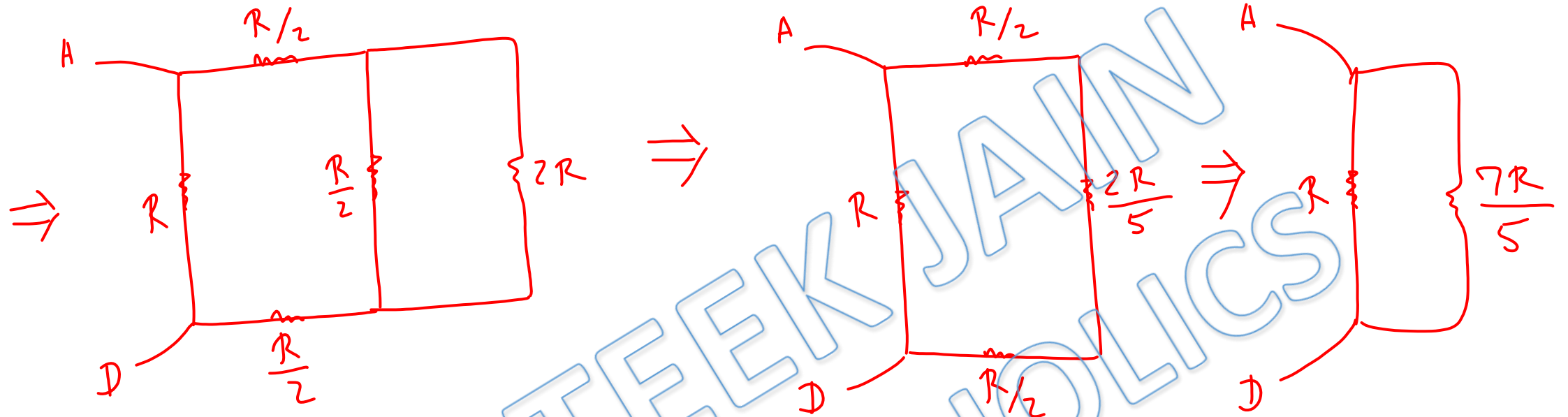


$$\Rightarrow R_{\text{eff}} = \frac{7R}{12}$$

Ans. a

Solution: 4

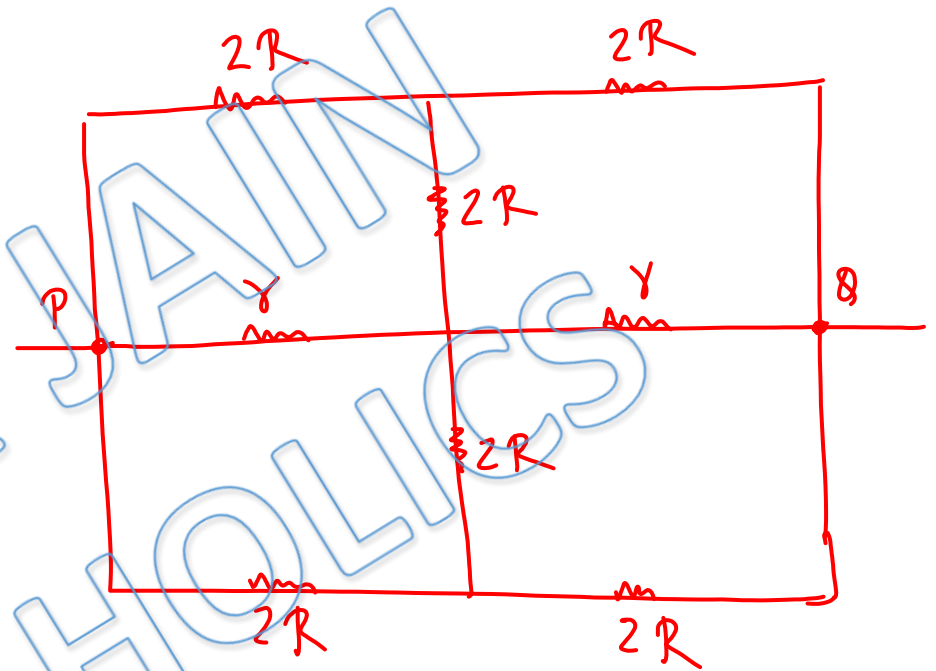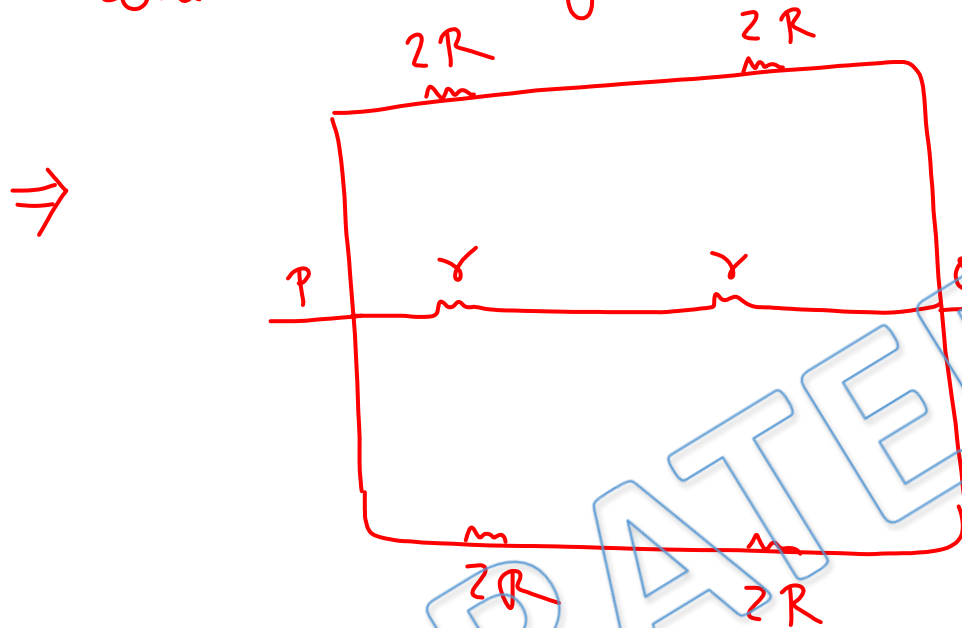This is balanced extended  
wheat stone bridge



⇒

$$\frac{1}{R_{\text{eff}}} = \frac{1}{4R} + \frac{1}{4R} + \frac{1}{2\gamma} = \frac{1}{2R} + \frac{1}{2\gamma} = \frac{\gamma + R}{2R\gamma}$$

⇒

$$R_{\text{eff}} = \frac{2R\gamma}{R + \gamma}$$

Ans. a

Solution: 5

Using symmetry we can say that

$$\begin{aligned} \text{Current in } P &= \text{Current in } P' \\ ,, ,, Q &= ,, ,, Q' \end{aligned}$$

Using KVL in loop  $abcd \rightarrow$

$$-2i_1 + 2(1-2i_1) + 10(1-i_1) = 0$$


$$\Rightarrow 12i_1 - 16i_1 = 0 \Rightarrow i_1 = \frac{3i}{4}$$

Using KVL in loop  $a'A d C B b' \rightarrow$

$$-10(1-i_1) - 2i_1 + \mathcal{E} = 0$$

$$\Rightarrow -10 \times \frac{1}{4} - 2 \times \frac{3i}{4} + \mathcal{E} = 0 \Rightarrow \mathcal{E} = \frac{16i}{4}$$

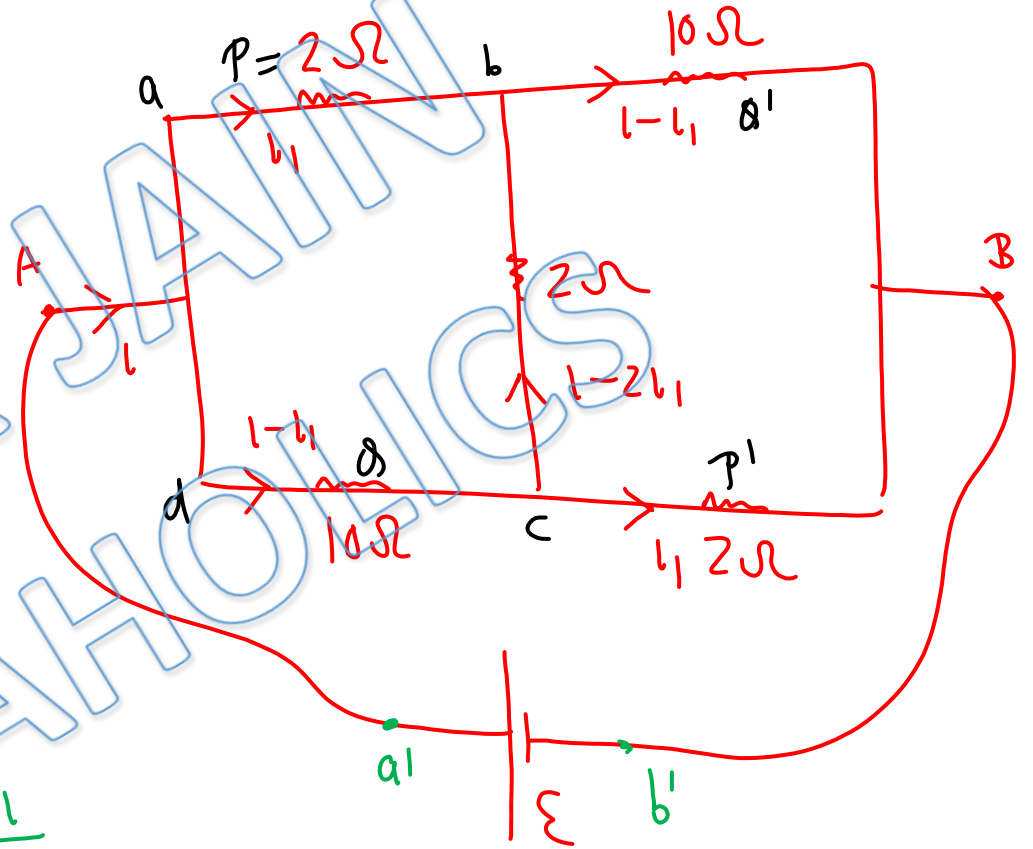
$$\Rightarrow R_{\text{eff}} = \frac{\mathcal{E}}{i} = 4\Omega$$



$$R_{\text{eff}} = \frac{\mathcal{E}}{i}$$




Ans. a

Solution: 6

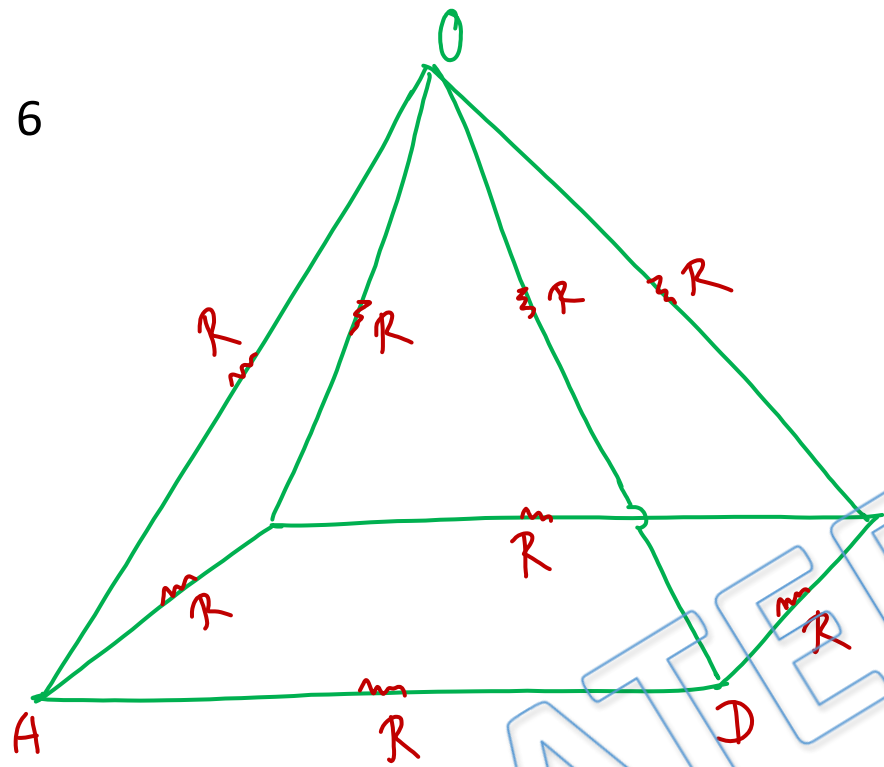

$$R_1 = \frac{8R/3 \times 2R/3}{8R/3 + 2R/3} = \frac{16R/9}{10R/3} = \frac{16R}{30} = \frac{8R}{15}$$


⇒

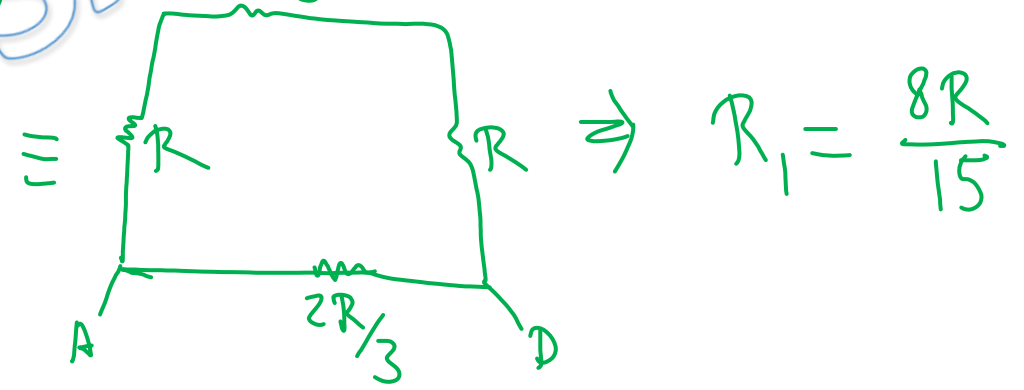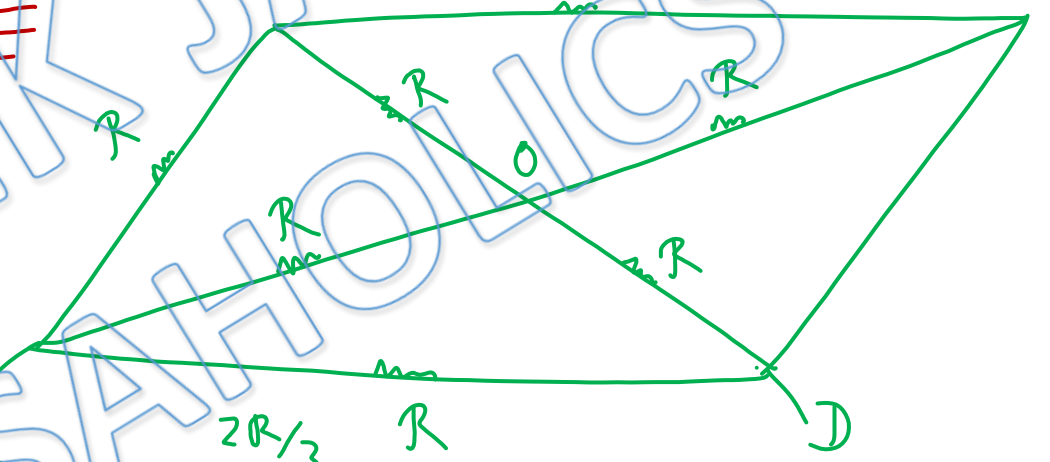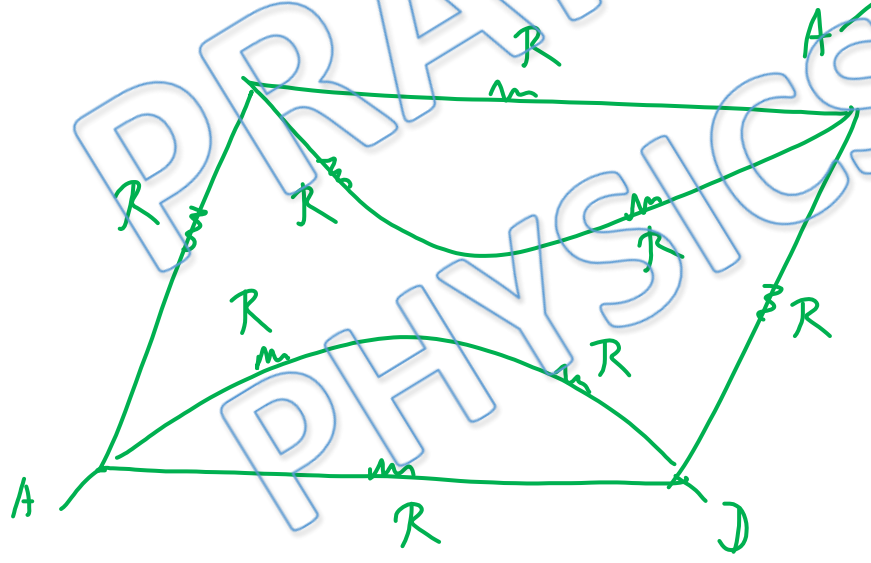


Ans. a




Using Concept of Symmetry,  $I = 0$

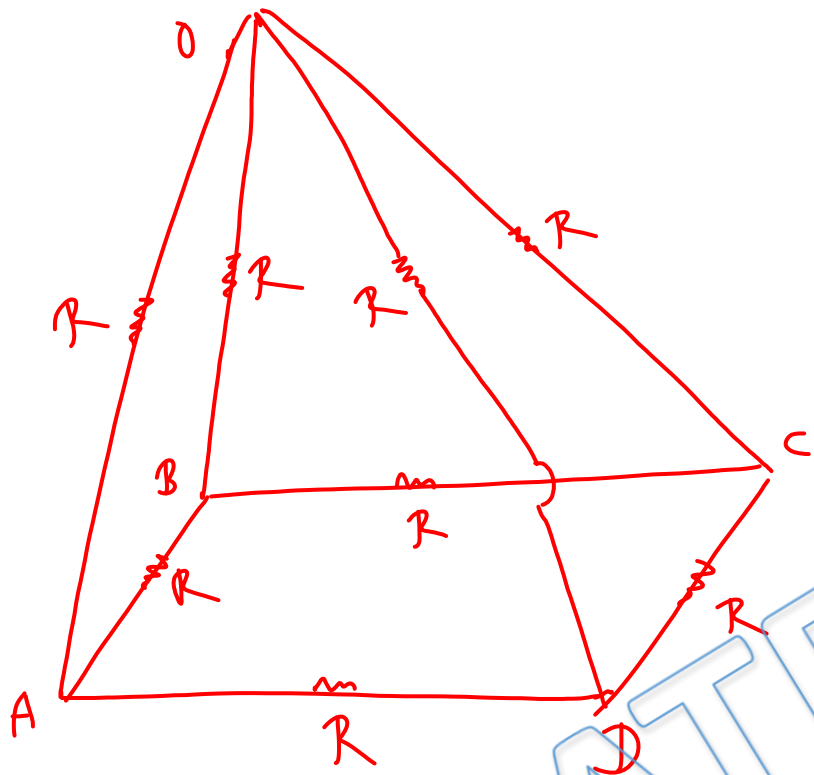

≡

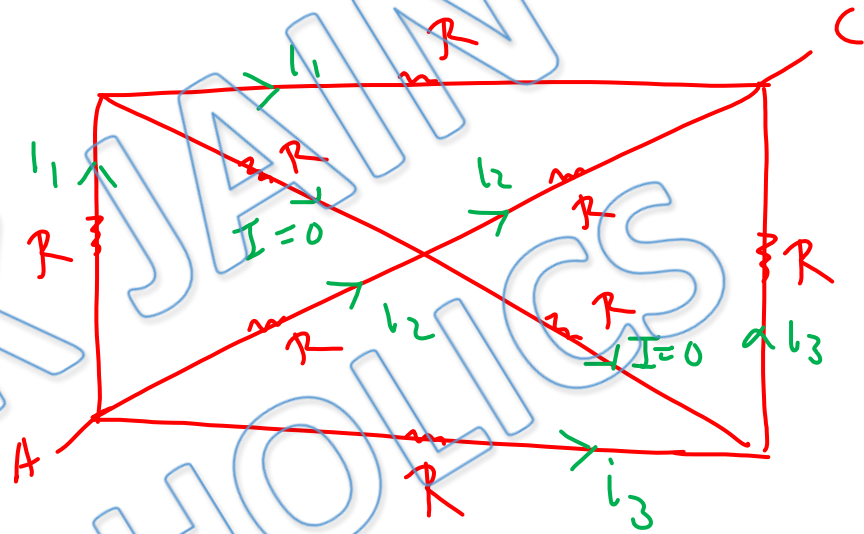

≡

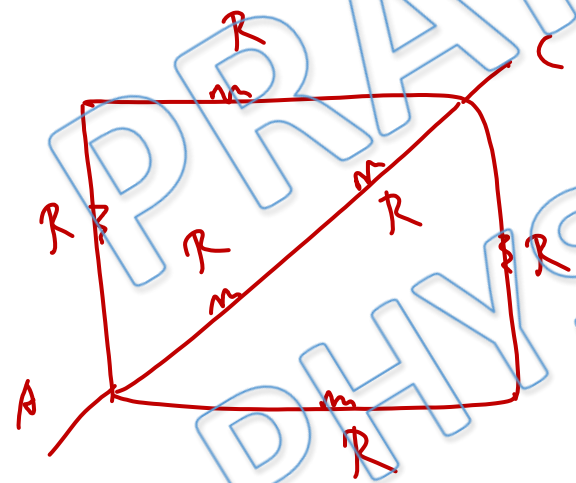


≡

$$R_2 = \frac{2R}{3}$$


$$\Rightarrow \frac{R_1}{R_2} = \frac{8R}{\frac{15}{5}} \times \frac{3}{2R} = \frac{4}{5}$$

Ans. a



Solution: 7

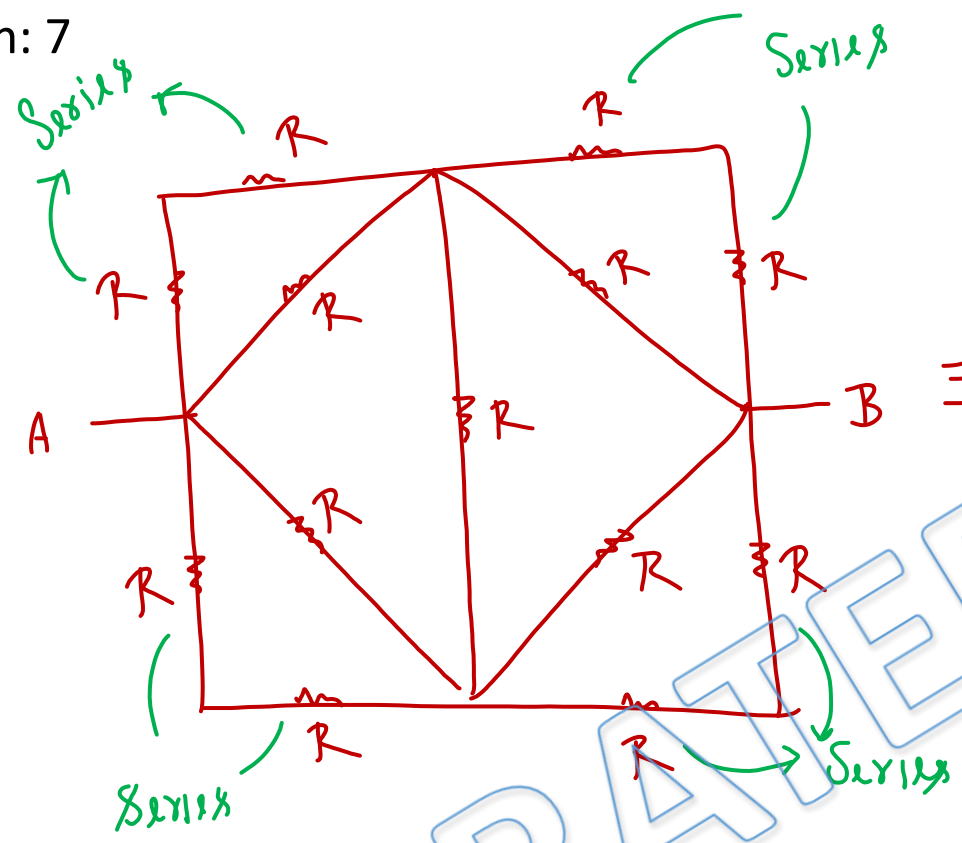

$\equiv$

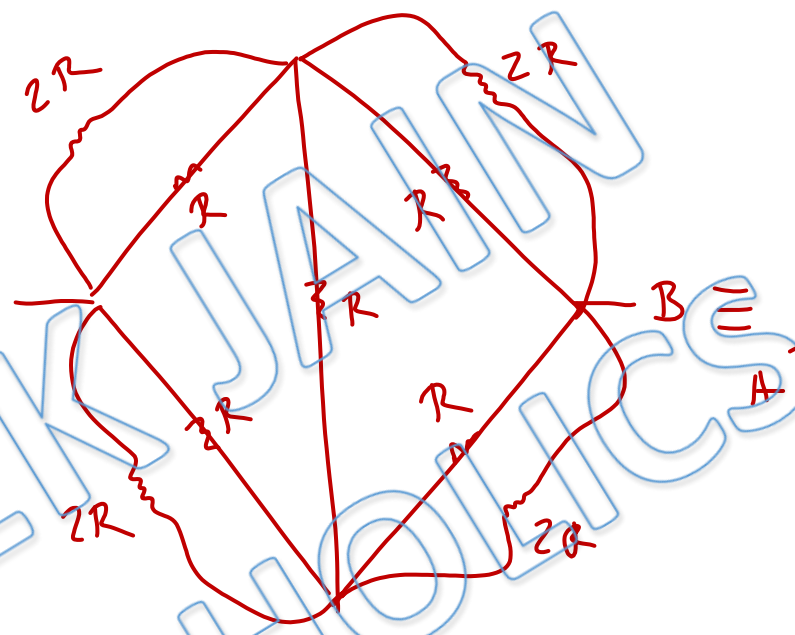


balanced  
wheat stone  
bridge

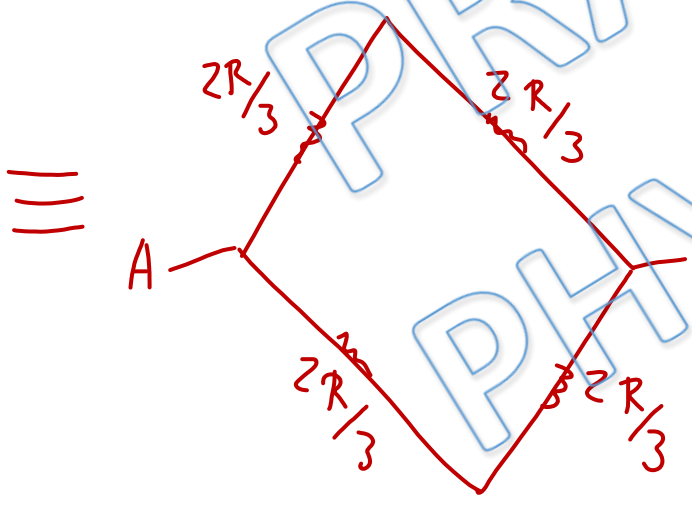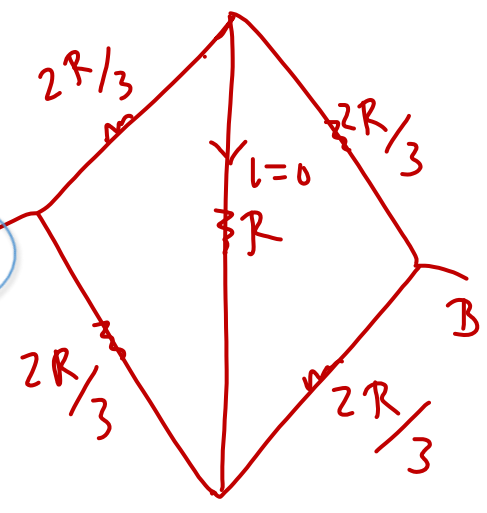

$\Rightarrow R_{AB} = \frac{2R}{3}$


Ans. c

Solution: 8

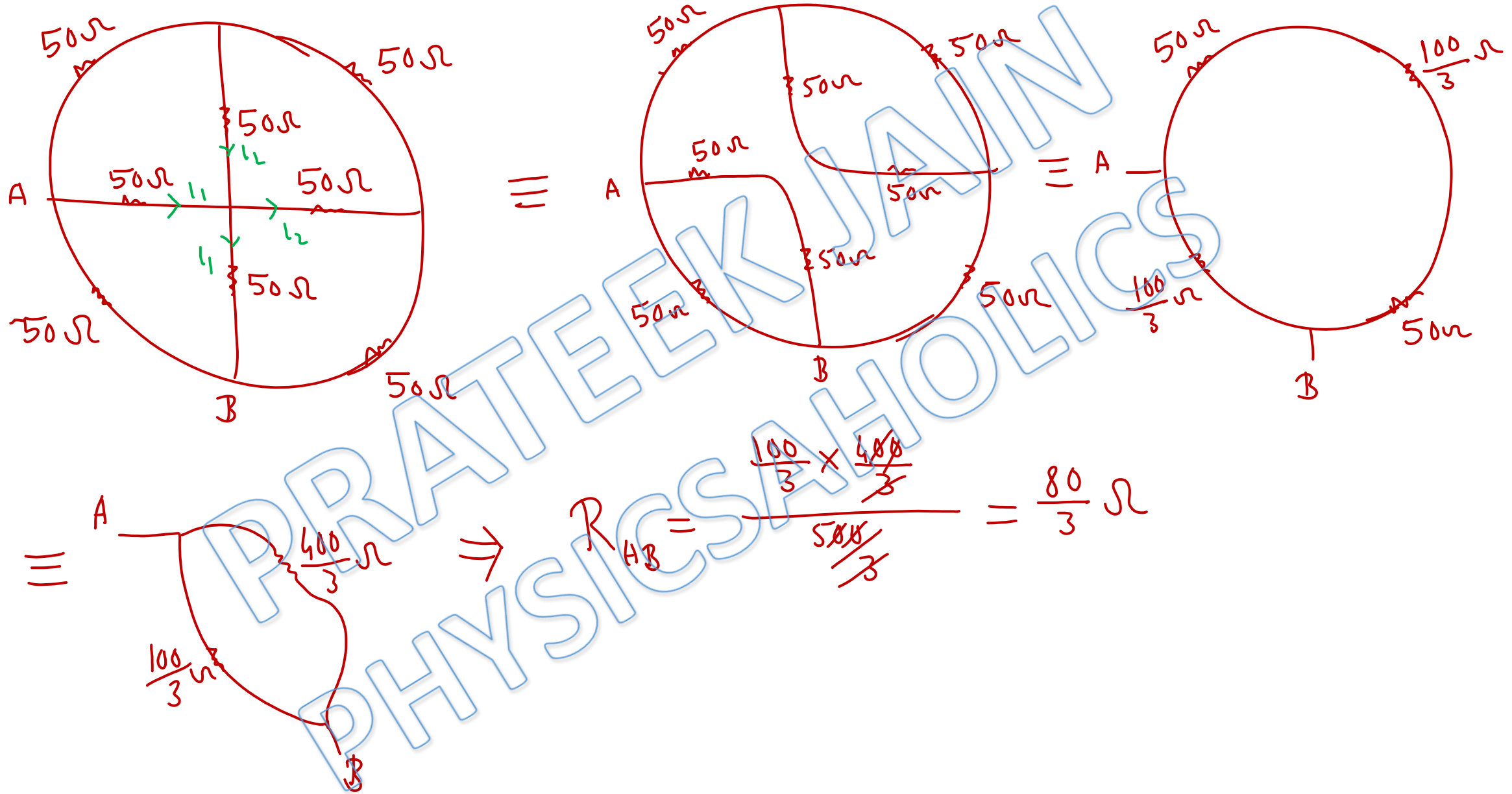


Ans. a

Solution: 9

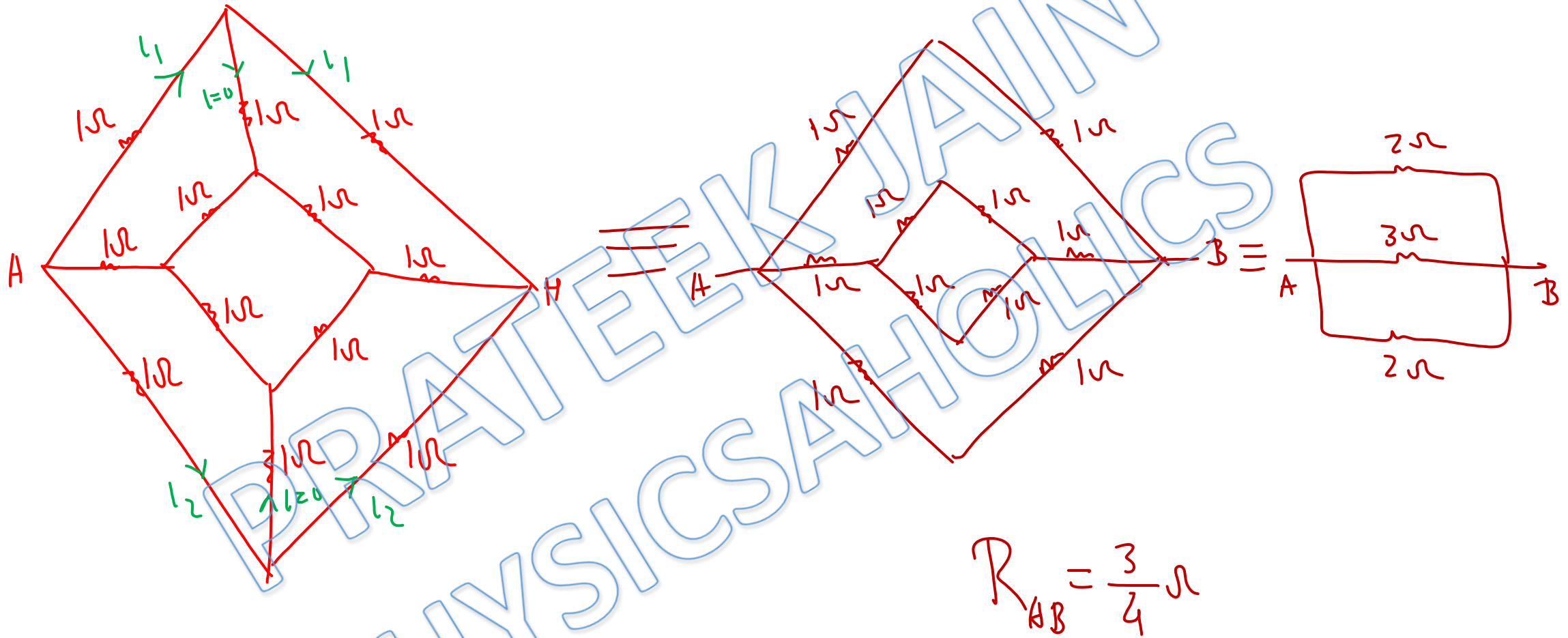

Ans. c


Solution: 10

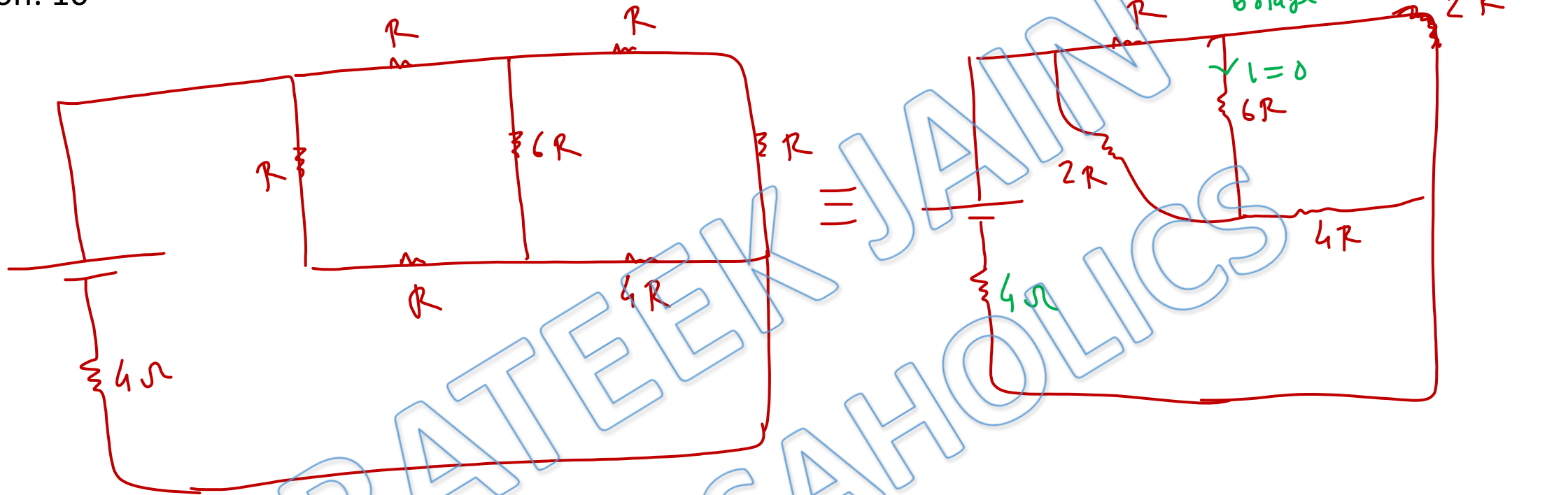

To produce maximum power in  $2R$


$$2R = 4\Omega$$

$$R = 2\Omega$$

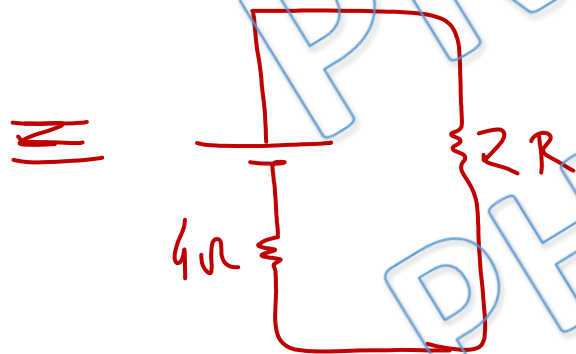

Ans. b

Solution: 11

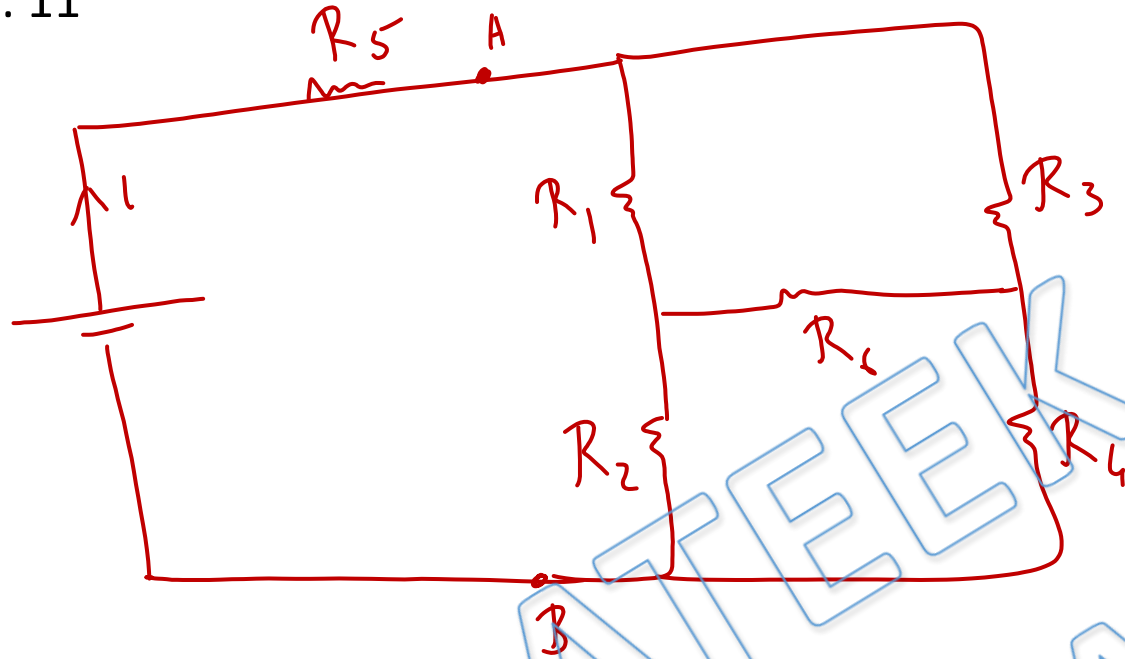


Circuit right to AB is  
wheat stone bridge.  $R_{eff}$  of circuit  
will be independent of  $R_5$  if  
bridge is balanced

$$\Rightarrow \frac{R_1}{R_2} = \frac{R_3}{R_4}$$

$$\Rightarrow R_1 R_4 = R_2 R_3$$


Ans. c

Solution: 12

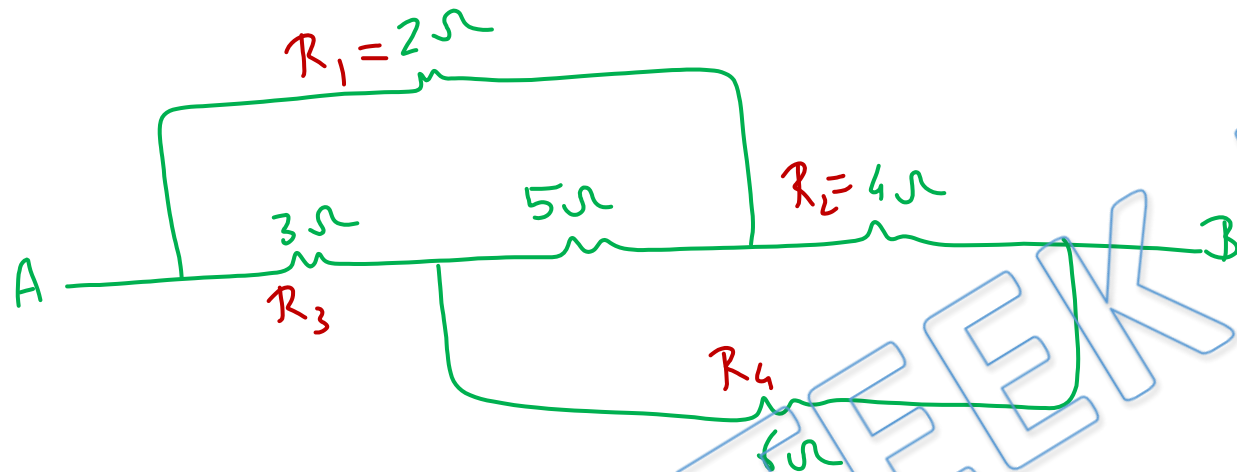

$$\text{Since } \frac{R_1}{R_2} = \frac{R_3}{R_4} = \frac{1}{2} \Rightarrow \text{bridge is balanced}$$

$\Rightarrow$  5Ω is useless  
2Ω

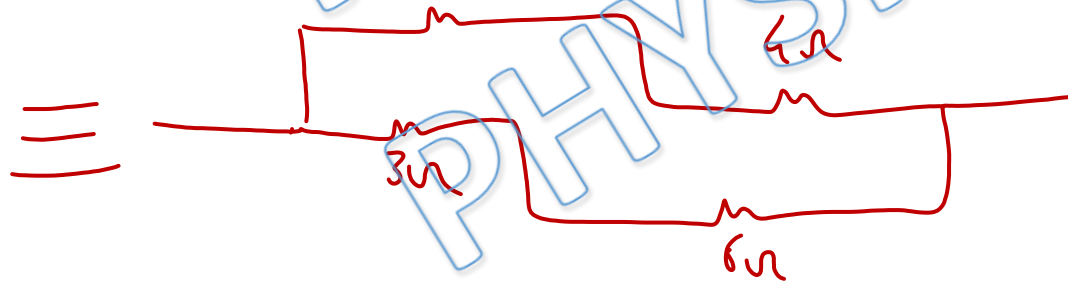


$$R_{AB} = \frac{2 \times 9}{\frac{15}{5}} = \frac{18}{5} \Omega$$

Ans. a, d

Solution: 13

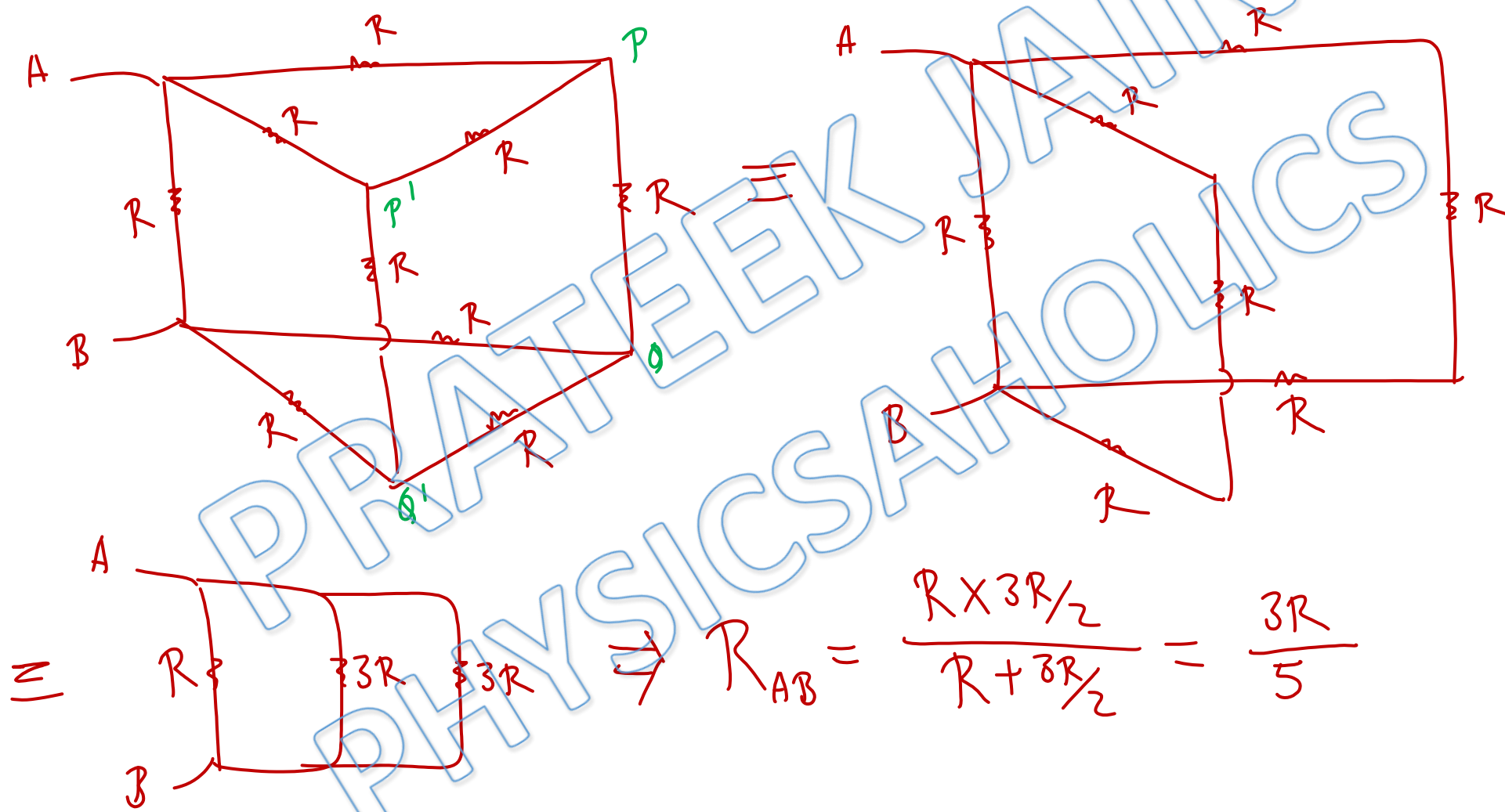$P$  &  $P'$  are symmetric points.  
 $A$  &  $A'$  ,, ,, ,, .




$$\Rightarrow R_{AB} = \frac{R \times 3R/2}{R + 3R/2} = \frac{3R}{5}$$



Ans. a



Solution: 14

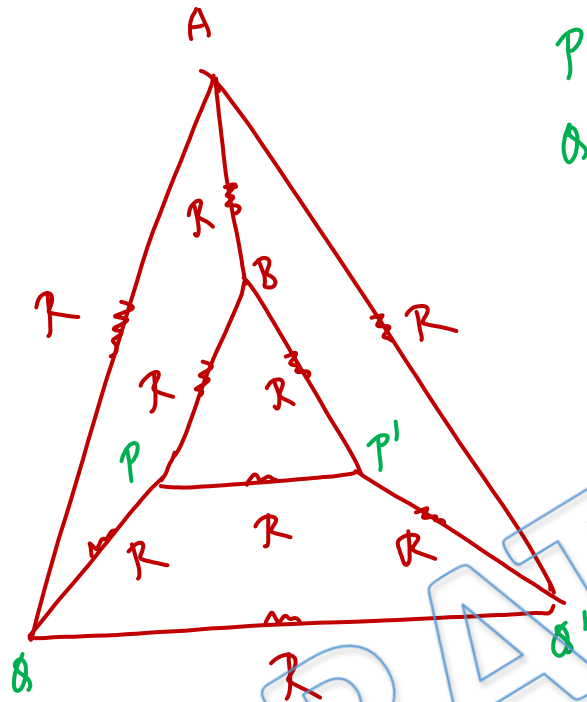

P & P' are symmetric  
O & O' " " "

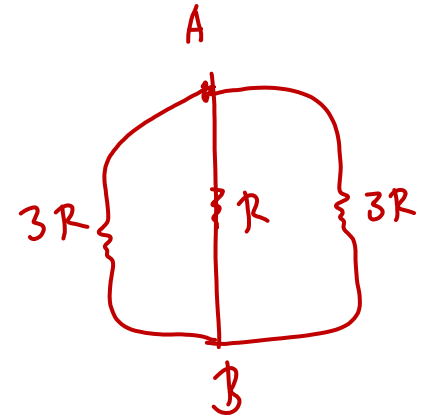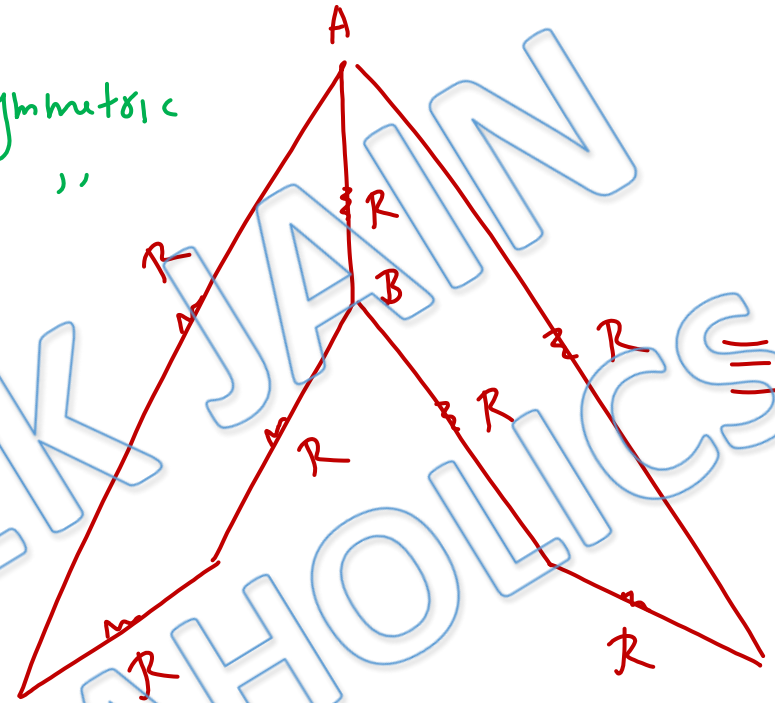


$$\frac{1}{R_{\text{eff}}} = \frac{1}{R} + \frac{1}{3R} + \frac{1}{3R} = \frac{3 + 1 + 1}{3R} = \frac{5}{3R}$$




$$R_{\text{eff}} = \frac{3R}{5}$$

Ans. a

Solution: 15

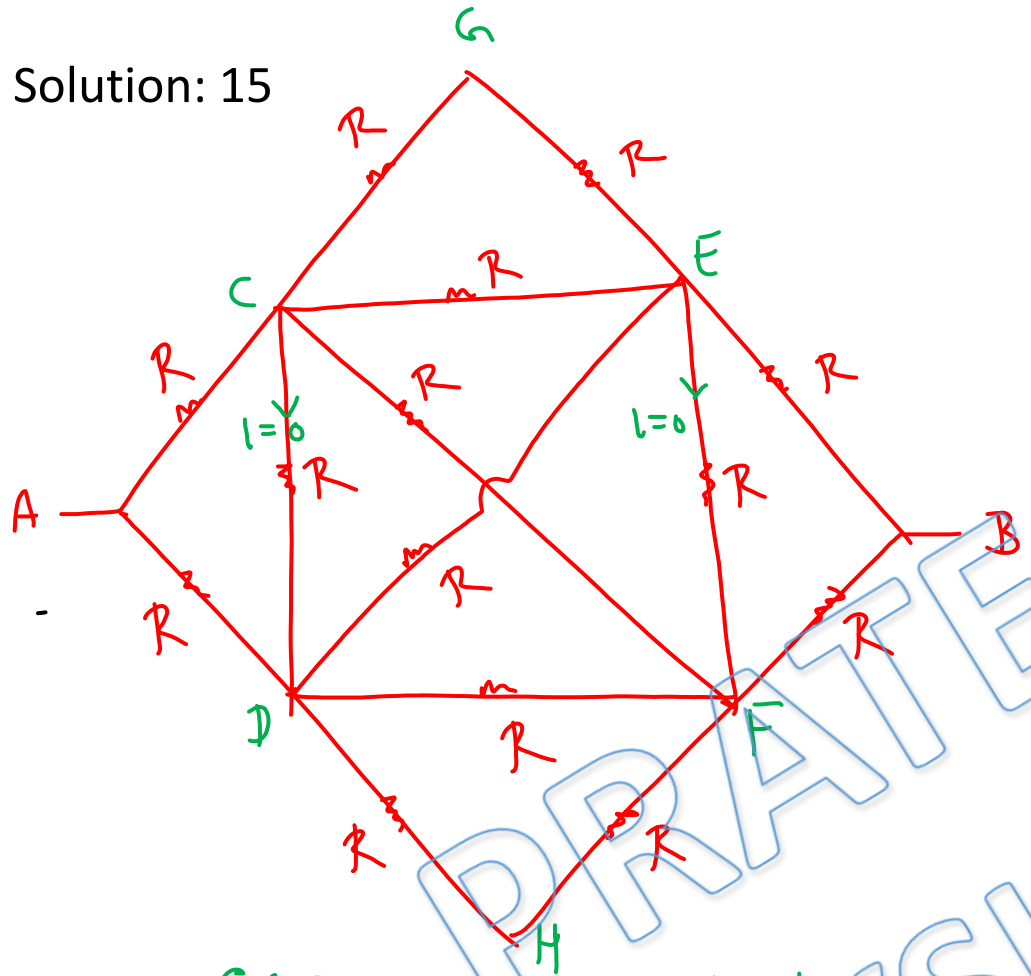

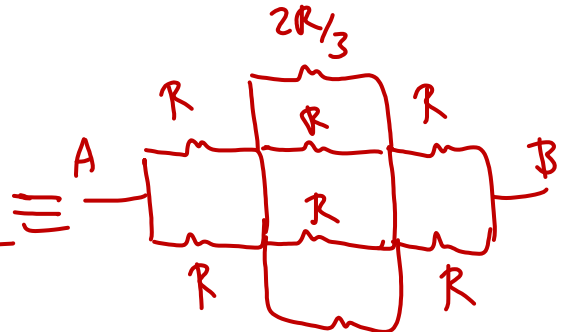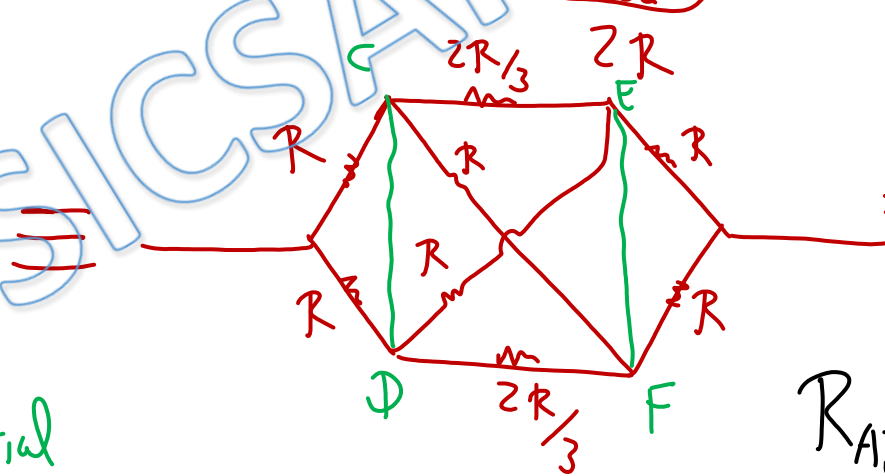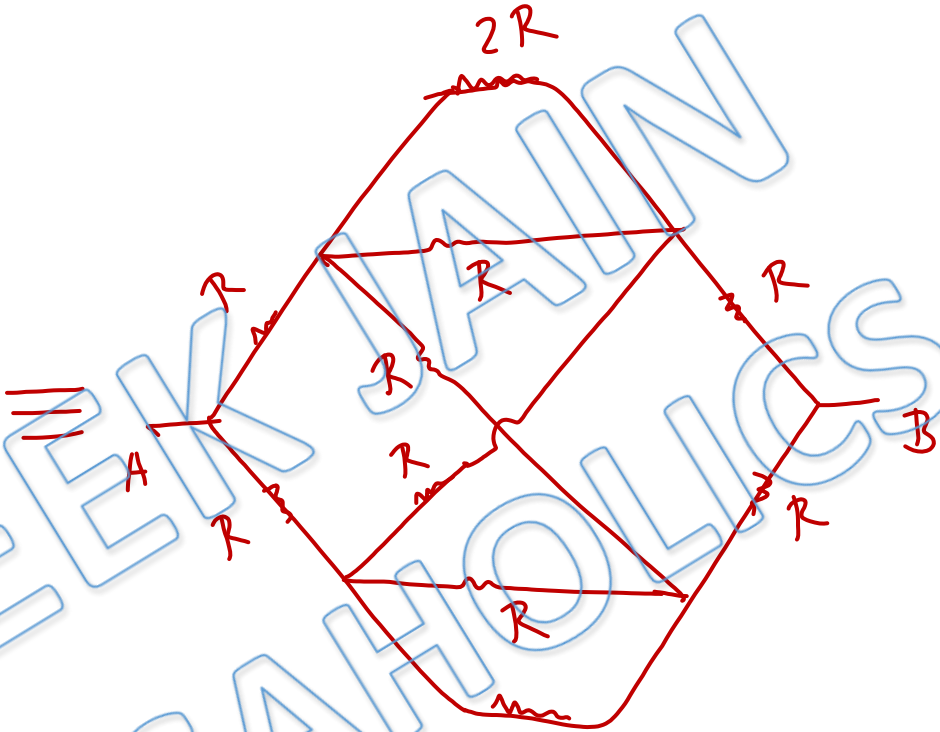C & D are symmetric points  
 E & F ,, ,, ,,  
 symmetric points have equal potential



$$R_{AB} = \frac{R}{2} + \frac{R}{5} + \frac{R}{2} = 1.2R$$

Ans. d

For Video Solution of this DPP, Click on below link

Video Solution  
on Website:-

<https://physicsaholics.com/home/courseDetails/55>

Video Solution  
on YouTube:-

<https://youtu.be/Mj1GqNdb4CQ>

Written Solution  
on Website:-

<https://physicsaholics.com/note/notesDetails/52>



[@Physicsaholics](#)

[@Physicsaholics\\_prateek](#)

[@NEET Physics](#)

[@IITJEE Physics](#)

[physicsaholics.com](#)



**CLICK**

Chalo Niklo