

DPP – 7 (Current Electricity)

Video Solution on Website:-

<https://physicsaholics.com/home/courseDetails/55>


Video Solution on YouTube:-

<https://youtu.be/DSR4Y2wiyDk>

Written Solution on Website:-


<https://physicsaholics.com/note/notesDetailis/52>

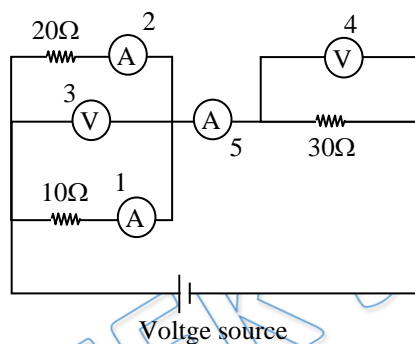- Q 1. If all meters are ideal and reading of voltmeter 3 is 6V. Power supplied by voltage source is -




- (A) 10 Watt (B) 38 Watt
(C) 20 Watt (D) 30 Watt

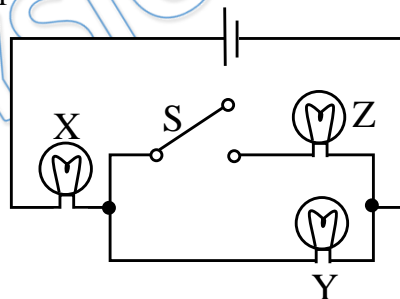- Q 2. If X, Y, and Z in figure are identical lamps, which of the following changes to the brightnesses of the lamps occur when switch S is closed?




- (A) X stays the same, Y decreases (C) X increases, Y stays the same
(B) X increases, Y decreases (D) X decreases, Y increases

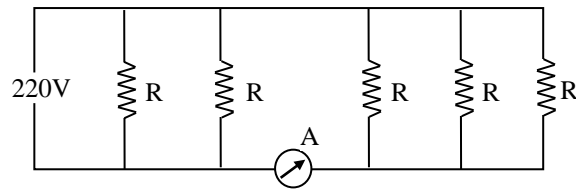- Q 3. Five identical lamps each resistance $R = 1100\text{ohm}$ are connected to 220V as shown in fig. The reading of ideal ammeter (A) is -




- (A) $1/5$ Amp. (B) $2/5$ Amp.
 (C) $3/5$ Amp (D) 1 Amp.

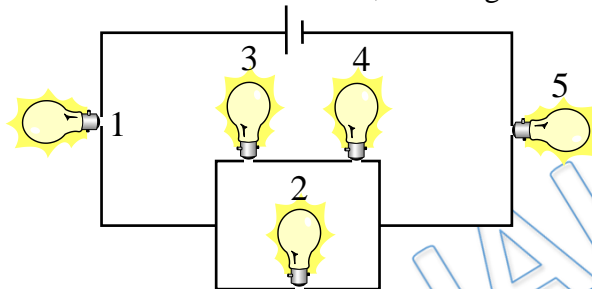Q 4. All bulbs in figure below are identical which, bulbs light most brightly-




- (A) 1 only (B) 2 only
 (C) 3 and 4 only (D) 1 and 5

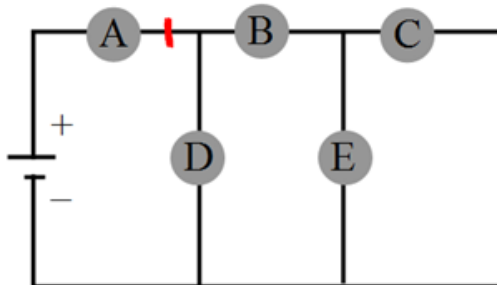Q 5. In the circuit diagram shown in figure, a fuse bulb can cause all other bulbs to go out. Identify the bulb –



- (A) B (B) C
 (C) A (D) D or E

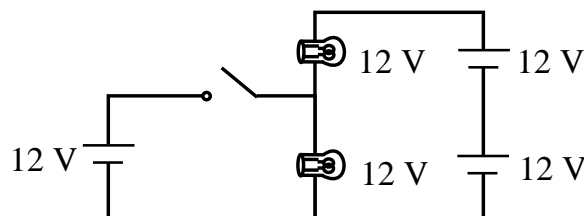
Q 6. The light bulbs A & B in the following circuits are identical. When the switch is closed -




- (A) Intensity of bulb A increase (C) Intensity of bulb B increase
 (B) Intensity of bulb A decrease (D) Nothing changes



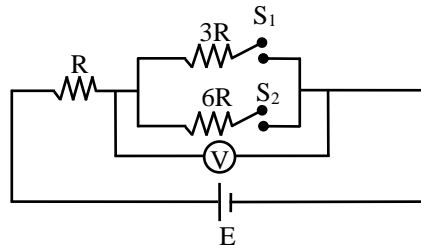
- Q 7. In the circuit shown in the figure, reading of voltmeter is V_1 when only S_1 is closed, reading of voltmeter is V_2 when only S_2 is closed and reading of voltmeter is V_3 when both S_1 and S_2 are closed. Then –



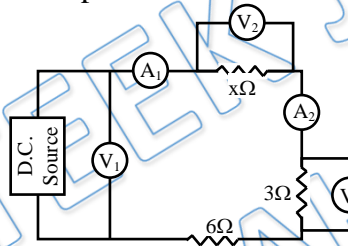- (A) $V_3 > V_2 > V_1$ (B) $V_2 > V_1 > V_3$
 (C) $V_3 > V_1 > V_2$ (D) $V_1 > V_2 > V_3$
- Q 8. In the electric circuit shown in figure, the reading of voltmeter V_1 is 26 volt, and the reading of ammeter A_1 is 2 ampere. The value of resistance x is –



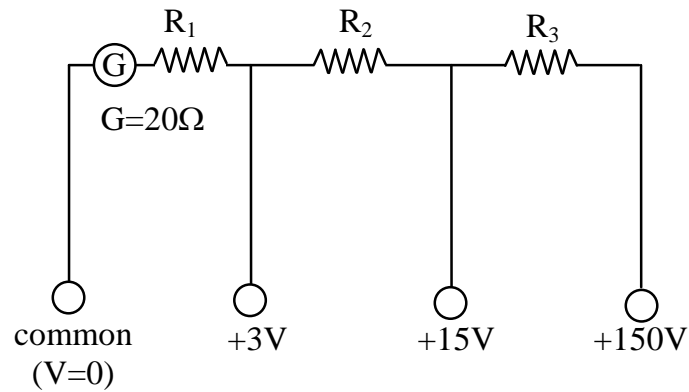- (A) 2 ohm (B) 4 ohm
 (C) 6 ohm (D) 8 ohm
- Q 9. A galvanometer of resistance 100 ohm gives a full scale deflection for a current of 10mA. To convert in into an ammeter of one ampere range, required shunt resistance would be:
- (A) 10^{-2} ohm (B) 1 ohm
 (C) 10^{-1} ohm (D) 10^{-3} ohm
- Q 10. The deflection in the galvanometer is reduced from 50 to 20 divisions when it is shunted by a resistance of 12 ohm. The resistance of galvanometer will be -
- (A) 18 ohm (B) 24 ohm
 (C) 30 ohm (D) 36 ohm
- Q 11. Internal electric connections of a multi range voltmeter are shown in the figure. The terminals are marked 3 volt, 5 volt, 150 volt, resistance of the galvanometer is 20 ohm and the value of current is 1 mA for the full scale deflection of the galvanometer. The resistance of R_1 in Kohm



- (A) 12
(B) 15
(C) 3
(D) 2.98

Q 12. The resistance of 100 ohm and 200 ohm are connected in series with the 220 V mains. When a voltmeter of 1000 ohm resistance is connected in parallel to 100 ohm, then the reading of voltmeter is –

- (A) 68.75 volt
(B) 6.87 volt
(C) 587.5 volt
(D) 58.75 volt

Q 13. The resistance of a moving coil galvanometer is 20 ohm. It requires 0.01 ampere current for full scale deflection. The value of resistance to convert in into a voltmeter of range 20 volt will be –

- (A) 198 ohm
(B) 1980 ohm
(C) 20 ohm
(D) 0 ohm



Answer Key

Q.1 d	Q.2 b	Q.3 c	Q.4 d	Q.5 c
Q.6 d	Q.7 b	Q.8 b	Q.9 b	Q.10 a
Q.11 d	Q.12 a	Q.13 b		

PRATEEK JAIN
PHYSICSAHOLICS


PLUS **ICONIC****

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

24 months	₹2,333/mo	>
No cost EMI	₹56,000	
18 months	₹2,625/mo	>
No cost EMI	₹47,250	
12 months	₹3,208/mo	>
No cost EMI	₹38,500	
6 months	₹4,667/mo	>
No cost EMI	₹28,000	

To be paid as a one-time payment

[View all plans](#)

 Add a referral code APPLY

PHYSICSLIVE


PLUS **ICONIC****

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

24 months	₹2,100/mo	>
No cost EMI	+10% OFF ₹50,400	
18 months	₹2,363/mo	>
No cost EMI	+10% OFF ₹42,525	
12 months	₹2,888/mo	>
No cost EMI	+10% OFF ₹34,650	
6 months	₹4,200/mo	>
No cost EMI	+10% OFF ₹25,200	

To be paid as a one-time payment

[View all plans](#)

 Awesome! **PHYSICSLIVE** code applied ✗

Use code **PHYSICSLIVE** to get 10% OFF on Unacademy PLUS.

Written Solution

**DPP-7 Current Electricity: Bulb Problems,
Galvanometer, Voltmeter , Ammeter**

By Physicsaholics Team

Solution: 1

$$\text{Current through } 20\text{ohm} = \frac{6}{20}$$

$$\text{current through } 10\text{ohm} = \frac{6}{10}$$

Total current supplied by voltage source

$$= \frac{6}{10} + \frac{6}{20}$$

$$= 27 \text{ Volt}$$


$$\text{Voltage of battery} = 6 + 27 = 33 \text{ volt}$$

$$\text{Power supplied} = \frac{9}{10} \times 33$$


$$= 29.7 \text{ or } 30 \text{ Watt}$$

Ans. d

Solution: 2

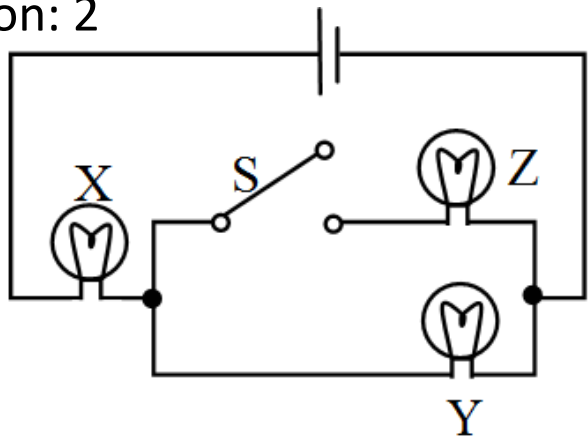


Before closing the Switch:-

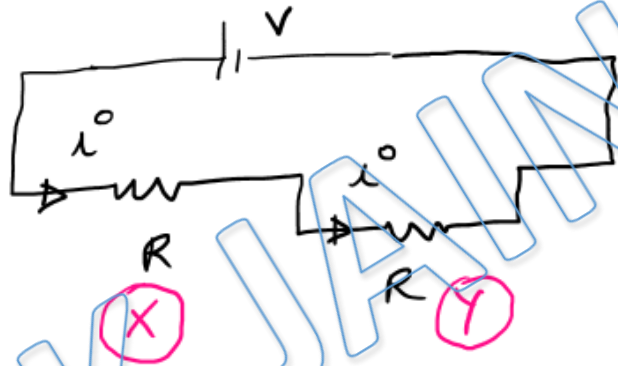

$$i^0 = \frac{V}{2R}$$

After closing the switch

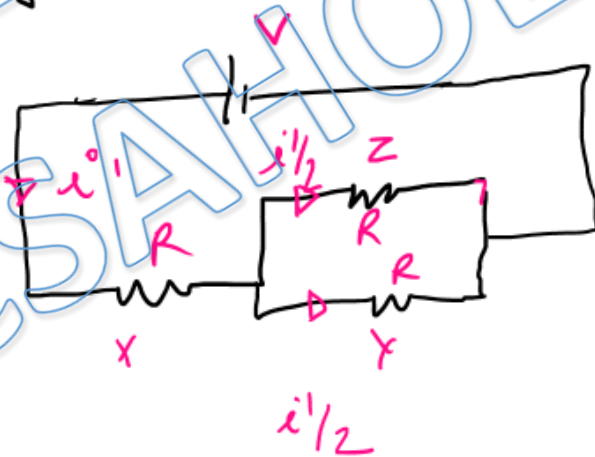


$$i^1 = \frac{V}{3R/2}$$

$$i^1 = \frac{2V}{3R}$$

as the current on x is inc. and on y dec. so the answer is b

Ans. b

Solution: 3

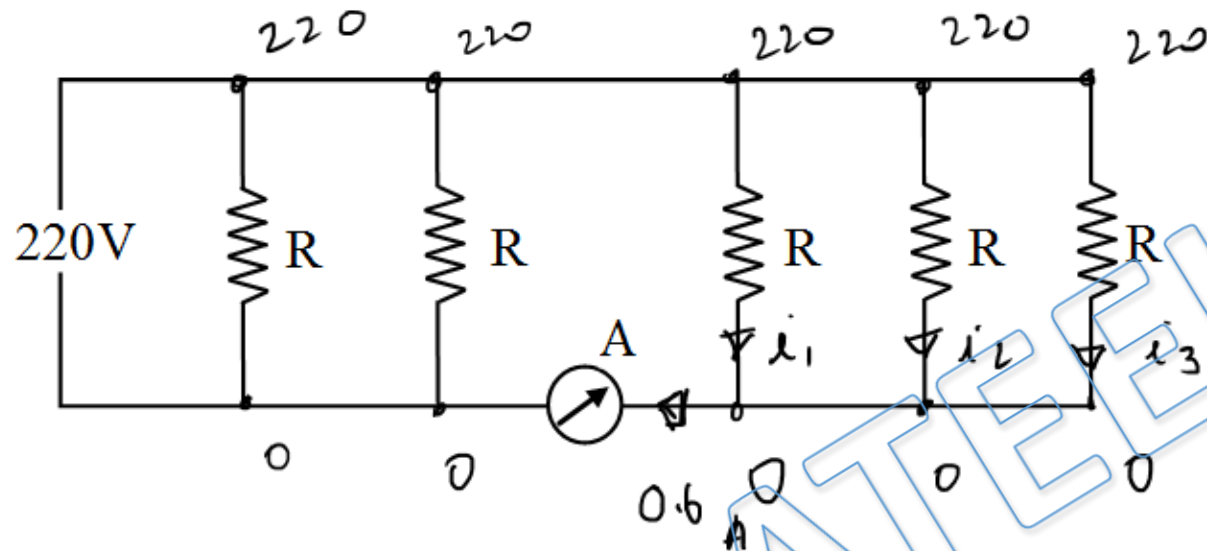

$$R = 1100 \Omega$$


$$i_1 + i_2 + i_3 = \frac{220}{1100} + \frac{220}{1100} + \frac{220}{1100}$$

$$= 0.6 \text{ A}$$

$$= \frac{3}{5} \text{ A}$$

Ans. c


Solution: 4

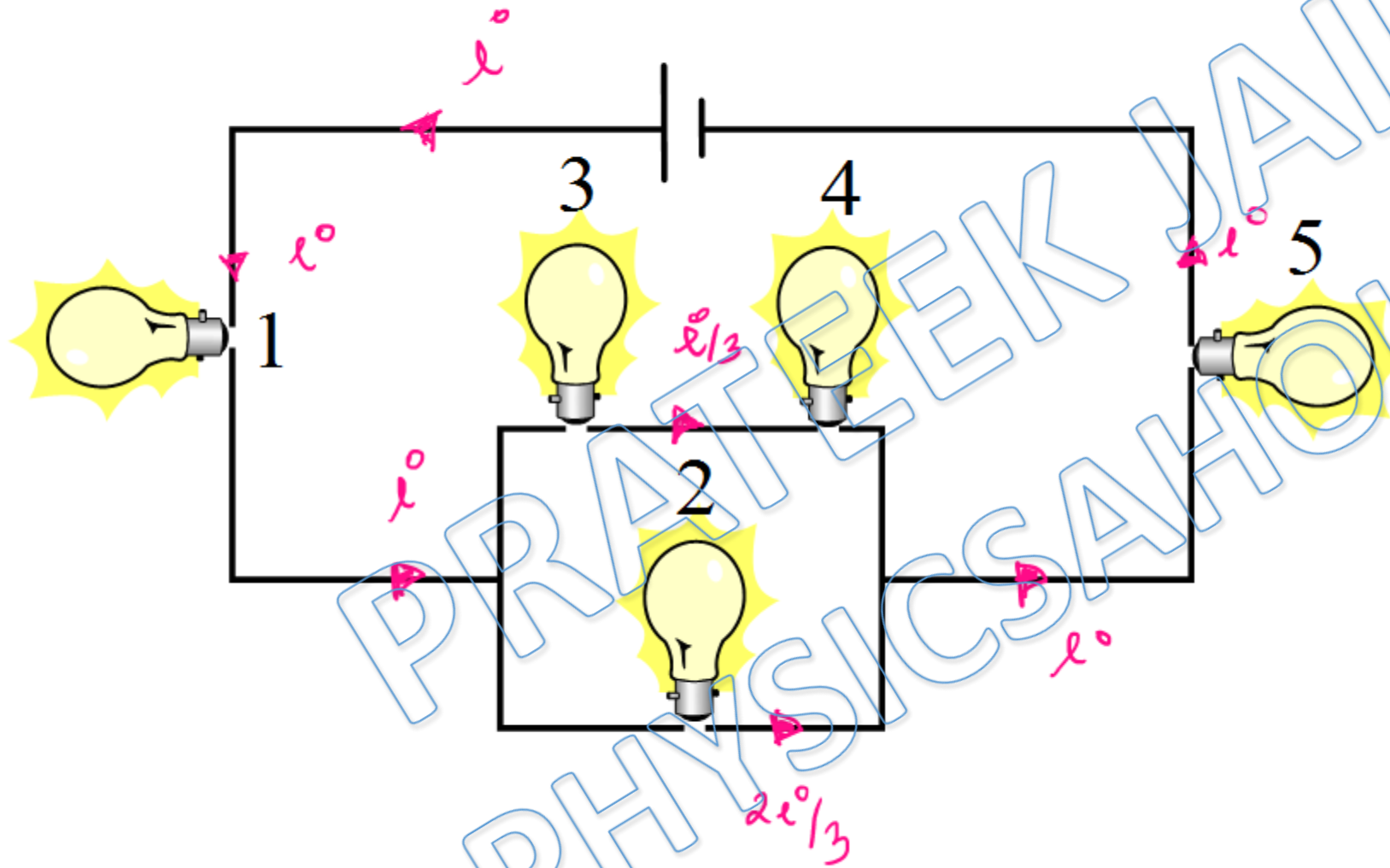

" So Bulb 1 & 5 will glow more as they are having max m current!"

Ans. d


Solution: 5

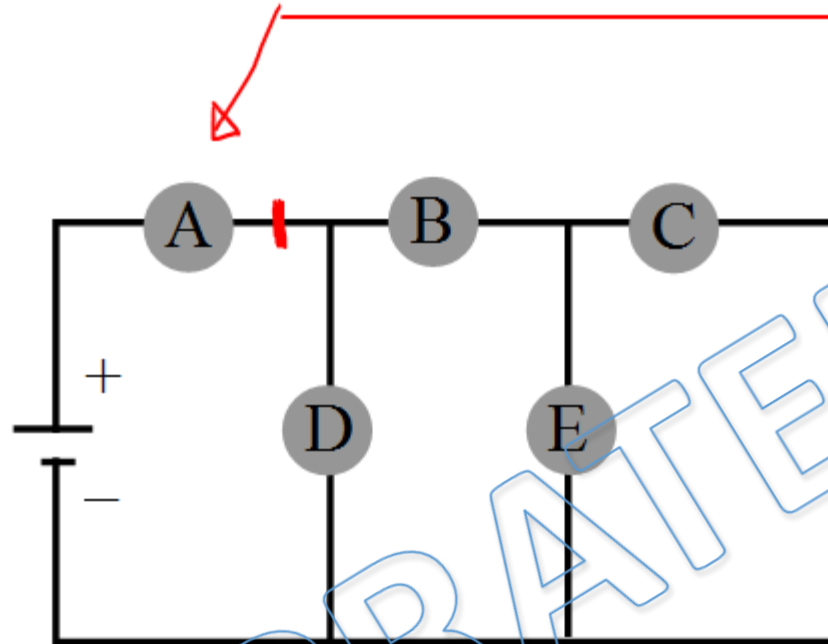


if we fuse a the source will disconnect from ckt and non of the bulb will lit.

Ans. c

Solution: 6

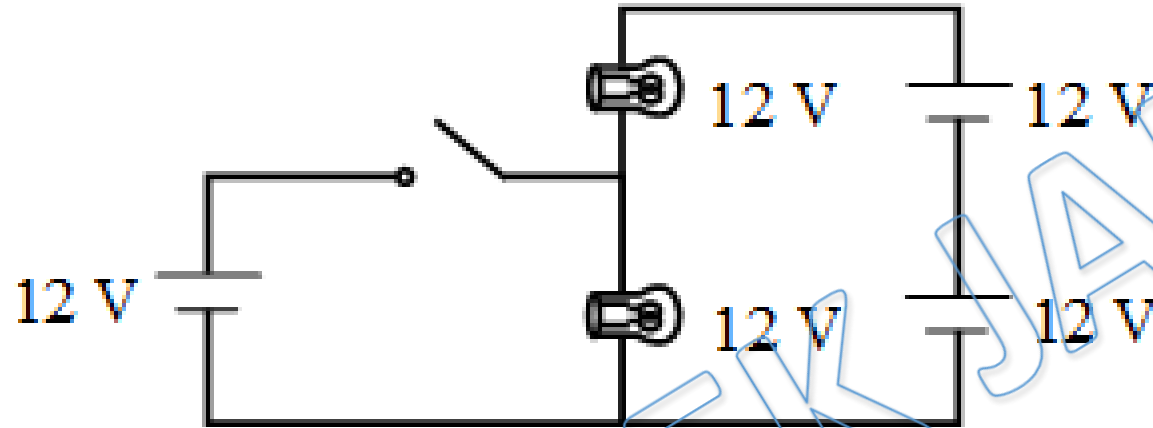


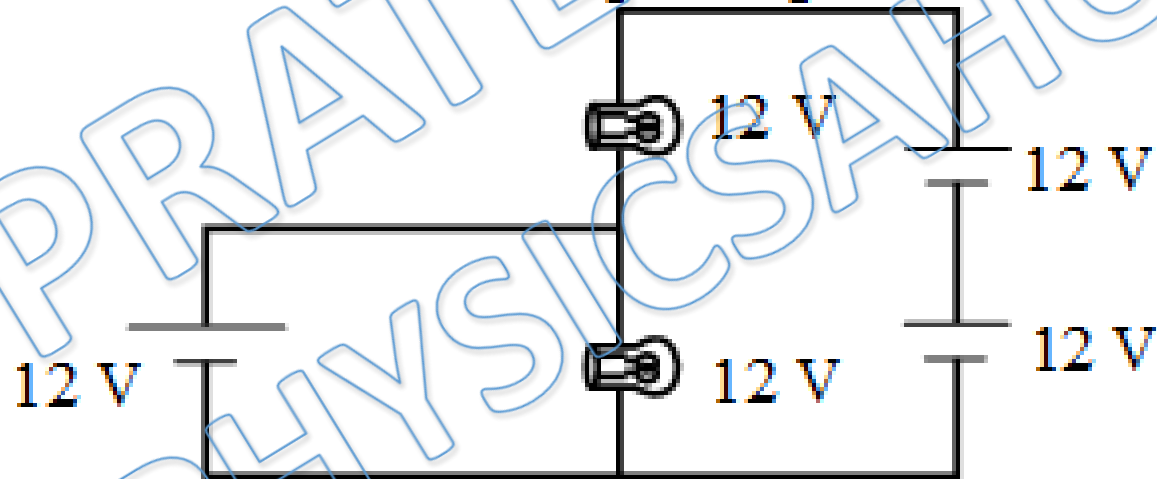After closing of switch voltage across A & B remain same \therefore Nothing change




Ans. d

Solution: 7

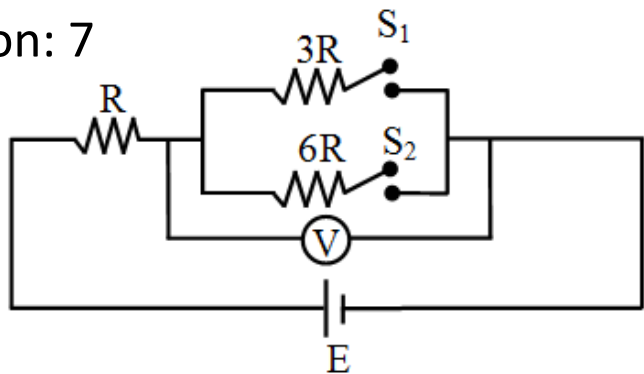

① When only S_1 is closed.

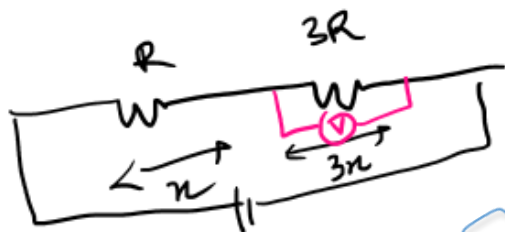

$$4x = E$$

$$x = E/4$$

$$V_1 = 3E/4$$

② When only S_2 is closed.




$$x + 6x = E$$

$$7x = E$$

$$x = E/7$$

$$V_2 = 6E/7$$

③ When both are closed.

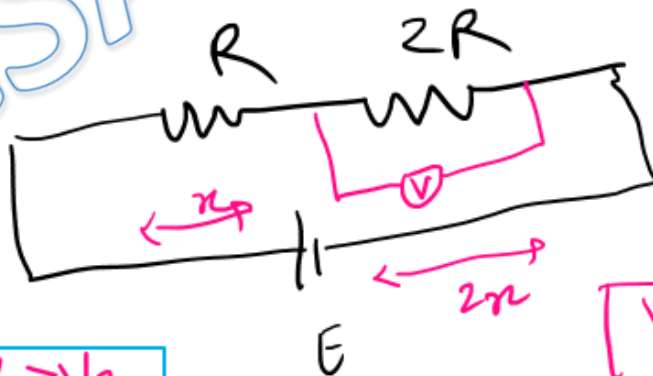

$$3x = E$$

$$x = E/3$$


$$V_3 = 2E/3$$

$$V_2 > V_1 > V_3$$



Ans. b

Solution: 8

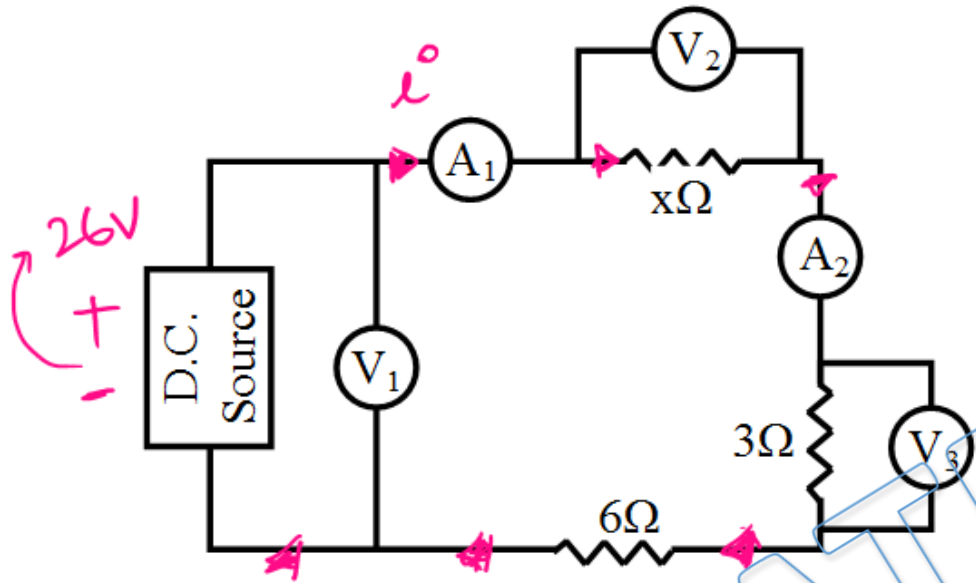

Series circuit.

As V_1 is parallel to source it must have an EMF of 26V & as A_1 is main current on the circuit.

$$I = \frac{V}{R_{eq}}$$

$$I = \frac{26}{6+3+x}$$

$$9+x = 13$$


$$x = 4\Omega$$

Ans. b

Solution: 9

Solⁿ \Rightarrow
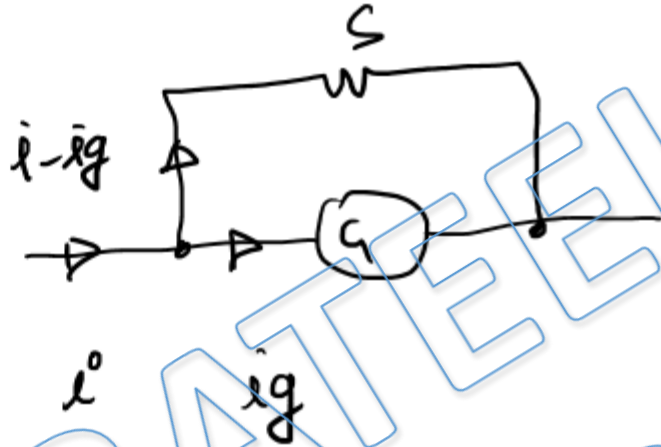
$$i_g = 10 \times 10^{-3} \text{ A}, \quad G = 100 \Omega$$



$$(i - i_g)S = i_g G$$


$$S = \frac{i_g G}{i - i_g} = \frac{10 \times 10^{-3} \times 100}{1}$$

$$\boxed{S = 1 \Omega}^A$$

Ans. b

Solution: 10

initially
←

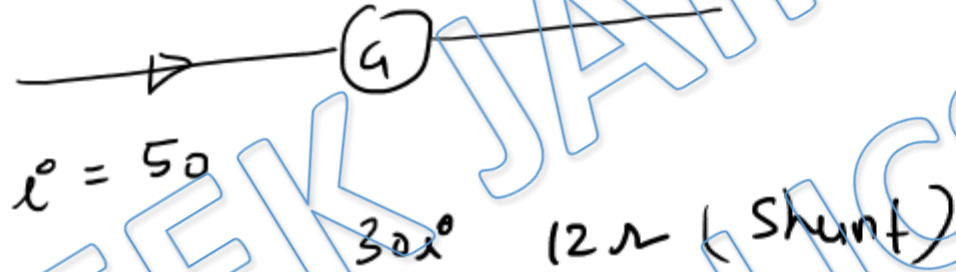

finally




In parallel combination $I \propto 1/R$

$$\frac{30\Omega}{20\Omega} = \frac{G}{12}$$

$$\Rightarrow \boxed{G = 18\Omega}$$

Ans. a

Solution: 11

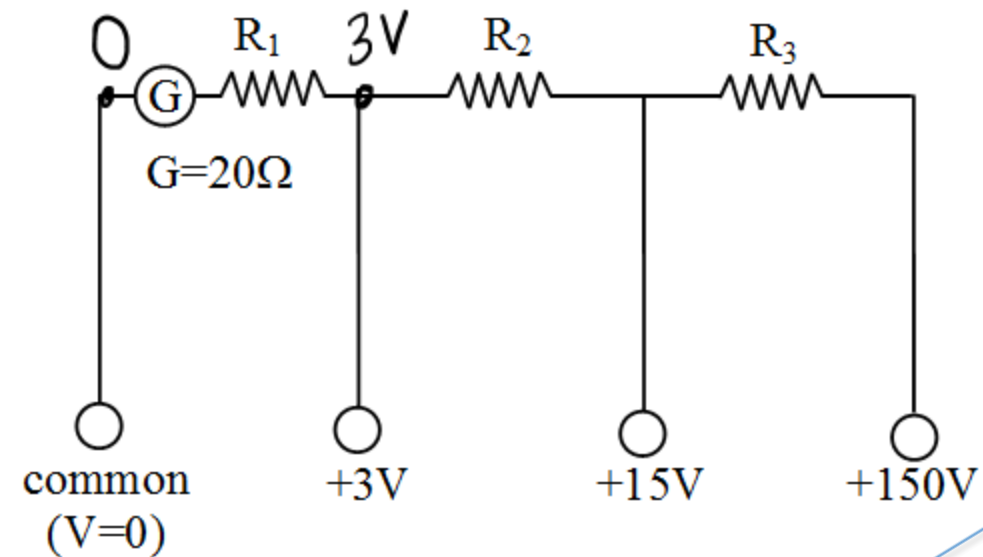

$$i^{\circ} = \frac{3}{20 + R_1}$$

$$(1 \times 10^{-3})(20 + R_1) = 3$$

$$R_1 = 3000 - 20 = 2980 \Omega$$

$$2.98 \text{ k}\Omega$$


Ans. d



Solution: 12

reading of voltmeter is—

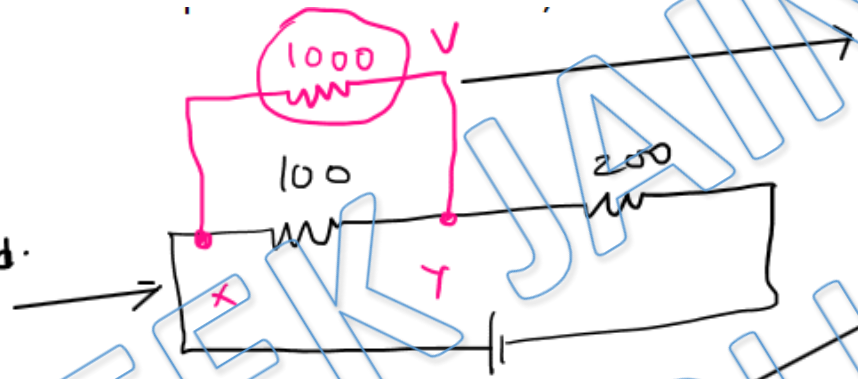
⇒ voltmeter will read the P.d. b/w x & y point.



$$R_{eq} = \frac{1000 \times 100}{1100} = \frac{1000}{11} \Omega$$

but the reading is
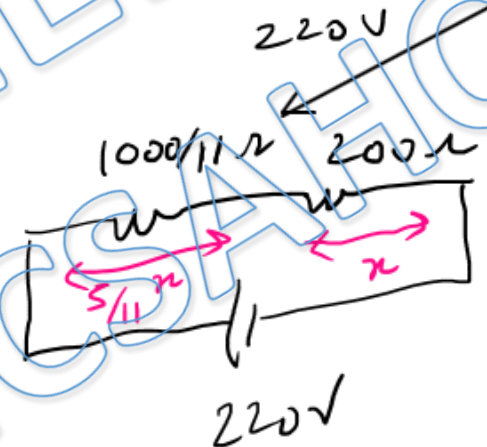
$$V_x - V_y = \frac{5}{11} \times 220 = \frac{5}{11} \times \frac{220 \times 11}{16} = 68.75 \text{ V}$$




$$\begin{aligned} x + \frac{5}{11}x &= 220 \\ \frac{16x}{11} &= 220 \\ x &= \frac{220 \times 11}{16} \end{aligned}$$

Ans. a



Solution: 13

$$i_g = 0.01 \text{ A}$$

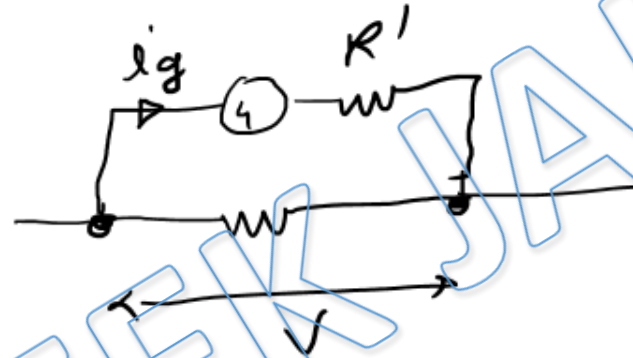

$$V = i_g \cdot (R + R')$$

$$20 = 0.01 (20 + R')$$

$$2000 - 20 = R'$$

$$R' = 1980 \Omega$$

For Video Solution of this DPP, Click on below link

Video Solution
on Website:-

<https://physicsaholics.com/home/courseDetails/55>

Video Solution
on YouTube:-

<https://youtu.be/DSR4Y2wiyDk>

Written Solution
on Website:-

<https://physicsaholics.com/note/notesDetails/52>



[@Physicsaholics](#)

[@Physicsaholics_prateek](#)

[@NEET Physics](#)

[@IITJEE Physics](#)

[physicsaholics.com](#)



CLICK

Chalo Niklo