


**DPP – 4 (Current Electricity)**

Video Solution on Website :- <https://physicsaholics.com/home/courseDetails/98>

Video Solution on YouTube:- <https://youtu.be/VQ1Y7ZGz3W4>


Written Solution on Website:- <https://physicsaholics.com/note/notesDetalis/53>

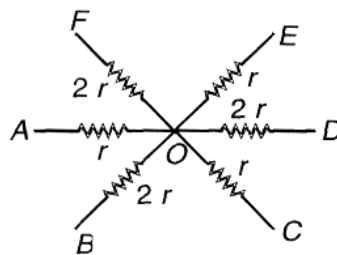Q 1. The terminal network shown in the figure consists of 6 resistors. The points A, C and E all are at potential 20 V while points B, D and F are at potential -10 volt then potential of junction O will be




- (a) Zero      (b) 10 V      (c) 15 V      (d) -5V

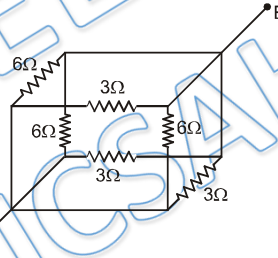Q 2. Find the equivalent resistance between points A and B :




- (a)  $2\Omega$       (b)  $\frac{2}{3}\Omega$       (c)  $\frac{3}{2}\Omega$       (d)  $\frac{1}{2}\Omega$

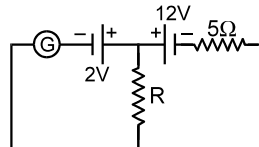Q 3. In the circuit shown, the galvanometer shows zero current. The value of resistance R is :




- (a) 1 Ω      (b) 2 Ω      (c) 4 Ω      (d) 9 Ω

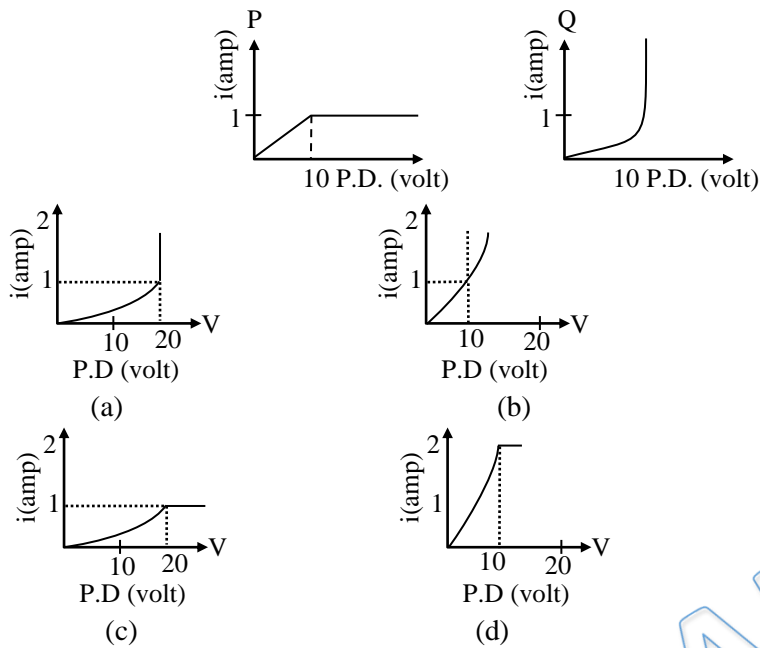Q 4. Two current elements P and Q have current voltage characteristics as shown below; Which of the graphs given below represents current voltage characteristics when P and Q are in series




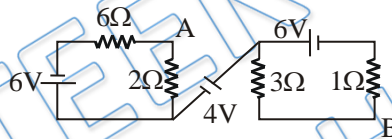Q 5. In the network shown in the figure below, calculate the potential difference between A and B ? ( $V_B - V_A$ ) =




- (a) 1V
- (b) -1 V
- (c) 2V
- (d) -2V

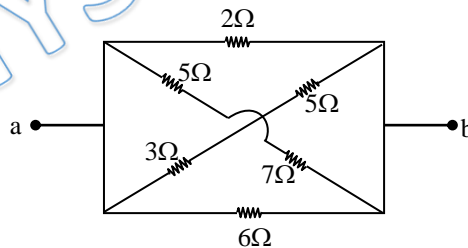Q 6. Find the equivalent resistance between a & b




- (a)  $\frac{7}{8} \Omega$
- (b)  $\frac{8}{7} \Omega$
- (c)  $\frac{6}{7} \Omega$
- (d)  $\frac{7}{6} \Omega$

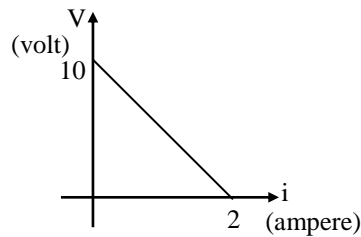Q 7. A battery of emf  $E$  and internal resistance  $r$  is connected across a resistance  $R$ . Resistance  $R$  can be adjusted to any value greater than or equal to zero. A graph is plotted between the current ( $i$ ) passing through the resistance and potential difference ( $V$ ) across it. Select the correct alternative(s) –




- (a) internal resistance of battery is 5ohm
- (b) emf of the battery is 20V
- (c) maximum current which can be taken from the battery is 4A
- (d) V-i graph can never be a straight line as shown in figure

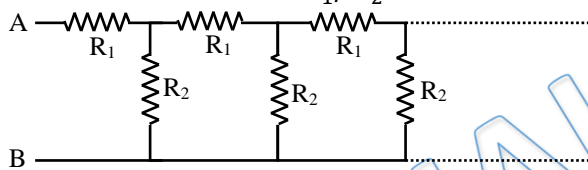Q 8. Consider an infinite ladder network. A voltage is applied between points A & B. If the voltage is halved after each section. Find the ratio  $R_1/R_2$ .




- (a) 1/2
- (b) 1/3
- (c) 2
- (d) None of these

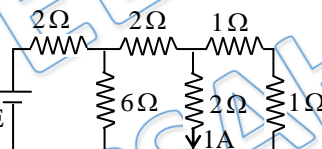Q 9. The emf of the battery shown in the figure is given by –



- (a) 6 V
- (b) 12 V
- (c) 18 V
- (d) 8 V

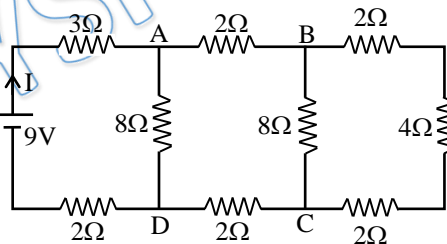Q 10. In the circuit shown in figure, the current through –




- (a) the 3ohm resistor is 0.50 A
- (b) the 3ohm resistor is 0.25 A
- (c) the 4ohm resistor is 0.50 A
- (d) the 4ohm resistor is 0.25 A

Q 11. There are two concentric spheres of radius  $a$  and  $b$  respectively. If the space between them is filled with medium of resistivity  $\rho$ , then the resistance of the inter gap between the two spheres will be

- (a)  $\frac{\rho}{4\pi(b+a)}$
- (b)  $\frac{\rho}{4\pi} \left( \frac{1}{b} + \frac{1}{a} \right)$
- (c)  $\frac{\rho}{4\pi} \left( \frac{1}{a^2} - \frac{1}{b^2} \right)$
- (d)  $\frac{\rho}{4\pi} \left( \frac{1}{a} - \frac{1}{b} \right)$




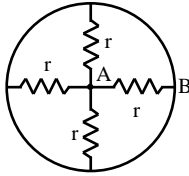Q 12. The equivalent resistance between point A and B is -



- (a)  $4r$
- (b)  $2r$
- (c)  $r$
- (d)  $r/4$

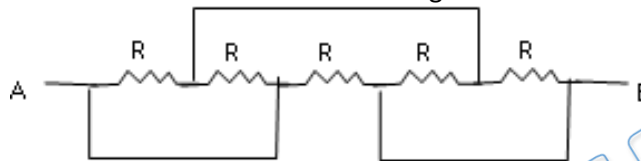Q 13. The equivalent resistance between A and B in the given circuit




- (a)  $R$
- (b)  $R/2$
- (c)  $R/3$
- (d)  $2R/3$

Q 14. A 10 V car battery with negligible internal resistance is connected to a series combination of a  $4\Omega$  resistor that obeys Ohm's law and a thermistor that does not obey Ohm's law, but instead has a current-voltage relation  $V = \alpha I + \beta I^2$  with  $\alpha = 2\Omega$  and  $\beta = 4\Omega/A$ . The current through the  $4\Omega$  resistor is

- (a) 1 A
- (b) 2 A
- (c)  $2/5$  A
- (d) 5 A

Q 15 Find current in wire AB ?

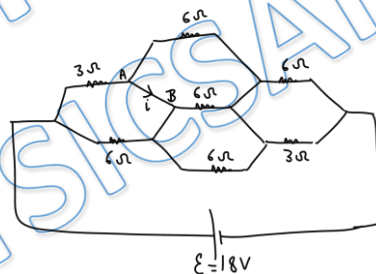

- (a) 1A
- (b) 2A
- (c) 3A
- (d) 4A



PRATEEK JAIN  
PHYSICSAHOLICS

## Answer Key

Q.1 b	Q.2 b	Q.3 a	Q.4 c	Q.5 a
Q.6 b	Q.7 a	Q.8 a	Q.9 b	Q.10 d
Q.11 d	Q.12 d	Q.13 b	Q.14 a	Q.15 a

PLUS **ICONIC\*\***

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

24 months ₹2,333/mo >  
No cost EMI ₹56,000

18 months ₹2,625/mo >  
No cost EMI ₹47,250

12 months ₹3,208/mo >  
No cost EMI ₹38,500

6 months ₹4,667/mo >  
No cost EMI ₹28,000

To be paid as a one-time payment

[View all plans](#)



Add a referral code

APPLY

# PHYSICSLIVE

Use code **PHYSICSLIVE** to get 10% OFF on Unacademy PLUS.

PLUS **ICONIC\*\***

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

24 months ₹2,100/mo >  
No cost EMI **+10% OFF** ₹50,400

18 months ₹2,363/mo >  
No cost EMI **+10% OFF** ₹42,525

12 months ₹2,888/mo >  
No cost EMI **+10% OFF** ₹34,650

6 months ₹4,200/mo >  
No cost EMI **+10% OFF** ₹25,200

To be paid as a one-time payment

[View all plans](#)



Awesome! **PHYSICSLIVE** code applied




# **Written Solution**

**DPP- 4 Current : K.V.L., Series and Parallel  
Combination**

**By Physicsaholics Team**

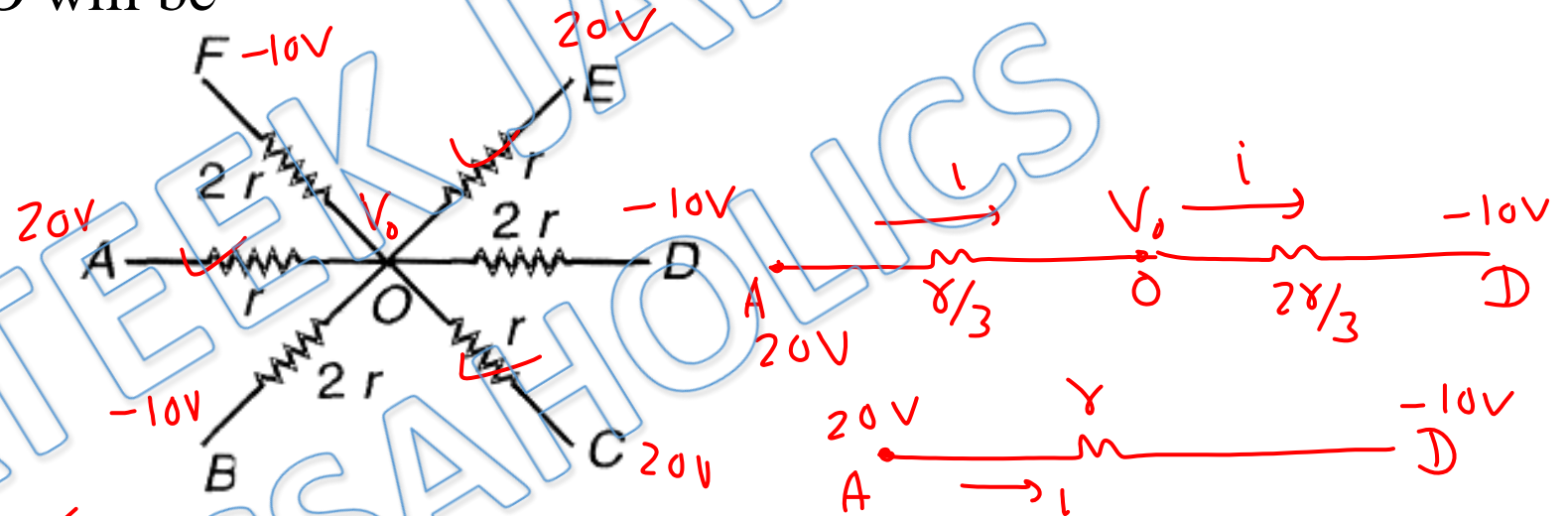Q.1) The terminal network shown in the figure consists of 6 resistors. The points A, C and E all are at potential 20 V while points B, D and F are at potential -10 volt then potential of junction O will be



(a) Zero

(b) 10 V

(c) 15 V

(d) -5V

$$i = \frac{30}{8}$$


for AO

$$i = \frac{20 - V_0}{8/3} = \frac{30}{8} \Rightarrow 20 - V_0 = 10$$

$$V_0 = 10V$$



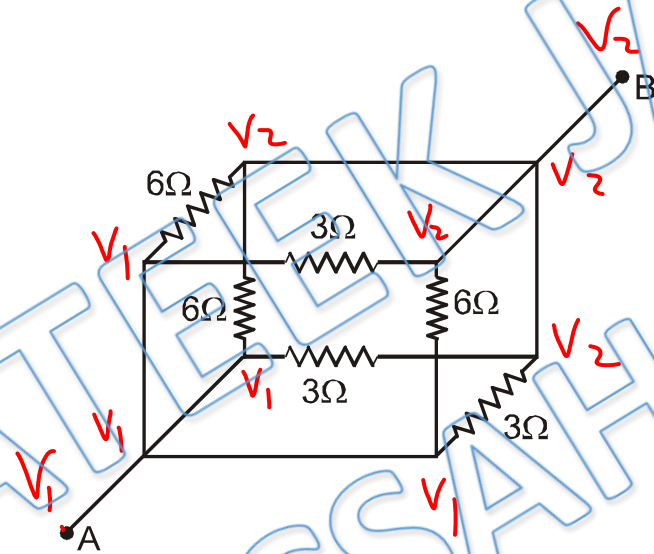Q.2) Find the equivalent resistance between points A and B :



$$\begin{aligned} \frac{1}{R} &= \frac{1}{3} + \frac{1}{3} + \frac{1}{3} + \frac{1}{6} + \frac{1}{6} + \frac{1}{6} \\ &= \frac{1}{1} + \frac{1}{2} = \frac{3}{2} \\ R &= \frac{2}{3} \Omega \end{aligned}$$



(a)  $2\Omega$

~~(b)  $\frac{2}{3}\Omega$~~

(c)  $\frac{3}{2}\Omega$

(d)  $\frac{1}{2}\Omega$

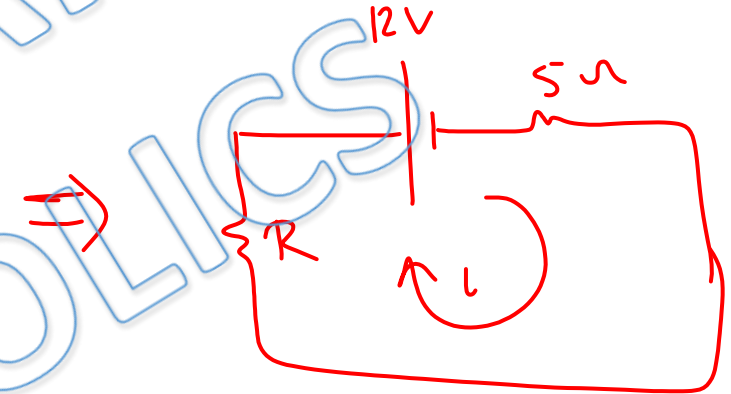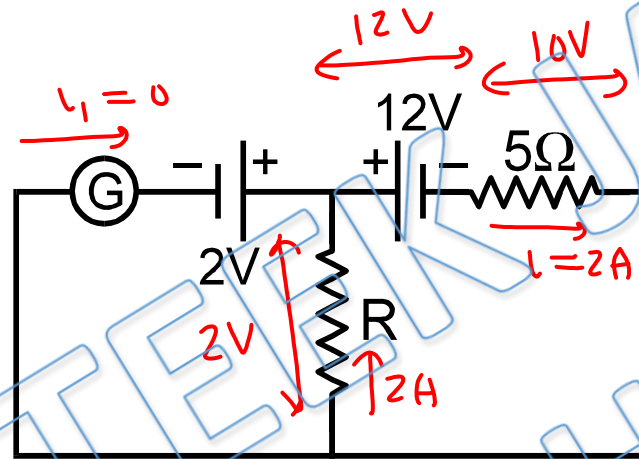Q.3) In the circuit shown, the galvanometer shows zero current. The value of resistance R is :



$$R = \frac{2V}{2A} = 1\Omega$$

$$I = \frac{12}{R+5}$$

(a)  $1\Omega$

(b)  $2\Omega$

(c)  $4\Omega$

(d)  $9\Omega$




Voltage across R

$$2V = IR = \frac{12R}{R+5}$$


$$2R + 10 = 12R$$

$$10R = 10, R = 1\Omega$$

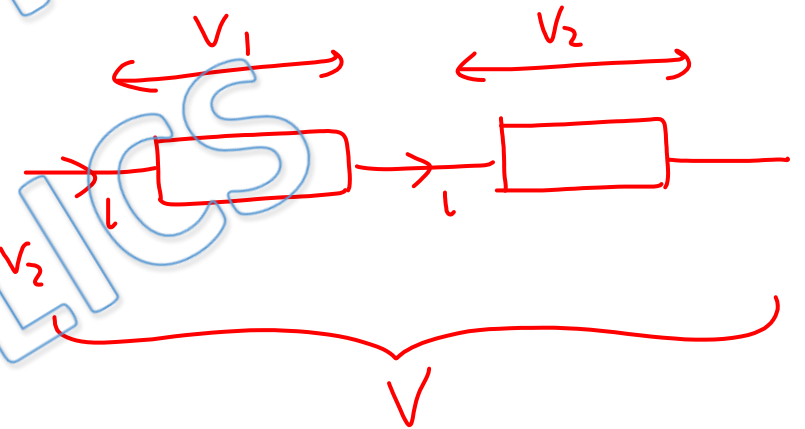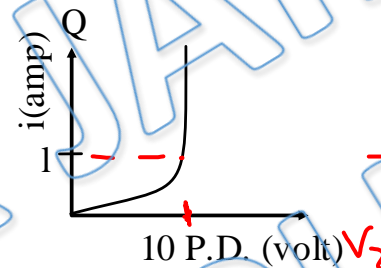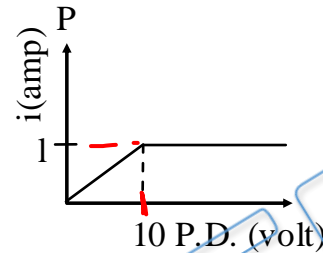
Q.4) Two current elements P and Q have current voltage characteristics as shown below; Which of the graphs given below represents current voltage characteristics when P and Q are in series




(a)

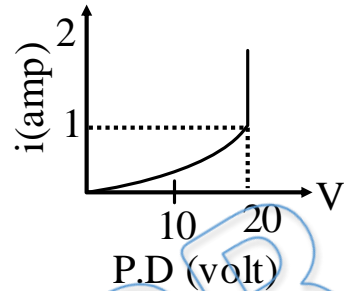


(b)

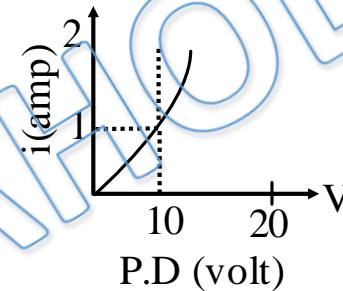

(c)

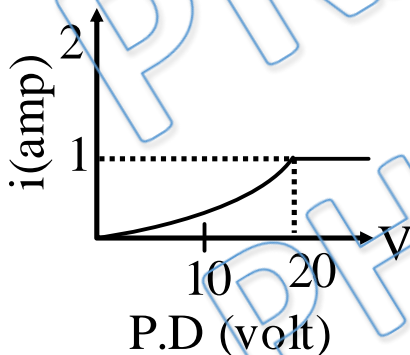

(d)

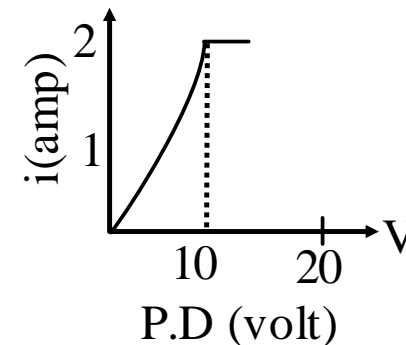

$$\begin{aligned}
 V &= 30 \\
 \Rightarrow V_2 &= 10V \\
 \Rightarrow V_1 &= 20V \\
 \Rightarrow i &= 1A
 \end{aligned}$$

Q.5) In the network shown in the figure below, calculate the potential difference between A and B ? ( $V_B - V_A$ ) =

- (a) 1V
- (b) -1 V
- (c) 2V
- (d) -2V

$$I_1 = \frac{6}{8} = \frac{3}{4} \text{ A}$$

$$I_2 = \frac{6}{3+1} = 1.5 \text{ A}$$


$$\Delta V = V_B - V_A$$

$$= +\left(\frac{3}{4} \times 2\right) + 4 - 3 \times 1.5$$

$$= 1.5 + 4 - 4.5$$

$$= 5.5 - 4.5$$

$$= 1 \text{ V}$$

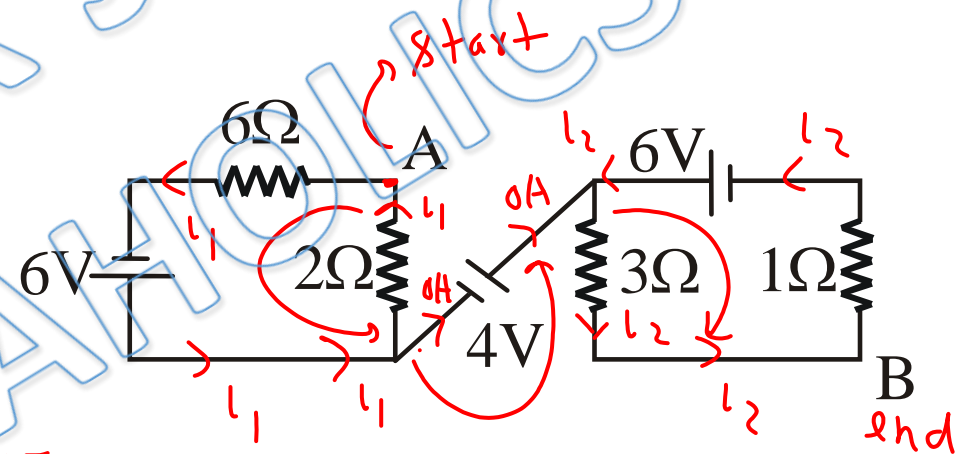



Q.6) Find the equivalent resistance between a & b

(a)  $\frac{7}{8}\Omega$

(b)  $\frac{8}{7}\Omega$

(c)  $\frac{6}{7}\Omega$

(d)  $\frac{7}{6}\Omega$

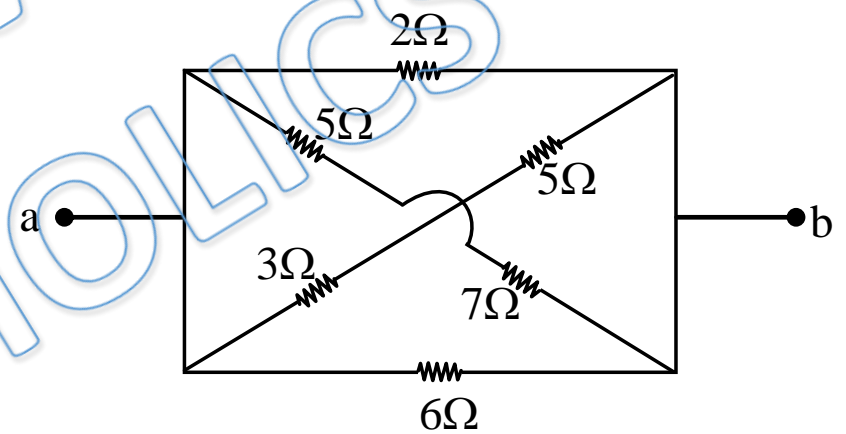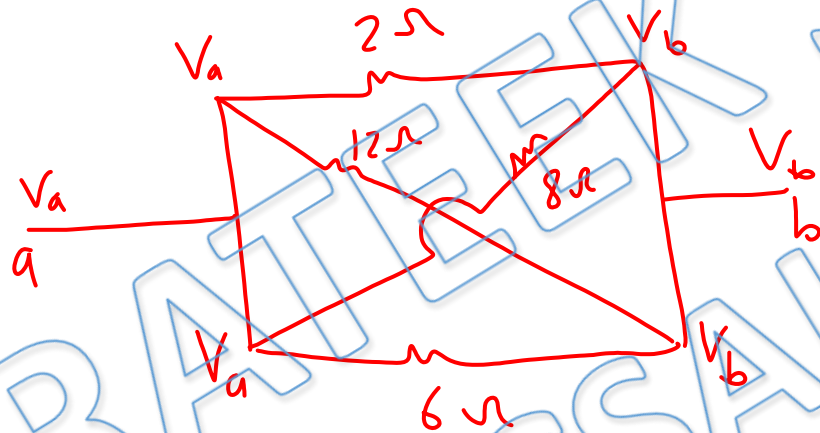


$$\begin{aligned} \frac{1}{R} &= \frac{1}{2} + \frac{1}{12} + \frac{1}{8} + \frac{1}{6} \\ &= \frac{12 + 2 + 3 + 4}{24} \\ &= \frac{21}{24} = \frac{7}{8} \end{aligned}$$

$$R = \frac{8}{7} \Omega$$

Q.7) A battery of emf  $E$  and internal resistance  $r$  is connected across a resistance  $R$ . Resistance  $R$  can be adjusted to any value greater than or equal to zero. A graph is plotted between the current ( $i$ ) passing through the resistance and potential difference ( $V$ ) across it. Select the correct alternative(s) -

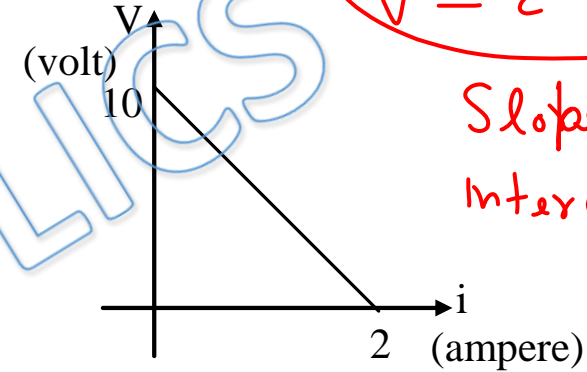- (a) internal resistance of battery is  $5\text{ohm}$
- (b) emf of the battery is  $20\text{V}$
- (c) maximum current which can be taken from the battery is  $4\text{A}$
- (d)  $V$ - $i$  graph can never be a straight line as shown in figure



$$V = \mathcal{E} - ir$$

$$\text{Slope} = -r$$


$$\text{Intercept} = \mathcal{E}$$

$$\mathcal{E} = 10\text{V}$$

$$-r = -10/2$$

$$r = 5\Omega$$

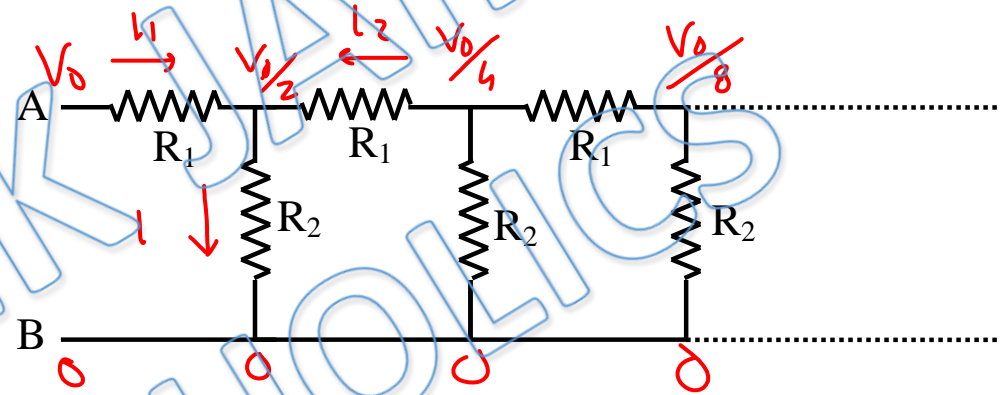Q.8) Consider an infinite ladder network. A voltage is applied between points A & B. If the voltage is halved after each section. Find the ratio  $R_1/R_2$ .



- (a) ~~1/2~~  
 (b) 1/3  
 (c) 2  
 (d) None of these



$$l = l_1 + l_2$$

$$\frac{V_0/2 - 0}{R_2} = \frac{V_0 - V_0/2}{R_1} + \frac{V_0/4 - V_0/2}{R_1}$$

$$\frac{V_0}{2R_2} = \frac{V_0/4}{R_1}$$

$$2R_2 = 4R_1 \Rightarrow \frac{R_1}{R_2} = \frac{1}{2}$$

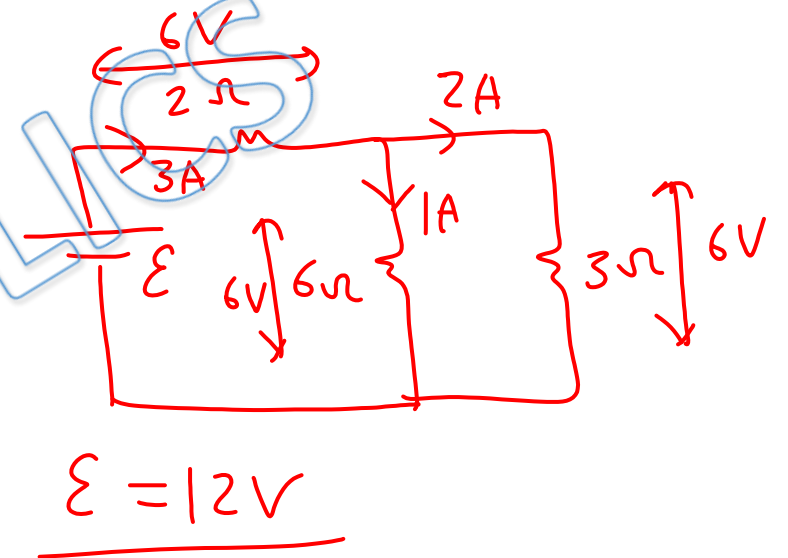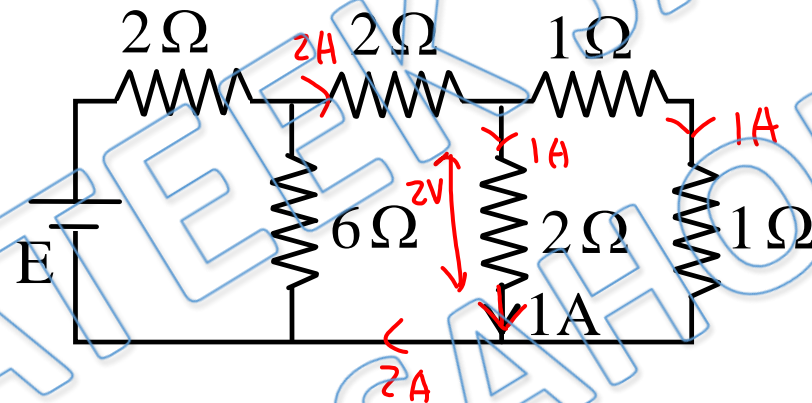Q.9) The emf of the battery shown in the figure is given by -



(a) 6 V

(b) 12 V

(c) 18 V


(d) 8 V



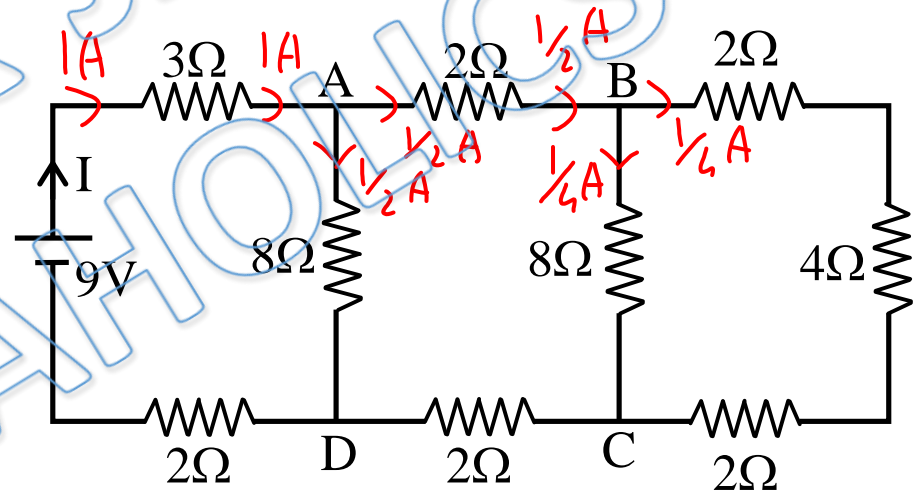Q.10) In the circuit shown in figure , the current through –

$$R_{\text{eff}} = 9\Omega \Rightarrow I = \frac{9}{9} = 1\text{A}$$

- ~~(a)~~ the 3ohm resistor is 0.50 A
- ~~(b)~~ the 3ohm resistor is 0.25 A
- ~~(c)~~ the 4ohm resistor is 0.50 A
- (d) the 4ohm resistor is 0.25 A



Q.11) There are two concentric spheres of radius  $a$  and  $b$  respectively. If the space between them is filled with medium of resistivity  $\rho$ , then the resistance of the inter gap between the two spheres will be

Resistance of differential shell

$$dR = \rho \frac{dx}{4\pi x^2}$$

all such shells are in series


(a)  $\frac{\rho}{4\pi(b+a)}$

(b)  $\frac{\rho}{4\pi} \left( \frac{1}{b} + \frac{1}{a} \right)$

(c)  $\frac{\rho}{4\pi} \left( \frac{1}{a^2} - \frac{1}{b^2} \right)$

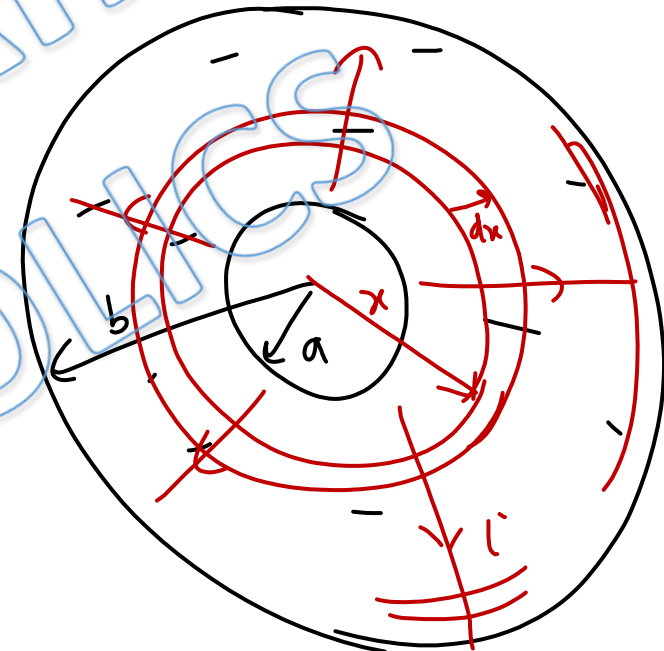(d)  $\frac{\rho}{4\pi} \left( \frac{1}{a} - \frac{1}{b} \right)$

$$R = \int dR = \frac{\rho}{4\pi} \int_a^b \frac{dx}{x^2} = \frac{\rho}{4\pi} \left( \frac{1}{a} - \frac{1}{b} \right)$$



Q.12) The equivalent resistance between point A and B is -


(a)  $4r$

(b)  $2r$


(c)  $r$

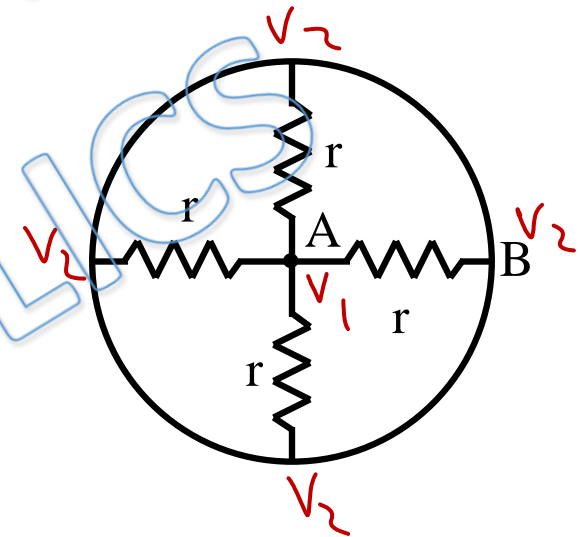(d)  $r/4$

$$\frac{1}{R} = \frac{1}{r} + \frac{1}{r} + \frac{1}{r} + \frac{1}{r}$$



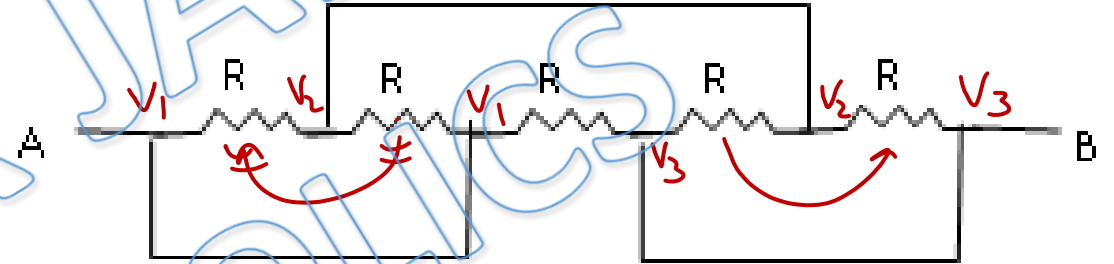Q.13) The equivalent resistance between A and B in the given circuit




(a)  $R$


~~(b)  $R/2$~~

(c)  $R/3$

(d)  $2R/3$

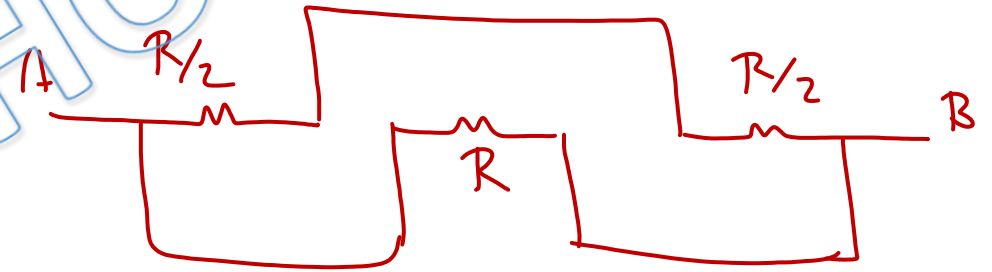

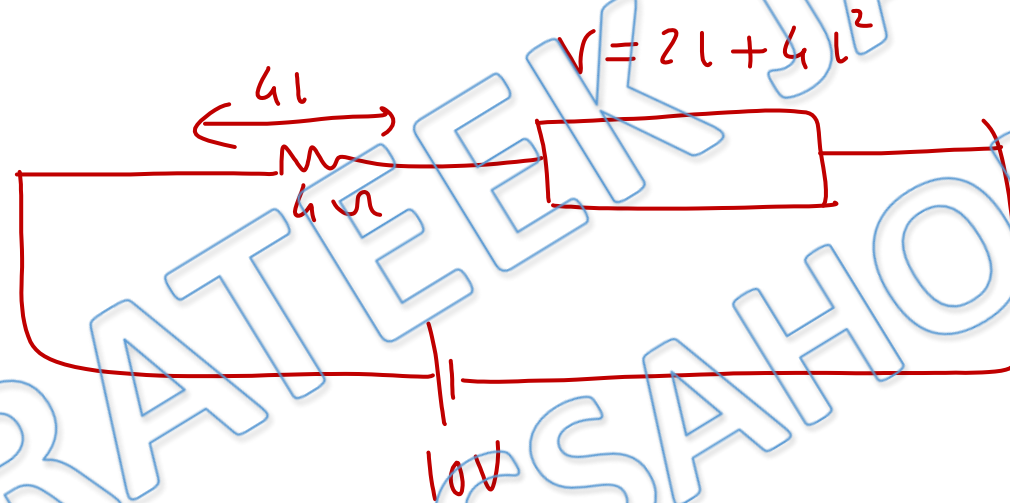Q.14) A 10 V car battery with negligible internal resistance is connected to a series combination of a  $4\Omega$  resistor that obeys Ohm's law and a thermistor that does not obey Ohm's law, but instead has a current-voltage relation  $V = \alpha I + \beta I^2$  with  $\alpha = 2\Omega$  and  $\beta = 4\Omega/A$ . The current through the  $4\Omega$  resistor is



$$4I^2 + 2I + 4I = 10$$

$$2I^2 + 3I = 5$$

$$I = 1A$$

(a) 1 A

(b) 2 A


(c) 2/5 A

(d) 5 A

Q.15) Find current in wire AB ?

$$R_{\text{eff}} = 2 + 2 + 2 \\ = 6\Omega$$

$$I_0 = \frac{18}{6} = 3A$$

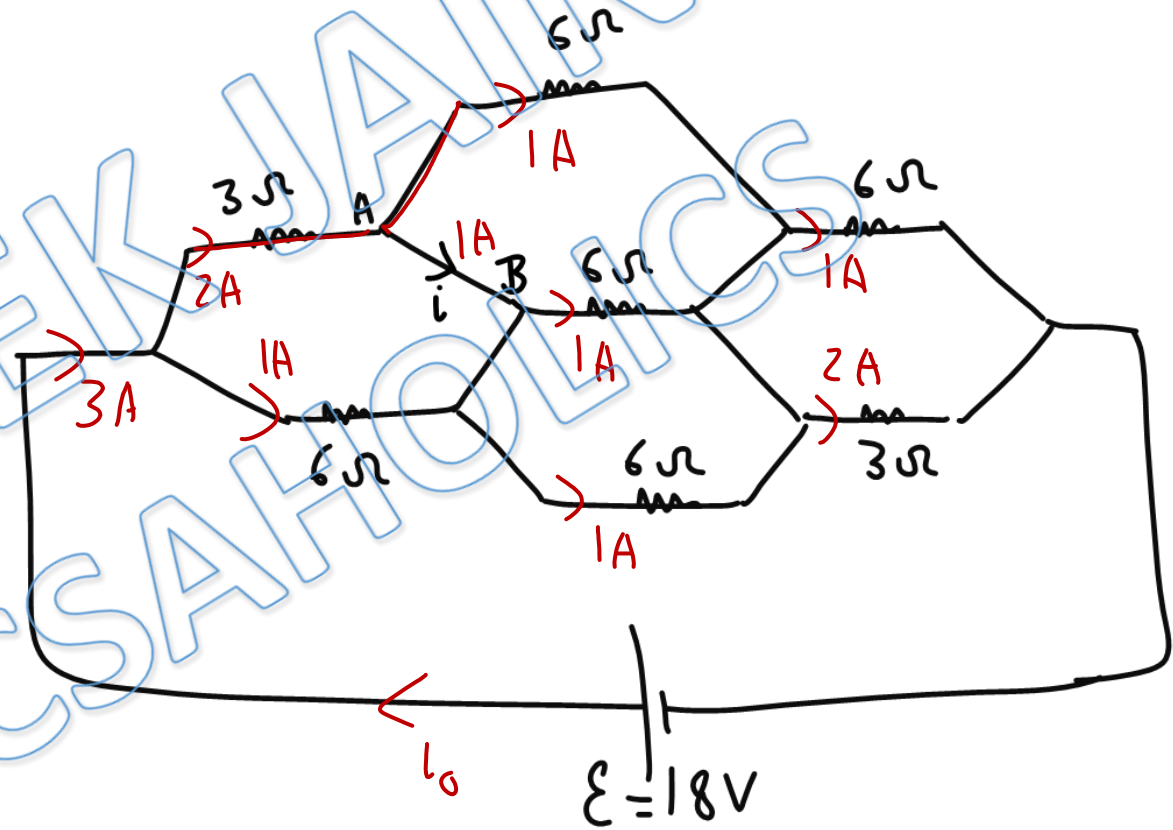

~~(a) 1A~~

(b) 2A

(c) 3A

(d) 4A

**For Video Solution of this DPP, Click on below link**

Video Solution  
on Website:-

<https://physicsaholics.com/home/courseDetails/98>

Video Solution  
on YouTube:-

<https://youtu.be/VQ1Y7ZGz3W4>

Written Solution  
on Website:-

<https://physicsaholics.com/note/notesDetails/53>

 **SUBSCRIBE**



[@Physicsaholics](#)

[@Physicsaholics\\_prateek](#)

[@NEET\\_Physics](#)

[@IITJEE-Physics](#)

[physicsaholics.com](#)

[Unacademy](#)



**CLICK**



Chalo Niklo