

## DPP – 5 (Current Electricity)

Video Solution on Website :-

<https://physicsaholics.com/home/courseDetails/98>


Video Solution on YouTube:-

<https://youtu.be/d5zMrnNvalE>


Written Solution on Website:-

<https://physicsaholics.com/note/notesDetails/53>

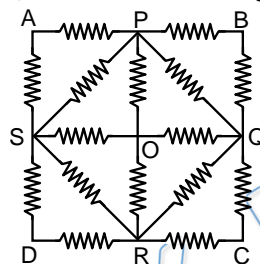
- Q 1. In figure point O is maintained zero volt and A, B, C and D are maintained at V volt. If all resistors have same resistance R, then current through branch



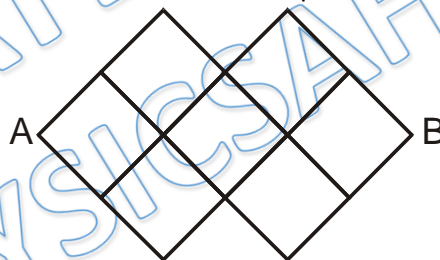- (a) OP is  $\frac{2V}{3R}$   
 (b) PQ is zero  
 (c) QR is  $\frac{V}{3R}$   
 (d) SD is  $\frac{V}{3R}$
- Q 2. In the shown wire frame, each side of a square (the smallest square) has a resistance R. The equivalent resistance of the circuit between the points A and B is :



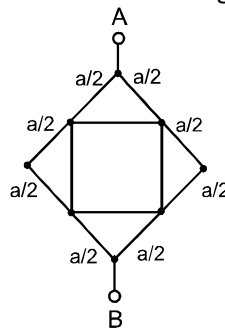
- (a) R      (b) 2R      (c) 4R      (d) 8R
- Q 3. Figure consists two squares made of uniform wire of resistance per unit length  $\lambda$ . Find out equivalent resistance between A and B. Side of large square is a.



- (a)  $\frac{(\sqrt{2}+1)\lambda a}{2}$   
 (b)  $\frac{\lambda a}{\sqrt{2}}$


- (c)  $\frac{\sqrt{2}\lambda a}{3}$   
 (d)  $\sqrt{2}\lambda a$

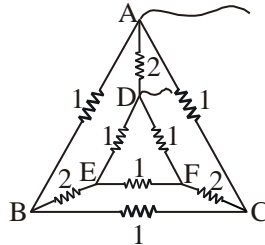Q 4. A network of nine conductors connects six points A, B, C, D, E and F as shown. The figures denote resistances in ohms. The equivalent resistance between A and D is




- (a)  $1\Omega$   
 (b)  $2\Omega$   
 (c)  $3\Omega$   
 (d)  $4\Omega$

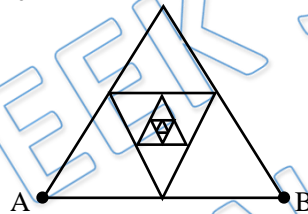Q 5. A frame made of thin homogeneous wire is shown in figure. Assume that the number of successively embedded equilateral triangle with sides decreasing by half tends to infinity. The side AB has a resistance  $R_0$ . Find the equivalent resistance between A and B.




- (a)  $\left(\frac{\sqrt{5}-1}{3}\right)R_0$   
 (b)  $\left(\frac{\sqrt{3}-1}{3}\right)R_0$   
 (c)  $\left(\frac{\sqrt{7}-1}{2}\right)R_0$   
 (d)  $\left(\frac{\sqrt{7}-1}{3}\right)R_0$

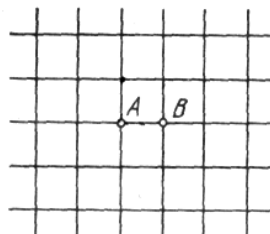Q 6. There is an infinite wire grid with square cells. The resistance of each wire between neighbouring joint connections is equal to  $R$ . Find the resistance of the whole grid between points A and B.




- (a)  $R$   
 (b)  $R/2$   
 (c)  $R/3$   
 (d)  $R/4$

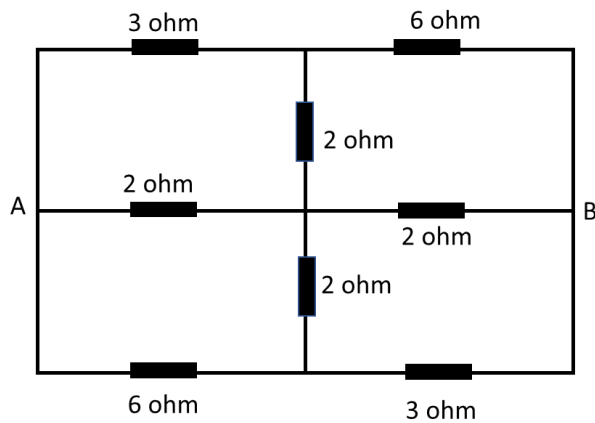Q 7. Effective resistance between A and B is




- (a)  $35/72$  ohm
- (b)  $72/35$  ohm
- (c)  $17/36$  ohm
- (d)  $36/17$  ohm

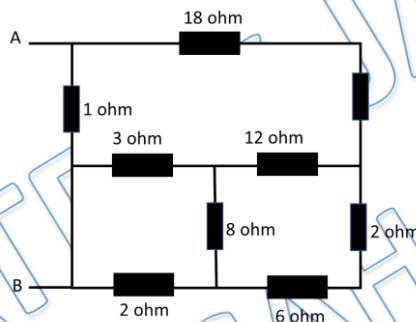Q 8. Effective resistance between A and B is




- (a) 2 ohm
- (b) 3 ohm
- (c) 6 ohm
- (d) 4 ohm

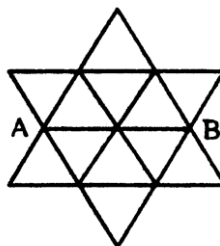Q 9. Find the equivalent resistance of the circuit between points A and B shown in figure is: (each branch is of resistance =  $1\Omega$ )




- (a) 3 ohm
- (b)  $17/30$  ohm
- (c)  $10/23$  ohm
- (d)  $22/35$  ohm

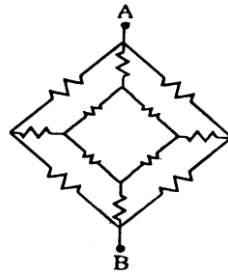Q 10. The figure shown a network of resistor each having value  $12\Omega$ . Find the equivalent resistance between points A and B.



- (a) 6 ohm
- (b) 3 ohm
- (c) 9 ohm
- (d) 2 ohm

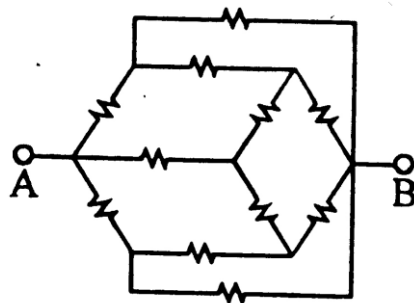Q 11. Calculate equivalent resistance of the network between points A and D .



- (a)  $3R/5$
- (b)  $5R/7$
- (c)  $R$
- (d)  $2R$

## Answer Key

Q.1 a, b, d	Q.2 b	Q.3 b	Q.4 a	Q.5 d
Q.6 b	Q.7 b	Q.8 c	Q.9 d	Q.10 c
Q.11 c				

PLUS

ICONIC \*\*

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

24 months ₹2,333/mo >  
No cost EMI ₹56,000

18 months ₹2,625/mo >  
No cost EMI ₹47,250

12 months ₹3,208/mo >  
No cost EMI ₹38,500

6 months ₹4,667/mo >  
No cost EMI ₹28,000

To be paid as a one-time payment

View all plans



Add a referral code

APPLY

# PHYSICSLIVE

PLUS

ICONIC \*\*

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

24 months ₹2,100/mo >  
No cost EMI +10% OFF ₹50,400

18 months ₹2,363/mo >  
No cost EMI +10% OFF ₹42,525

12 months ₹2,888/mo >  
No cost EMI +10% OFF ₹34,650

6 months ₹4,200/mo >  
No cost EMI +10% OFF ₹25,200

To be paid as a one-time payment

View all plans



Awesome! PHYSICSLIVE code applied



Use code **PHYSICSLIVE** to get 10% OFF on Unacademy PLUS.

# **Written Solution**


**DPP- 5 Current :Wheat Stone Bridge,Symmetric  
Circuits**

**By Physicsaholics Team**

Q.1) In figure point O is maintained zero volt and A, B, C and D are maintained at V volt. If all resistors have same resistance R, then current through branch

$$V_p = V_q = V_r = V_s$$

by symmetry

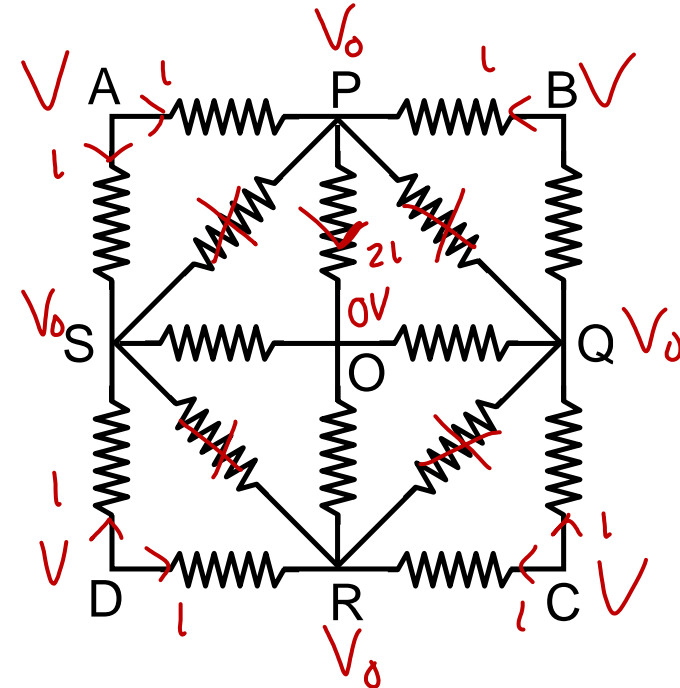

~~(a) OP is  $\frac{2V}{3R}$~~   
 (c) QR is  $\frac{V}{3R}$

~~(b) PQ is zero~~

Using junction law  
 at P →

~~(d) SD is  $\frac{V}{3R}$~~



$$\frac{V - V_0}{R} + \frac{V - V_0}{R} = \frac{V_0 - 0}{R}$$

$$2V - 2V_0 = V_0 \Rightarrow 3V_0 = 2V \Rightarrow V_0 = \frac{2V}{3}$$

$$i = \frac{V - 2V/3}{R} = \frac{V}{3R}$$

$$2i = \frac{2V}{3R}$$

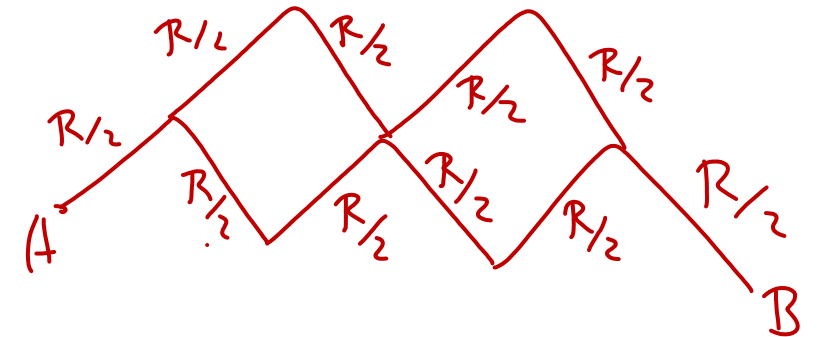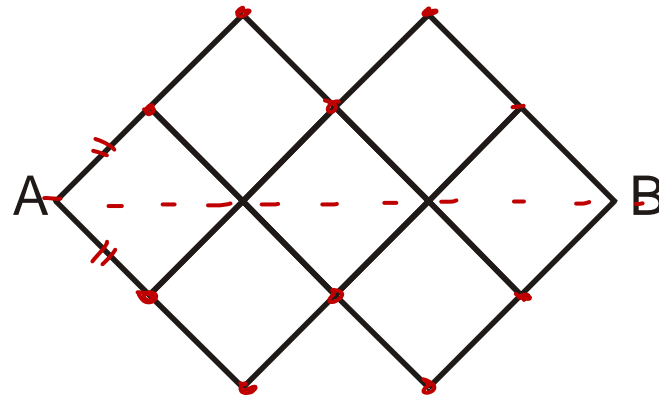Q.2) In the shown wire frame, each side of a square (the smallest square) has a resistance  $R$ . The equivalent resistance of the circuit between the points A and B is :



$$R_{\text{eff}} = \frac{R}{2} + R + R + \frac{R}{2}$$

(a)  $R$

(b)  $2R$

(c)  $4R$

(d)  $8R$



Q.3) Figure consists two squares made of uniform wire of resistance per unit length  $\lambda$ . Find out equivalent resistance between A and B. Side of large square is a


$P_1$  &  $P_2$  are at same potential  
 $S_1$  &  $S_2$  " " " "

(a)  $\frac{(\sqrt{2}+1)\lambda a}{2}$


(b)  $\frac{\lambda a}{\sqrt{2}}$

(c)  $\frac{\sqrt{2}\lambda a}{3}$

(d)  $\sqrt{2}\lambda a$

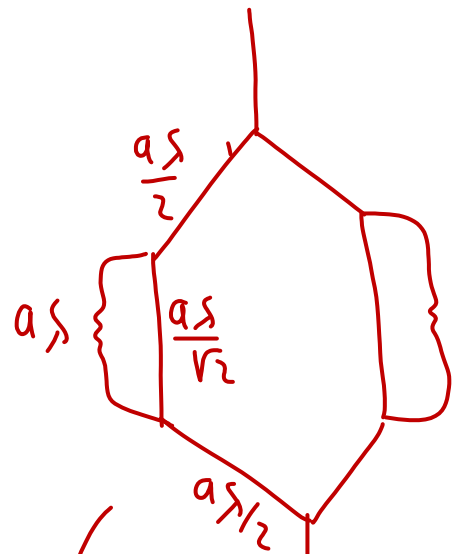
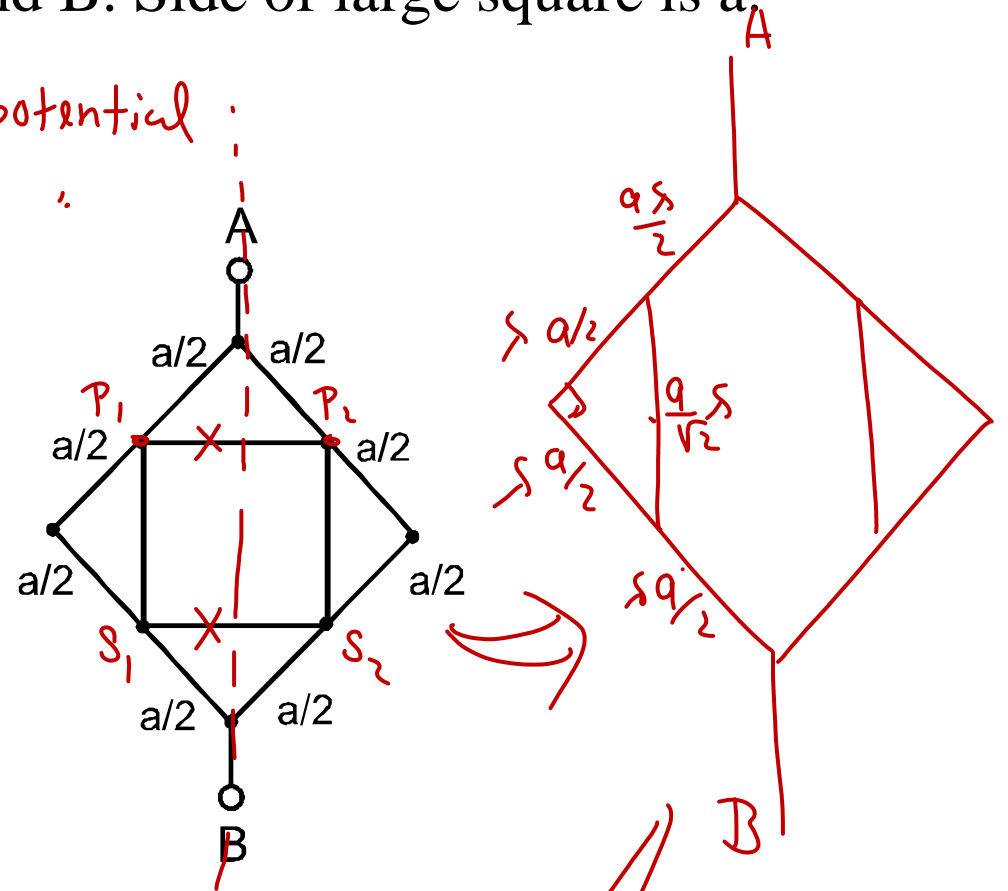
$$R_{eff} = \left( a\lambda + \frac{a\lambda \cdot \frac{a\lambda}{\sqrt{2}}}{a\lambda + \frac{a\lambda}{\sqrt{2}}} \right)^{1/2}$$





$$\begin{aligned} R_{\text{eff}} &= \frac{a_s}{2} \left[ 1 + \frac{1}{\sqrt{2} + 1} \right] \\ &= \frac{a_s}{2} \left[ 1 + \frac{1}{\sqrt{2} + 1} \times \frac{\sqrt{2} - 1}{\sqrt{2} - 1} \right] \\ &= \frac{a_s}{2} \left[ 1 + \sqrt{2} - 1 \right] \\ &= \frac{a_s}{\sqrt{2}} \end{aligned}$$

Ans. b

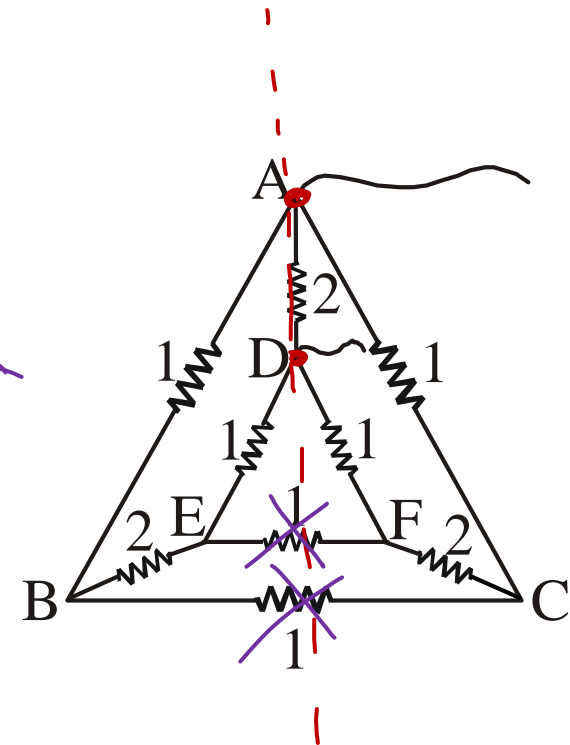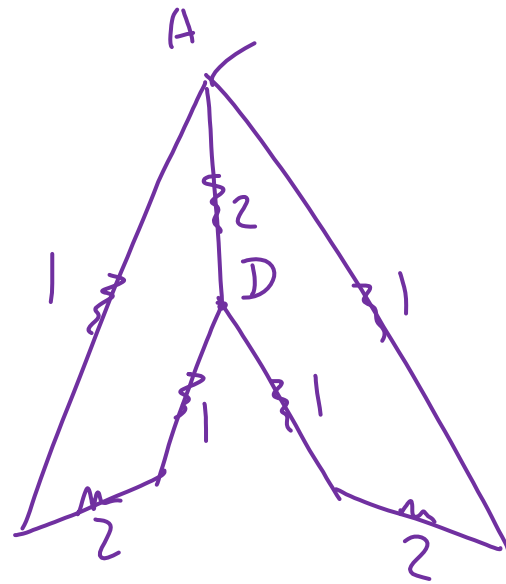Q.4) A network of nine conductors connects six points A, B, C, D, E and F as shown. The figures denote resistances in ohms. The equivalent resistance between A and D is

$$\underline{V_B = V_C}, \quad \underline{V_E = V_F}$$



(a)  $1\Omega$

(b)  $2\Omega$

(c)  $3\Omega$

(d)  $4\Omega$

$$\frac{1}{R_{eff}} = \frac{1}{4} + \frac{1}{4} + \frac{1}{2} = 1$$


$$R_{eff} = 1\Omega$$

$$R_0 + \frac{R R_0}{2R_0 + R} = \frac{2R_0^2 + R R_0 + R R_0}{2R_0 + R} = \frac{2R_0(R_0 + R)}{2R_0 + R}$$



Q.5) A frame made of thin homogeneous wire is shown in figure. Assume that the number of successively embedded equilateral triangle with sides decreasing by half tends to infinity. The side AB has a resistance  $R_0$ . Find the equivalent resistance between A and B.

effective resistance b/w A & B =  $R = ?$

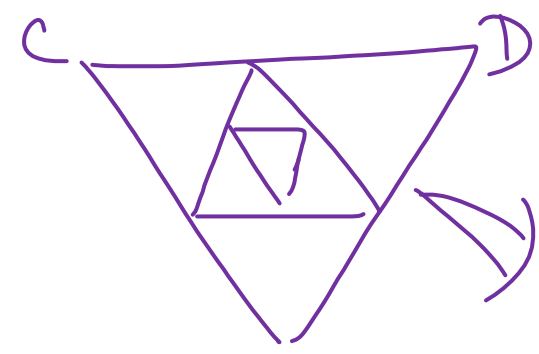
- (a)  $\left(\frac{\sqrt{5}-1}{3}\right)R_0$
- (b)  $\left(\frac{\sqrt{3}-1}{3}\right)R_0$
- (c)  $\left(\frac{\sqrt{7}-1}{2}\right)R_0$
- (d)  $\left(\frac{\sqrt{7}-1}{3}\right)R_0$



$$R_{CD} = R/2$$

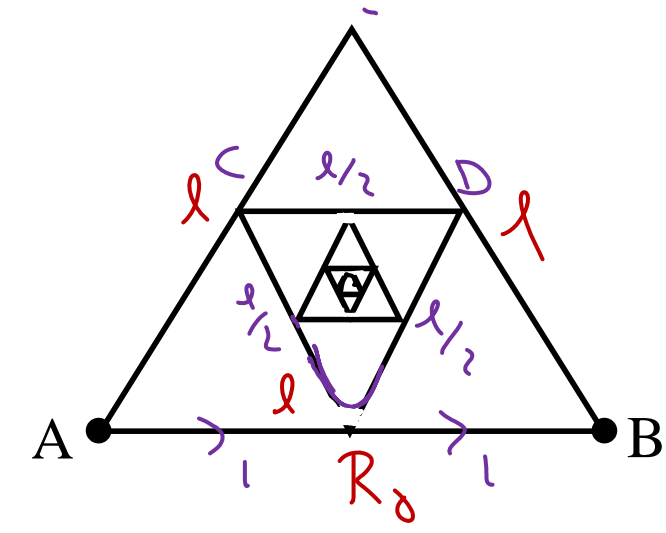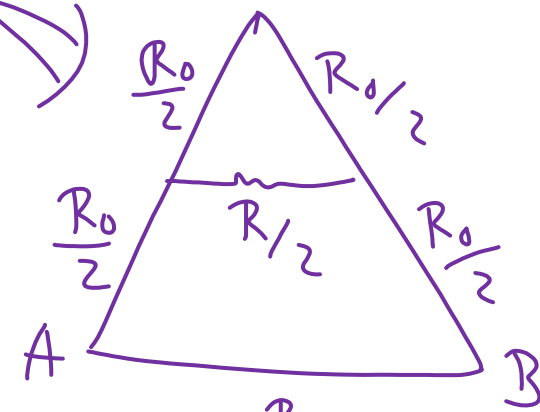
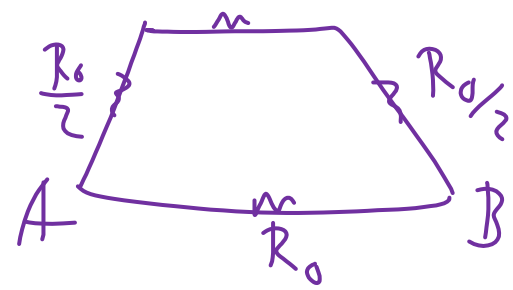
$$\frac{R_0 R/2}{R_0 + R/2} = \frac{R R_0}{2R_0 + R}$$



$$\frac{1}{R} = \frac{1}{R_0} + \frac{2R_0 + R}{2R_0(R_0 + R)}$$

$$\frac{1}{R} - \frac{1}{R_0} = \frac{2R_0 + R}{2R_0(R_0 + R)}$$

$$\Rightarrow \frac{R_0 - R}{R R_0} = \frac{2R_0 + R}{2R_0(R_0 + R)}$$

$$\Rightarrow 2(R_0^2 - R^2) = 2R_0R + R^2$$

$$\Rightarrow 0 = 3R^2 - 2R_0^2 + 2RR_0$$


$$R = \frac{-2R_0 + \sqrt{4R_0^2 + 24R_0^2}}{6} = \frac{-2R_0 + 2R_0\sqrt{7}}{6}$$

$$= \frac{R_0}{3}(\sqrt{7} - 1)$$

Ans. d

Q.6) There is an infinite wire grid with square cells. The resistance of each wire between neighbouring joint connections is equal to  $R$ . Find the resistance of the whole grid between points  $A$  and  $B$ .

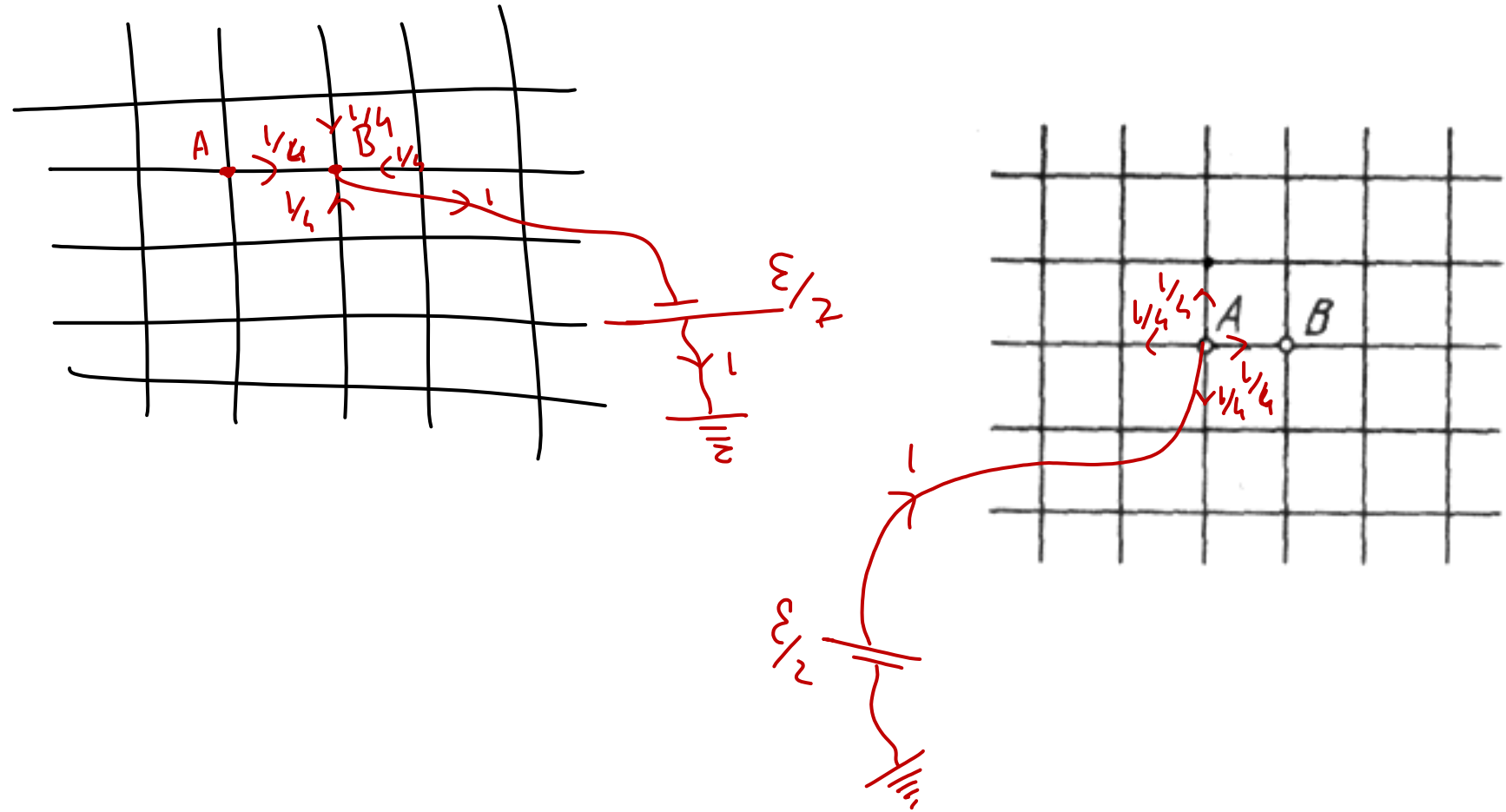
- (a)  $R$
- ~~(b)  $R/2$~~
- (c)  $R/3$
- (d)  $R/4$



for wire AB

$$\mathcal{E} = \frac{l}{2} R$$

$$\frac{\mathcal{E}}{l} = R/2$$

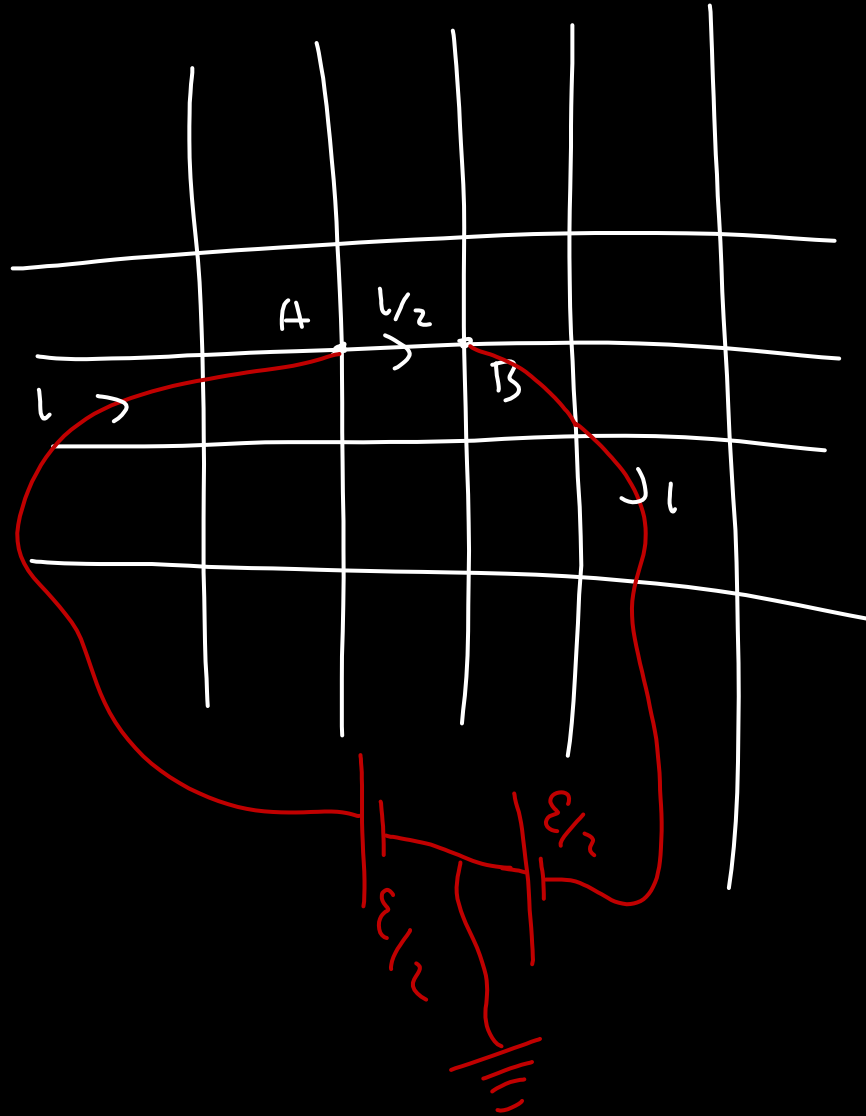



Total  $\mathcal{E}_{mf}$  applied  
 $= \mathcal{E}$

$$R_{eff} = \frac{\mathcal{E}}{l} = \frac{R}{2}$$


Ans. b

Q.7) Effective resistance between A and B is

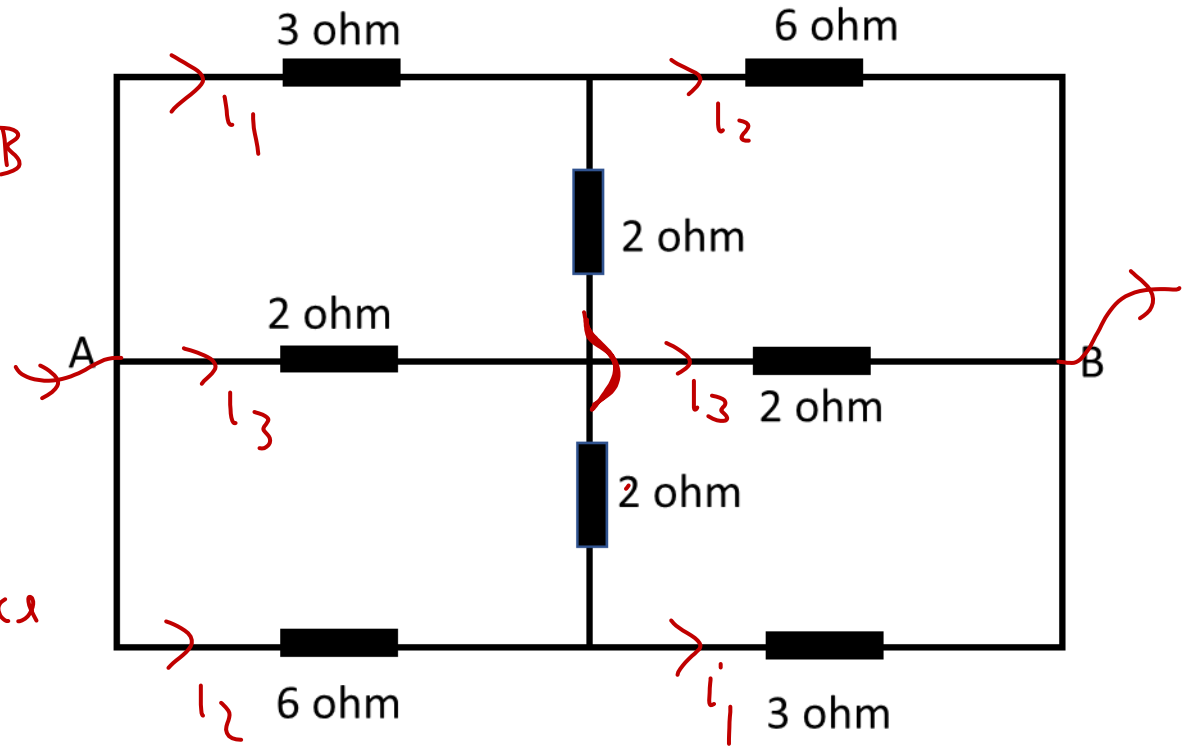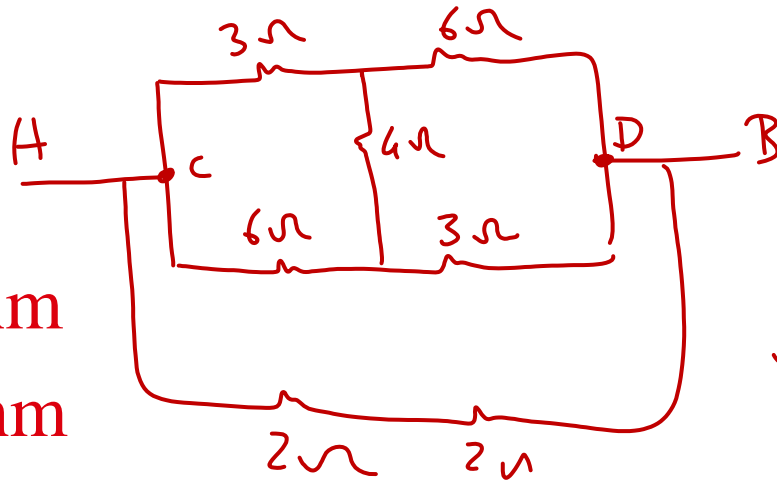- (a)  $35/72$  ohm
- (b)  $72/35$  ohm
- (c)  $17/36$  ohm
- (d)  $36/17$  ohm



To find effective resistance  
b/w C & D

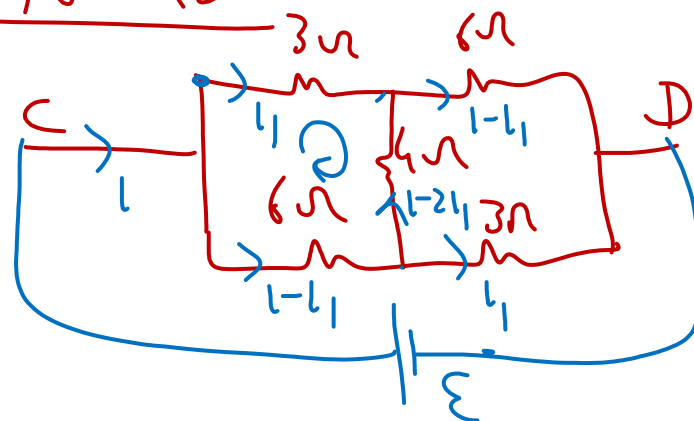

$$-3i_1 + 4(1-2i_1) + 6(1-i_1) = 0$$

$$17i_1 = 10i$$

$$i_1 = \frac{10i}{17}$$



$$I_1 = 10I/17$$

$$+ \mathcal{E} - 6(I - I_1) - 3I_1 = 0$$

$$\Rightarrow \mathcal{E} - 6 \times \frac{7}{17} I - \frac{30}{17} I = 0 \Rightarrow \mathcal{E} = \frac{72}{17} I$$

$$\Rightarrow R_{CD} = \frac{\mathcal{E}}{I} = \frac{72}{17} \text{ ohm}$$


$$\frac{1}{R_{AB}} = \frac{1}{4} + \frac{17}{72} = \frac{18 + 17}{72} = \frac{35}{72}$$

$$R_{AB} = \frac{72}{35} \Omega$$

Ans. b


Q.8) Effective resistance between A and B is

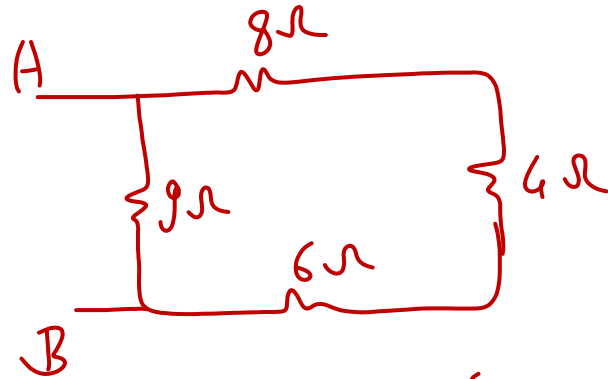- (a) 2 ohm
- (b) 3 ohm
- (c) 6 ohm
- (d) 4 ohm



$$R_{AB} = \frac{9 \times 8}{9 + 8} = 6 \Omega$$
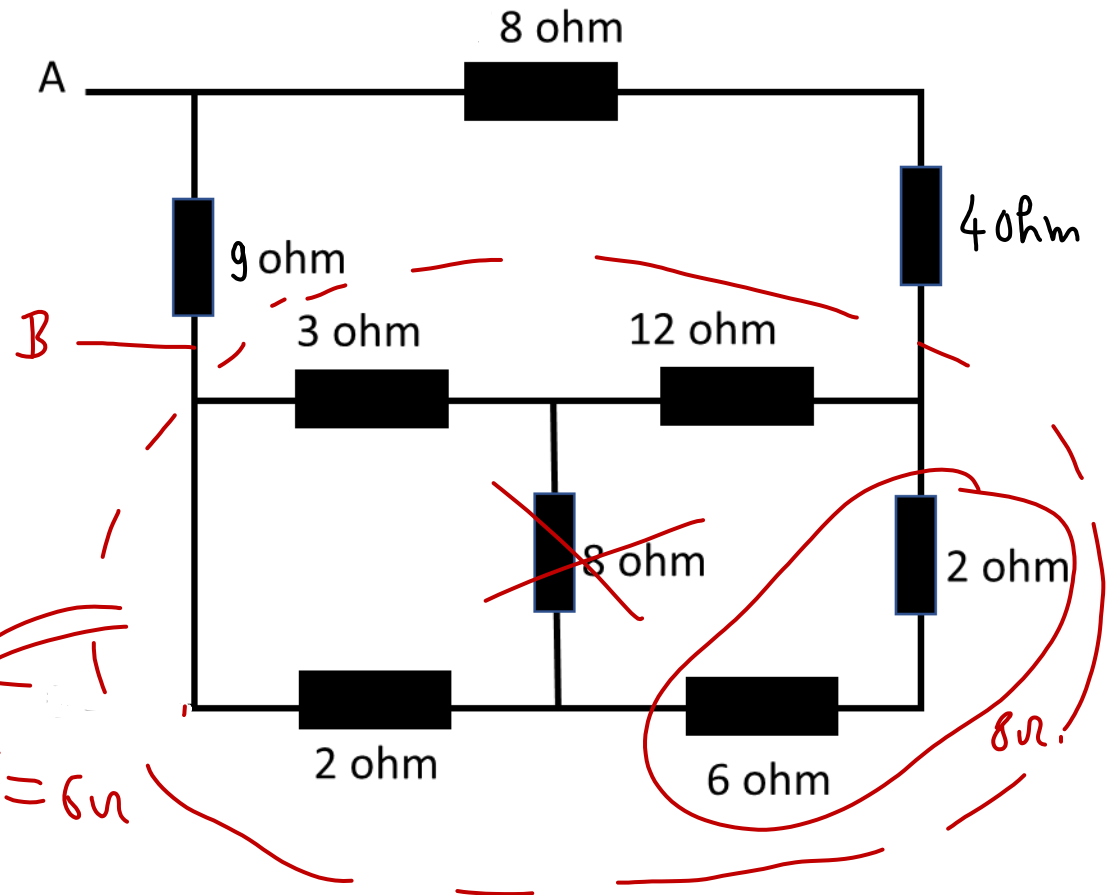
$$\frac{15 \times 2}{15 + 2} = 6 \Omega$$






$$\frac{R \times R/2}{R + R/2} = \frac{R}{3}$$


$$\frac{R \times R/3}{R + R/3} = \frac{R}{4}$$

Q.9) Find the equivalent resistance of the circuit between points A and B shown in figure is: (each branch is of resistance =  $1\Omega$ )

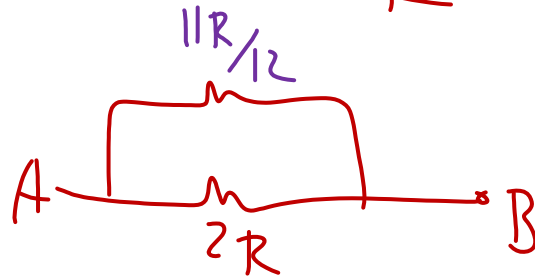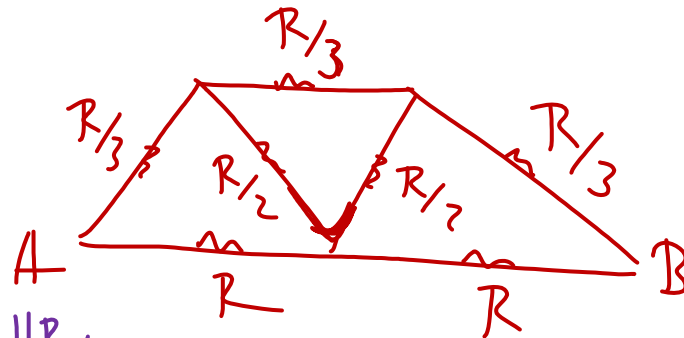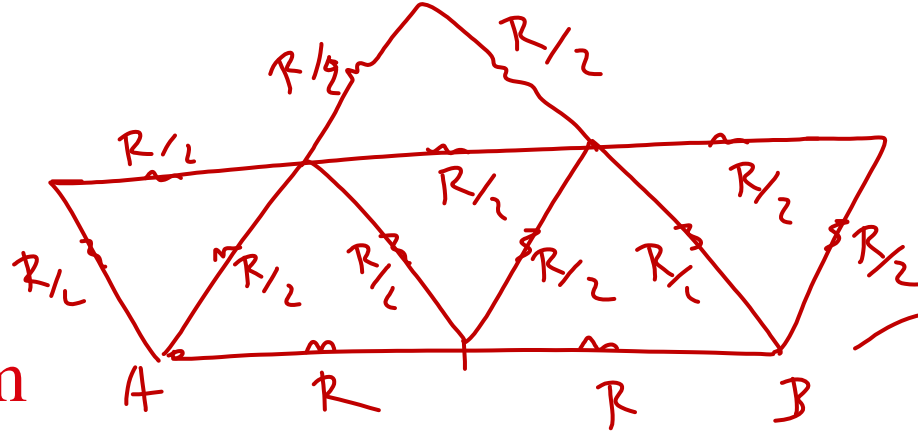- (a) 3 ohm
- (b)  $17/30$  ohm
- (c)  $10/23$  ohm
- (d)  $22/35$  ohm


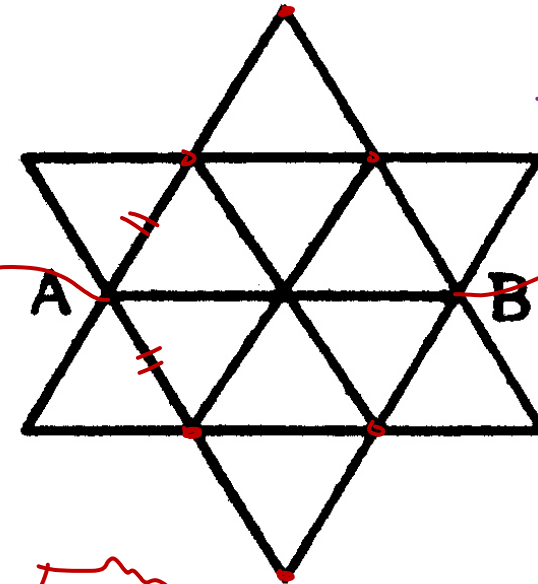
$$\frac{1}{R_{eff}} = \frac{1}{2R} + \frac{12}{11R} = \frac{11 + 24}{22R} = \frac{35}{22R} \Rightarrow R_{AB} = \frac{22R}{35}$$





$$\frac{\frac{2R}{3} + \frac{R}{4}}{\frac{8R + 3R}{12}} = \frac{11R}{12}$$




Q.10) The figure shown a network of resistor each having value  $12\Omega$ . Find the equivalent resistance between points A and B.

$$V_{P_1} = V_{P_2} \quad \& \quad V_{S_1} = V_{S_2}$$

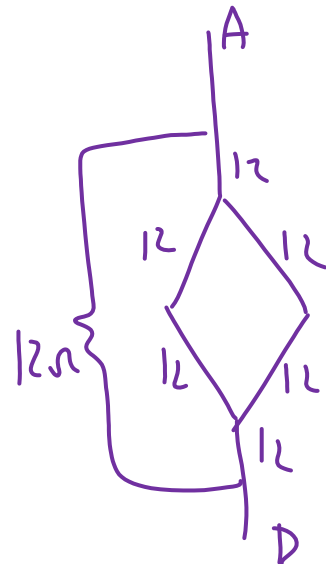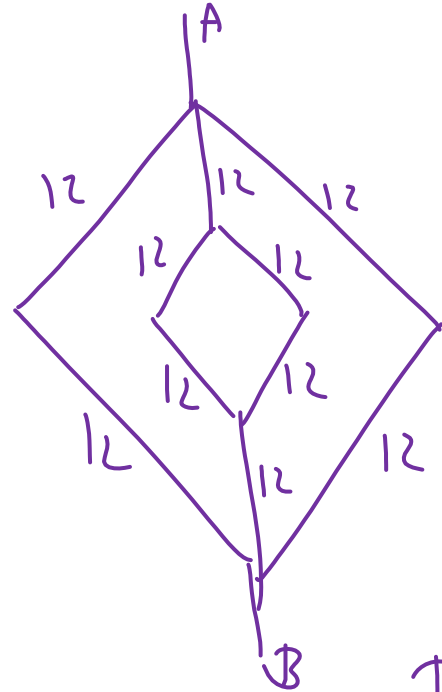- (a) 6 ohm
- (b) 3 ohm
- (c) 9 ohm
- (d) 2 ohm





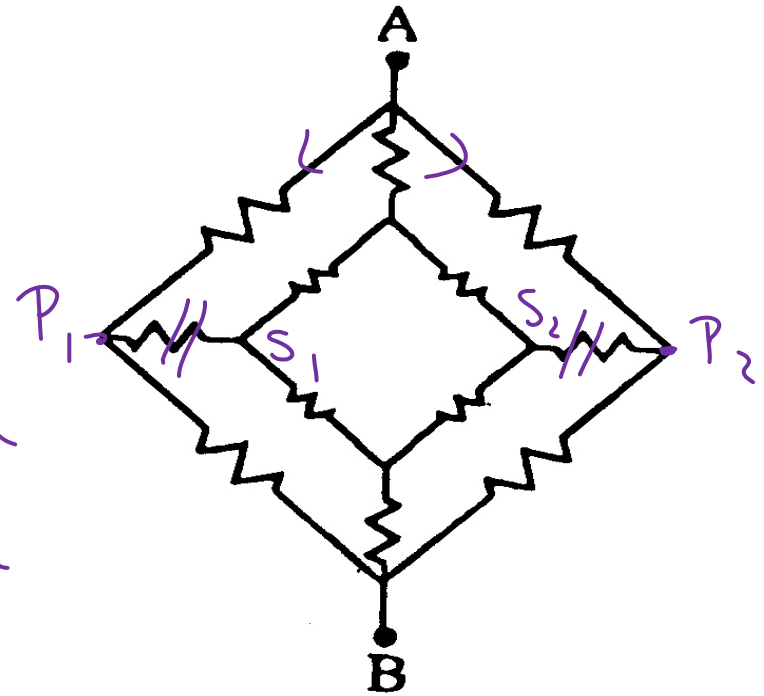
$$R_{AB} = \frac{9 \times 12}{\frac{36 \times 12}{48}} = 9 \Omega$$



Q.11) Calculate equivalent resistance of the network between points A and D .

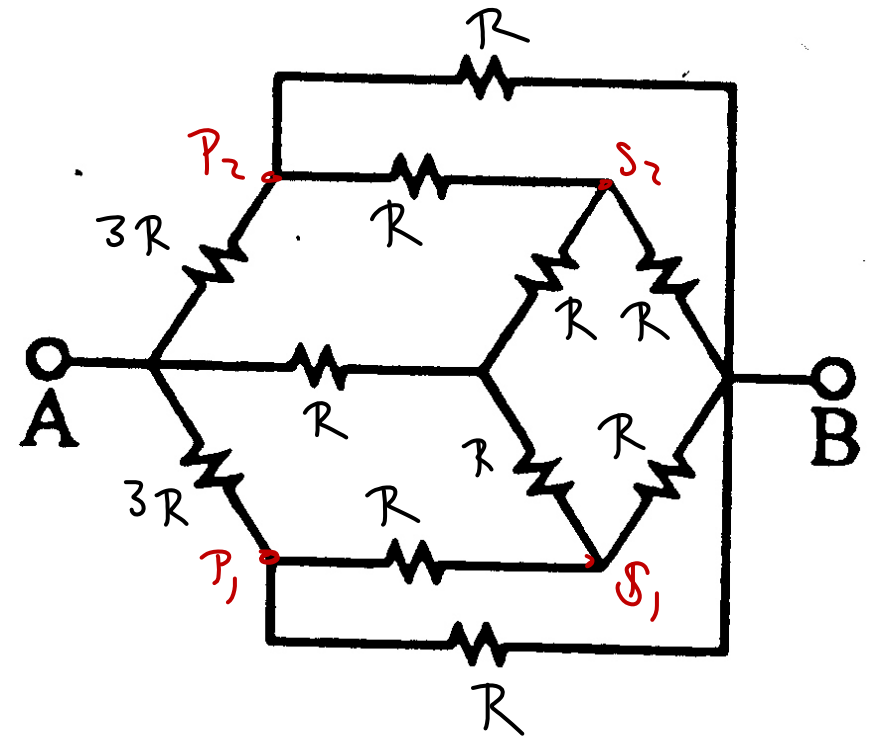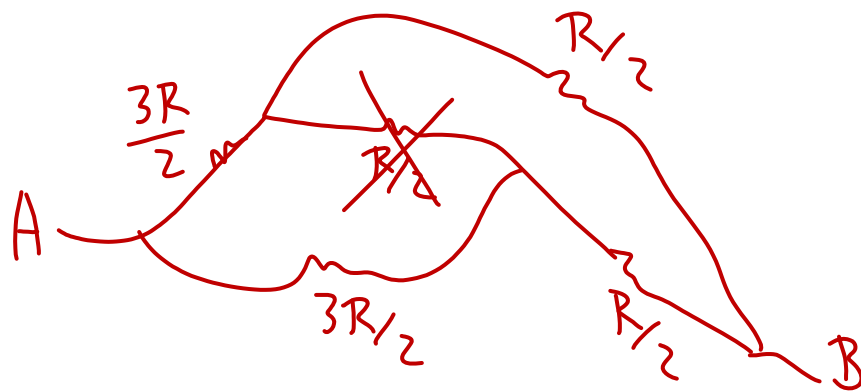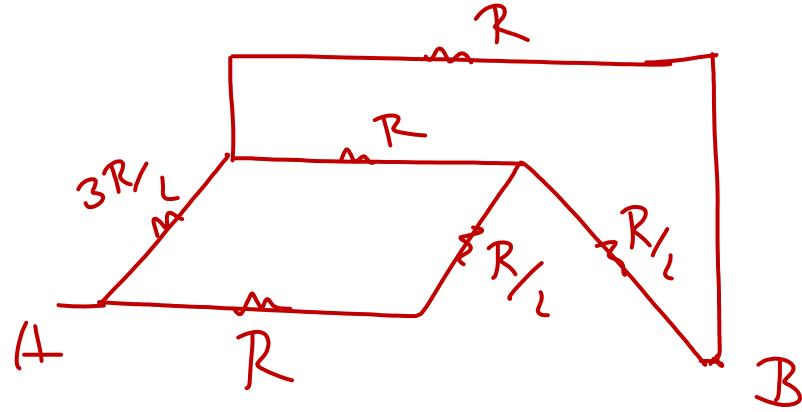- (a)  $3R/5$
- (b)  $5R/7$
- ~~(c)  $R$~~
- (d)  $2R$



**For Video Solution of this DPP, Click on below link**

Video Solution  
on Website:-

<https://physicsaholics.com/home/courseDetails/98>

Video Solution  
on YouTube:-

<https://youtu.be/d5zMrmNvale>

Written Solution  
on Website:-

<https://physicsaholics.com/note/notesDetails/53>

 **SUBSCRIBE**



[@Physicsaholics](#)

[@Physicsaholics\\_prateek](#)

[@NEET\\_Physics](#)

[@IITJEE-Physics](#)

[physicsaholics.com](#)

[Unacademy](#)



**CLICK**

Chalo Niklo