



Video Solution on Website:-

<https://physicsaholics.com/home/courseDetails/79>

Video Solution on YouTube:-


https://youtu.be/ggMttZ_Ai3c

Written Solution on Website:-

<https://physicsaholics.com/note/notesDetails/61>


- Q 1. An e.m.f. of 5 volt is produced by a self inductance, when the current changes at a steady rate from 3 A to 2 A in 1 millisecond. The value of self inductance is
(a) Zero (b) 5 H
(c) 5000 H (d) 5 mH
- Q 2. An average emf of 25 V is induced in an inductor when the current in it is changed from 2.5 A in one direction to the same value in the opposite direction in 0.1s. Find the self-inductance of the inductor.
(a) 0.5 H (b) 1 H
(c) 5H (d) 50 mH
- Q 3. The current in ampere through an inductor is $I = (10+20t)$. Here t is in second. The induced emf in the inductor 4V. The self inductance of the inductor is, $L = \dots$ H
(a) 2 (b) 20
(c) 0.2 (d) 0.02
- Q 4. In an inductor of inductance $L = 100$ mH, a current of $I = 10$ A flowing. The energy stored in the inductor is
(a) 5 J (b) 10 J
(c) 100 J (d) 1000 J
- Q 5. The magnetic potential energy stored in a certain inductor is 25 mJ, when the current in the inductor is 60 mA. This inductor is of inductance
(a) 13.89 H (b) 0.138 H
(c) 1.389 H (d) 138.8 H
- Q 6. In what form is the energy stored in an inductor of A coil of inductance L is carrying a steady current i. What is the nature of its stored energy
(a) Magnetic (b) Electrical
(c) Both magnetic and electrical (d) Heat
- Q 7. A coil of self-inductance 50 henry is joined to the terminals of a battery of e.m.f. 2 volts through a resistance of 10 ohm and a steady current is flowing through the circuit. If the battery is now disconnected, the time in which the current will decay to $1/e$ of its steady value is
(a) 500 seconds (b) 50 seconds
(c) 5 seconds (d) 0.5 seconds

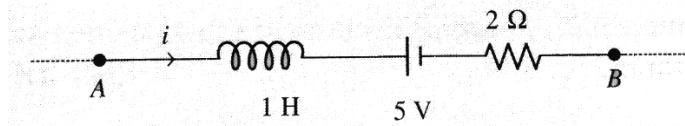- Q 8. AB is a part of circuit. Find the potential difference $V_A - V_B$ if current $I = 2A$ and is constant




- (a) 9V (b) 10 V
(c) 8V (d) zero

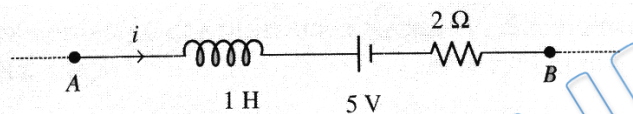- Q 9. AB is a part of circuit. Find the potential difference $V_A - V_B$ if
(a) current $I = 2A$ and is increasing at the rate of $1 A/s$
(b) current $I = 2A$ and is decreasing at the rate of $1 A/s$




- (a) 8V, 9V (b) 8V, 6V
(c) 9V, 8V (d) 10V, 8V

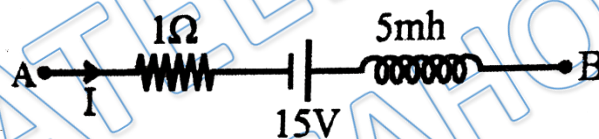- Q 10. If $I = 5A$ and decreasing at a rate of $10^3 A/sec$, then potential difference $V_B - V_A$ will be




- (a) 5V (b) 10V
(c) 15V (d) 20V

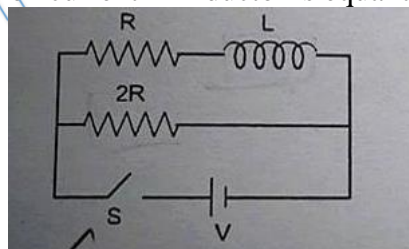- Q 11. Consider a L-R circuit shown in figure. There is no current in circuit switch S is closed at $t = 0$, time instant when current in inductor is equal to current in resistor $2R$ will be:



- (a) $\frac{L}{R} \ln 2$ (b) $\frac{2L}{R} \ln 2$
(c) $\frac{L}{2R} \ln 2$ (d) $\frac{L}{2R}$

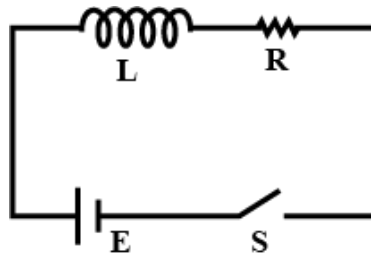- Q 12. In the circuit shown in figure switch S is closed at time $t = 0$. The charge which passes through the battery in one time constant is



(a) $\frac{eR^2E}{L}$
 (c) $\frac{EL}{eR^2}$

(b) $E \left(\frac{L}{R} \right)$
 (d) $\frac{eL}{ER}$

PRATEEK JAIN
PHYSICSAHOLICS

Answer Key

Q.1 d	Q.2 a	Q.3 c	Q.4 a	Q.5 a
Q.6 a	Q.7 c	Q.8 a	Q.9 d	Q.10 c
Q.11 a	Q.12 c			

PLUS

ICONIC **

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

24 months ₹2,333/mo >
No cost EMI ₹56,000

18 months ₹2,625/mo >
No cost EMI ₹47,250

12 months ₹3,208/mo >
No cost EMI ₹38,500

6 months ₹4,667/mo >
No cost EMI ₹28,000

To be paid as a one-time payment

[View all plans](#)



Add a referral code

APPLY

PHYSICSLIVE

Use code **PHYSICSLIVE** to get 10% OFF on Unacademy PLUS.

PLUS

ICONIC **

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

24 months ₹2,100/mo >
No cost EMI +10% OFF ₹50,400

18 months ₹2,363/mo >
No cost EMI +10% OFF ₹42,525

12 months ₹2,888/mo >
No cost EMI +10% OFF ₹34,650

6 months ₹4,200/mo >
No cost EMI +10% OFF ₹25,200

To be paid as a one-time payment

[View all plans](#)



Awesome! **PHYSICSLIVE** code applied



Written Solution

DPP- 4 EMI: Self inductance, RL Circuit, Energy stored in Inductor

By Physicsaholics Team

Solution: 1

$$\phi = LI$$

$$\varepsilon = -L \frac{dI}{dt}$$

$$5 = -L \left(\frac{2-3}{10^{-3}} \right)$$

$$5 = -L \left(-\frac{1}{10^{-3}} \right)$$

$$L = 5 \times 10^{-3} \text{ H}$$

$$\boxed{L = 5 \text{ mH}} \text{ Ans.}$$

Ans. d

Solution: 2

$$E = L \frac{dI}{dt}$$

$$\frac{dI}{dt} = \frac{2 \times 2.5}{0.1} = \frac{5}{0.1} = 50 \text{ Amp/sec}$$

$$25 = L \times 50$$

$$L = \frac{25}{50}$$

$$L = 0.5 \text{ H} \quad \text{Ans.}$$

Ans. a

Solution: 3

$$E = L \frac{dI}{dt}$$

$$E = L \frac{d}{dt} (10 + 20t)$$

$$E = L (20)$$

$$\phi = L \times 20$$

$$L = \frac{\phi}{20} = \frac{1}{5}$$

$$L = 0.2 \text{ H} \quad \text{Ans}$$

Ans. c

Solution: 4

$$U = \frac{1}{2} L I^2$$

$$U = \frac{1}{2} \times 100 \times 10^{-3} \times (10)^2$$

$$U = \frac{1}{2} \times 10^{-1} \times 100$$

$$U = 5 \text{ J} \quad \text{Ans.}$$

PRATEEK JAIN
PHYSICSAHOLICS

Ans. a

Solution: 5

$$U = \frac{1}{2} L I^2$$

$$25 \times 10^{-3} \text{ J} = \frac{1}{2} \times L \times (60 \times 10^{-3})^2$$

$$L = \frac{50 \times 10^{-3}}{(60)^2 \times 10^{-6}}$$

$$L = \frac{50 \times 10^{-3} \times 10^6}{(60)^2}$$

$$L = \frac{50 \times 10^3}{36 \times 10^2} = \frac{500}{36}$$

$$L = 13.89 \text{ H}$$

Ans. a

Solution: 6

An inductor stores energy in its magnetic field.

PRATEEK JAIN
PHYSICSAHOLICS

Ans. a

Solution: 7

$$I = I_0 e^{-t/\tau}$$

$$\tau = L/R$$

and $\tau = \frac{L}{R}$
 $= \frac{50}{10}$

$$\tau = 5 \text{ sec}$$

for; $I = I_0/e$

$$\frac{I_0}{e} = I_0 e^{-t/\tau}$$

$$\frac{1}{e} = e^{-t/\tau}$$

$$\ln \frac{1}{e} = -\frac{t}{\tau} \ln e$$

$$-1 = -\frac{t}{\tau}$$

$$t = \tau$$


\therefore time

$$t = 5 \text{ sec}$$

Ans.

Ans. c

Solution: 8

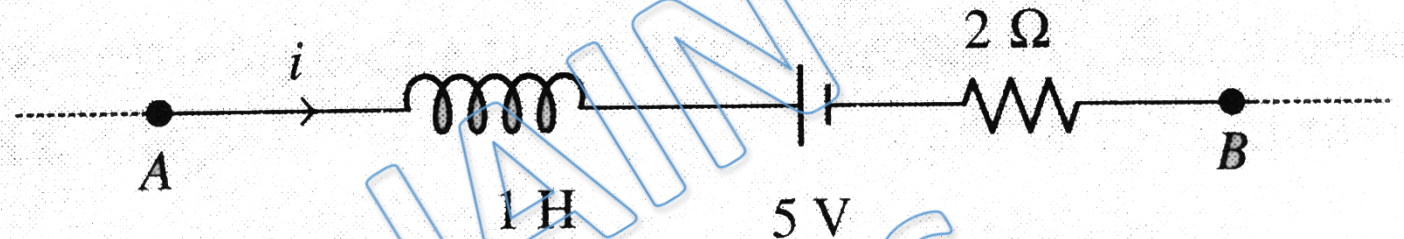

$$V_A - L \frac{dI}{dt} - 5 = IR = V_B$$


$$\begin{aligned} V_A - V_B &= L \frac{dI}{dt} + 5 + IR \\ &= 1 \times 0 + 5 + 2 \times 2 \\ &= 0 + 5 + 4 \end{aligned}$$

$$\left[\begin{aligned} \because I &= \text{constant} \\ \therefore \frac{dI}{dt} &= 0 \end{aligned} \right]$$

$$\boxed{V_A - V_B = 9V} \quad \text{Ans.}$$

Ans. a

Solution: 9

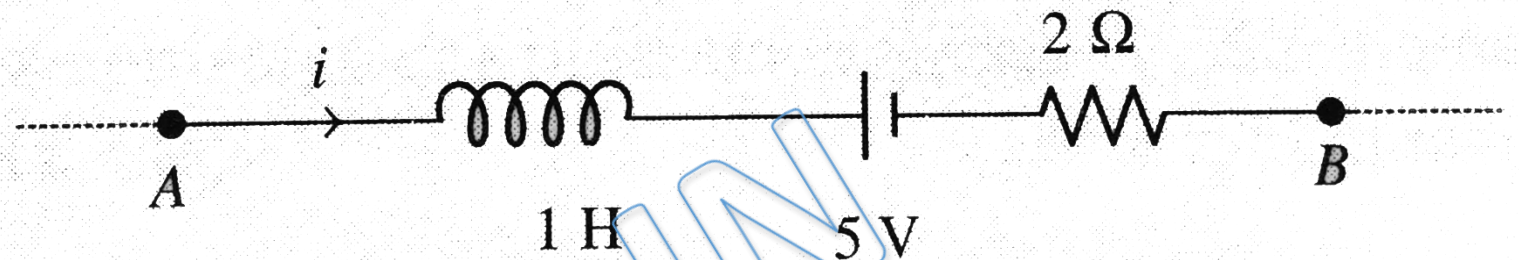

Case-1

$$i = 2A ; \frac{di}{dt} = 1 A/s$$

$$V_A - L \frac{di}{dt} - 5 = iR = V_B$$

$$V_A - V_B = L \frac{di}{dt} + 5 + iR$$

$$= 1 \times (1) + 5 + 2 \times 2$$

$$= 1 + 5 + 4$$

$$V_A - V_B = 10 \text{ Volt} \quad \text{Ans.}$$

Case-2

$$i = 2A ; \frac{di}{dt} = -1 A/s$$

$$V_A - L \frac{di}{dt} - 5 = iR = V_B$$

$$V_A - V_B = L \frac{di}{dt} + 5 + iR$$

$$= 1 \times (-1) + 5 + 2 \times 2$$

$$= -1 + 5 + 4$$

$$V_A - V_B = 8 \text{ Volt} \quad \text{Ans.}$$

Ans. d

Solution: 10

$$V_A - IR + 15 - L \frac{dI}{dt} = V_B$$

$$V_A - V_B = IR - 15 + L \frac{dI}{dt}$$

$$I = 5 \text{ A}$$

$$\frac{dI}{dt} = -10^3 \text{ A/sec}$$

$$V_A - V_B = 5 \times 1 - 15 + (5 \times 10^{-3}) (-10^3)$$

$$V_A - V_B = 5 - 15 - 5$$

$$V_A - V_B = -15 \text{ V}$$

$$\Rightarrow \boxed{V_B - V_A = 15 \text{ Volt}} \text{ Ans.}$$



Ans. c

Solution: 11

$$I_2 = \frac{V}{2R}$$

$$I_1 = (I_1)_{\max} (1 - e^{-t/\tau})$$

$$(I_1)_{\max} = \frac{V}{R}$$

$$I_1 = \frac{V}{R} (1 - e^{-t/\tau})$$

$$\tau = L/R$$

when; $I_1 = I_2 = \frac{V}{2R}$

$$\frac{V}{2R} = \frac{V}{R} (1 - e^{-t/\tau})$$

$$\frac{1}{2} = (1 - e^{-t/\tau})$$


$$e^{-t/\tau} = \frac{1}{2}$$

$$e^{-t/\tau} = \frac{1}{2}$$

$$\ln e^{-t/\tau} = \ln \frac{1}{2} \Rightarrow \frac{t}{\tau} = \ln 2$$

$$t = \tau \ln 2$$
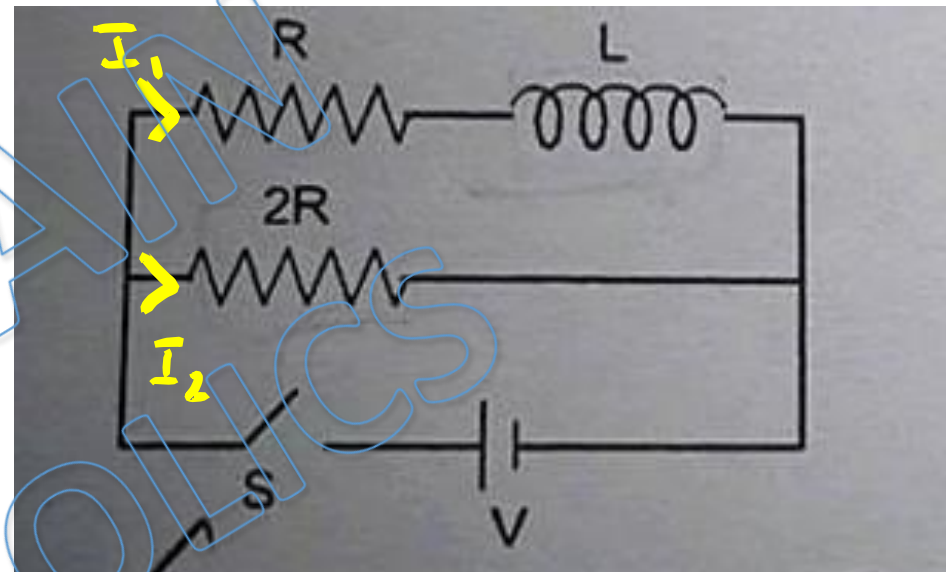
$$t = \frac{L}{R} \ln 2 \quad \text{Ans.}$$



Ans. a

Solution: 12

$$t=0 \text{ to } t=z = \frac{L}{R}$$

$$I = I_0 (1 - e^{-t/\tau})$$

$$\frac{dq}{dt} = \frac{E}{R} (1 - e^{-t/\tau})$$

$$\int dq = \int_0^z \frac{E}{R} (1 - e^{-t/\tau}) dt$$

$$\Delta q = \frac{E}{R} \left(t - \frac{e^{-t/\tau}}{-1/\tau} \right)_0^z = \frac{E}{R} \left[t + \tau e^{-t/\tau} \right]_0^z = \frac{E}{R} [z + \tau e^{-1} - 0 - \tau]$$

$$\Delta q = \frac{E}{R} \left[z + \frac{z}{e} - \tau \right] = \frac{E}{R} \left[\frac{z}{e} \right] = \frac{E}{R} \left[\frac{L}{R} \right]$$

$$\Delta q = \frac{EL}{eR^2} \text{ Ans.}$$

Ans. c

For Video Solution of this DPP, Click on below link

Video Solution
on Website:-

<https://physicsaholics.com/home/courseDetails/79>

Video Solution
on YouTube:-

https://youtu.be/ggMttZ_Ai3c

Written Solution
on Website:-

<https://physicsaholics.com/note/notesDetails/61>



[@Physicsaholics](#)

[@Physicsaholics_prateek](#)

[@NEET_Physics](#)

[@IITJEE_Physics](#)

[physicsaholics.com](#)



CLICK

Chalo Niklo