



DPP - 7 (EMI)

Video Solution on Website:-

<https://physicsaholics.com/home/courseDetails/79>


Video Solution on YouTube:-

<https://youtu.be/cBIWLGP3oyI>

Written Solution on Website:-

<https://physicsaholics.com/note/notesDetails/61>

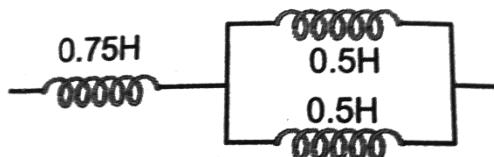- Q 1. Two inductors of 10mH respectively are connected together in a series combination so that their magnetic fields aid each other giving cumulative coupling. Their mutual inductance is given as 5mH. Calculate the total inductance of the series combination
- (a) 15 mH (b) 20 mH
(c) 25 mH (d) 30 mH
- Q 2. Three inductors of 10mH, 40mH and 50mH are connected together in a series combination with no mutual inductance between them. Calculate the total inductance of the series combination.
- (a) 100 mH (b) 6.89 mH
(c) 50 mH (d) 10 mH
- Q 3. Three pure inductors each of 2H are connected as shown in the figure. The equivalent inductance of the circuit between A & B is
-
- (a) $\frac{8}{6}$ H (b) 6H
(c) 2H (d) none of these
- Q 4. The equivalent inductance of two inductors is `2.4 H` when connected in parallel and `10 H` when connected in series. Then find inductance of inductors ?
- (a) 6H, 4H (b) 3H, 6H
(c) 6H, 3H (d) 12.4H, 7.6H
- Q 5. Three inductances are connected as shown below. Assuming no coupling, the resultant inductance will be-



- (a) 0.25 H (b) 0.5 H



Physicsaholics

(c) 0.75 H

(d) 1 H

- Q 6. A capacitor of capacity $2 \mu\text{F}$ is charged to a potential difference of 12V. It is then connected across an inductor of inductance $6 \mu\text{H}$. What is the current (in A) in the circuit at a time when the potential difference across the capacitor is 6V

(a) 2

(b) 4

(c) 6

(d) 8

- Q 7. In an LC circuit the capacitor has maximum charge q_0 . The value of $\left(\frac{dI}{dt}\right)_{max}$ is:

(a) $\frac{q_0}{LC}$

(b) $\frac{q_0}{\sqrt{LC}}$

(c) $\frac{q_0}{LC} - 1$

(d) $\frac{q_0}{LC} + 1$

- Q 8. A $16 \mu\text{F}$ capacitor is charged to a 20 Volt potential. Battery is then disconnected and inductor of inductance 40 mH is connected across the capacitor, So that LC oscillations are step-up. Maximum current in the coil is

(a) 0.4 A

(b) 2 A

(c) 0.8 A

(d) 0.2 A

- Q 9. A charged $30 \mu\text{F}$ capacitor is connected to a 27 mH inductor. What is the angular frequency of free oscillations of the circuit ?

(a) $1.1 \times 10^3 \text{ rad/s}$

(b) 10^4 rad/s

(c) $2.1 \times 10^2 \text{ rad/s}$

(d) $11 \times 10^3 \text{ rad/s}$

- Q 10. A 1.5 mH inductor in an LC circuit stores a maximum energy of $30 \mu\text{J}$. What is the maximum current in the circuit ?


(a) 2 A

(b) 4.4 A

(c) 1.2 A

(d) 0.2 A

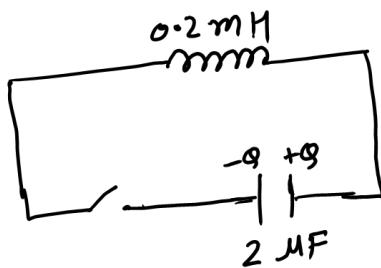- Q 11. Fig. shows LC circuit with initial charge on capacitor $200 \mu\text{C}$. If at $t = 0$, switch is closed, find the first instant when energy stored in inductor becomes one third that of capacitor:



(a) $8 \mu\text{ sec}$

(b) $10.5 \mu\text{ sec}$

(c) $2.5 \mu\text{ sec}$

(d) $1 \mu\text{ sec}$



Physicsaholics

Answer Key

Q.1 d	Q.2 a	Q.3 a	Q.4 a	Q.5 d
Q.6 c	Q.7 b	Q.8 a	Q.9 a	Q.10 d
Q.11 b				

PRATEEK JAIN
PHYSICSAHOLICS

PLUS

ICONIC *

- India's Best Educators
- Interactive Live Classes
- Structured Courses & PDFs
- Live Tests & Quizzes
- Personal Coach
- Study Planner

24 months ₹2,333/mo
No cost EMI ₹56,000 >

18 months ₹2,625/mo
No cost EMI ₹47,250 >

12 months ₹3,208/mo
No cost EMI ₹38,500 >

6 months ₹4,667/mo
No cost EMI ₹28,000 >

To be paid as a one-time payment

[View all plans](#)



Add a referral code

APPLY

PHYSICSLIVE

PLUS

ICONIC *

- India's Best Educators
- Interactive Live Classes
- Structured Courses & PDFs
- Live Tests & Quizzes
- Personal Coach
- Study Planner

24 months ₹2,100/mo
No cost EMI +10% OFF ₹50,400 >

18 months ₹2,363/mo
No cost EMI +10% OFF ₹42,525 >

12 months ₹2,888/mo
No cost EMI +10% OFF ₹34,650 >

6 months ₹4,200/mo
No cost EMI +10% OFF ₹25,200 >

To be paid as a one-time payment

[View all plans](#)



Awesome! PHYSICSLIVE code applied



Written Solution

DPP- 7 EMI: Combination of inductor (series and parallel), LC oscillations

By Physicsaholics Team

Solution: 1

current in both the solenoids is in same direction

$$\therefore L_{eq} = L_1 + L_2 + 2M$$

$$L_{eq} = 10 + 10 + 25$$

$$= 30$$

$$L_{eq} = 30 \text{ mH}$$

Ans.

Ans. d

Solution: 2

In Series Combination

$$L_{eq} = L_1 + L_2 + L_3$$

$$= 10 + 40 + 50$$


$$L_{eq} = 100 \text{ mH}$$

Ans.

PRATEEK JAIN
PHYSICS AHOLICS

Ans. a

Solution: 3

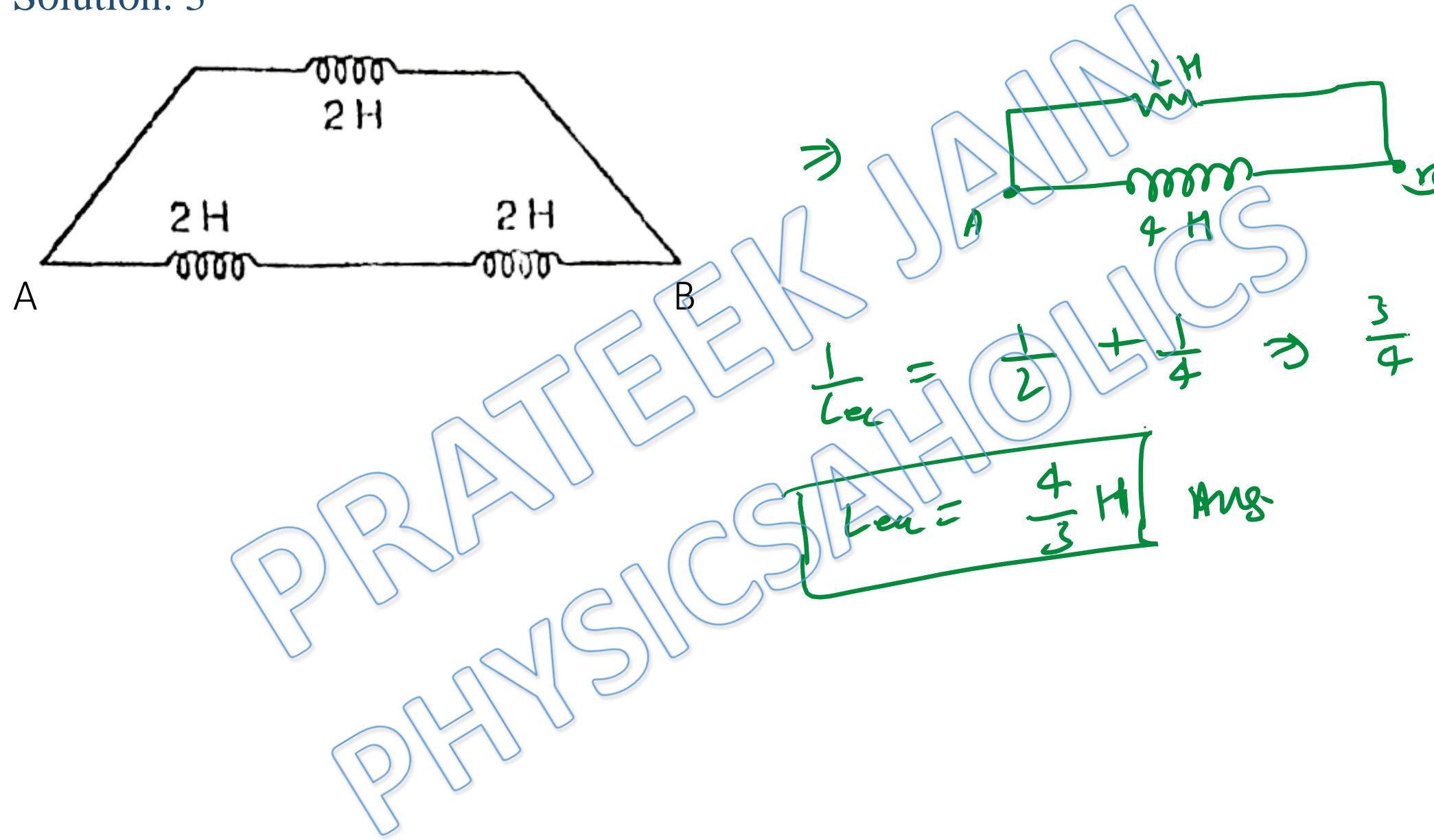

Solution: 4

In series

$$L_{\text{eq}} = L_1 + L_2 = 10 \text{ H} \quad \text{--- (1)}$$

In parallel

$$\frac{1}{L_{\text{eq}}} = \frac{1}{L_1} + \frac{1}{L_2} = \frac{1}{2.4} \quad \text{--- (2)}$$

$$L_{\text{eq}} = \frac{L_1 L_2}{L_1 + L_2} = 2.4 \text{ H} \quad \text{--- (3)}$$

from eq (1) & (2)

$$\frac{L_1 L_2}{10} = 2.4$$

$$\boxed{L_1 L_2 = 24} \quad \text{--- (3)}$$

from eq (1)

$$L_2 = 10 - L_1$$

Put in eq (3)

$$L_1(10 - L_1) = 24$$

$$10L_1 - L_1^2 = 24$$

$$L_1^2 - 10L_1 + 24 = 0$$

$$L_1^2 - 6L_1 - 4L_1 + 24 = 0$$

$$L_1 = 4 \text{ H}, \text{ or } 6 \text{ H}$$



$$\text{if } L_1 = 4 \text{ H}; L_2 = 6 \text{ H}$$

$$\text{and if } L_1 = 6 \text{ H}; L_2 = 4 \text{ H}$$

$\therefore \boxed{6 \text{ H and } 4 \text{ H}}$ Ans.

Ans. a

Solution: 5

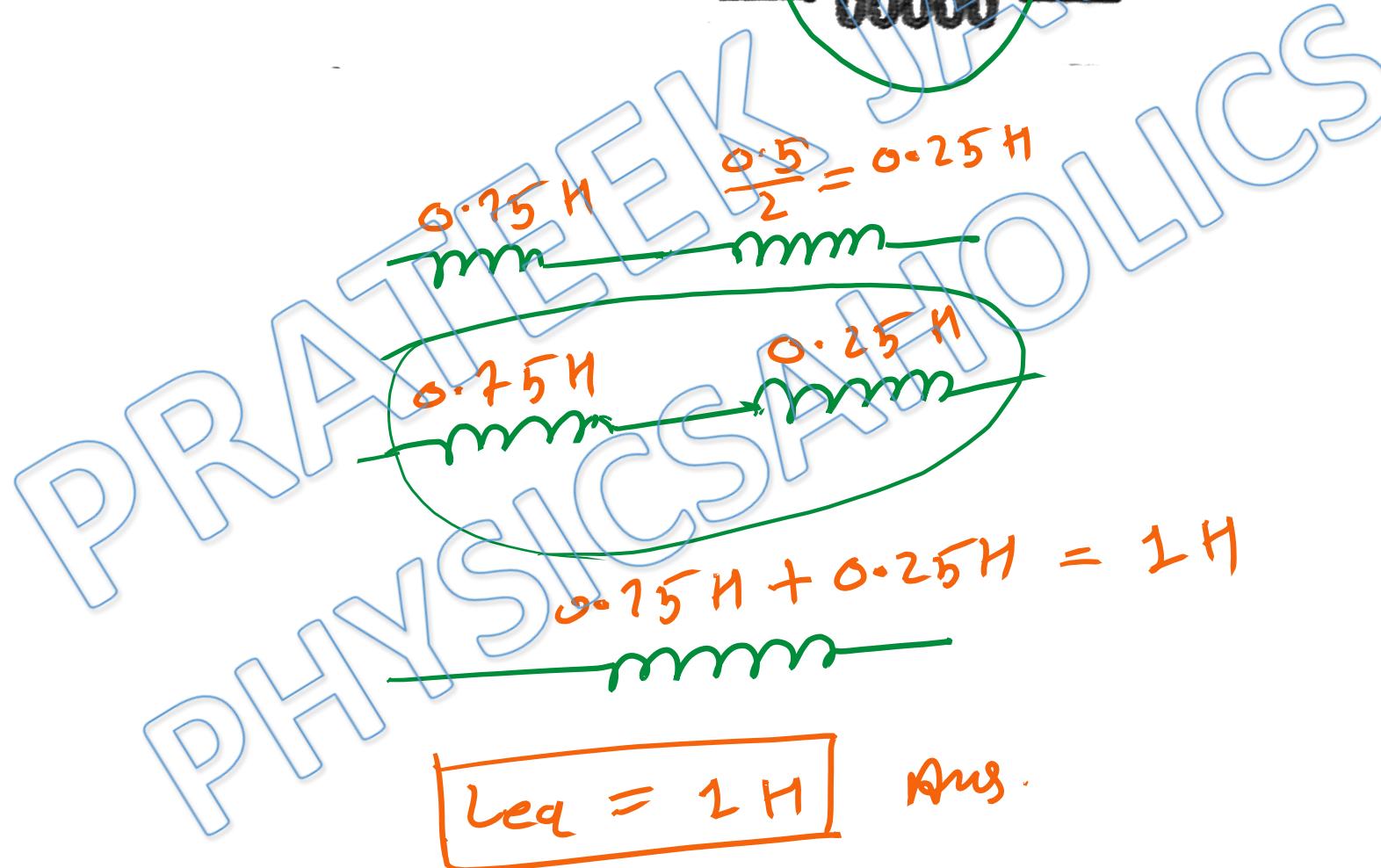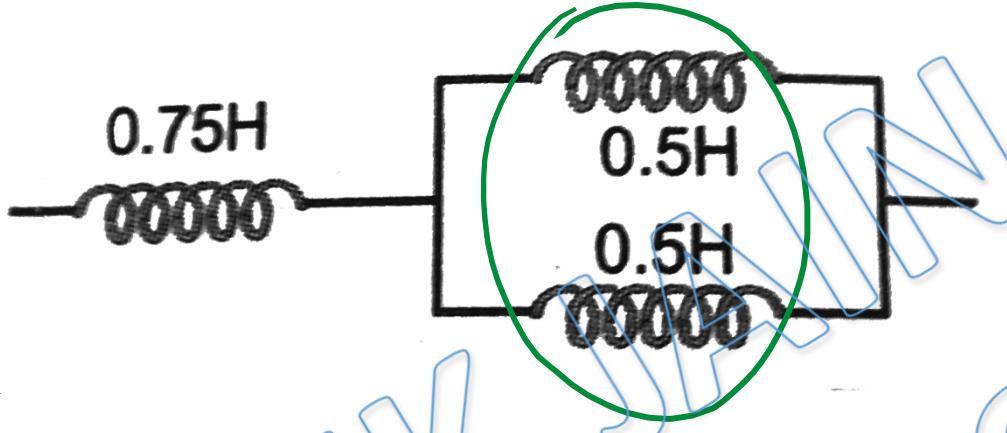

Ans. d

Solution: 6

$$U_i = \frac{1}{2}CV^2 = \frac{1}{2} \times 2\text{mF} \times (12)^2 = 144 \text{ mJ}$$

\rightarrow $V = 12 \text{ volt}$

$$Q = CV = 2\text{mF} \times 12 = 24 \mu\text{C}$$

when, $V_c = 6 \text{ V}$

$$q = L \times 6 = 12 \mu\text{J}$$

$$U_c = \frac{1}{2}CV_c^2 = \frac{1}{2C} = \frac{(12 \times 10^{-6})^2}{2(2 \times 10^{-6})} = \frac{12^2}{2 \times 2} \mu\text{J} = 36 \mu\text{J}$$

$$\therefore U_t = U_i - U_c = 144 - 36 = 108 \mu\text{J}$$

$$108 \mu\text{J} = \frac{1}{2}LI^2$$

$$108 \times 10^{-6} = \frac{1}{2} \times (6 \text{ mH}) \times I^2$$

$$I^2 = 36$$

$$I = 6 \text{ amp}$$

Ans.

Ans. c

Solution: 7

$$i = V_0 \omega \sin \omega t$$

$$\frac{di}{dt} = V_0 \omega^2 \cos \omega t$$

$$\left(\frac{di}{dt} \right)_{\max} = V_0 \omega$$

$$= \frac{V_0}{L C}$$

Ans(a)

Solution: 8

$$q_0 = CV \\ = 16 \mu F \times 20V$$

$$q_0 = 320 \mu C$$

$$I_{max} = q_0 \omega$$

$$\omega = \frac{1}{LC} = \frac{1}{(16 \times 10^{-6} \times 4 \times 10^{-3})} = 4 \times 2 \times 10^{-4}$$

$$\omega = \frac{10\pi}{8} = \frac{10}{8} \times 10^3 \text{ rad/s}$$

$$\therefore I_{max} = 320 \times \frac{10}{8} \times 10^3 \times 10^{-6}$$

$$I_{max} = 0.4 \text{ amp}$$

Ans.

Ans. a

Solution: 9

$$\omega = \frac{1}{JLC}$$

$$\omega = \frac{1}{\sqrt{27 \times 10^3 \times 30 \times 10^{-8}}} = \frac{1}{9 \times 10^{-4}}$$

$$\omega = \frac{10}{9} \times 10^3$$

$$\boxed{\omega = 1.1 \times 10^3 \text{ rad/s}}$$

Ans.

Ans. a

Solution: 10

$$V_L = \frac{1}{2} L I^2$$

$$(V_L)_{\max} = \frac{1}{2} L (I_{\max})^2$$

$$(30 \times 10^{-6}) = \frac{1}{2} (1.5 \times 10^{-3}) I_m^2$$

$$+ 60 \times 10^{-6} = 45 \times 10^{-6} I_m^2$$

$$I_m^2 = 4 \times 10^{-2}$$

$$I_m = 2 \times 10^{-1}$$

$$I_{\max} = 0.2 \text{ amp}$$

Ans.

Ans. d

Solution: 11 given, $V_L = \frac{1}{3} V_C$

at initial condition

$$V = \frac{qL}{2C} = \frac{(2 \times 10^6) L}{2 \times 2 \times 10^{-6}} = \frac{4 \times 10^4 \times 10^{-6}}{4}$$

$$V = 10^{-2} J \quad \text{①}$$

$$q = 2 \times 10^4 C$$

$$\text{so, when } V_L = \frac{1}{3} V_C$$

$$V_C = V - V_L = V - \frac{1}{3} V_C$$

$$V_C + \frac{1}{3} V_C = V$$

$$\frac{4}{3} V_C = V$$

$$V_C = \frac{3}{4} V$$

$$V_C = \frac{3}{4} \times 10^{-2} J$$

$$\Rightarrow V_C = \frac{3}{4} \times 10^{-2} J$$

$$\frac{qL}{2C} = \frac{3}{4} \times 10^{-2}$$

$$qL = (2 \times 2 \times 10^{-6}) \times \frac{3}{4} \times 10^{-2}$$

$$qL = 3 \times 10^{-8}$$

$$q = \sqrt{3} \times 10^{-4} C$$

$$q = q_0 \sin(\omega t + \frac{\pi}{2})$$

$$\sqrt{3} \times 10^{-4} = 2 \times 10^{-4} \sin(\omega t + \frac{\pi}{2})$$

$$\frac{\sqrt{3}}{2} = \sin(\omega t + \frac{\pi}{2}) = \cos \omega t$$

$$\cos \omega t = \frac{\sqrt{3}}{2} \Rightarrow \omega t = \frac{\pi}{6}$$

$$t = \frac{\lambda}{\omega} = \frac{\lambda \sqrt{L/C}}{6} = \frac{\pi}{6} \sqrt{0.2 \times 10^3 \times 2 \times 10^6}$$

$$\boxed{t = 10.5 \text{ ms}} \quad \text{Ans.}$$

Ans. b

For Video Solution of this DPP, Click on below link

**Video Solution
on Website:-**

<https://physicsaholics.com/home/courseDetails/79>

**Video Solution
on YouTube:-**

<https://youtu.be/cBIWLGP3oyI>

**Written Solution
on Website:-**

<https://physicsaholics.com/note/notesDetails/61>



SUBSCRIBE



[@Physicsaholics](#)

[@Physicsaholics_prateek](#)

[@NEET_Physics](#)
[@IITJEE_Physics](#)

[physicsaholics.com](#)



CLICK

chalon Niklo