

DPP – 6 (Current Electricity)

Video Solution on Website :-

<https://physicsaholics.com/home/courseDetails/98>


Video Solution on YouTube:-

<https://youtu.be/cDFoPKOXFKU>

Written Solution on Website:-


<https://physicsaholics.com/note/notesDetalis/53>

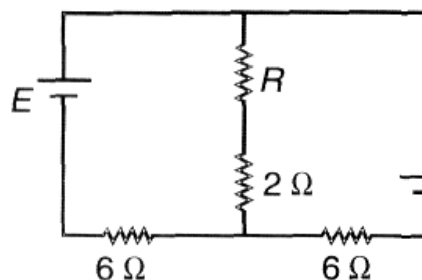- Q 1. In the circuit shown in figure the emf of battery are E . At what value of R thermal power generated in it will be maximum?




- (a) $\frac{6}{5}$ ohm
 (b) $\frac{5}{6}$ ohm
 (c) 5 ohm
 (d) 14 ohm

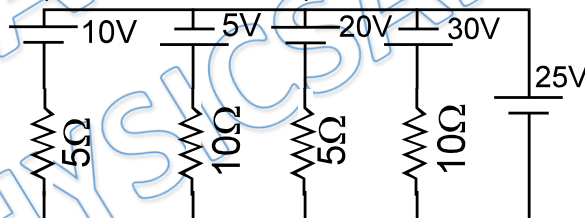- Q 2. In the figure shown: (All batteries are ideal)



- (a) current through 5 V cell is 2 A
 (b) current through 25 V cell is 12.5 A
 (c) current through 10 V cell is 15 A
 (d) current through 30 V cell is 3 A

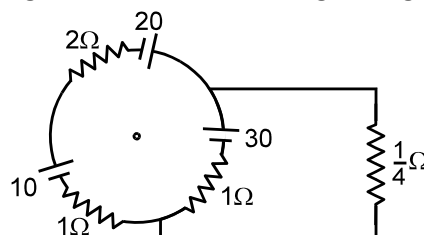
- Q 3. In the following circuit diagram, the current flowing through resistor of $\frac{1}{4} \Omega$ is



- (a) 1A
 (b) 60 A
 (c) 30 A
 (d) None of these




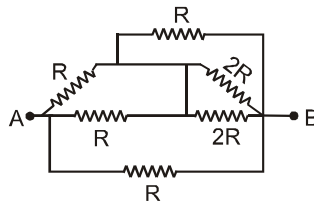- Q 4. What is power delivered by an ideal battery of emf ϵ when it is connected across terminal A and B as shown in figure



- (a) $\frac{\epsilon^2}{R}$ (b) $\frac{\epsilon^2}{2R}$ (c) $\frac{2\epsilon^2}{R}$ (d) $\frac{4\epsilon^2}{R}$

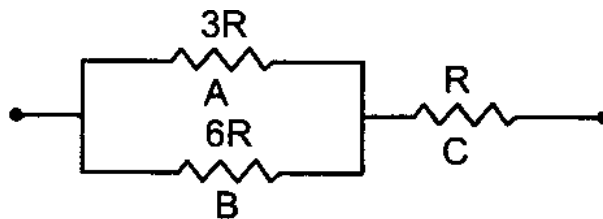- Q 5. The three resistances A, B and C have values $3R, 6R$ and R respectively. When some potential difference is applied across the network, the thermal powers dissipated by A, B and C are in the ratio




- (a) 2 : 3 : 4 (b) 2 : 4 : 3 (c) 4 : 2 : 3 (d) 3 : 2 : 4

- Q 6. Two cells of the same emf 'e' but different internal resistances, r_1 & r_2 are connected in series with an external resistance R.

Column I	Column II
(A) value of current through R	(P) potential drop across second cell is zero
(B) when external resistance R is $r_1 - r_2$	(Q) $\frac{2e}{R+r_1+r_2}$
(C) when external Resistance R is $r_1 + r_2$	(R) potential drop across first cell is zero
(D) when external resistance R is $r_2 - r_1$	(S) maximum power output across resistance R

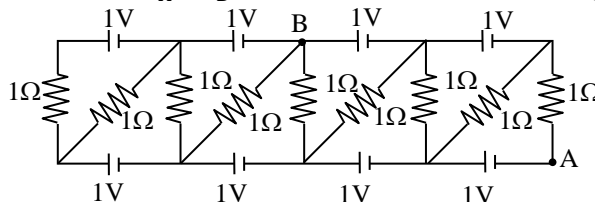- Q 7. Find the potential difference $V_A - V_B$ for the circuit shown in the figure.




- (a) $-\frac{14}{9} v$
 (b) $-\frac{16}{9} v$
 (c) $-\frac{11}{9} v$




(d) $-\frac{22}{9}v$

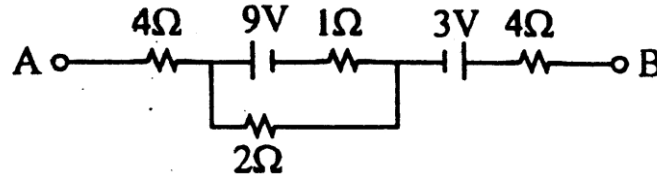- Q 8. In the circuit shown in figure potential difference between point A and B is 16 V. Find the current passing through 2Ω resistance.




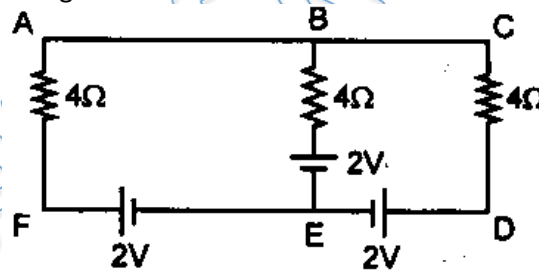- (a) 5A
 (b) 2.5 A
 (c) 3.5 A
 (d) 4.5 A
- Q 9. A constant voltage is applied to a metal wire. The current passing through the wire heat the wire to certain temperature. If half of the wire is cooled by pocering cold water then
- (a) Temperature of other half increases
 (b) Temperature of other half decreases
 (c) Temperature of other half remain same
 (d) Current through other half decreases
- Q 10. In the circuit shown in figure:



- (a) current in wire AF is 1 A
 (b) current in wire CD is 1 A
 (c) current in wire BE is 2 A
 (d) none of the above
- Q 11. Current capacity of a cylindrical fuse wire is directly proportional to nth power of radius of wire mth power of length of wire , then m + n is
- (a) 1
 (b) 2
 (c) 1.5
 (d) 2.5

- Q 12. In given circuit $V_Q - V_P$ is

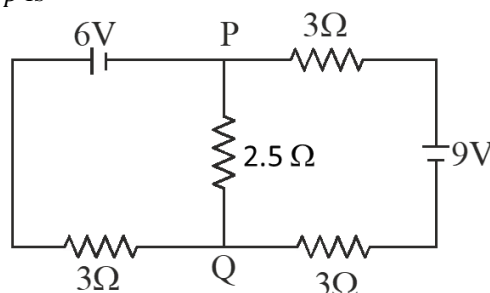


- (a) 0.5 V



- (b) -5V
- (c) 0.25 V
- (d) -0.25 V

Q 13. Find current in resistance A

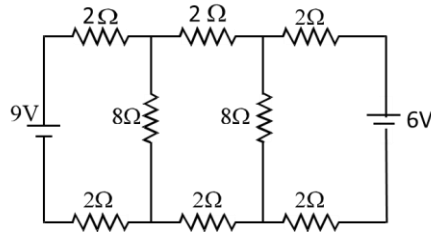

- (a) $3/14$ A
- (b) $2/15$ A
- (c) $2/7$ A
- (d) $6/13$ A

PRATEEK JAIN
PHYSICSAHOLICS

Answer Key

Q.1 c	Q.2 b	Q.3 c	Q.4 c	Q.5 c
Q.7 d	Q.8 c	Q.9 a	Q.10 d	Q.11 c
Q.12 a	Q.13 a			

Q.6 A (Q); B (R); C (S); D (P)

PLUS

ICONIC **

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

24 months ₹2,333/mo >
No cost EMI ₹56,000

18 months ₹2,625/mo >
No cost EMI ₹47,250

12 months ₹3,208/mo >
No cost EMI ₹38,500

6 months ₹4,667/mo >
No cost EMI ₹28,000

To be paid as a one-time payment

View all plans



Add a referral code

APPLY

PHYSICSLIVE

PLUS

ICONIC **

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

24 months ₹2,100/mo >
No cost EMI +10% OFF ₹50,400

18 months ₹2,363/mo >
No cost EMI +10% OFF ₹42,525

12 months ₹2,888/mo >
No cost EMI +10% OFF ₹34,650

6 months ₹4,200/mo >
No cost EMI +10% OFF ₹25,200

To be paid as a one-time payment

View all plans



Awesome! PHYSICSLIVE code applied



Use code **PHYSICSLIVE** to get 10% OFF on Unacademy PLUS.


Written Solution

**DPP- 6 Current :Combination of Batteries, Heat
and Power of Resistance and Battery**


By Physicsaholics Team

Q.1) In the circuit shown in figure the emf of battery are E . At what value of R thermal power generated in it will be maximum?

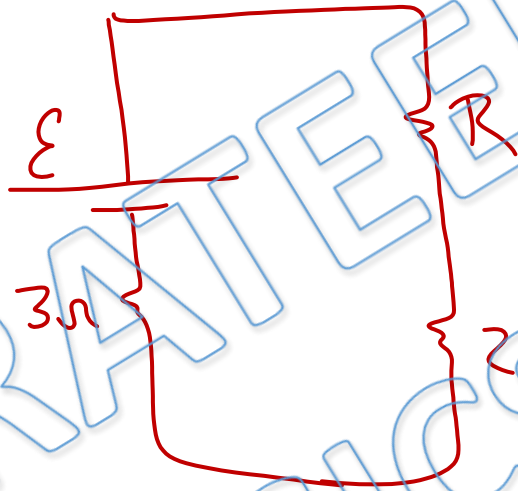- (a) $\frac{6}{5}$ ohm
- (b) $\frac{5}{6}$ ohm
- ~~(c) 5 ohm~~
- (d) 14 ohm




for max power
 $R = r = 5 \Omega$

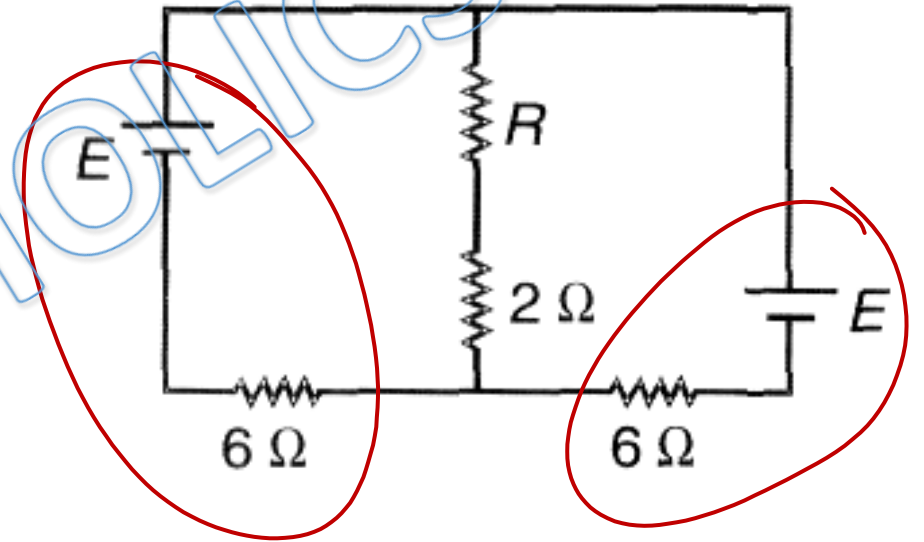

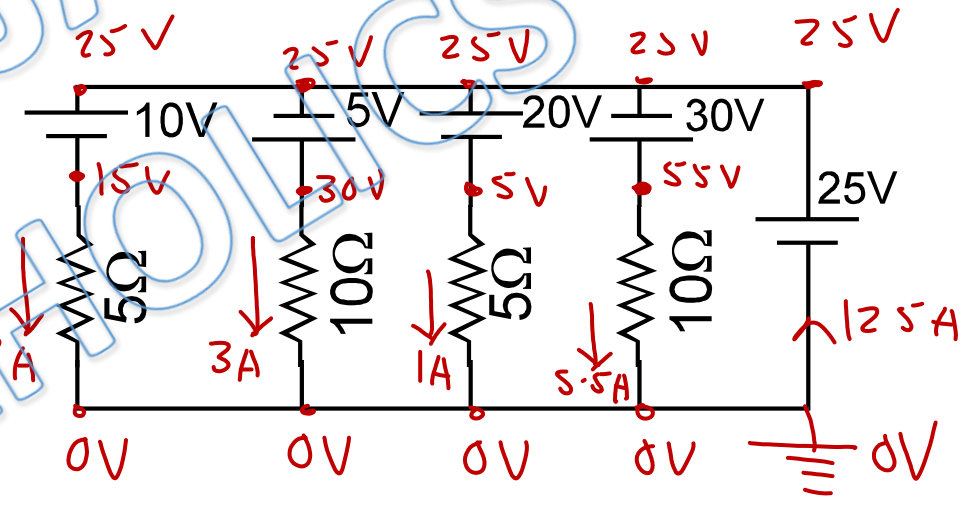Q.2) In the figure shown: (All batteries are ideal)



- ~~(a)~~ current through 5 V cell is 2 A
- ~~(b)~~ current through 25 V cell is 12.5 A
- ~~(c)~~ current through 10 V cell is 15 A
- ~~(d)~~ current through 30 V cell is 3 A



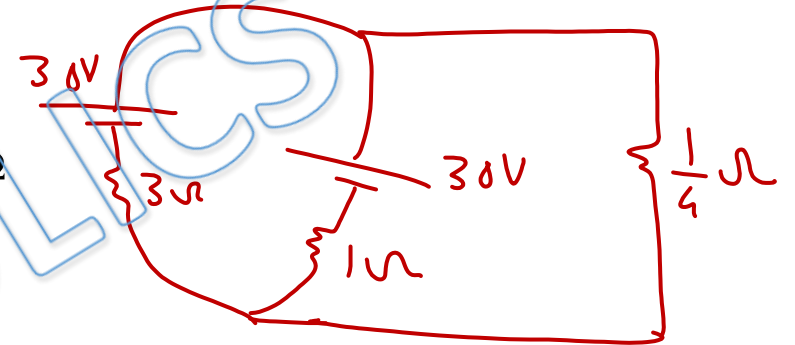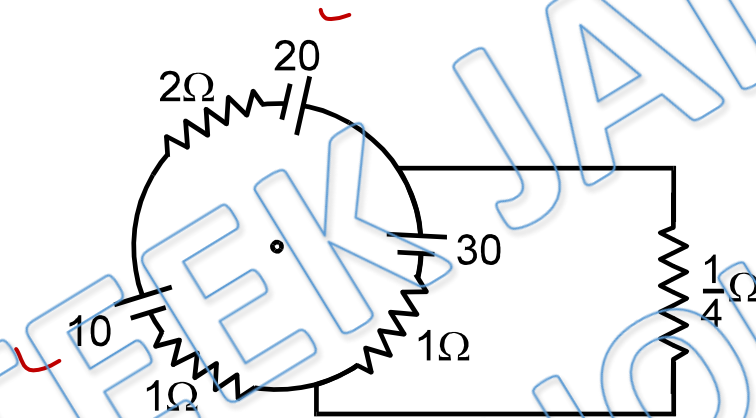Q.3) In the following circuit diagram, the current flowing through resistor of $\frac{1}{4} \Omega$ is

$$\begin{aligned} \mathcal{E}_{\text{eff}} &= \frac{\mathcal{E}_1 + \mathcal{E}_2}{\frac{1}{\mathcal{R}_1} + \frac{1}{\mathcal{R}_2}} \\ &= \mathcal{E} = 30\text{V} \end{aligned}$$

$$\mathcal{R}_{\text{eff}} = \frac{3 \times 1}{3 + 1} = \frac{3}{4} \Omega$$




(a) 1A

(b) 60 A



(c) 30 A

(d) None of these

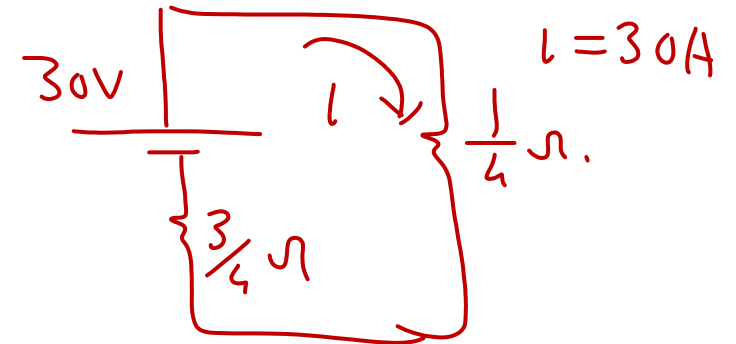

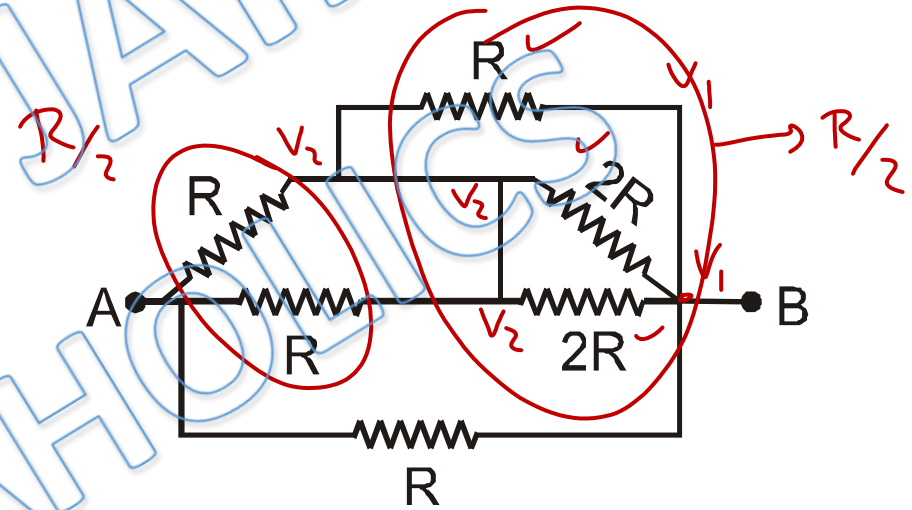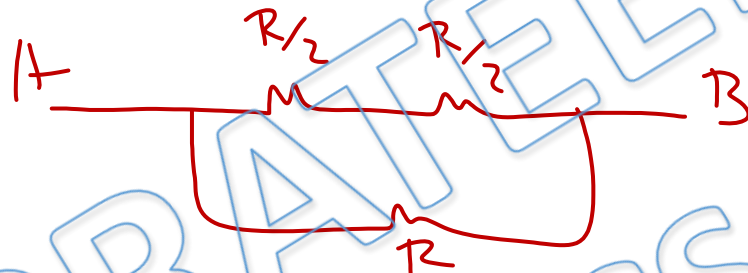Q.4) What is power delivered by an ideal battery of emf ϵ when it is connected across terminal A and B as shown in figure

$$P = \frac{V^2}{R_{\text{eff}}} = \frac{2\epsilon^2}{R}$$



(a) $\frac{\epsilon^2}{R}$

(b) $\frac{\epsilon^2}{2R}$


(c) $\frac{2\epsilon^2}{R}$

(d) $\frac{4\epsilon^2}{R}$

$$R_{AB} = R/2$$

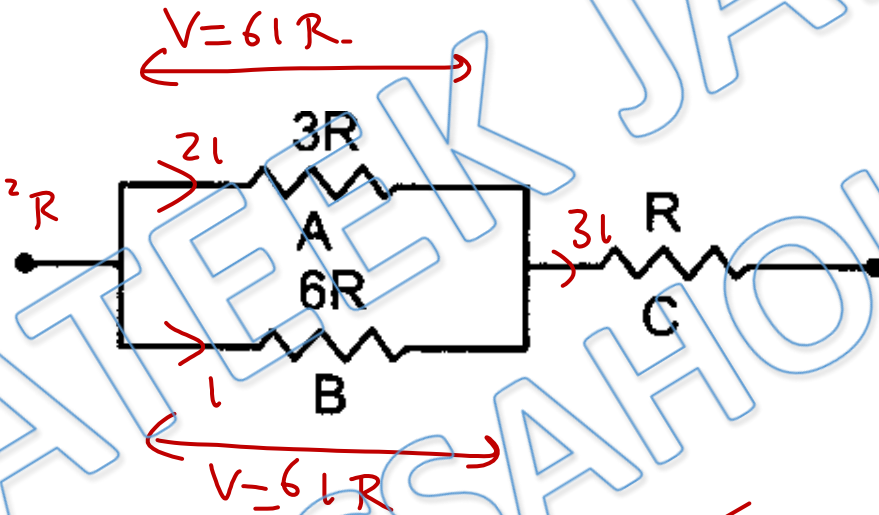Q.5) The three resistances A, B and C have values $3R, 6R$ and R respectively. When some potential difference is applied across the network, the thermal powers dissipated by A, B and C are in the ratio

$$\begin{aligned}
 &P_A : P_B : P_C \\
 &= (4I^2 \times 3R) : I^2 \times 6R : 9I^2 R \\
 &= 12 : 6 : 9 \\
 &= 4 : 2 : 3
 \end{aligned}$$



(a) $2 : 3 : 4$

(b) $2 : 4 : 3$

(c) $4 : 2 : 3$

(d) $3 : 2 : 4$

Q.6) Two cells of the same emf 'e' but different internal resistances, r_1 & r_2 are connected in series with an external resistance R.

Column I

- (A) value of current through R → (P)
- (B) when external resistance R is $r_1 - r_2$ → (Q)
- (C) when external resistance R is $r_1 + r_2$ → (R)
- (D) when external resistance R is $r_2 - r_1$ → (S)

$$i = \frac{ze}{r_1 - r_2 + r_1 + r_2}$$

$$= \frac{e}{r_1}$$

$i r_1 = e$


$V_1 = 0$

Column II

potential drop across second cell is zero

$$\frac{ze}{R + r_1 + r_2}$$

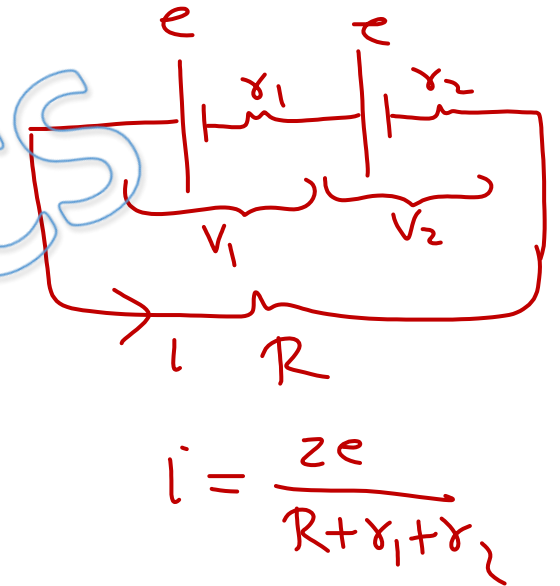potential drop across first cell is zero
maximum power output across resistance R



$$i = \frac{ze}{R + r_1 + r_2}$$

Q.7) Find the potential difference $V_A - V_B$ for the circuit shown in the figure.

$$5 \times \left(\frac{V_0}{1} \right) + 4 \left(\frac{V_0 - 1}{1} \right) = 0$$

$$5V_0 + 4V_0 - 4 = 0$$

$$V_0 = \frac{4}{9}$$


(a) $-\frac{14}{9} \text{ V}$

(b) $-\frac{16}{9} \text{ V}$

(c) $-\frac{11}{9} \text{ V}$

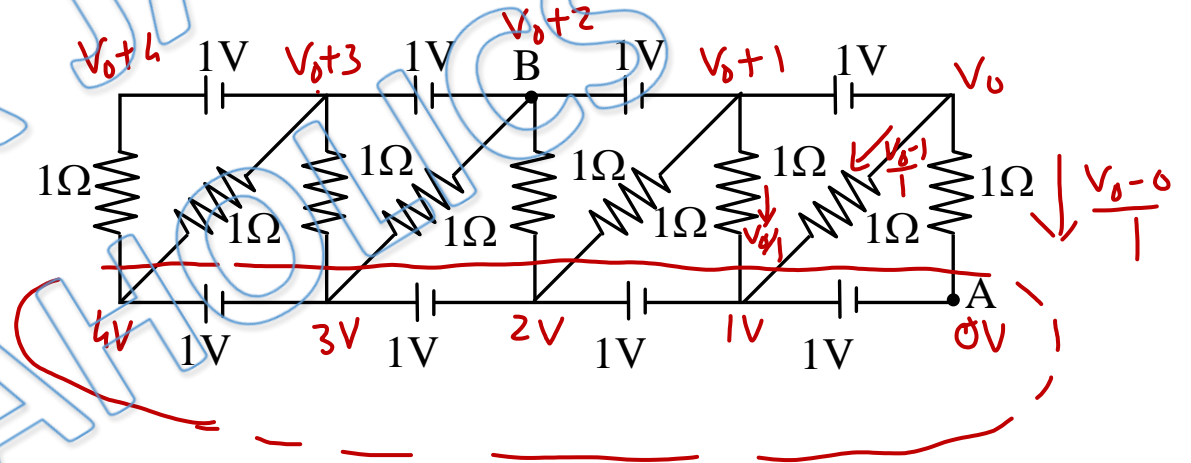(d) $-\frac{22}{9} \text{ V}$


$$\begin{aligned} V_A - V_B &= 0 - (V_0 + 2) \\ &= -\left(2 + \frac{4}{9}\right) \\ &= -\frac{22}{9} \text{ V} \end{aligned}$$



~~25~~

$$26 \overline{) \begin{array}{r} 91 \\ 78 \\ \hline 130 \end{array}} \quad (3.5)$$

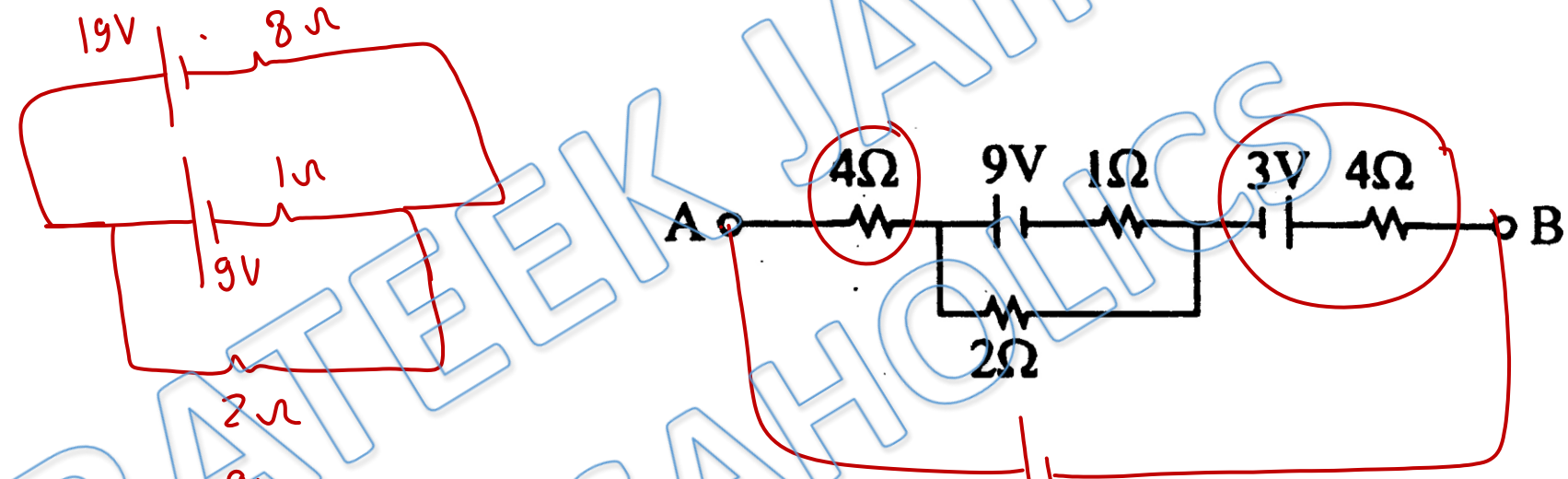Q.8) In the circuit shown in figure potential difference between point A and B is 16 V. Find the current passing through 2Ω resistance.




- (a) 5A
- (b) 2.5 A
- (c) 3.5 A
- (d) 4.5 A

$$I = \frac{\frac{91}{9}}{2 + \frac{8}{9}} = \frac{91}{26}$$

$$V_{eff} = \frac{19 + 72}{9} = \frac{91}{9} V$$




$$R_{eff} = \frac{8 \times 1}{9}$$

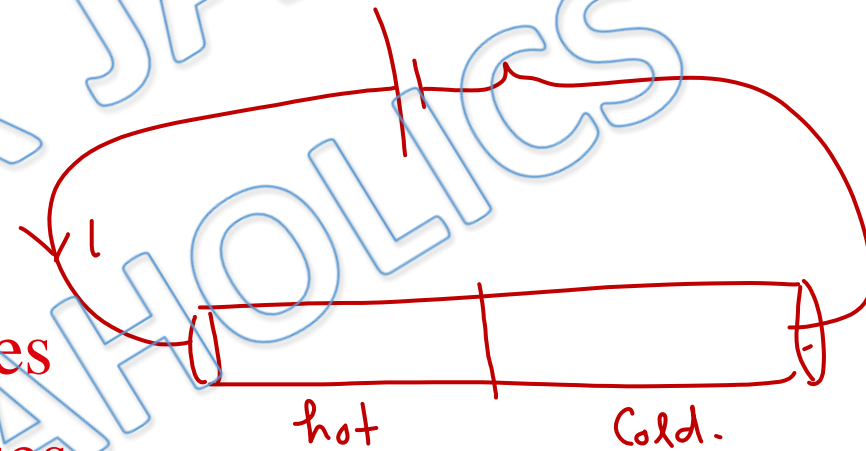Q.9) A constant voltage is applied to a metal wire. The current passing through the wire heat the wire to certain temperature. If half of the wire is cooled by pocering cold water then



- (a) Temperature of other half increases
- (b) Temperature of other half decreases
- (c) Temperature of other half remain same
- (d) Current through other half decreases

Q.10) In the circuit shown in figure:

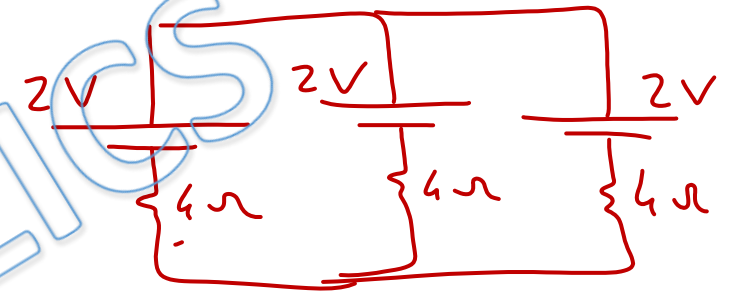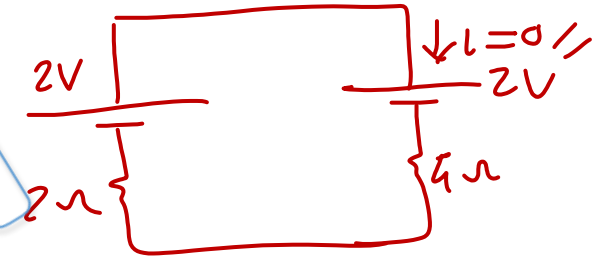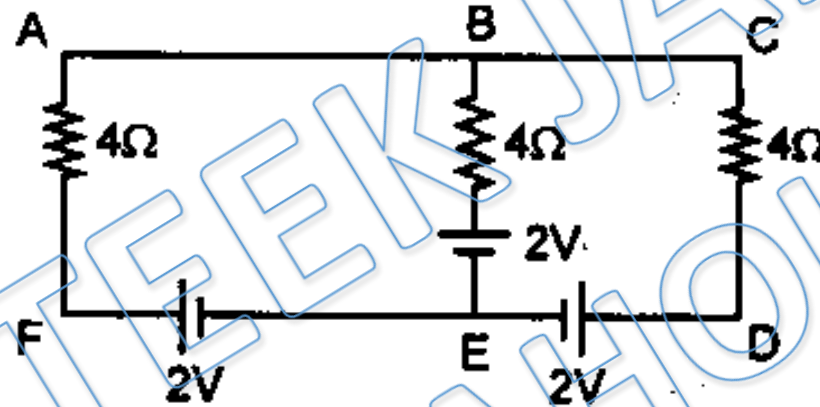

(a) current in wire AF is 1 A

(b) current in wire CD is 1 A

(c) current in wire BE is 2 A

(d) none of the above

Q.11) Current capacity of a cylindrical fuse wire is directly proportional to n'th power of radius of wire m'th power of length of wire, then m + n is

and

T_0 → ~~melting~~ melting point
 I → Current Capacity



- (a) 1
- (b) 2
- (c) 1.5
- (d) 2.5

$$n = 3/2$$

$$m = 0$$

$$I^2 R = e \sigma A T_0^4$$

$$I^2 \frac{\rho l}{\pi r^2} = e \sigma 2\pi r l T_0^4$$

$$I^2 \propto r^3 l^0$$

$$I \propto r^{3/2} l^0$$

Surface Area.





Q.12) In given circuit $V_Q - V_P$ is

~~(a) 0.5 V~~

(b) -5V

(c) 0.25 V

(d) -0.25 V

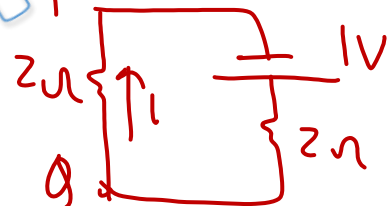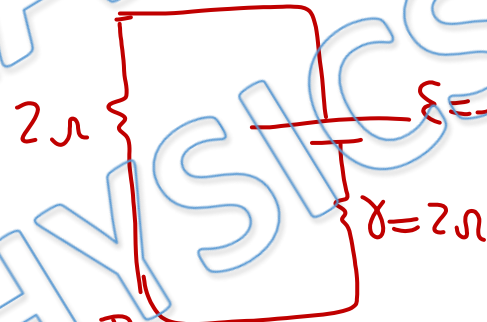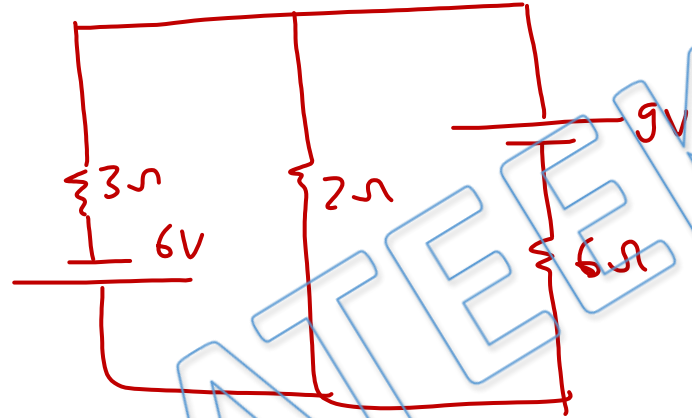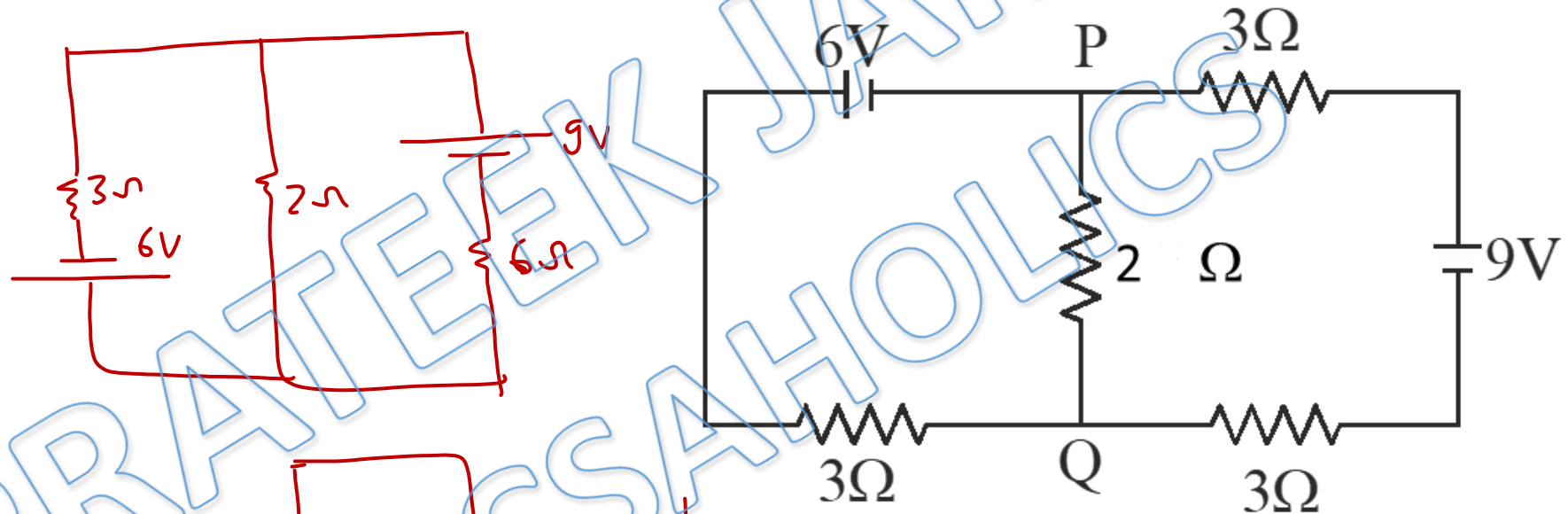

$$\xi = \frac{27 - 36}{9} = -1V$$

$$\gamma = \frac{3 \times 6}{3 + 6} = 2\Omega$$

$$i = \frac{1}{4} A$$



$$V_Q - V_P = \frac{1}{4} \times 2 = \underline{\underline{-0.25V}}$$

Q.13) Find current in resistance A


$$\mathcal{E}_1 = \frac{9 \times 8 + 0 \times 4}{12} = 6V$$

$$\frac{8 \times 4}{12}$$
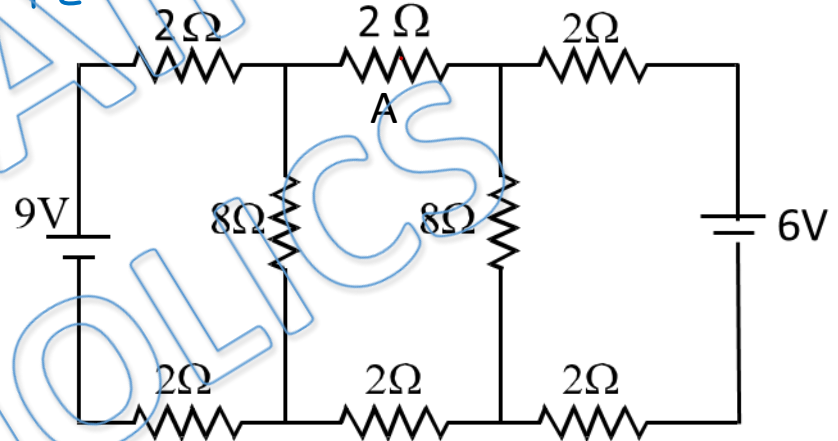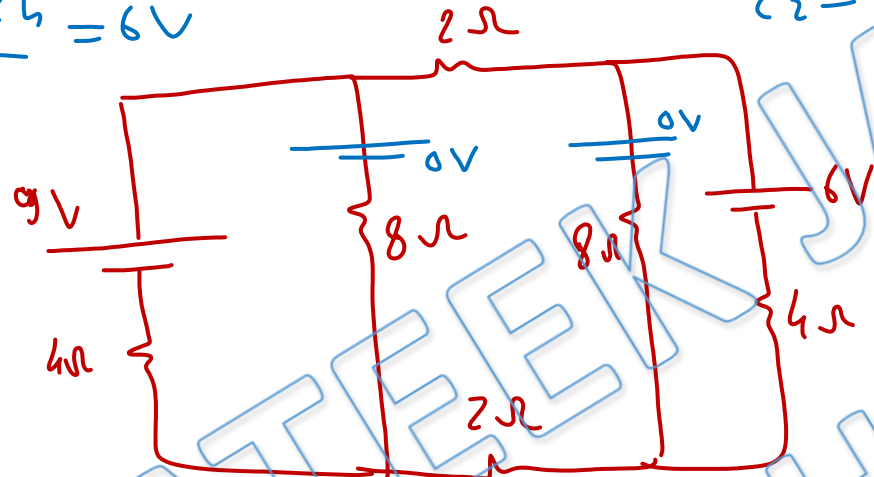
$$\mathcal{E}_2 = \frac{4 \times 8 + 0 \times 4}{12} = 4V$$



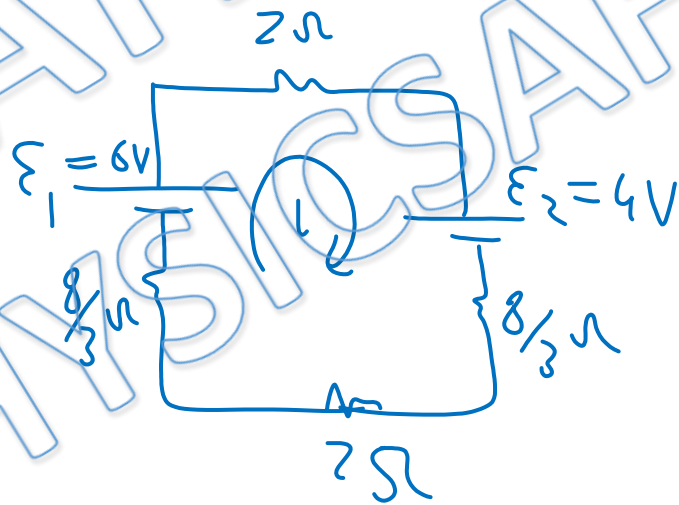- (a) 3/14 A
- (b) 2/15 A
- (c) 2/7 A
- (d) 6/13 A



$$i = \frac{6 - 4}{2 + 2 + \frac{8}{3} + \frac{8}{3}}$$

$$= \frac{2}{4 + \frac{16}{3}}$$

$$= \frac{1}{2 + \frac{8}{3}} = \frac{3}{14}$$

For Video Solution of this DPP, Click on below link

Video Solution
on Website:-

<https://physicsaholics.com/home/courseDetails/98>

Video Solution
on YouTube:-

<https://youtu.be/cDFoPKOXFKU>

Written Solution
on Website:-

<https://physicsaholics.com/note/notesDetalis/53>

 **SUBSCRIBE**



[@Physicsaholics](#)

[@Physicsaholics_prateek](#)

[@NEET_Physics](#)

[@IITJEE-Physics](#)

[physicsaholics.com](#)

[Unacademy](#)



CLICK

Chalo Niklo