


## DPP – 2 (Alternating Current)

Video Solution on Website :- <https://physicsaholics.com/home/courseDetails/102>

Video Solution on YouTube:- <https://youtu.be/O3WmlqLxMJg>


Written Solution on Website:- <https://physicsaholics.com/note/notesDetailis/60>

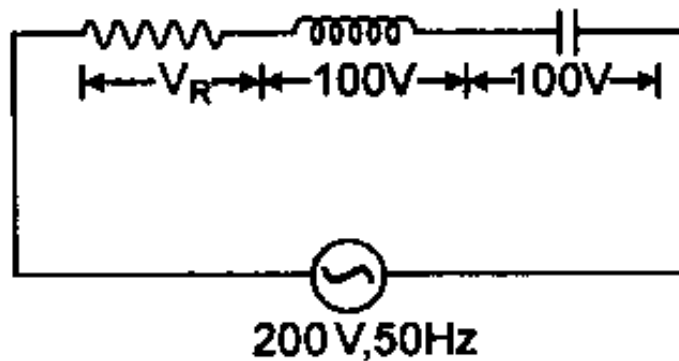Q 1. In the circuit shown in figure current in the circuit is:



- (a) 1.27A      (b) 2.23 A      (c) 4.26 A      (d) 3.87 A

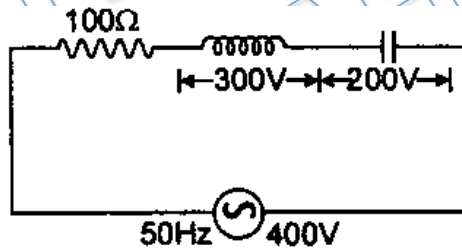Q 2. 110 V (rms) is applied across a series circuit having resistance  $11 \Omega$  and impedance  $22 \Omega$ . The power consumed is:



- (a) 275 W      (b) 366 W      (c) 550 W      (d) 1100 W


Q 3. At a frequency  $\omega_0$  the reactance of a certain capacitor equals that of a certain inductor. If the frequency is changed to  $2\omega_0$ , what is the ratio of the reactance of the inductor to that of the capacitor?

- (a) 4 : 1      (b)  $\sqrt{2} : 1$       (c) 1 :  $2\sqrt{2}$       (d) 1 : 2

Q 4. An alternating voltage given by  $V = 300\sqrt{2} \sin(50t)$  (in volts) is connected across a  $1\mu\text{F}$  capacitor through an AC ammeter. The reading of the ammeter will be:


- (a) 10 mA      (b) 40 mA      (c) 100 mA      (d) 15 mA

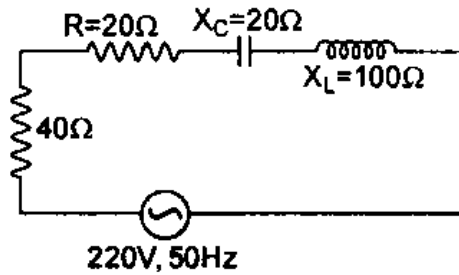Q 5. The power factor of the circuit shown in the figure is:



- (a) 0.4                      (b) 0.2                      (c) 0.8                      (d) 0.6

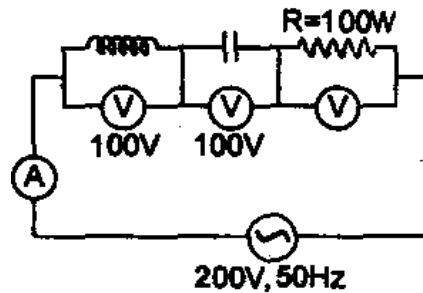Q 6. What will be the reading of the voltmeter across the resistance and ammeter in the circuit shown in the figure?



- (a) 300 V, 2 A                      (b) 800 V, 2 A                      (c) 100 V, 2 A                      (d) 200 V, 2 A

Q 7. When 100 V. DC is applied across a solenoid a current of 1 A flows in it. When 100 V, AC is applied across the same coil, the current drops to 0.5 A. The frequency of the AC is 50 Hz. The impedance and inductance of the solenoid are:

- (a) 100 Ω, 0.75 H                      (b) 1000, 0.60H  
(c) 2000, 0.55H                      (d) 2000, 0.75H

Q 8. In a series LCR the voltage across resistance, capacitance and inductance is 10 V each. If the capacitance is short circuited, the voltage across the inductance will be:

- (a)  $\frac{10}{\sqrt{2}}$  V                      (b) 10 V                      (c)  $10\sqrt{2}$  V                      (d) 20 V

Q 9. Choose the wrong statement:

- (a) The peak voltage across the inductor can be greater than the peak voltage of the source in an LCR circuit.  
(b) In a circuit containing a capacitor and an AC source the current is zero at the instant the source voltage is maximum.  
(c) An AC source is connected to a capacitor. The rms current in the circuit gets increased if a dielectric slab is inserted into the capacitor.  
(d) None of the above

Q 10. An AC source producing emf  $V = V_0 [\sin \omega t + \sin 2\omega t]$  is connected in series with a capacitor and a resistor. The current found in the circuit is  $i = i_1 \sin (\omega t + \phi_1) + i_2 \sin (2\omega t + \phi_2)$ . Then :

- (a)  $i_1 = i_2$   
(b)  $i_1 < i_2$   
(c)  $i_1 > i_2$   
(d)  $i_1$  may be less than, equal to or greater than  $i_2$





PRATEEK JAIN  
PHYSICSAHOLICS

## Answer Key

Q.1 d	Q.2 a	Q.3 a	Q.4 d	Q.5 d
Q.6 d	Q.7 c	Q.8 a	Q.9 d	Q.10 b
Q.11 c	Q.12 c	Q.13 d	Q.14 d	

PLUS **ICONIC\*\***

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

24 months ₹2,333/mo >  
No cost EMI ₹56,000

18 months ₹2,625/mo >  
No cost EMI ₹47,250

12 months ₹3,208/mo >  
No cost EMI ₹38,500

6 months ₹4,667/mo >  
No cost EMI ₹28,000

To be paid as a one-time payment

[View all plans](#)



Add a referral code

APPLY

# PHYSICSLIVE

Use code **PHYSICSLIVE** to get 10% OFF on Unacademy PLUS.

PLUS **ICONIC\*\***

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

24 months ₹2,100/mo >  
No cost EMI **+10% OFF** ₹50,400

18 months ₹2,363/mo >  
No cost EMI **+10% OFF** ₹42,525

12 months ₹2,888/mo >  
No cost EMI **+10% OFF** ₹34,650

6 months ₹4,200/mo >  
No cost EMI **+10% OFF** ₹25,200

To be paid as a one-time payment

[View all plans](#)



Awesome! **PHYSICSLIVE** code applied




# Written Solution

**DPP-2 AC: Pure Resistive, Pure Inductive & Pure Capacitive AC circuit, R-L AC Circuit, R-L-C AC circuit, Power Dissipation in AC Circuit**

**By Physicsaholics Team**

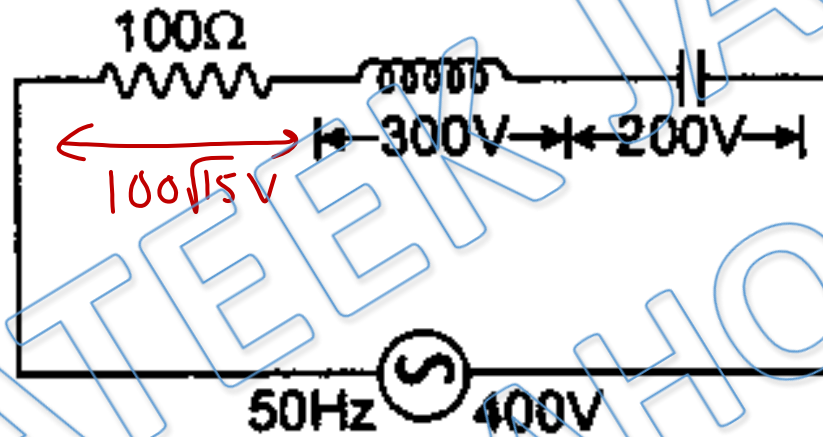Q.1) In the circuit shown in figure current in the circuit is:



$$V_{rms}^2 = V_{R_{rms}}^2 + (V_{C_{rms}} - V_{L_{rms}})^2$$

$$(400)^2 = V_{R_{rms}}^2 + (200 - 300)^2$$

$$V_{R_{rms}} = \sqrt{(400)^2 - (100)^2}$$

$$= 100\sqrt{15}$$

(a) Zero

(b) 2.23 A

(c) 4.26 A

(d) 3.87 A

$$i_{rms} = \frac{V_{R_{rms}}}{R} = \frac{100\sqrt{15}}{100} = 3.87A$$

Z

Q.2) 110 V (rms) is applied across a series circuit having resistance 11  $\Omega$  and impedance 22  $\Omega$ . The power consumed is:

$$\begin{aligned} P &= V_{\text{rms}} I_{\text{rms}} \cos \phi \\ &= \frac{V_{\text{rms}}^2}{Z} \times \frac{R}{Z} = \frac{V_{\text{rms}}^2 R}{Z^2} = \frac{110^2 \times 11}{22 \times 22} \\ &= 275 \text{ Watt} \end{aligned}$$

(a) 275 W

(b) 366 W

(c) 550 W

(d) 1100 W



Q.3) At a frequency  $\omega_0$  the reactance of a certain capacitor equals that of a certain inductor. If the frequency is changed to  $2\omega_0$ , what is the ratio of the reactance of the inductor to that of the capacitor?

$$X_c = X_L$$
$$\frac{1}{\omega_0 C} = \omega_0 L$$

$$\omega_0 \rightarrow 2\omega_0$$

$\Rightarrow X_L$  increases to 2 times  
 $X_C$  decreases to  $\frac{1}{2}$  times

$$\frac{X_L}{X_C} \text{ increases to 4 times}$$

(a) 4 : 1

(b)  $\sqrt{2} : 1$

(c)  $1 : 2\sqrt{2}$

(d) 1 : 2

Q.4) An alternating voltage given by  $V = 300 \sqrt{2} \sin(50t)$  (in volts) is connected across a  $1 \mu\text{F}$  capacitor through an AC ammeter. The reading of the ammeter will be:

$$V_0$$

$$V_{\text{rms}} = \frac{V_0}{\sqrt{2}} = 300$$

$$X_c = \frac{1}{\omega C} = \frac{10^6}{50} = \frac{100 \times 10^4}{50}$$

$$= 2 \times 10^4 \Omega$$

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{X_c} = \frac{300}{2 \times 10^4} = \frac{150}{10^4} \times 10^{-3} = 15 \text{ mA}$$


(a) 10 mA

(b) 40 mA

(c) 100 mA

(d) ~~30 mA~~  $\frac{15 \text{ mA}}$

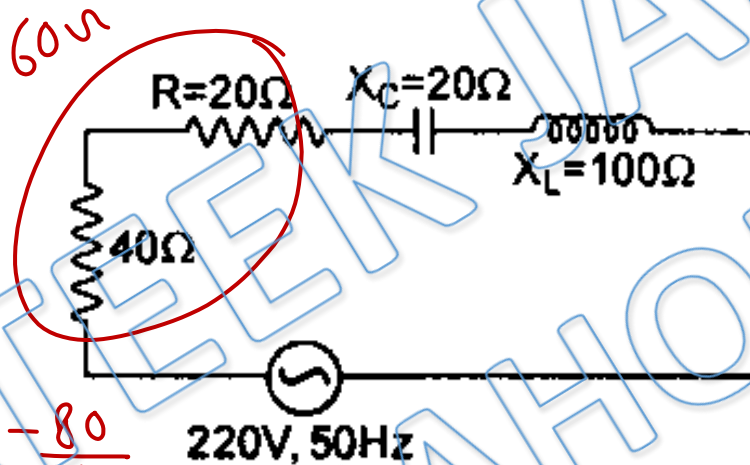Q.5) The power factor of the circuit shown in the figure is:



$$\tan \phi = \frac{X_c - X_L}{R}$$

$$= \frac{20 - 100}{60} = -\frac{80}{60}$$

$$= -\frac{4}{3}$$

(a) 0.4

(b) 0.2

(c) 0.8

(d) 0.6


$$R = 60$$

$$Z = \sqrt{(60)^2 + (20 - 100)^2}$$

$$= 100$$

$$\cos \phi = \frac{R}{Z} = \frac{60}{100}$$

$$= .6$$

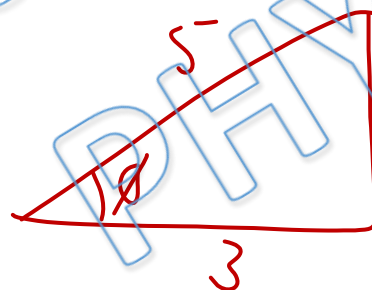

$$\cos \phi = \frac{3}{5}$$

Q.6) What will be the reading of the voltmeter across the resistance and ammeter in the circuit shown in the figure?

Since  $V_C = V_L$


⇒ Circuit is in resonance

$V_{R_{total}} = 200V$

$i_{rms} = \frac{V_{rms}}{R} = \frac{200}{100} = 2A$

$V_{rms}^2 = V_{R_{rms}}^2 + (V_{C_{rms}} - V_{L_{rms}})^2$   
 $(200)^2 = V_{R_{rms}}^2 + (100 - 100)^2$

$V_{R_{rms}} = 200V$

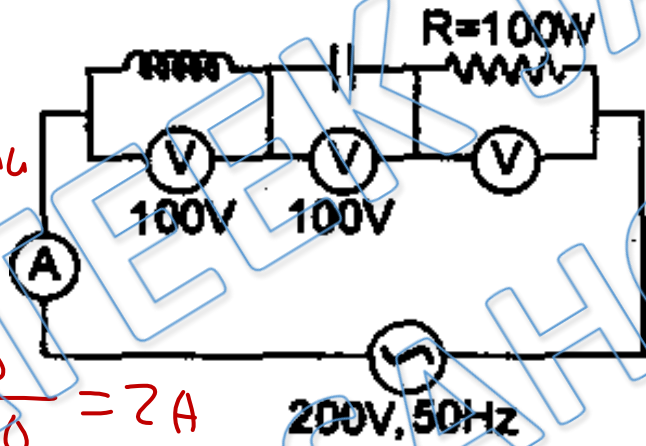



(a) 300 V, 2 A

(b) 800 V, 2 A

(c) 100 V, 2 A

✓ (d) 200 V, 2 A

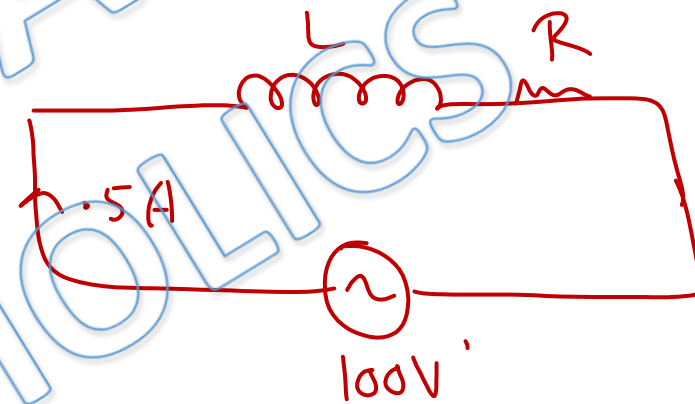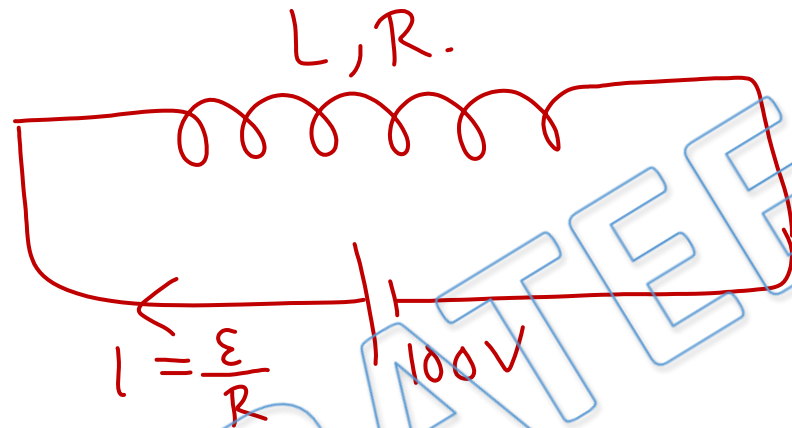Q.7) When 100 V. DC is applied across a solenoid a current of 1 A flows in it. When 100 V, AC is applied across the same coil, the current drops to 0.5 A. The frequency of the AC is 50 Hz. The impedance and inductance of the solenoid are:



(a) 1000, 0.75 H

$$\frac{100}{R} = 1A$$

(b) 1000, 0.60H

$$Z = \frac{100}{0.5} = 200\Omega$$

(c) 200, 0.55H

$$R = 100\Omega$$

(d) 200, 0.75H

$$Z^2 = R^2 + X_L^2$$



$$X_L = \sqrt{(200)^2 - (100)^2}$$

$$= 100\sqrt{3}$$

$$\omega L = 100\sqrt{3} \Rightarrow L = \frac{100\sqrt{3}}{100\pi} = \frac{1.73}{3.14}$$

$$V_C = V_L \Rightarrow \text{Resonance}$$

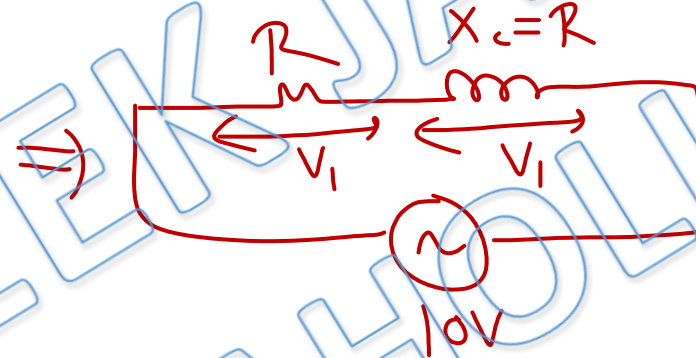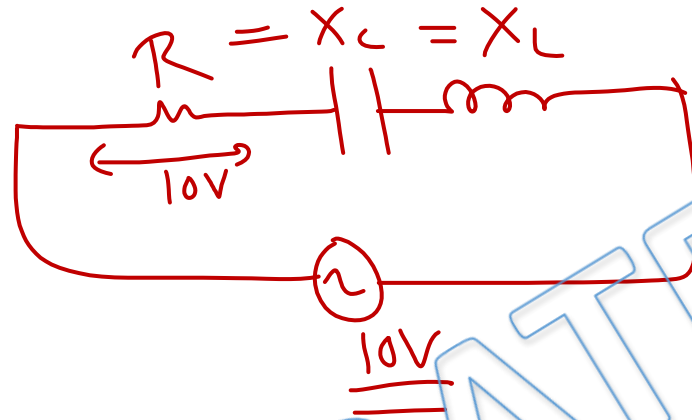Q.8) In a series LCR the voltage across resistance, capacitance and inductance is 10 V each. If the capacitance is short circuited, the voltage across the inductance will be:



$$V_{RL}^2 = V_R^2 + V_L^2$$

$$100 = V_1^2 + V_1^2$$

$$V_1^2 = \frac{100}{2}$$

$$V_1 = \frac{10}{\sqrt{2}} \text{ V}$$

(a)  $\frac{10}{\sqrt{2}} \text{ V}$

(b) 10 V


(c)  $10\sqrt{2} \text{ V}$

(d) 20 V

$$V_R = V_L = V_C$$

$$\Rightarrow iR = iX_L = iX_C$$

Q.9) Choose the wrong statement:

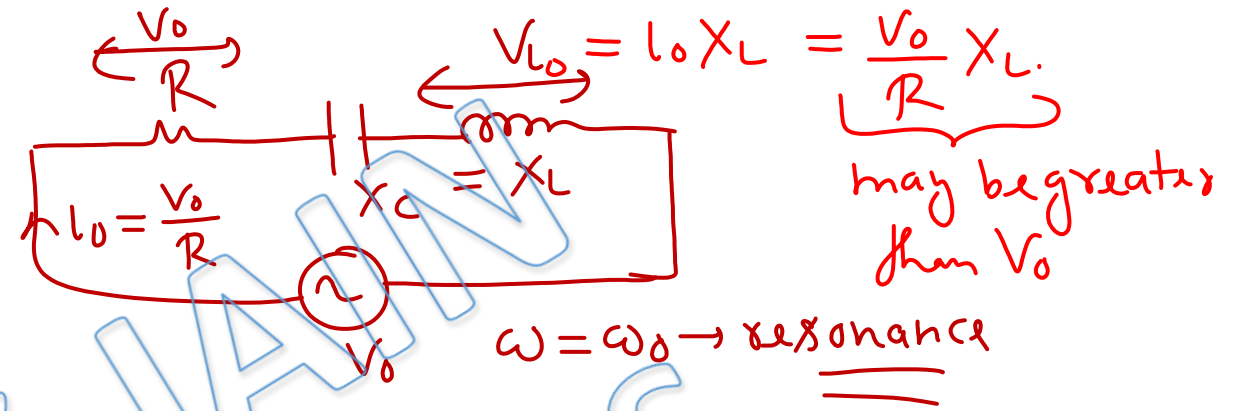

(a) The peak voltage across the inductor can be greater than the peak voltage of the source in an LCR circuit.

(b) In a circuit containing a capacitor and an AC source the current is zero at the instant the source voltage is maximum. (Since there is a phase difference of  $\pi/2$ )

(c) An AC source is connected to a capacitor. The rms current in the circuit gets increased if a dielectric slab is inserted into the capacitor.

(d) ~~None of the above~~

$C \uparrow \Rightarrow X_C \downarrow \Rightarrow I_{rms} = \frac{V_{rms}}{X_C}$   
 $\downarrow$  increases

Q.10) An AC source producing emf  $V = V_0 [\sin \omega t + \sin 2\omega t]$  is connected in series with a capacitor and a resistor. The current found in the circuit is  $i = i_1 \sin (\omega t + \phi_1) + i_2 \sin (2\omega t + \phi_2)$ . Then :

$$Z = \sqrt{R^2 + \frac{1}{\omega^2 C^2}}$$

$$V = V_0 \sin \omega t + V_0 \sin 2\omega t$$

$$i = i_1 \sin(\omega t + \phi_1) + i_2 \sin(2\omega t + \phi_2)$$

(a)  $i_1 = i_2$

(b)  $i_1 < i_2$

(c)  $i_1 > i_2$


(d)  $i_1$  may be less than, equal to or greater than  $i_2$

$$i_1 = \frac{V_0}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}}$$

$$i_2 = \frac{V_0}{\sqrt{R^2 + \frac{1}{4\omega^2 C^2}}}$$



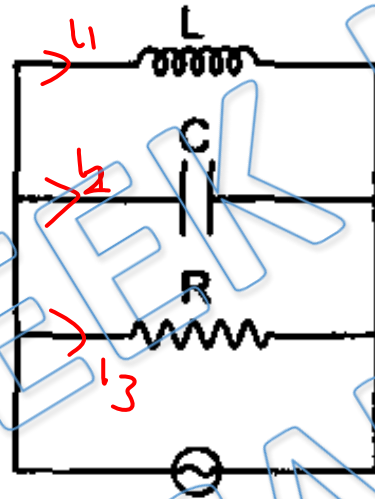Q.11) Figure shows a parallel LCR circuit connected to a 200 V, AC source.  $L = 5\text{H}$ ,  $C = 80\ \mu\text{F}$  and  $R = 40\ \Omega$  at resonance let  $i_1$ ,  $i_2$  and  $i_3$  be the rms current through L, C and R. Then:  $X_C = X_L = 250\ \Omega$



Current in Induction

$$i_1 = \frac{V_0}{X_L} \sin(\omega t - \pi/2)$$

Current in Capacitor

$$i_2 = \frac{V_0}{X_C} \sin(\omega t + \pi/2)$$

$$V = V_0 \sin \omega t$$

$$i_3 = \frac{V_0}{R} \sin \omega t$$

$$i_{rms} = \frac{V_0}{\sqrt{2} R}$$

$$= \frac{200}{40\sqrt{2}} = \frac{5}{\sqrt{2}}$$

$$\begin{aligned} \omega_0 &= \frac{1}{\sqrt{LC}} \\ &= \frac{1}{\sqrt{5 \times 80 \times 10^{-6}}} \\ &= \frac{1000}{20} \\ &= 50 \end{aligned}$$

$$\begin{aligned} X_L &= \omega L = 50 \times 5 \\ &= \underline{250\ \Omega} \star \end{aligned}$$

(a)  $i_1 = i_2$  and  $i_1 > i_2$

(b)  $i_1 = 0 = i_2$

(c)  $i_1 = i_2$  and  $i_1 < i_3$


(d)  $i_1 = i_2$  and  $i_3 \ll i_1$

$$\begin{aligned} i_1 &= -\left(\frac{V_0}{X_L}\right) \cos \omega t \\ i_2 &= \left(\frac{V_0}{X_C}\right) \cos \omega t \end{aligned}$$

$$i_{rms} = i_{2,rms} = \frac{V_0}{\sqrt{2} X_L} = \frac{200}{\sqrt{2} \times 250} = \frac{4}{5\sqrt{2}}$$

$$\omega = 100\pi$$

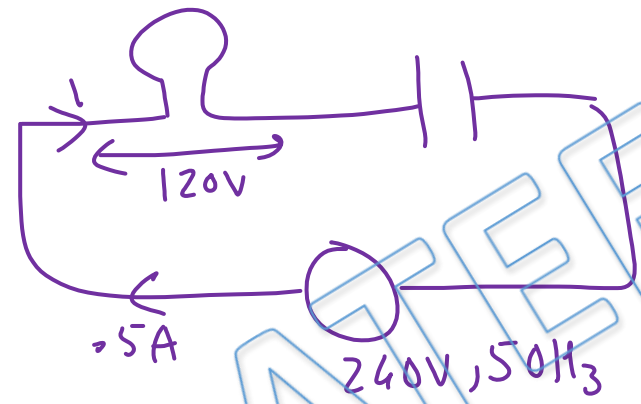Q.12) A 120 V, 60 W lamp is run from a 240V, 50 Hz mains supply using a capacitor connected in series with the lamp and supply. What is value of the capacitor required to operate the lamp at its normal rating?



$$Z = \frac{V_{rms}}{I_{rms}} = \frac{240}{0.5} = 480\Omega$$

$$Z^2 = R^2 + X_c^2$$

- (a) 3.8  $\mu\text{F}$       (b) 6.6  $\mu\text{F}$       (c) 7.7  $\mu\text{F}$       (d) 13.3  $\mu\text{F}$

$$P = VI$$

$$I = \frac{P}{V} = \frac{60}{120} = \frac{1}{2} \text{ A}$$

$$R = \frac{V}{I} = \frac{120}{\frac{1}{2}} = 240$$

$$X_c = \sqrt{(480)^2 - (240)^2}$$

$$X_c = 240\sqrt{3}$$

$$\frac{1}{100\pi C} = 240\sqrt{3}$$

$$C = \frac{1}{100\pi \times 240\sqrt{3}} \text{ F}$$

$$C = \frac{1000\phi\phi\phi}{1\phi\phi\pi \times 240\sqrt{3}} \mu F$$

$$= \frac{125}{3\sqrt{3}\pi} \mu F$$

$$= \frac{125}{3 \times 3.14 \times 1.73}$$

$$= \frac{125}{16.2}$$

$$= 7.7 \mu F$$

$$\begin{array}{r} 314 \times 173 \\ \hline \end{array}$$

$$942$$

$$2198$$

$$31400$$

$$\hline 54322 \Rightarrow 5.4$$

Ans. c

Q.13) A series circuit has an impedance of  $50.0\Omega$  and a power factor of 0.63 at 60 Hz. The voltage lags the current. To raise the power factor of the circuit:

$$X_c > X_L$$

$$\tan \phi = \frac{X_c - X_L}{R}$$

(a) an inductor should be placed in series

(b) a capacitor should be placed in series

(c) a resistance should be placed in series

(d) an inductor or a resistance should be placed in series

$$\text{Power factor} = \cos \phi \uparrow$$

$$\Rightarrow \phi \downarrow$$


$$\Rightarrow \tan \phi \downarrow$$

$$\downarrow X_c \downarrow \text{ or } X_L \uparrow \text{ or } R \uparrow$$

$\downarrow$   
add L in Series       $\downarrow$   
add R in Series

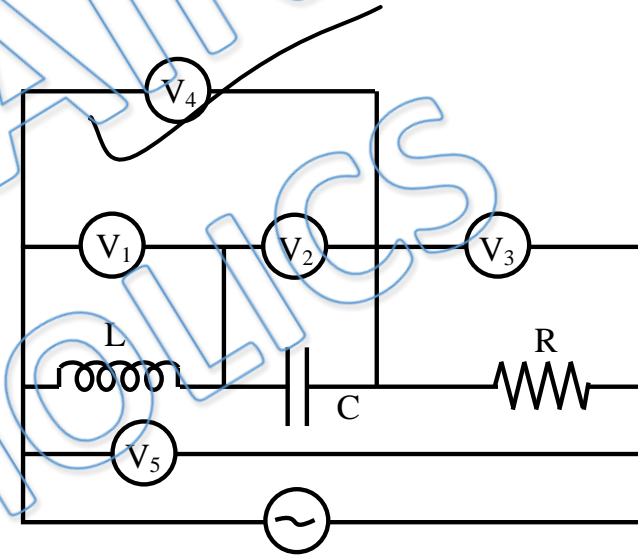Q.14) In the adjoining A.C. circuit the voltmeter whose reading will be zero at resonance is-

In resonance  
rms voltage across combination  
of L & C = 0



(a)  $V_1$

(b)  $V_2$

(c)  $V_3$

~~(d)  $V_4$~~

**For Video Solution of this DPP, Click on below link**

Video Solution  
on Website:-

<https://physicsaholics.com/home/courseDetails/102>

Video Solution  
on YouTube:-

<https://youtu.be/O3WmlqLxMJg>

Written Solution  
on Website:-

<https://physicsaholics.com/note/notesDetails/60>

 SUBSCRIBE



[@Physicsaholics](#)

[@Physicsaholics\\_prateek](#)

[@NEET\\_Physics](#)

[@IITJEE-Physics](#)

[physicsaholics.com](#)

[Unacademy](#)



**CLICK**

Chalo Niklo