

DPP – 2 (Capacitor)

Video Solution on Website:-

<https://physicsaholics.com/home/courseDetails/65>


Video Solution on YouTube:-

<https://youtu.be/pGZdLYUMDlq>

Written Solution on Website:-

<https://physicsaholics.com/note/notesDetails/62>

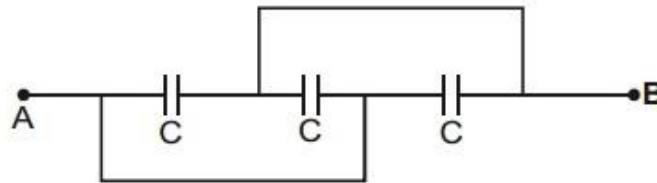Q 1. Find the equivalent capacitance of the given circuit:



- (a) $\frac{3C}{2}$ (b) $\frac{C}{3}$
 (c) $3C$ (d) C


Q 2. A capacitor $C_1 = 4 \mu F$ is connected in series with another capacitor $C_2 = 1 \mu F$. The combination is connected across a D.C. source of voltage 200 V. The ratio of potential across C_1 and C_2 is:

- (a) 1 : 4 (b) 4 : 1
 (c) 1 : 2 (d) 2 : 1

Q 3. The equivalent capacitance of three capacitors of capacitance C_1 , C_2 and C_3 connected in parallel is 12 units and the product $C_1 C_2 C_3 = 48$. When the capacitors C_1 and C_2 are connected in parallel the equivalent capacitance is 6 units. Then the capacitance are :

- (a) 1.5, 2.5, 8 (b) 2, 3, 7
 (c) 4, 2, 6 (d) 1, 5, 6

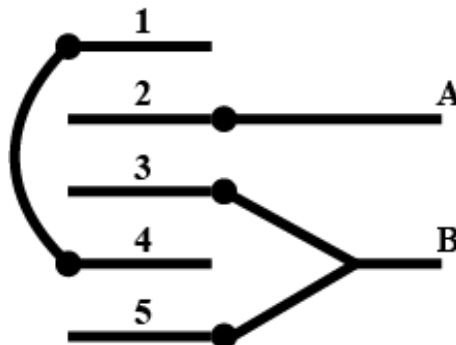Q 4. Five identical metal plates 1, 2, 3, 4 and 5 each of area A on one side are fixed parallel and equidistant (d) to each other. The plates 1 and 4 are joined by a conductor, and plates 3 and 5 are also joined by a conductor as shown in figure. Then, the capacitance of this system between A and B is-



- (a) $\frac{5\epsilon_0 A}{d}$ (b) $\frac{4\epsilon_0 A}{d}$




- (c) $\frac{5\epsilon_0 A}{3d}$ (d) none of these

Q 5. Three capacitors of capacitances 2 pF, 3pF and 4pF are connected in parallel. What is the total capacitance of the combination?


- (a) 9 pF (b) 1 pF
(c) 5 pF (d) 15 pF

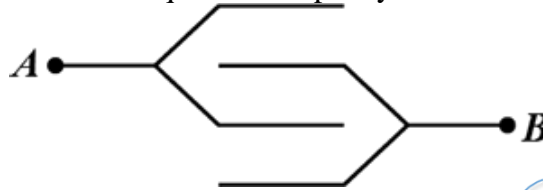Q 6. Four plates of same area of cross-section A are joined as shown in figure. The distance between each plate is d. The equivalent capacity between A and B will be



- (a) $\frac{2\epsilon_0 A}{d}$ (b) $\frac{\epsilon_0 A}{d}$
(c) $\frac{3\epsilon_0 A}{d}$ (d) $\frac{3\epsilon_0 A}{2d}$

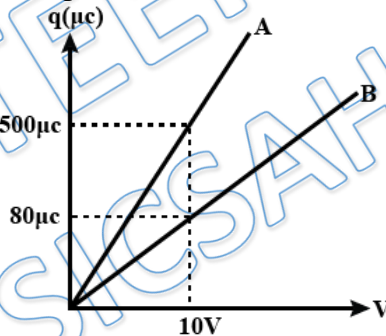Q 7. Plot A&B represent variation of charge with potential difference across the combination (series and parallel) of two capacitors. Then find the value of capacitance of capacitors.



- (a) 20 μ F, 30 μ F (b) 10 μ F, 40 μ F
(c) 10 μ F, 15 μ F (d) 25 μ F, 25 μ F

Q 8. Find the total capacitance for three capacitors of 10f, 15f and 35f in parallel with each other?


- (a) 20 F (b) 50 F
(c) 60 F (d) 10 F

Q 9. Five identical parallel conducting plates each of area A have separation 'd' between successive surface. The plates are connected to the terminal of a battery as shown in the figure. The effective capacitance of the circuit is




- (a) $\frac{A\epsilon_0}{4d}$ (b) $\frac{4A\epsilon_0}{d}$
 (c) $\frac{A\epsilon_0}{3d}$ (d) $\frac{3A\epsilon_0}{4d}$

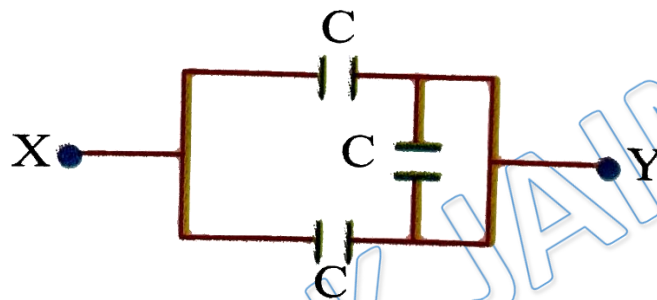Q 10. The equivalent capacity between the points X and Y in the circuit with $C=1\mu\text{F}$.




- (a) $2\mu\text{F}$ (b) $3\mu\text{F}$
 (c) $1\mu\text{F}$ (d) $0.5\mu\text{F}$

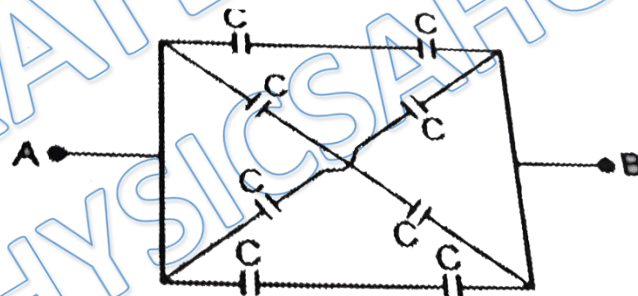Q 11. In the adjoining circuit, the capacity between the points A and B will be -




- (a) C (b) 2C
 (c) 3C (d) 4C

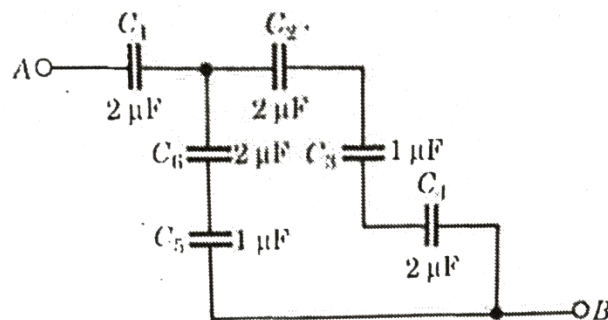Q 12. Calculate the equivalent capacitance between the points A and B of the circuit given below.




- (a) $\frac{14}{19} \mu\text{F}$ (b) $\frac{13}{17} \mu\text{F}$
 (c) $\frac{21}{13} \mu\text{F}$ (d) $\frac{11}{21} \mu\text{F}$

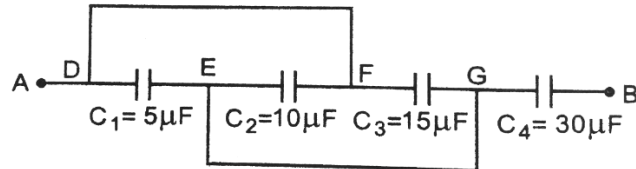Q 13. Calculate the equivalent capacitance between the points A and B in the combination shown in Fig.




- (a) $15 \mu\text{F}$ (b) $10 \mu\text{F}$
 (c) $20 \mu\text{F}$ (d) 25Mf

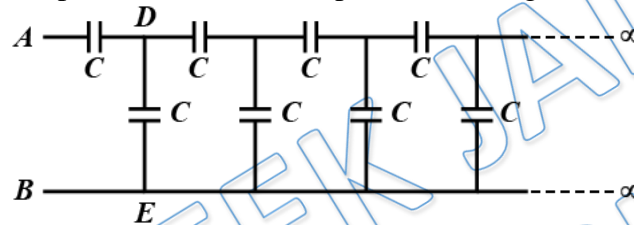Q 14. The capacitance of a infinite circuit formed by the repetition of the same link consisting of two identical capacitors, each with capacitance C (figure), is :




- (a) zero (b) $\frac{\sqrt{5}-1}{2} C$
 (c) $\frac{\sqrt{5}+1}{2} C$ (d) infinite

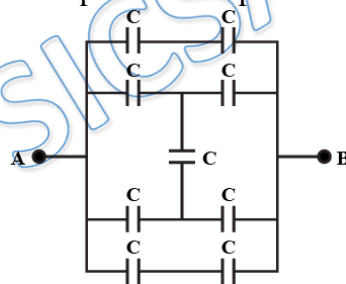Q 15. The resultant capacity between point A and point B in the following circuit will be:




- (a) C (b) $\frac{C}{2}$
 (c) $2C$ (d) $3C$

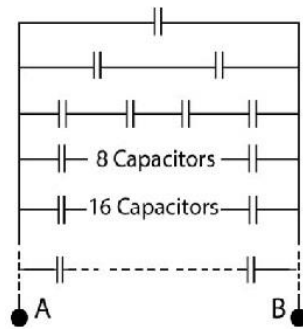Q 16. An infinite number of identical capacitors, each of capacitance $1 \mu\text{F}$ are connected as shown in the figure. Then the equivalent capacitance between A and B is :




- (a) $1 \mu\text{F}$ (b) $2 \mu\text{F}$
 (c) $\frac{1}{2} \mu\text{F}$ (d) infinite

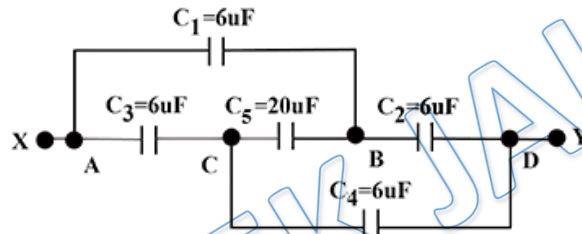Q 17. What is the equivalent capacitance between X and Y?



- (a) $10 \mu\text{F}$ (b) $15 \mu\text{F}$
 (c) $18 \mu\text{F}$ (d) $6 \mu\text{F}$

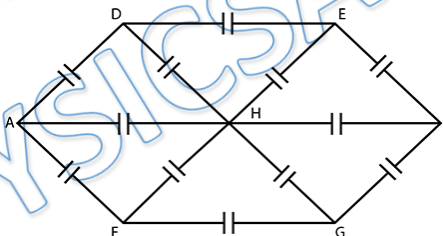Q 18. What is the equivalent capacitance between A and B if capacitance of each capacitor is C?



- (a) $\frac{5C}{4}$ (b) $\frac{3C}{2}$
 (c) $\frac{2C}{3}$ (d) $\frac{4C}{5}$



Answer Key

Q.1 c	Q.2 a	Q.3 c	Q.4 c	Q.5 a
Q.6 c	Q.7 b	Q.8 c	Q.9 b	Q.10 a
Q.11 b	Q.12 a	Q.13 a	Q.14 b	Q.15 c
Q.16 b	Q.17 d	Q.18 a		

PRATEEK JAIN
PHYSICSAHOLICS

PLUS **ICONIC****

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

24 months ₹2,333/mo >
No cost EMI ₹56,000

18 months ₹2,625/mo >
No cost EMI ₹47,250

12 months ₹3,208/mo >
No cost EMI ₹38,500

6 months ₹4,667/mo >
No cost EMI ₹28,000

To be paid as a one-time payment

[View all plans](#)



Add a referral code

APPLY

PHYSICSLIVE

Use code **PHYSICSLIVE** to get 10% OFF on Unacademy PLUS.

PLUS **ICONIC****

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

24 months ₹2,100/mo >
No cost EMI **+10% OFF** ₹50,400

18 months ₹2,363/mo >
No cost EMI **+10% OFF** ₹42,525

12 months ₹2,888/mo >
No cost EMI **+10% OFF** ₹34,650

6 months ₹4,200/mo >
No cost EMI **+10% OFF** ₹25,200

To be paid as a one-time payment

[View all plans](#)



Awesome! **PHYSICSLIVE** code applied





Written Solution

DPP 2 - Combination of Series and Parallel Capacitor

By Physicsaholics Team

Solution: 1

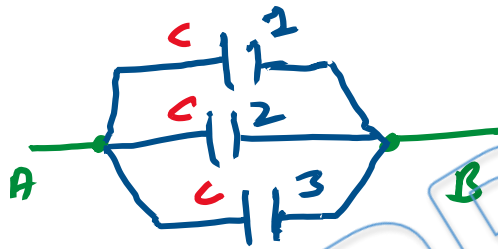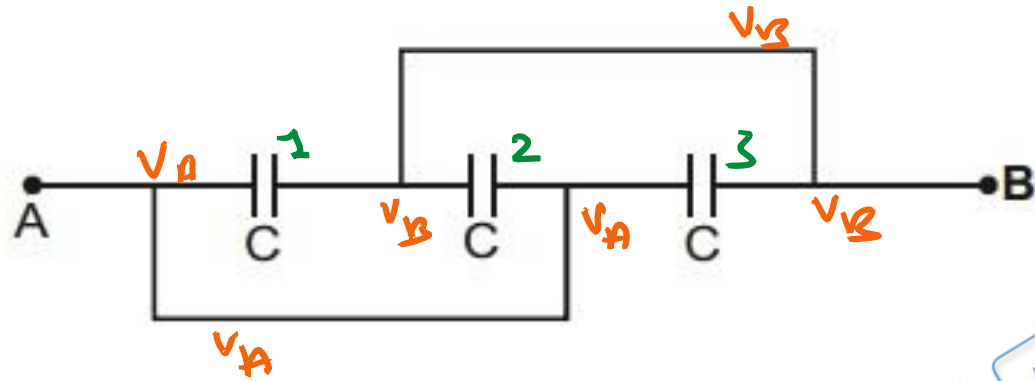


$$C_{eq} = C_1 + C_2 + C_3 \\ = C + C + C$$

$$C_{eq} = 3C \quad \text{Ans}$$

Ans. c

Solution: 2

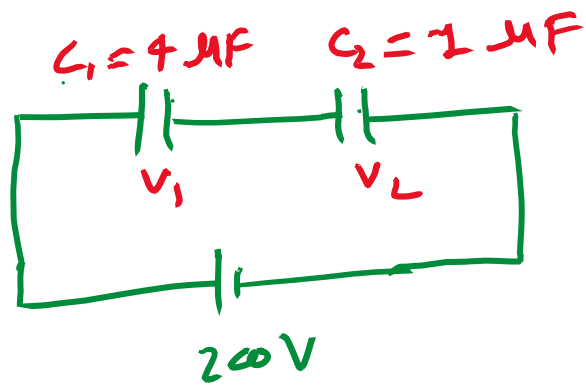

$\therefore C_1$ & C_2 both are in series

so, charge on both capacitors will be equal

$$Q = C_1 V_1 = C_2 V_2$$

$$(4 \mu\text{F}) V_1 = (1 \mu\text{F}) V_2$$

$$V_2 = 4 V_1$$

$$\Rightarrow \frac{V_1}{V_2} = \frac{1}{4} \quad \underline{\text{Ans}}$$

Ans. a

Solution: 3
in parallel;

$$12 = C_1 + C_2 + C_3 \quad \text{--- (1)}$$

given; $C_1 C_2 C_3 = 48$ --- (2)

when, C_1 & C_2 in parallel

$$C_1 + C_2 = 6 \quad \text{--- (3)}$$

put $C_1 + C_2$ in eqⁿ (1)

$$12 = 6 + C_3$$

$$C_3 = 6 \text{ unit}$$

put value of C_3 in eqⁿ (2)

$$C_1 C_2 (6) = 48$$

$$\Rightarrow C_1 C_2 = 8 \quad \text{--- (4)}$$

$$C_1 = \frac{8}{C_2}$$

put 'C' in eqⁿ (3)

$$\frac{8}{C_2} + C_2 = 6 \Rightarrow C_2^2 - 6C_2 + 8 = 0$$

$$C_2 = \frac{-(-6) \pm \sqrt{(-6)^2 - 4 \times 1 \times 8}}{2(1)}$$

$$C_2 = \frac{6 \pm \sqrt{36 - 32}}{2} = \frac{6 \pm 2}{2}$$

$$C_2 = 4 \text{ or } 2$$

when; $C_2 = 4$; $\Rightarrow C_1 = 2$

when; $C_2 = 2$; $\Rightarrow C_1 = 4$

So, $C_1, C_2, C_3 \equiv$


2, 4, 6
4, 2, 6

As




Ans. c

Solution: 4

$$C = \frac{\epsilon_0 A}{d}$$

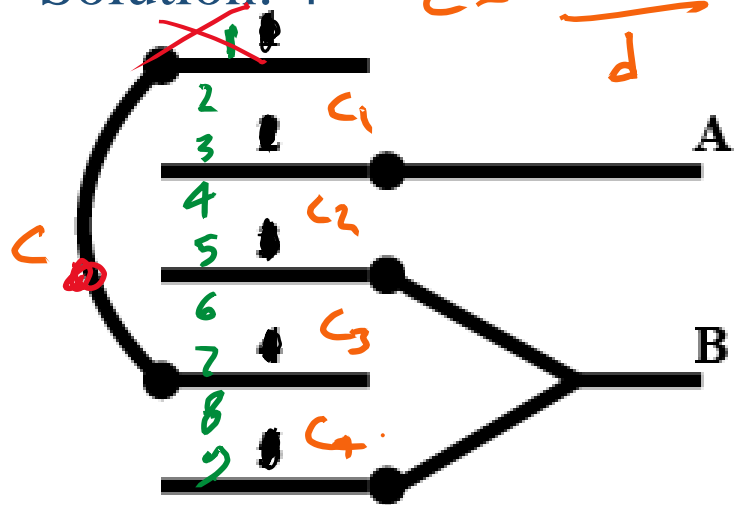

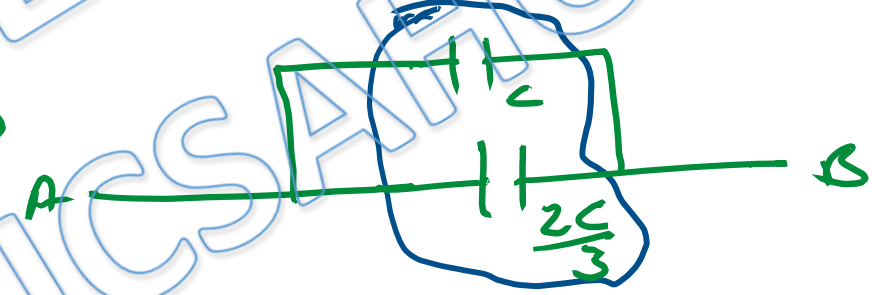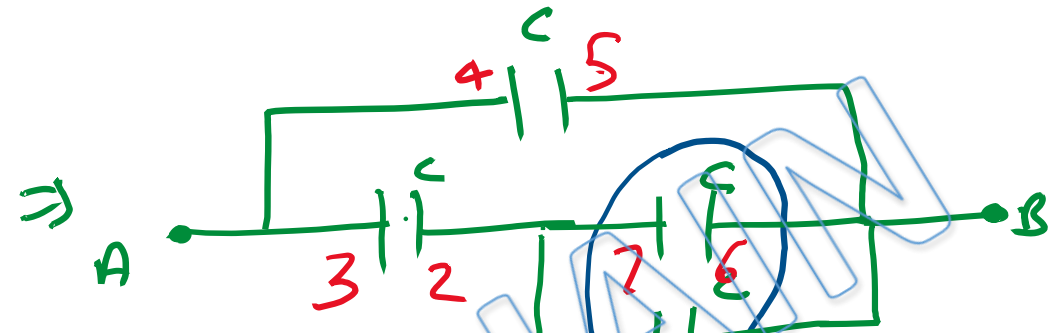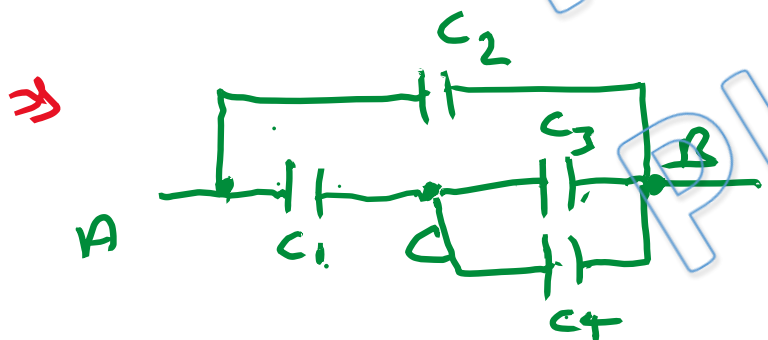- $C_1 \rightarrow$ between A & C
- $C_2 \rightarrow$ between A & B
- $C_3 \rightarrow$ between B & C
- $C_4 \rightarrow$ between B & C



$$\Rightarrow C_{eq} = C + \frac{2C}{3}$$


$$C_{eq} = \frac{5C}{3}$$

$$\Rightarrow C_{eq} = \frac{5\epsilon_0 A}{3d}$$

Ans

Ans. c

Solution: 5

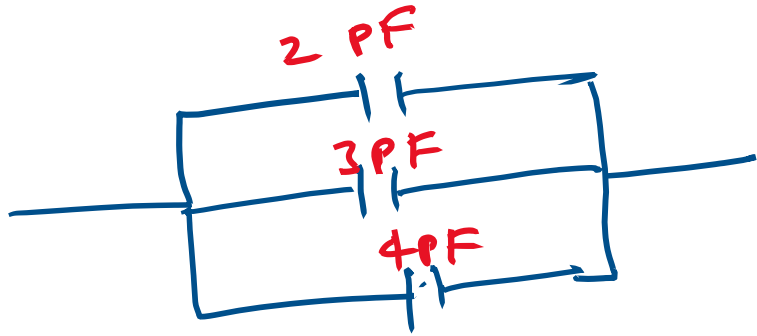


$$C_{eq} = C_1 + C_2 + C_3$$
$$= 2 \text{ pF} + 3 \text{ pF} + 4 \text{ pF}$$

$$C_{eq} = 9 \text{ pF} \quad \text{Ans.}$$

Ans. a

Solution: 6

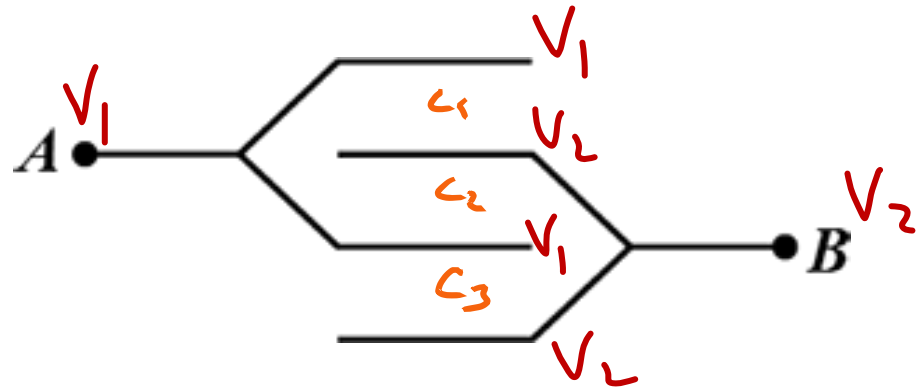

$$C_{eq} = 3 \left(\frac{\epsilon_0 A}{d} \right)$$

$$C_{eq} = \frac{3\epsilon_0 A}{d} \quad \underline{\text{Ans}}$$

C_1 , C_2 & C_3 have equal Potential difference.

so; all capacitors are in parallel


⇒



$$C_{eq} = 3C$$

Ans. c

Solution: 7

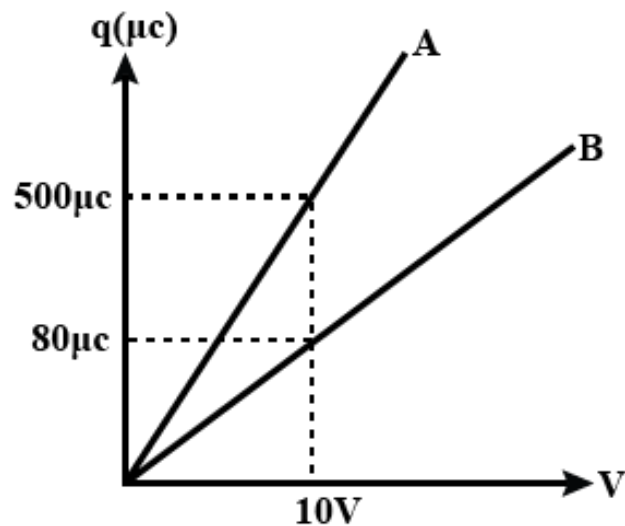

Let capacitance are C_1 & C_2

\therefore (C) in parallel $>$ (C) in series

$$q = CV$$

$q \propto C$ (for $V = \text{constant}$)

$$\therefore q_A > q_B \Rightarrow C_A > C_B$$

so; $A \rightarrow$ for parallel
 $B \rightarrow$ for series.

$$C_A = C_1 + C_2, \quad C_B = \frac{C_1 C_2}{C_1 + C_2}$$

$$q_A = C_A \cdot V \quad q_B = C_B \cdot V$$

$$C_A = \frac{500 \mu C}{10} = 50 \mu F, \quad C_B = \frac{80 \mu C}{10} = 8 \mu F$$

$$C_A \cdot C_B = C_1 C_2 = \frac{40}{100} \times 10^{-9} = 4 \times 10^{-10} \quad \text{--- (1)}$$

$$\frac{C_A}{C_B} = \frac{(C_1 + C_2)^2}{C_1 C_2} = \frac{50}{8} = \frac{25}{4}$$

$$(C_1 + C_2)^2 = \frac{25}{4} \times 4 \times 10^{-10} = 25 \times 10^{-10}$$

$$C_1 + C_2 = 5 \times 10^{-5} \text{ F} \quad \text{--- (2)}$$

from (1) & (2)

$$\left. \begin{aligned} C_1 &= 1 \times 10^{-5} \text{ F} = 10 \mu F \\ C_2 &= 4 \times 10^{-5} \text{ F} = 40 \mu F \end{aligned} \right\} \text{Ans}$$

Ans. b

Solution: 8

in parallel combination

$$C = C_1 + C_2 + C_3$$

$$C = 10 + 15 + 35$$



$$C = 60 \text{ F}$$

Ans

PRATEEK JAIN
PHYSICSAHOLICS

Ans. c

Solution: 9

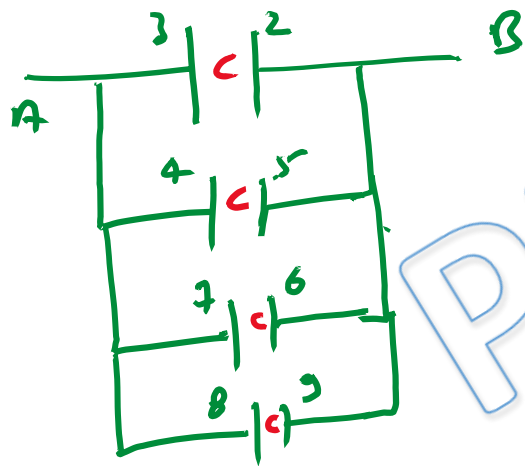
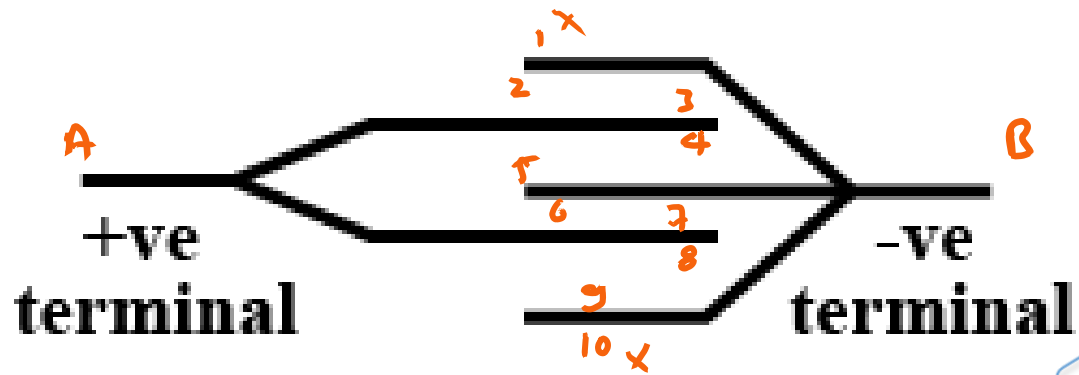


$$\Rightarrow C_{eq} = 4C = \frac{4 \epsilon_0 A}{d}$$

$$C_{eq} = \frac{4 \epsilon_0 A}{d} \text{ Ans.}$$

Ans. b

Solution: 10

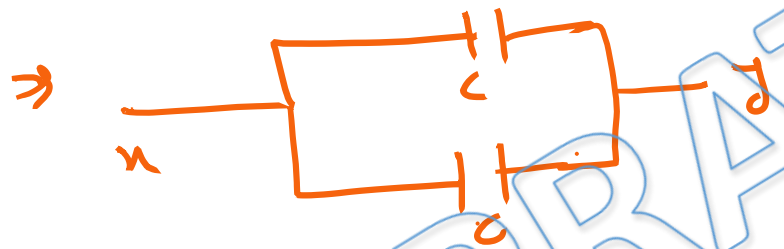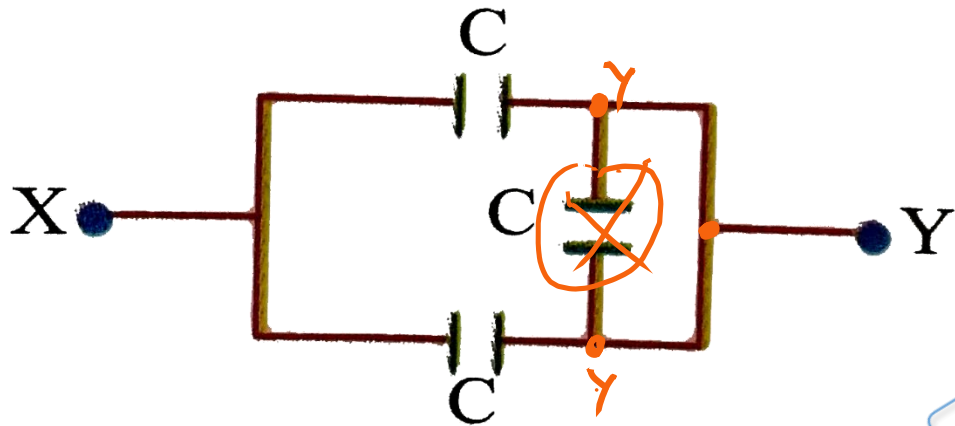

$$C_{eq} = 2C$$


$$[\because C = 1 \mu F]$$

$$C_{eq} = 2 \mu F$$


Ans.

Ans. a

Solution: 11

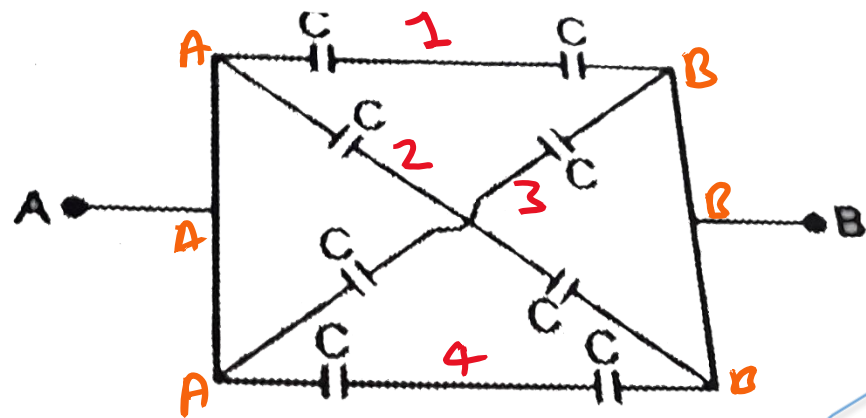

⇒

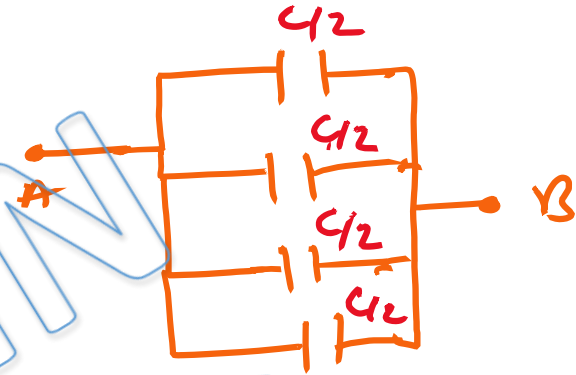


$$C_{eq} = 4 \left(\frac{C}{2} \right)$$

$$C_{eq} = 2C$$


∴ from diagram we can see that potential difference between branch 1, 2, 3 & 4 is same ($V_A - V_B$) so; 1, 2, 3 & 4 all branches are in parallel

⇒

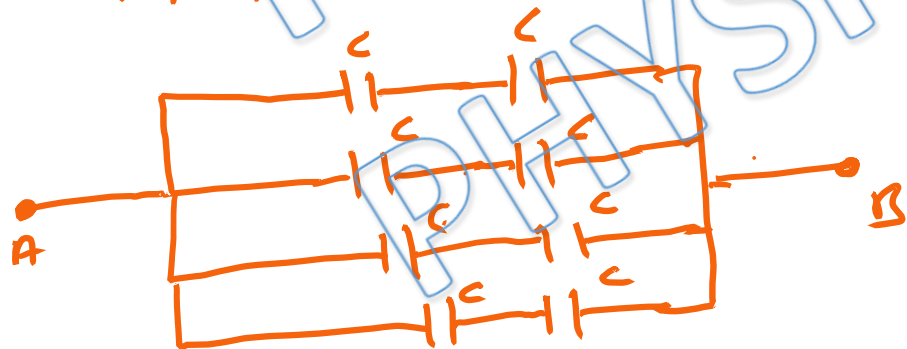



Ans. b

Solution: 12

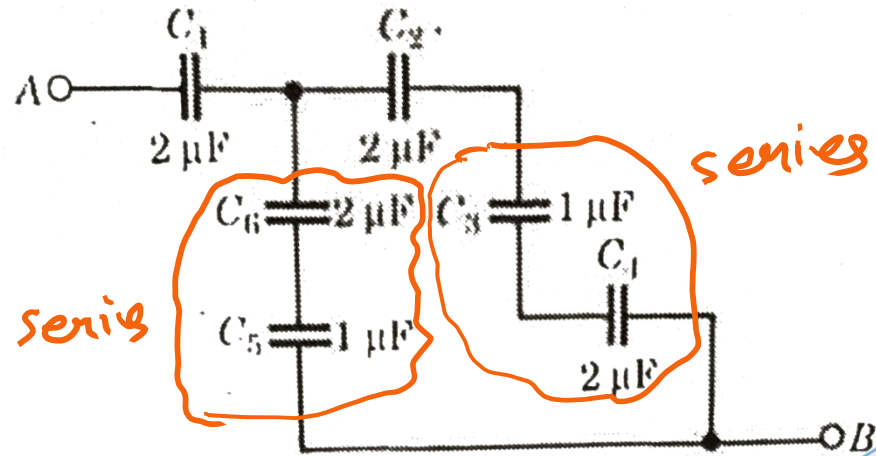




$$C_{eq} = \frac{2 \times \frac{7}{6}}{2 + \frac{7}{6}} = \frac{14/6}{19/6}$$
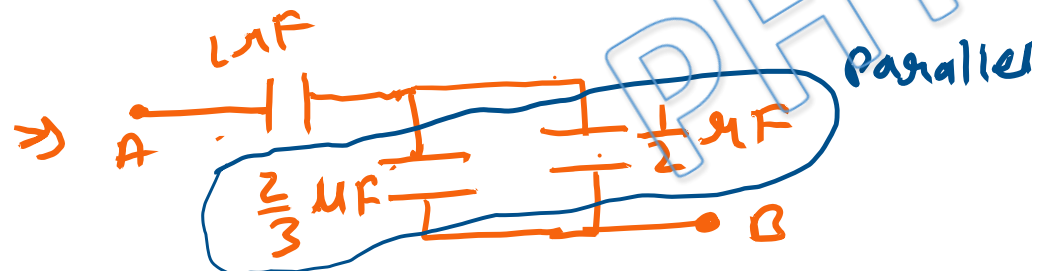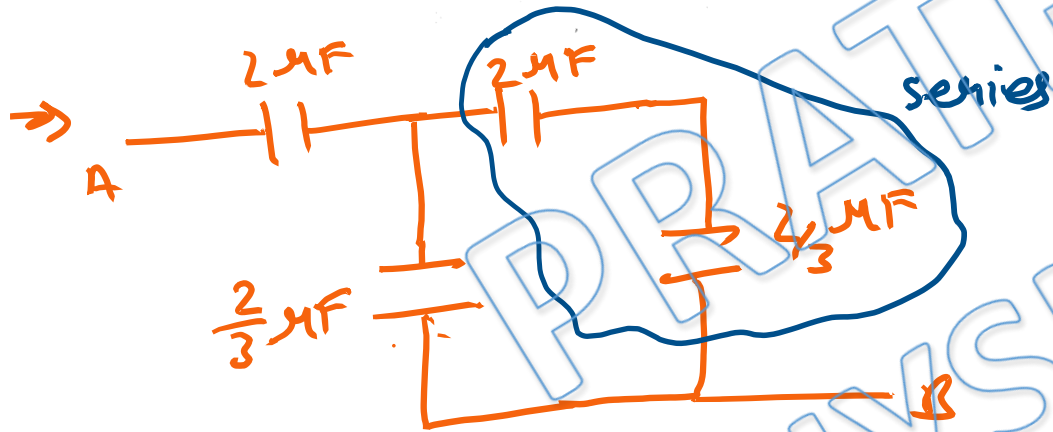
$$C_{eq} = \frac{14}{19} \mu\text{F} \quad \text{Ans.}$$




Ans. a

Solution: 13

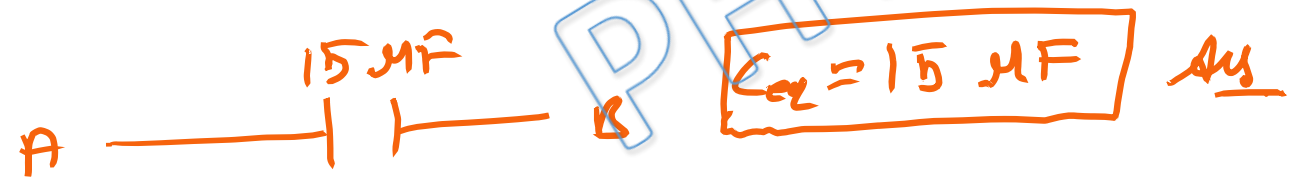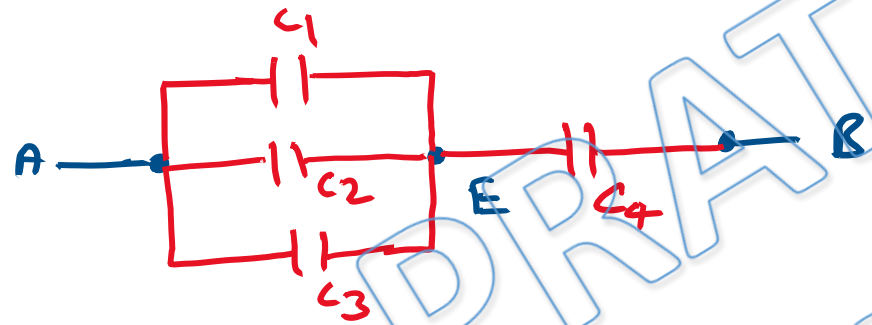
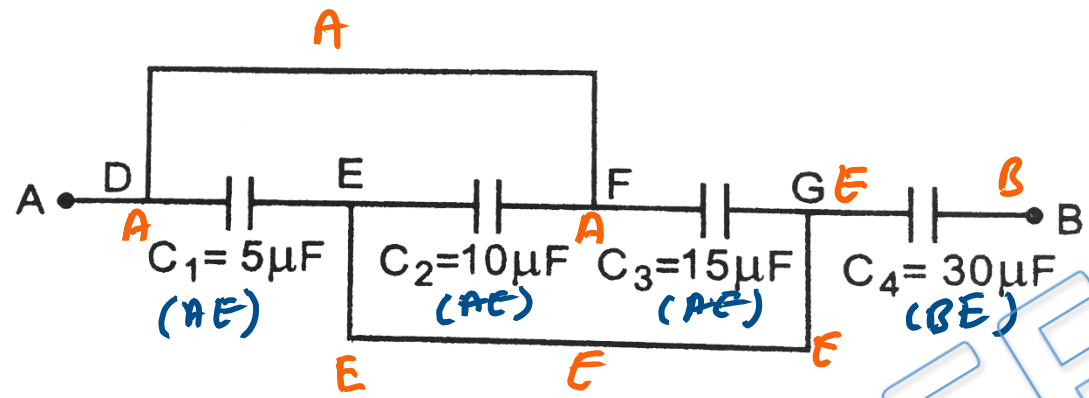


Ans. a

Solution: 14

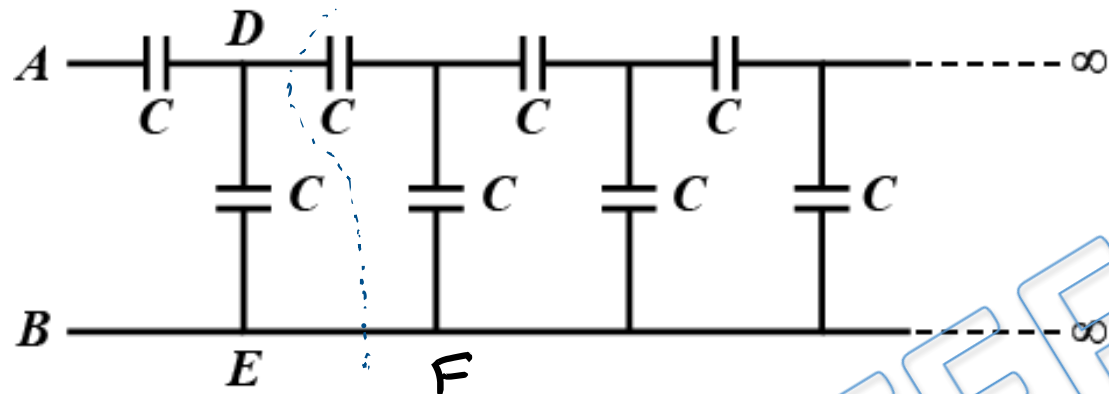

$C_{AB} = C_{DE} = C_{eq}$

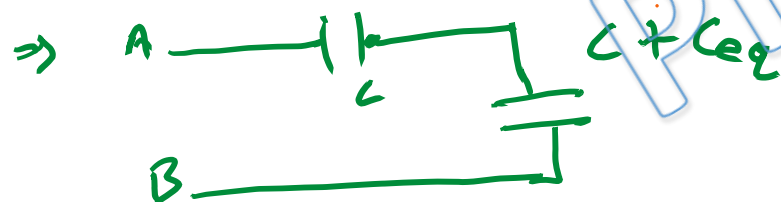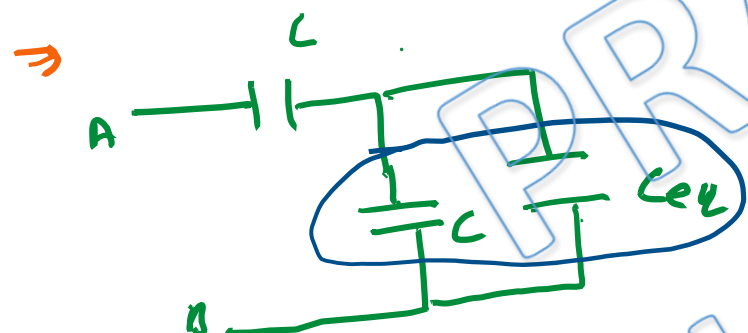

$\therefore C_{AB} = C_{eq}$
 $\Rightarrow C_{eq} = \frac{C(C + C_{eq})}{C + (C + C_{eq})}$

let $C_{eq} = x$

$x = \frac{C(C + x)}{C + C + x} = \frac{C^2 + Cx}{2C + x}$

$2Cx + x^2 = C^2 + Cx$

$x^2 + (x - C^2) = 0$

$x = \frac{-C \pm \sqrt{C^2 - 4(1)(-C^2)}}{2}$

$x = \frac{-C \pm \sqrt{5C^2}}{2} = \frac{-C \pm \sqrt{5}C}{2}$



$x = \frac{-C + \sqrt{5}C}{2}, \frac{-C - \sqrt{5}C}{2}$

$\Rightarrow x = \frac{\sqrt{5} - 1}{2} C$

Ans


Ans. b

Solution: 15

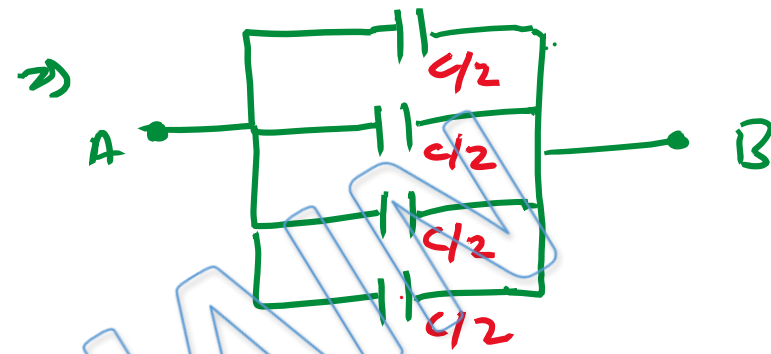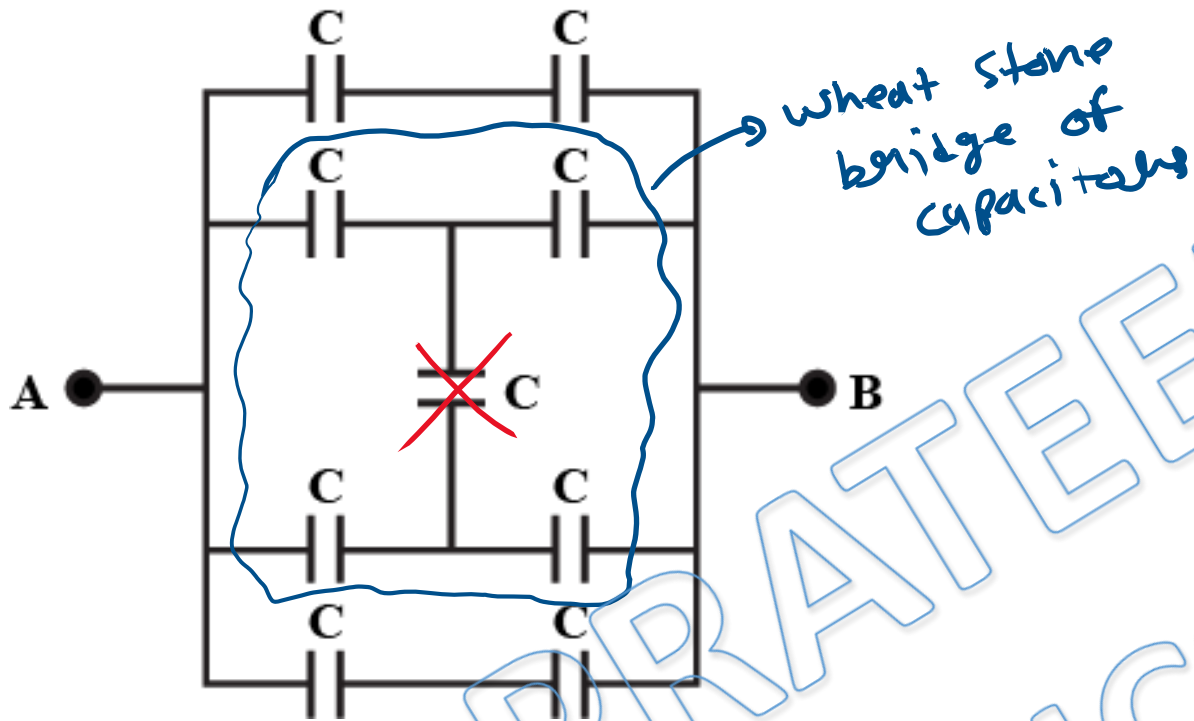


$$C_{eq} = 4 \left(\frac{C}{2} \right)$$
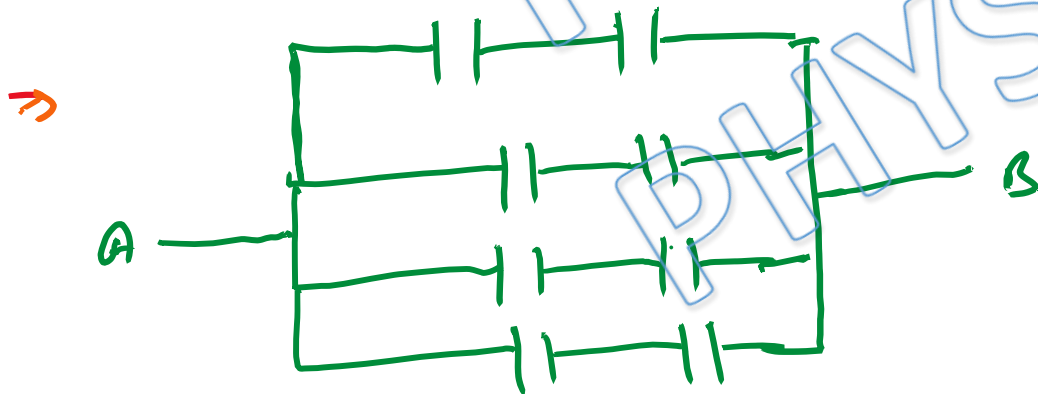
$$C_{eq} = 2C \quad \underline{\text{Ans}}$$




Ans. c

Solution: 16

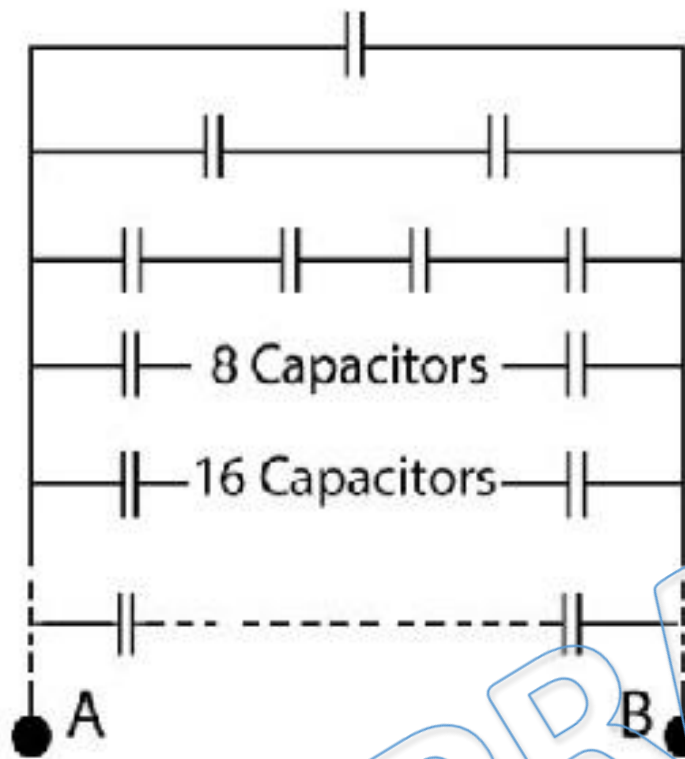

→

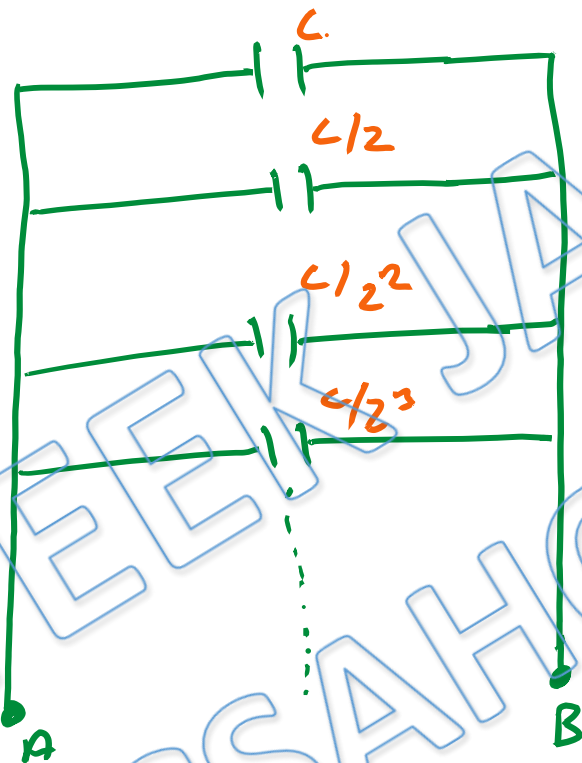

$$a=1, \quad r=\frac{1}{2}$$

$$C_{eq} = C \left[\frac{1}{1-\frac{1}{2}} \right]$$

$$C_{eq} = C \left[\frac{1}{\frac{1}{2}} \right]$$

$$C_{eq} = 2C \quad \underline{\text{Ans}}$$



$$C_{eq} = C + \frac{C}{2} + \frac{C}{2^2} + \frac{C}{2^3} + \frac{C}{2^4} + \dots \infty$$

$$S_n = \frac{a}{1-r} \quad [\text{sum of } \infty \text{ G.P., where } r < 1]$$

$$\text{So, } C_{eq} = C \left[1 + \frac{1}{2} + \frac{1}{2^2} + \frac{1}{2^3} + \frac{1}{2^4} + \dots \right]$$


Ans. b

Solution: 17

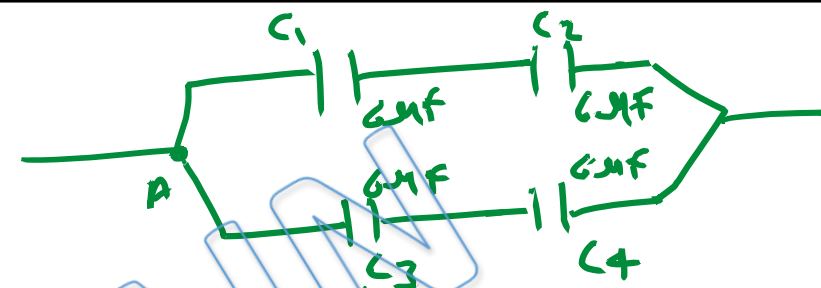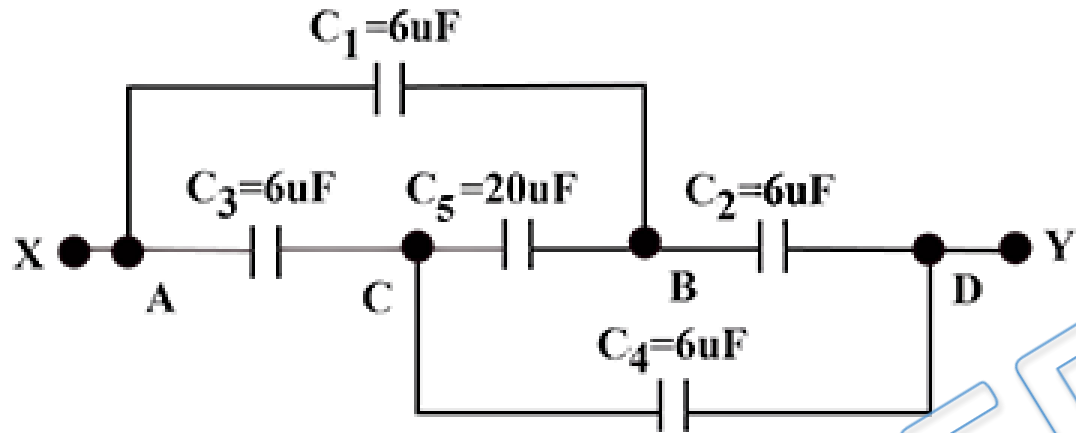

here $C_1 = C_2 = C_3 = C_4 = C = 6\mu\text{F}$
 so, $C_{eq} = C$


$C_{eq} = 6\mu\text{F}$

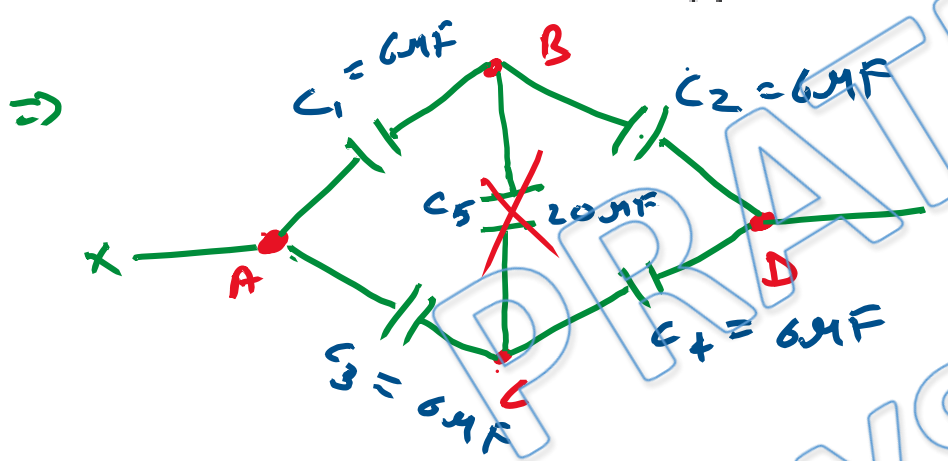


\therefore here; $C_1 C_4 = C_3 C_2$
 so; wheat stone bridge is balanced.

Ans. d

Solution: 18

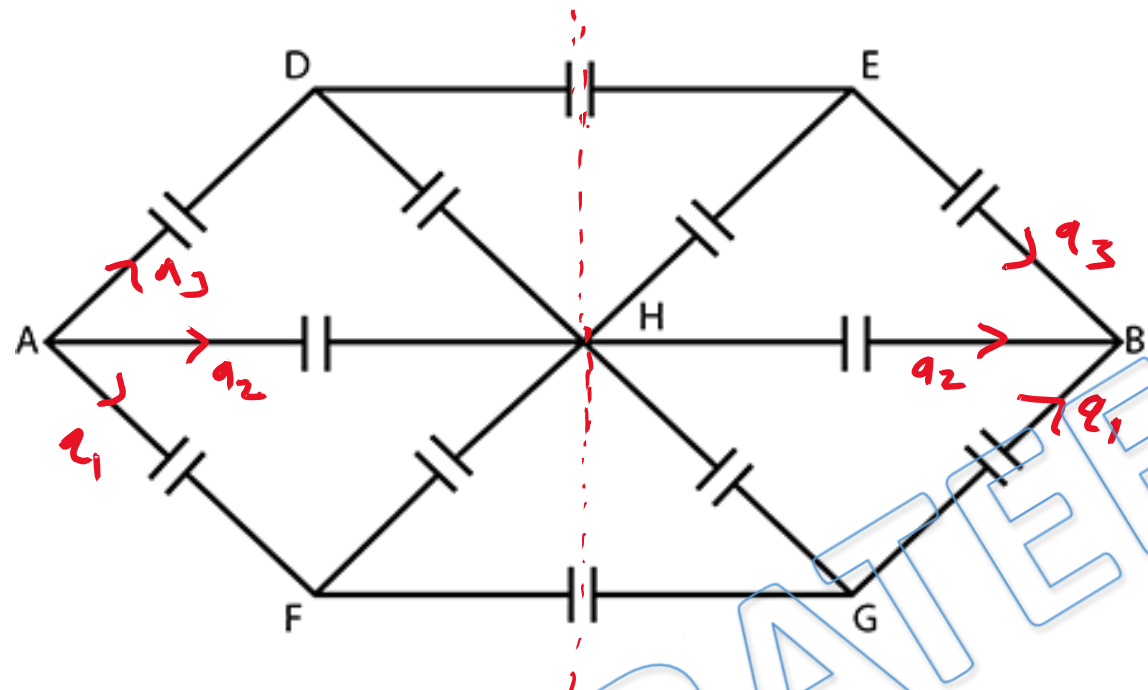

so, we can break the joint at 'H'

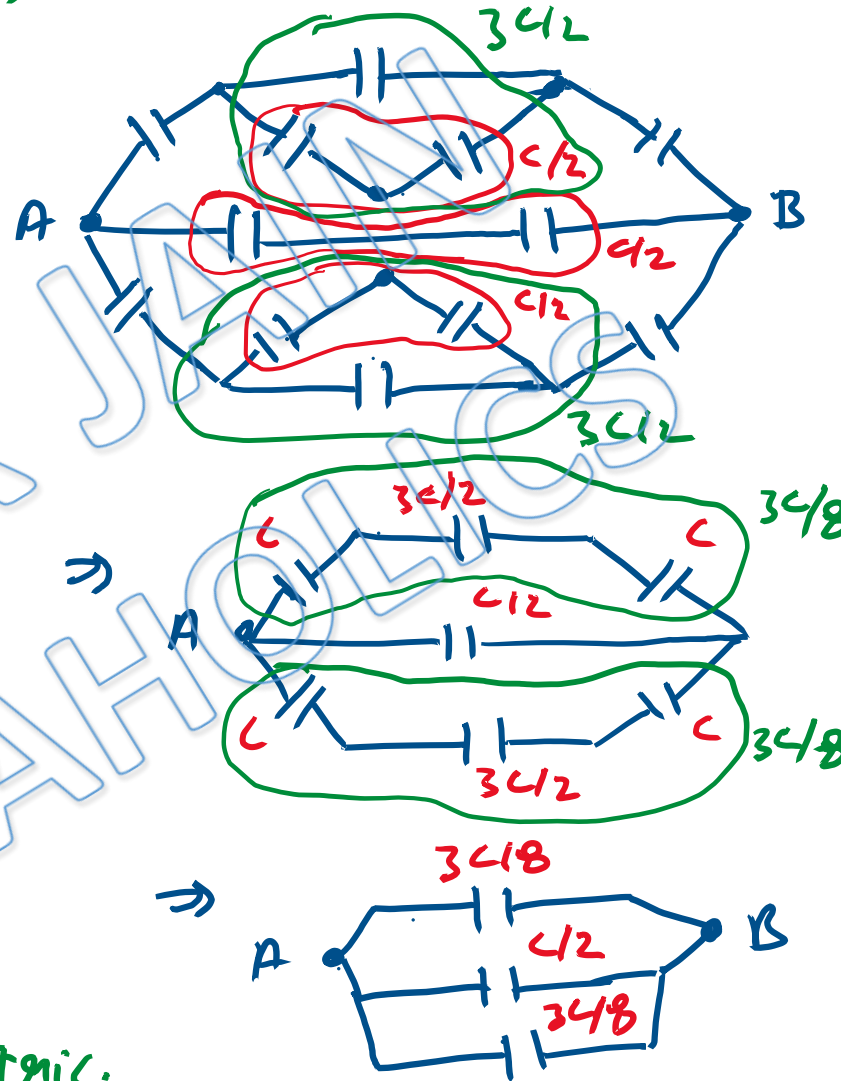

∴ circuit is symmetric

Let q_1, q_2, q_3 charges enters at 'A'
 then q_1, q_2 & q_3 charges will be ejected
 from circuit at 'B' & circuit is symmetric.
 → so, here charge is flowing forward
 only.

$$C_{eq} = \frac{5C}{4}$$

Ans →

Ans. a

For Video Solution of this DPP, Click on below link

Video Solution
on Website:-

<https://physicsaholics.com/home/courseDetails/65>

Video Solution
on YouTube:-

<https://youtu.be/pGZdLYUMDIg>

Written Solution
on Website:-

<https://physicsaholics.com/note/notesDetails/62>

 **SUBSCRIBE**



[@Physicsaholics](#)

[@Physicsaholics_prateek](#)

[@NEET_Physics](#)

[@IITJEE_Physics](#)

[physicsaholics.com](#)



CLICK

Chalo Niklo