



## DPP – 3 (Alternating Current)

Video Solution on Website :-

<https://physicsaholics.com/home/courseDetails/102>

Video Solution on YouTube:-

<https://youtu.be/bzdzlVidAuM>

Written Solution on Website:-

<https://physicsaholics.com/note/notesDetails/60>

- Q 1. Which of these is not correct regarding eddy currents?  
(a) Eddy currents result due to motion of a metallic plate in magnetic field  
(b) Eddy currents are minimised in transformer by using laminated core with metal laminations separated by some insulating material  
(c) In induction furnace, eddy currents in metal to be melted raise temperature of the metal, melting it  
(d) Eddy currents are named so, as they propagate similar to swirling eddies in water
- Q 2. The windings of a transformer have an inductance  $L_1 = 6 \text{ H}$ ,  $L_2 = 0.06 \text{ H}$  and a coefficient of coupling  $K = 0.9$ . Find the emf induced in both windings when the primary current increases at the rate of  $1000 \text{ A/s}$ . ( $L_1$  is inductance of primary winding)  
(a) 270 V  
(b) 540 V  
(c) 135 V  
(d) 220 V
- Q 3. A 220 volt input is supplied to a transformer. The output circuit draws a current of 2.0 ampere at 440 volts. If the efficiency of the transformer is 80%, the current drawn by the primary windings of the transformer is –  
(a) 3.6 ampere                      (b) 2.8 ampere  
(c) 2.5 ampere                      (d) 5.0 ampere
- Q 4. The primary of a 1 : 3 step - up transformer is connected to a source and the secondary is connected to a resistor R. The power dissipated by R in this situation is P. If R is connected directly to the source it will dissipate a power of :  
(a)  $P/9$                       (b)  $P/3$                       (c) P                      (d) 3P
- Q 5. An ideal efficient transformer has a primary power input of 10kW. The secondary current when the transformer is on load is 25A. If the primary : secondary turns ratio is 8 : 1, then the potential difference applied to the primary coil is  
(a)  $\frac{10^4 \times 8^2}{25} \text{ V}$                       (b)  $\frac{10^4 \times 8}{25} \text{ V}$                       (c)  $\frac{10^4}{25 \times 8} \text{ V}$                       (d)  $\frac{10^4}{25 \times 8^2} \text{ V}$
- Q 6. A transformer is used to light a 140 watt, 24 volt lamp from 240 V AC mains. The current in the main cable is 0.7 amp. The efficiency of the transformer is :  
(a) 48%                      (b) 63.8%                      (c) 83.3%                      (d) 90%
- Q 7. A step down transformer reduces 220 V to 110 V. The primary draws 5 ampere of current and secondary supplies 9 ampere. The efficiency of transformer is –



- (a) 20%                      (b) 44%                      (c) 90%                      (d) 100%

- Q 8. In a transformer  $N_p = 500$ ,  $N_s = 5000$ . Input voltage is 20V and frequency is 50Hz. What are the output voltage and frequency –
- (a) 200 V, 40 Hz                      (b) 100 V, 50 Hz  
(c) 200 V, 50 Hz                      (d) 150 V, 40 Hz
- Q 9. A step up transformer is used on 120 V line to provide a P.D. of 2400 V. If the number of turns in primary is 75, then the number of turns in the secondary shall be
- (a) 25                      (b) 150                      (c) 1500                      (d) 500
- Q 10. In a step down transformer having primary to secondary turn ratio 20 : 1, the input voltage applied is 250 volts and output current is 8 amp. Assuming 100% efficiency, calculate the power input
- (a) 10 W  
(b) 20 W  
(c) 50 W  
(d) 100 W

PRATEEK JAIN  
PHYSICSAHOLICS



## Answer Key

Q.1 a	Q.2 b	Q.3 d	Q.4 a	Q.5 b
Q.6 c	Q.7 c	Q.8 c	Q.9 c	Q.10 d

PRATEEK JAIN  
PHYSICSAHOLICS

PLUS

ICONIC \*\*

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

24 months ₹2,333/mo >  
No cost EMI ₹56,000

18 months ₹2,625/mo >  
No cost EMI ₹47,250

12 months ₹3,208/mo >  
No cost EMI ₹38,500

6 months ₹4,667/mo >  
No cost EMI ₹28,000

To be paid as a one-time payment

View all plans



Add a referral code

APPLY

# PHYSICSLIVE

PLUS

ICONIC \*\*

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

24 months ₹2,100/mo >  
No cost EMI +10% OFF ₹50,400

18 months ₹2,363/mo >  
No cost EMI +10% OFF ₹42,525

12 months ₹2,888/mo >  
No cost EMI +10% OFF ₹34,650

6 months ₹4,200/mo >  
No cost EMI +10% OFF ₹25,200

To be paid as a one-time payment

View all plans



Awesome! PHYSICSLIVE code applied





Use code **PHYSICSLIVE** to get 10% OFF on Unacademy PLUS.

# Written Solution

**DPP- 3 Alternating Current : Transformer**

**By Physicsaholics Team**

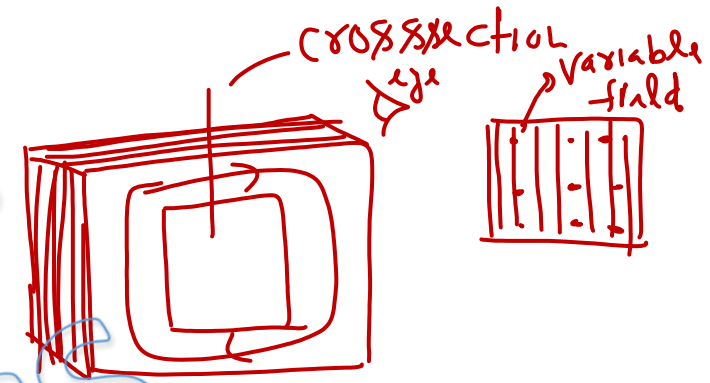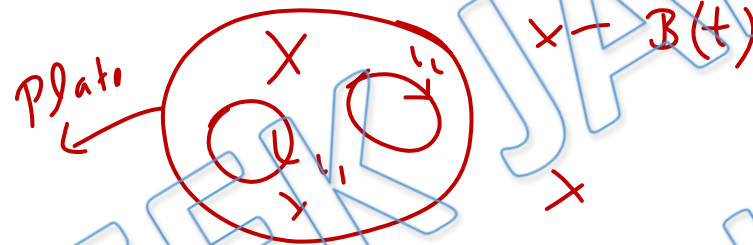Q.1) Which of these is not correct regarding eddy currents?



- (a) Eddy currents result due to motion of a metallic plate in magnetic field
- (b) Eddy currents are minimised in transformer by using laminated core with metal laminations separated by some insulating material
- (c) In induction furnace, eddy currents in metal to be melted raise temperature of the metal, melting it
- (d) Eddy currents are named so, as they propagate similar to swirling eddies in water

Q.2) The windings of a transformer have an inductance  $L_1 = 6 \text{ H}$ ,  $L_2 = 0.06 \text{ H}$  and a coefficient of coupling  $K = 0.9$ . Find the emf induced in both windings when the primary current increases at the rate of  $1000 \text{ A/s}$ . ( $L_1$  is inductance of primary winding)

$$M = K \sqrt{L_1 L_2}$$
$$= 0.9 \sqrt{6 \times 0.06} = 0.54$$

(a) 270 V

(b) 540 V ✓

(c) 135 V

(d) 220 V

$$\mathcal{E} = M \frac{di}{dt}$$
$$= 0.54 \times 1000$$
$$= 540 \text{ V}$$

Q.3) A 220 volt input is supplied to a transformer. The output circuit draws a current of 2.0 ampere at 440 volts. If the efficiency of the transformer is 80%, the current drawn by the primary windings of the transformer is –

$$\eta = \frac{V_o I_o}{V_{in} I_{in}} \times 100$$

$$80 = \frac{440}{220} \times \frac{2}{I_{in}} \times 100$$

$$I_{in} = \frac{4 \times 10}{8} = 5 \text{ A}$$

- (a) 3.6 ampere      (b) 2.8 ampere  
(c) 2.5 ampere      (d) 5.0 ampere



$\rightarrow V_{in}$

Q.4) The primary of a 1 : 3 step - up transformer is connected to a source and the secondary is connected to a resistor R. The power dissipated by R in this situation is P. If R is connected directly to the source it will dissipate a power of :

$$P = \frac{V_0^2}{R} = \frac{9V_{in}^2}{R}$$

(a) P/9

(b) P/3

(c) P

(d) 3P

If source is connected directly to R

$$P' = \frac{V_{in}^2}{R} = \frac{P}{9}$$

$$P_{in} = P_{out}$$

Q.5) An ideal efficient transformer has a primary power input of 10kW. The secondary current when the transformer is on load is 25A. If the primary : secondary turns ratio is 8 : 1, then the potential difference applied to the primary coil is

$$P_o = 10000 \text{ W}, I_o = 25 \text{ A}$$

$$\Rightarrow V_o = \frac{P_o}{I_o} = \frac{10000}{25} = 400 \text{ V}$$

$$\frac{V_{in}}{V_o} = \frac{N_1}{N_2} \Rightarrow \frac{V_{in}}{400} = \frac{8}{1} \Rightarrow V_{in} = 3200$$

(a)  $\frac{10^4 \times 8^2}{25} \text{ V}$

(b)  $\frac{10^4 \times 8}{25} \text{ V}$

(c)  $\frac{10^4}{25 \times 8} \text{ V}$

(d)  $\frac{10^4}{25 \times 8^2} \text{ V}$

Q.6) A transformer is used to light a 140 watt, 24 volt lamp from 240 V AC mains. The current in the main cable is 0.7 amp. The efficiency of the transformer is :

$$\eta = \frac{V_o I_o}{V_{in} I_{in}} \times 100$$
$$= \frac{24 \times 140}{240 \times 0.7} \times 100 = \frac{500}{6} = 83.3\%$$

(a) 48%

(b) 63.8%

(c) 83.3%

(d) 90%

Q.7) A step down transformer reduces 220 V to 110 V. The primary draws 5 ampere of current and secondary supplies 9 ampere. The efficiency of transformer is -

$$\eta = \frac{V_s I_s}{V_p I_p} \times 100$$
$$= \frac{110 \times 9}{220 \times 5} \times 100 = 90\%$$

(a) 20%

(b) 44%

(c) 90%

(d) 100%

Q.8) In a transformer  $N_p = 500$ ,  $N_s = 5000$ . Input voltage is 20V and frequency is 50Hz. What are the output voltage and frequency -

$$\text{Output freq} = \text{input freq} = 50\text{Hz}$$

$$\frac{V_o}{V_i} = \frac{N_s}{N_p}$$

$$\frac{V_o}{20} = \frac{5000}{500}$$

$$V_o = 200\text{V}$$

(a) 200 V, 40 Hz

(c) 200 V, 50 Hz

(b) 100 V, 50 Hz

(d) 150 V, 40 Hz

Q.9) A step up transformer is used on 120 V line to provide a P.D. of 2400 V. If the number of turns in primary is 75, then the number of turns in the secondary shall be -

$$\frac{V_o}{V_{in}} = \frac{N_2}{N_1}$$

$$\frac{\overset{2400}{\cancel{2400}}}{\overset{120}{\cancel{120}}} = \frac{N_2}{75}$$

$$N_2 = \underline{1500}$$

(a) 25

(b) 150

(c) 1500

(d) 500

Q.10) In a step down transformer having primary to secondary turn ratio 20 : 1, the input voltage applied is 250 volts and output current is 8 amp. Assuming 100% efficiency, calculate the power input

$$\frac{V_{in}}{V_o} = \frac{N_1}{N_2}$$

$$\text{Power input} = \text{Power output}$$

(a) 10 W

(b) 20 W

(c) 50 W

(d) 100 W

$$= V_o I_o$$

$$= \left(\frac{N_2}{N_1}\right) \times V_{in} \times I_o$$

$$= \frac{1}{20} \times 250 \times 8$$

$$= 100 \text{ W}$$

**For Video Solution of this DPP, Click on below link**

Video Solution  
on Website:-

<https://physicsaholics.com/home/courseDetails/102>

Video Solution  
on YouTube:-

<https://youtu.be/bzdzIVidAuM>

Written Solution  
on Website:-

<https://physicsaholics.com/note/notesDetails/60>



 SUBSCRIBE



[@Physicsaholics](#)

[@Physicsaholics\\_prateek](#)

[@NEET\\_Physics](#)

[@IITJEE-Physics](#)

[physicsaholics.com](#)

[Unacademy](#)



**CLICK**

Chalo Niklo