


## DPP – 3 (Capacitor)

Video Solution on Website :- <https://physicsaholics.com/home/courseDetails/103>

Video Solution on YouTube:- [https://youtu.be/jrt2B\\_rC\\_fA](https://youtu.be/jrt2B_rC_fA)


Written Solution on Website:- <https://physicsaholics.com/note/notesDetalis/63>

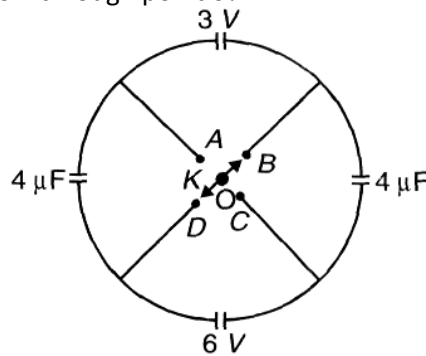- Q 1. In figure, there is a four way key at the middle. If key is thrown from situation BD to AD, then how much charge will flow through point O?




- (a)  $24 \mu\text{C}$   
 (b)  $36 \mu\text{C}$   
 (c)  $72 \mu\text{C}$   
 (d)  $12 \mu\text{C}$

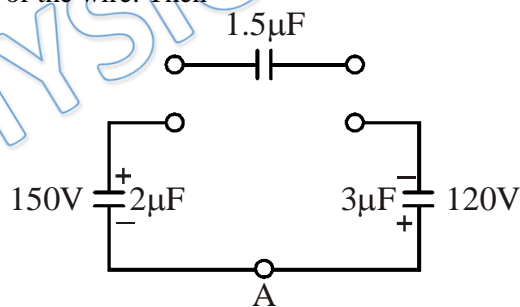- Q 2. Two capacitors of  $2 \mu\text{F}$  and  $3 \mu\text{F}$  are charged to 150 volt and 120 volt respectively. The plates of capacitor are connected as shown in the figure. A discharged capacitor of capacity  $1.5 \mu\text{F}$  falls to the free ends of the wire. Then




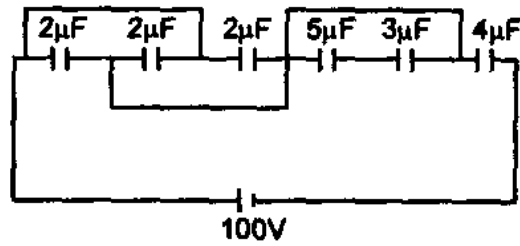- (a) charge on the  $1.5 \mu\text{F}$  capacitor is  $180 \mu\text{C}$   
 (b) charge on the  $2 \mu\text{F}$  capacitor is  $120 \mu\text{C}$   
 (c) positive charge flows through A from right to left.  
 (d) positive charge flows through A from left to right.
- Q 3. In the circuit shown in figure charge stored in the capacitor of capacity  $5 \mu\text{F}$  is:




- (a)  $60 \mu\text{C}$       (b)  $20 \mu\text{C}$       (c)  $30 \mu\text{C}$       (d) zero

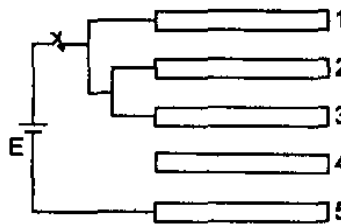- Q 4. Five conducting plates are placed parallel to each other. Separation between them is  $d$  and area of each plate is  $A$ . Plate number 1, 2 and 3 are connected with each other and at the same time through a cell of emf  $E$ . The charge on plate number 1 is:



- (a)  $\frac{E\epsilon_0 A}{d}$       (b)  $\frac{E\epsilon_0 A}{2d}$   
 (c)  $\frac{2E\epsilon_0 A}{d}$       (d) zero

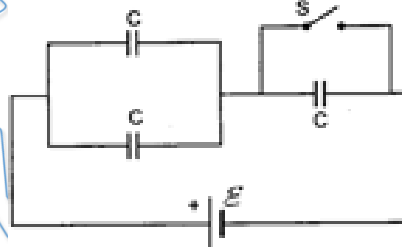
- Q 5. In the circuit shown, each capacitor has a capacitance  $C$ . The emf of the cell is  $\xi$ . If the switch  $S$  is closed,



- (a) some charge will flow out of the positive terminal of the cell  
 (b) some charge will enter the positive terminal of the cell  
 (c) the amount of charge flowing through the cell will be  $C\xi$ .  
 (d) the amount of charge flowing through the cell will be  $\frac{4}{3}C\xi$ .
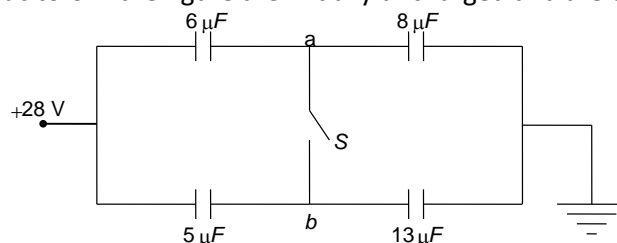
### COMPREHENSION (Q.6 TO Q.9)

The capacitors in the figure are initially uncharged and are connected as



- Q 6. What is the potential difference  $V_{ab}$ ?

- (a) 4.2 V (b) 5.2 V  
(c) 6.2 V (d) 7.2 V

Q 7. Now the key  $S$  is closed. What is the potential of point  $a$ ?

- (a) 9.2 V (b) 9.4 V  
(c) 9.6 V (d) 7.8 V


Q 8. How much charge flowed through the switch when it was closed?

- (a)  $3.36 \mu\text{C}$  (b)  $33.6 \mu\text{C}$   
(c)  $336 \mu\text{C}$  (d)  $0.336 \mu\text{C}$

Q 9. The charge on capacitor  $5 \mu\text{F}$  is

- (a)  $96 \mu\text{C}$  (b)  $98 \mu\text{C}$   
(c)  $94 \mu\text{C}$  (d)  $92 \mu\text{C}$

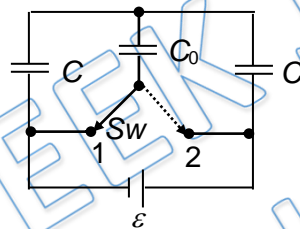
Q 10. What amount of charge (in coulomb) will be supplied by cell shown in figure after the switch  $S_w$  is shifted from position 1 to position 2? Given  $C = 1\text{F}$ ,  $C_0 = 4\text{F}$  and  $\varepsilon = 12\text{V}$



Q 11. A capacitor of capacitance  $C_0$  is charged to a potential  $V_0$  and then isolated. A small uncharged capacitor  $C$  is then charged from  $C_0$ , discharged and charged again; the process being repeated  $n$  times. Due to this, potential of the larger capacitor is decreased to  $V$ . Value of  $C$  is -

- (a)  $C_0(V_0/V)^{1/n}$  (b)  $C_0((V_0/V)^{1/n} - 1)$  (c)  $C_0((V_0/V) - 1)^n$  (d)  $C_0[(\frac{V}{V_0})^n + 1]$

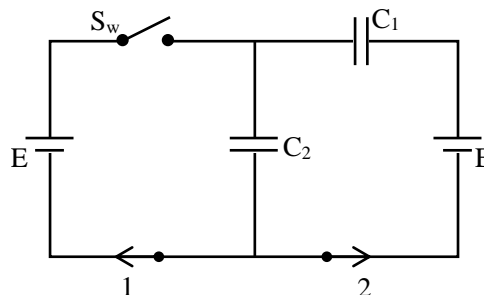Q 12. What charges will flow after the shorting of the switch  $S_w$  in the circuit illustrated in Fig. through section 1 and 2 in the directions indicated by the arrows? Given  $C_1 = C_2 = 2 \mu\text{F}$  and  $E = 1 \text{V}$ .



- (a)  $2\mu\text{C}$ ,  $1\mu\text{C}$   
(b)  $2\mu\text{C}$ ,  $2\mu\text{C}$   
(c)  $-2\mu\text{C}$ ,  $2\mu\text{C}$



(d)  $2\mu\text{C}$ ,  $-1\mu\text{C}$

## Answer Key

Q.1 c	Q.2 a, b, c	Q.3 d	Q.4 d	Q.5 a, d
Q.6 a	Q.7 c	Q.8 b	Q.9 d	Q.10 8
Q.11 b	Q.12 d			

PRATEEK JAIN  
PHYSICSAHOLICS

PLUS **ICONIC\*\***

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

24 months ₹2,333/mo >  
No cost EMI ₹56,000

18 months ₹2,625/mo >  
No cost EMI ₹47,250

12 months ₹3,208/mo >  
No cost EMI ₹38,500

6 months ₹4,667/mo >  
No cost EMI ₹28,000

To be paid as a one-time payment

[View all plans](#)



Add a referral code

APPLY

# PHYSICSLIVE

Use code **PHYSICSLIVE** to get 10% OFF on Unacademy PLUS.

PLUS **ICONIC\*\***

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

24 months ₹2,100/mo >  
No cost EMI **+10% OFF** ₹50,400

18 months ₹2,363/mo >  
No cost EMI **+10% OFF** ₹42,525

12 months ₹2,888/mo >  
No cost EMI **+10% OFF** ₹34,650

6 months ₹4,200/mo >  
No cost EMI **+10% OFF** ₹25,200

To be paid as a one-time payment

[View all plans](#)



Awesome! **PHYSICSLIVE** code applied




# **Written Solution**

**DPP-3 Capacitor- Kirchoff's 1st & 2nd Law**

**By Physicsaholics Team**

(Q.1) In figure, there is a four way key at the middle. If key is thrown from situation BD to AD, then how much charge will flow through point 0?

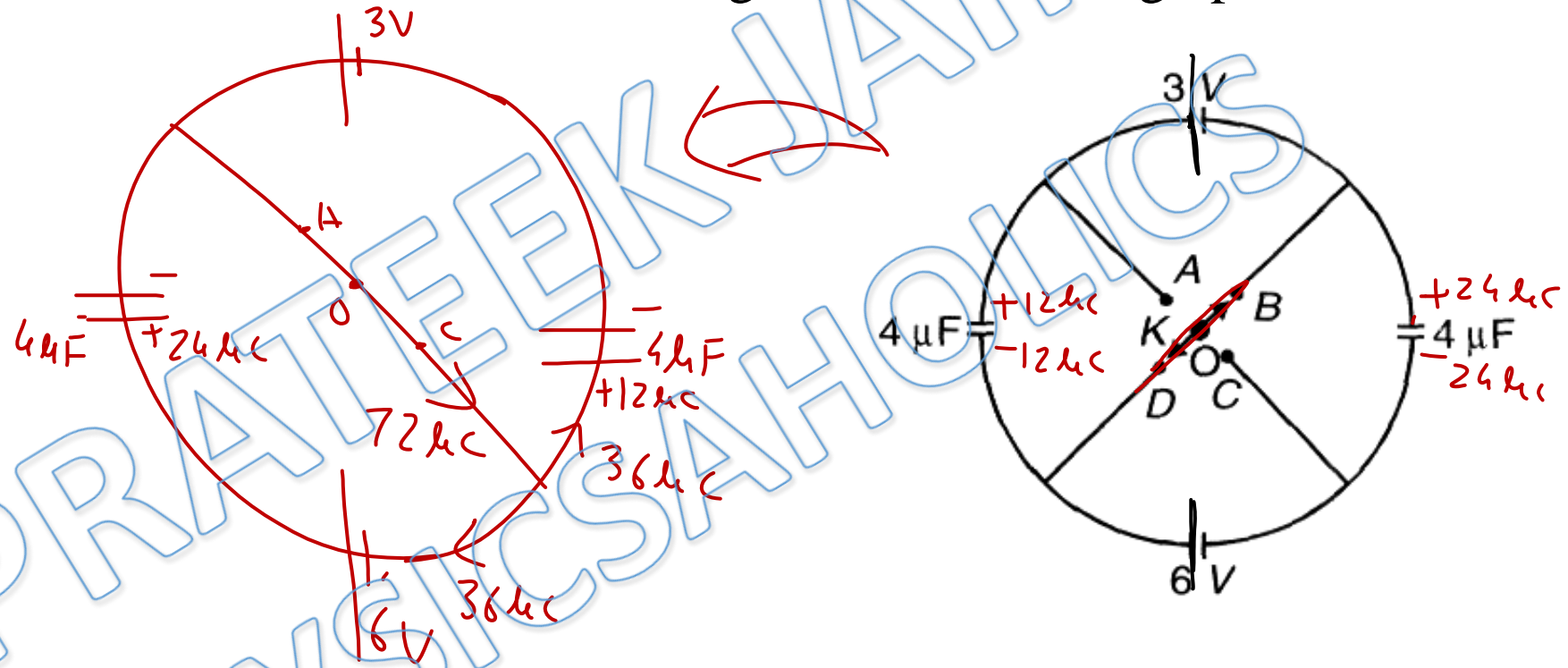- (a)  $24 \mu\text{C}$
- (b)  $36 \mu\text{C}$
- ~~(c)  $72 \mu\text{C}$~~
- (d)  $12 \mu\text{C}$




(Q.2) Two capacitors of  $2\ \mu\text{F}$  and  $3\ \mu\text{F}$  are charged to 150 volt and 120 volt respectively. The plates of capacitor are connected as shown in the figure. A discharged capacitor of capacity  $1.5\ \mu\text{F}$  falls to the free ends of the wire. Then

$$\Delta V = (+150 + 0 + 120) - \frac{q}{2\ \mu} - \frac{q}{1.5\ \mu} - \frac{q}{3\ \mu} = 0$$


$$270 = \frac{q}{\mu} \left( \frac{1}{2} + \frac{2}{3} + \frac{1}{3} \right) = \frac{q}{\mu} \left( \frac{3+4+2}{6} \right)$$

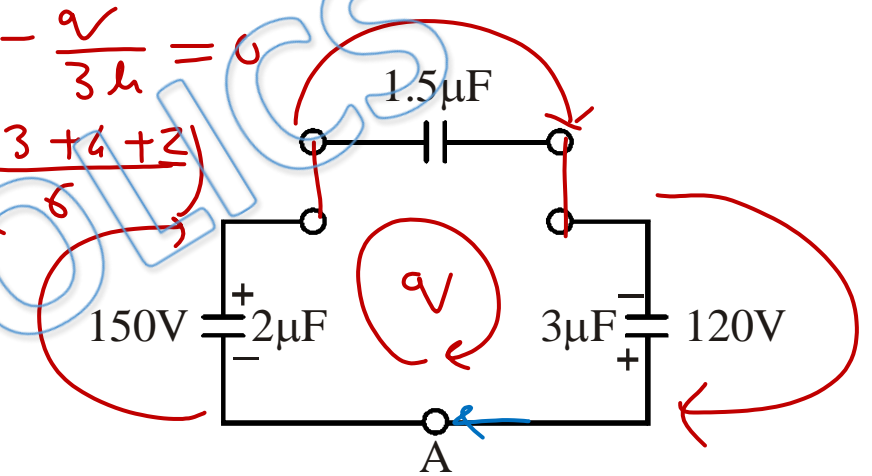- (a) charge on the  $1.5\ \mu\text{F}$  capacitor is  $180\ \mu\text{C}$
- (b) charge on the  $2\ \mu\text{F}$  capacitor is  $120\ \mu\text{C}$
- (c) positive charge flows through A from right to left.
- (d) positive charge flows through A from left to right.



$$270 = \frac{q}{6\ \mu} = \frac{3}{2\ \mu} q$$
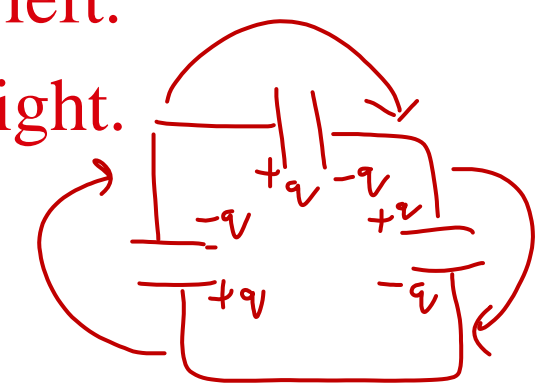
$$q = \frac{270 \times 2\ \mu}{3} = 180\ \mu\text{C} \quad \text{Charge on } 2\ \mu\text{F} = 150 \times 2\ \mu - q$$







(Q.3) In the circuit shown in figure charge stored in the capacitor of capacity 5  $\mu\text{F}$  is:

- (a)  $60 \mu\text{C}$
- (c)  $30 \mu\text{C}$

- (b)  $20 \mu\text{C}$
- (d) zero

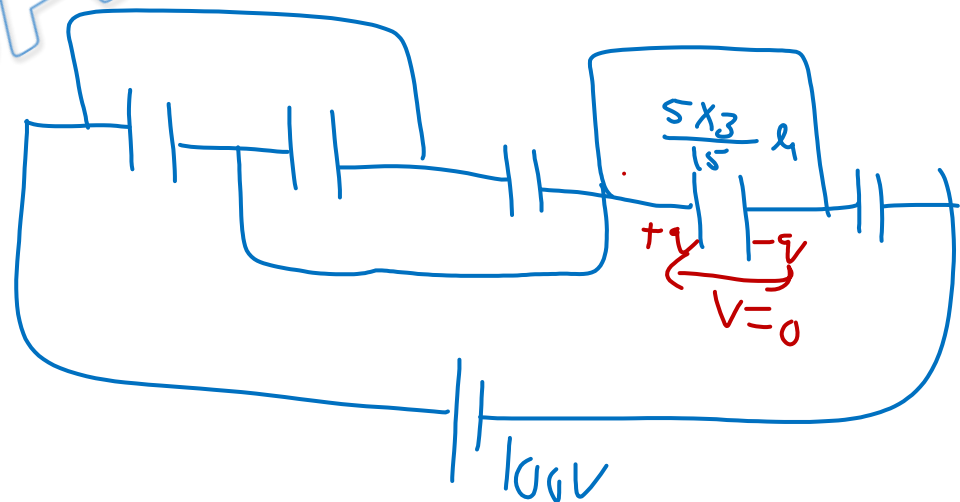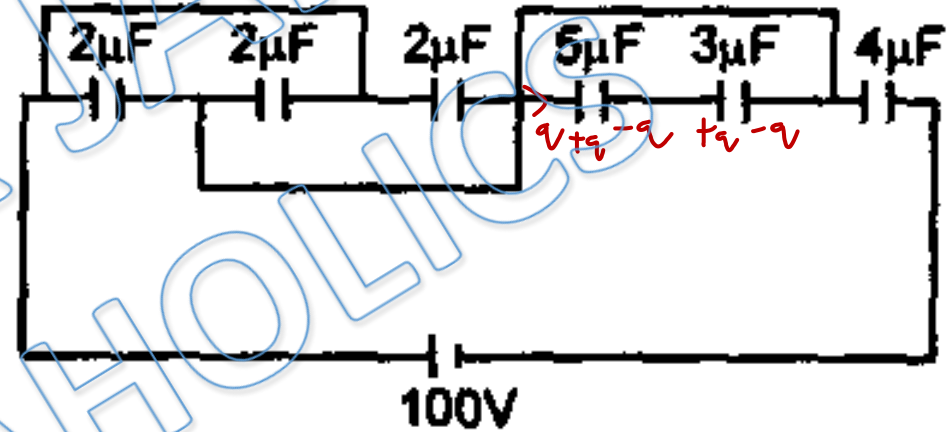


(Q.4) Five conducting plates are placed parallel to each other. Separation between them is  $d$  and area of each plate is  $A$ . Plate number 1, 2 and 3 are connected with each other and at the same time through a cell of emf  $E$ . The charge on plate number 1 is:

(a)  $\frac{E\epsilon_0 A}{d}$


(b)  $\frac{E\epsilon_0 A}{2d}$

(c)  $\frac{2E\epsilon_0 A}{d}$


~~(d) zero~~

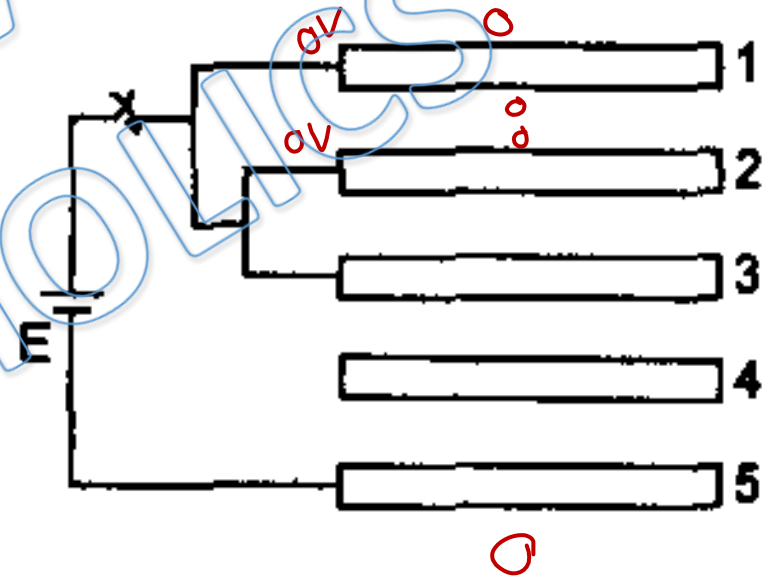

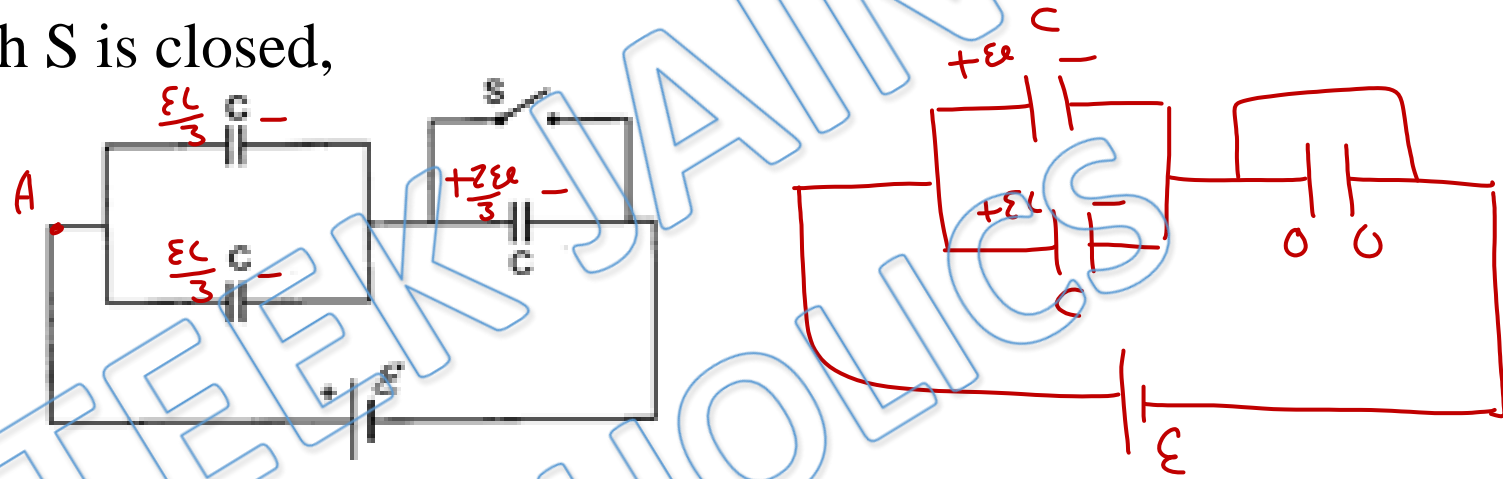(Q.5) In the circuit shown, each capacitor has a capacitance  $C$ . The emf of the cell is  $\xi$ . If the switch  $S$  is closed,



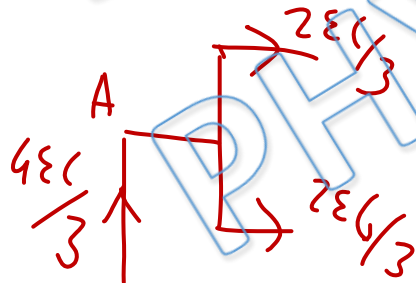
- (a) some charge will flow out of the positive terminal of the cell
- (b) some charge will enter the positive terminal of the cell
- (c) the amount of charge flowing through the cell will be  $C\xi$ .
- (d) the amount of charge flowing through the cell will be  $\frac{4}{3}C\xi$ .


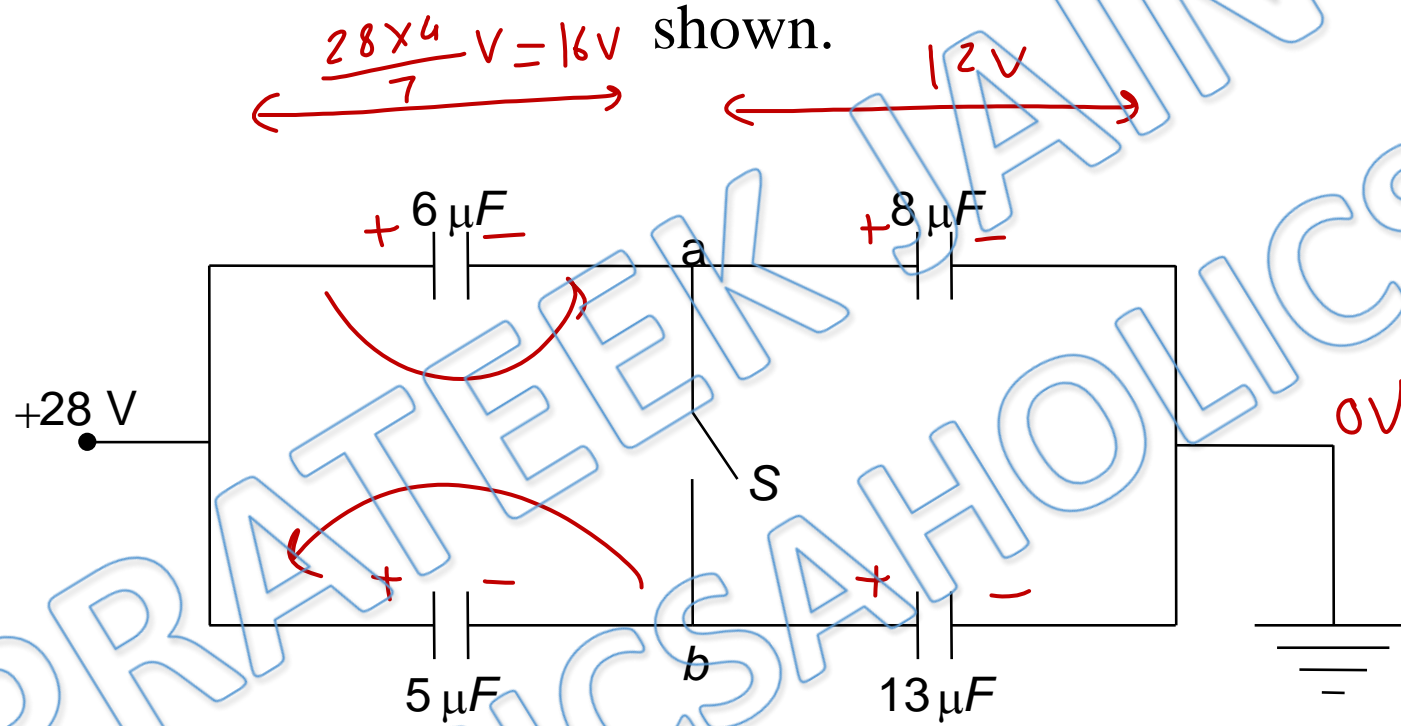
## LINKED COMPREHENSION TYPE (Q.6 TO Q.9)

The capacitors in the figure are initially uncharged and are connected as

$$\begin{aligned} & 28 - \frac{182}{9} \\ &= \frac{252 - 182}{9} \\ &= \frac{170}{9} \text{ V} \end{aligned}$$



$$\frac{13}{18} \times 28 = \frac{182}{9} \text{ V}$$

$$V_a - V_b = \frac{182}{9} - 16 = \frac{182 - 144}{9} = \frac{38}{9} = 4.2 \text{ V}$$

(Q.6) What is the potential difference  $V_{ab}$ ?

~~(a) 4.2 V~~

(c) 6.2 V

(b) 5.2 V


(d) 7.2 V

PRATEEK JAIN  
PHYSICSAHOLICS


(Q.7) Now the key  $S$  is closed. What is the potential of point  $a$ ?

- (a) 9.2 V
- (c) 9.6 V



- (b) 9.4 V
- (d) 7.8 V

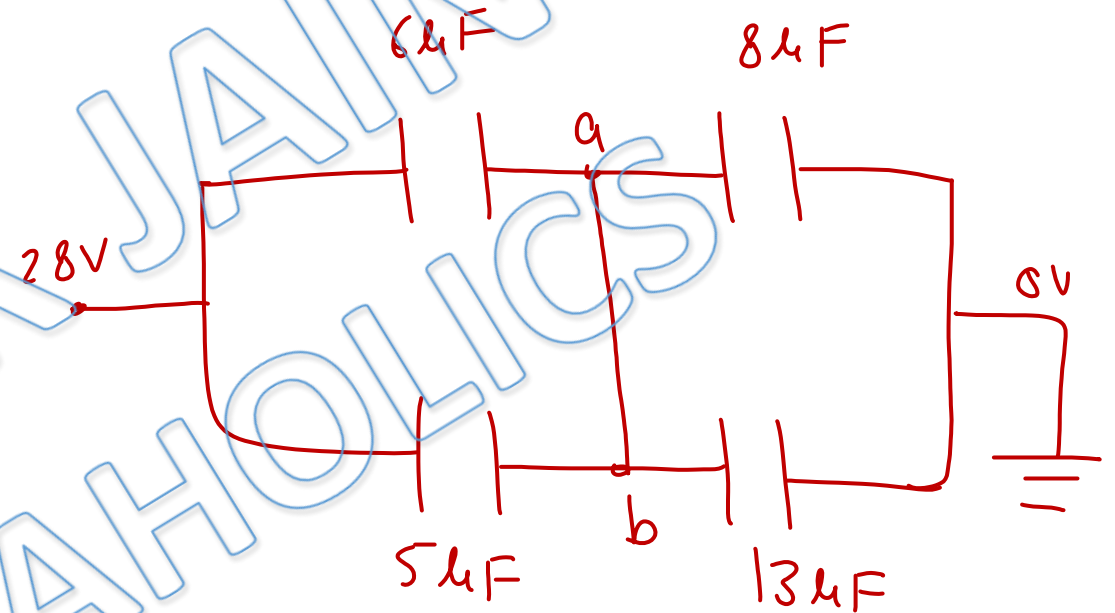

$$V_a = \frac{77}{8} = 9.6$$

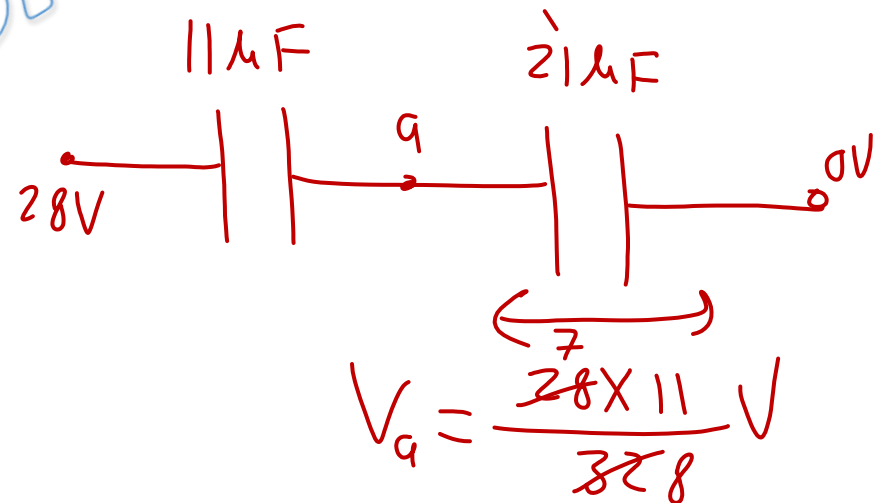

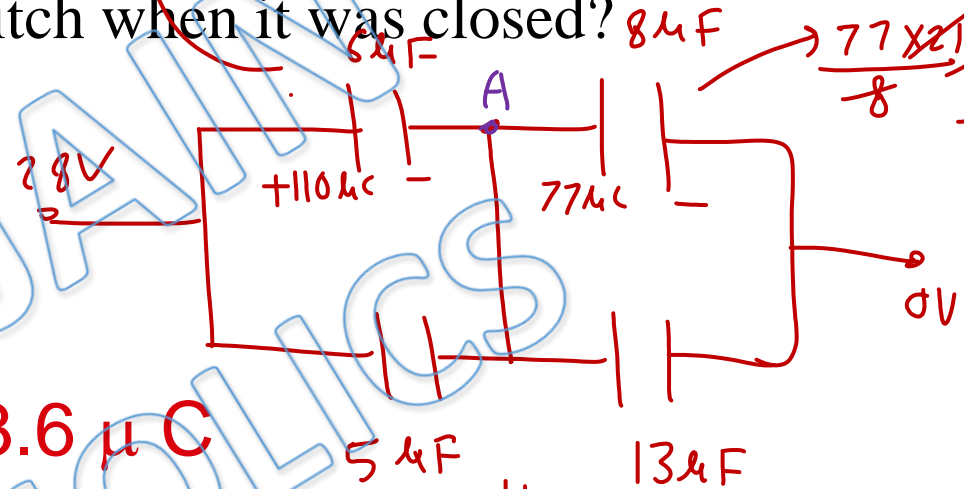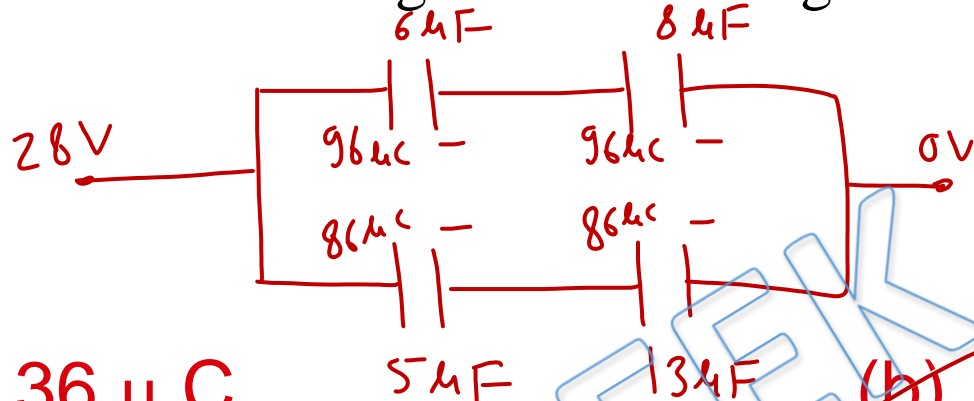(Q.8) How much charge flowed through the switch when it was closed?



(a)  $3.36 \mu C$


(b)  $33.6 \mu C$

(c)  $336 \mu C$

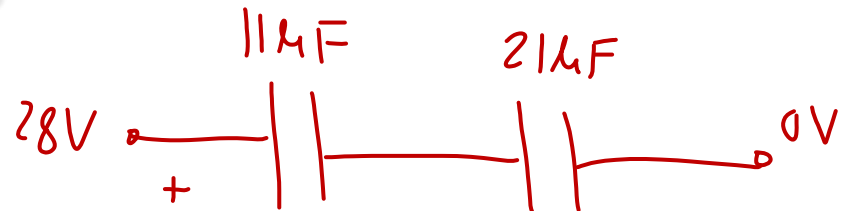(d)  $0.336 \mu C$

$$\frac{8 \times 6}{14} \times 28 = 96 \mu C$$


$$\frac{13 \times 5}{18} \times 28 = \frac{13 \times 70}{9} = \frac{780}{9} \mu C = 86 \mu C$$



$$\frac{11 \times 21}{32} \times 28 = \frac{77 \times 21}{8}$$

$$\frac{77 \times 21}{8} \times \frac{8}{21} = \frac{21 \times 21}{4} = \frac{441}{4} = 110$$
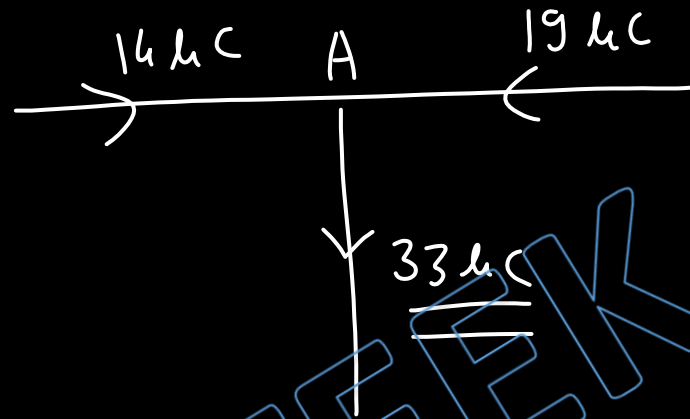
$$\frac{77 \times 21}{8} \times \frac{8}{21}$$



PRATEEK JAIN  
PHYSICSAHOLICS

Ans. b



(Q.9) The charge on capacitor  $5 \mu\text{F}$  is

$$\frac{110}{6\cancel{\mu}} = \frac{q_{s^-}}{5\cancel{\mu}}$$

(a)  $96 \mu\text{C}$

(b)  $98 \mu\text{C}$

(c)  $94 \mu\text{C}$

(d)  $92 \mu\text{C}$

$$\begin{aligned} q_{s^-} &= \frac{55^- \times 5^-}{3} \\ &= \frac{275^-}{3} \\ &= 91.6 \mu\text{C}. \end{aligned}$$




(Q.10) What amount of charge (in coulomb) will be supplied by cell shown in figure after the switch  $S_w$  is shifted from position 1 to position 2?  
 Given  $C = 1\text{F}$ ,  $C_0 = 4\text{F}$  and  $\varepsilon = 12\text{V}$

$$C_{\text{eff}} = \frac{1 \times 5}{6} \text{ F}$$

$$= \frac{5}{6} \text{ F}$$

$$q_{\text{eff}} = \frac{5}{6} \times 12$$

$$= 10 \text{ C}$$

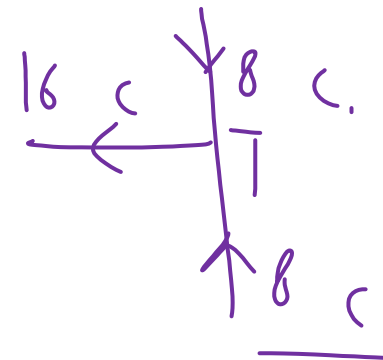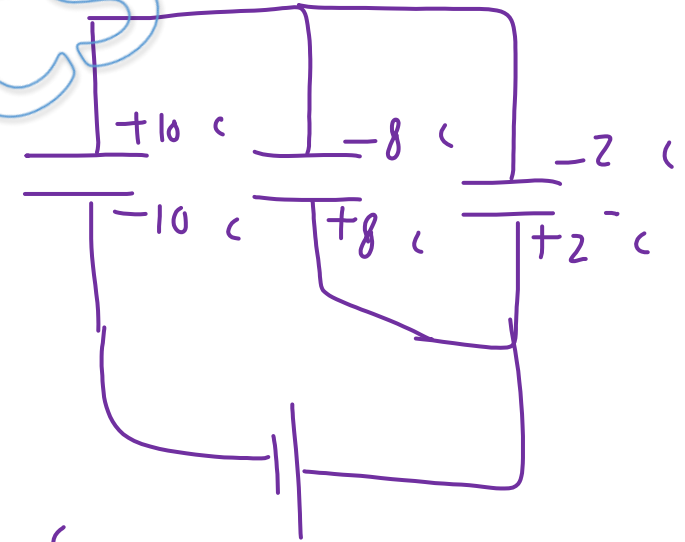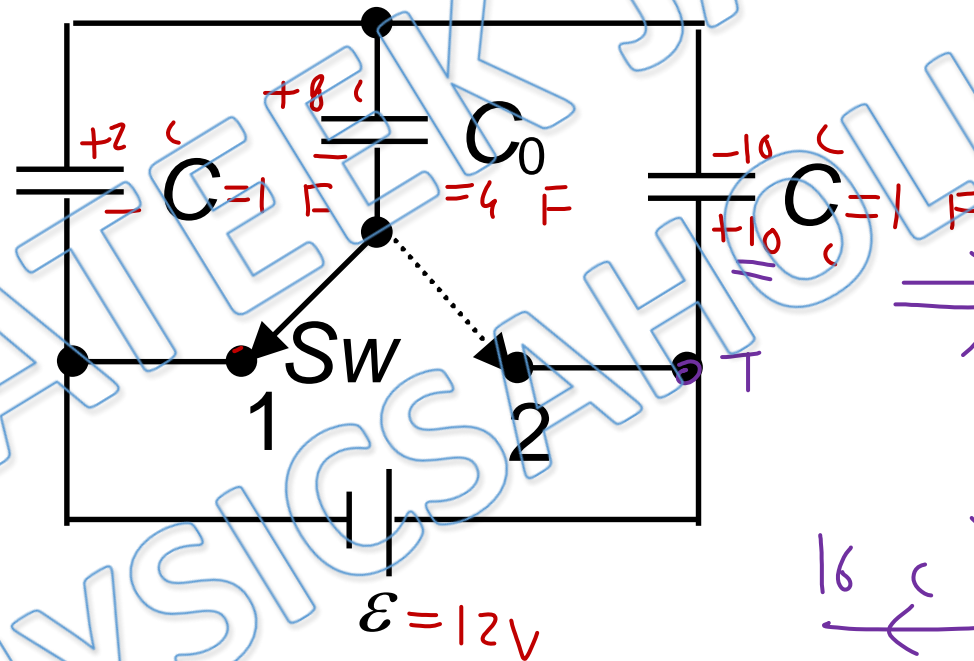

(Q.11) A capacitor of capacitance  $C_0$  is charged to a potential  $V_0$  and then isolated. A small uncharged capacitor  $C$  is then charged from  $C_0$ , discharged and charged again; the process being repeated  $n$  times. Due to this, potential of the larger capacitor is decreased to  $V$ . Value of  $C$  is -

(a)  $C_0(V_0/V)^{1/n}$

~~(b)  $C_0((V_0/V)^{1/n} - 1)$~~


(c)  $C_0((V_0/V) - 1)^n$

(d)  $C_0[(\frac{V}{V_0})^n + 1]$

by (0) charge

$$C_0 V_0 = C_0 V + C V$$
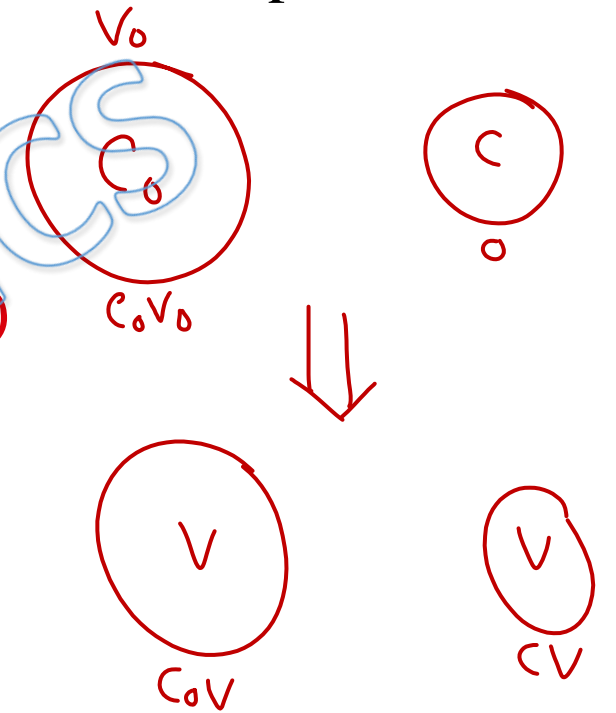
$$\Rightarrow = \frac{C_0 V_0}{C_0 + C} = \left( \frac{C_0}{C_0 + C} \right) V_0$$



After repeating process  $n$  times,

$$V = \left( \frac{C_0}{C_0 + c} \right)^n V_0$$

$$\left( \frac{C_0 + c}{C_0} \right)^n = \frac{V_0}{V}$$

$$1 + \frac{c}{C_0} = \left( \frac{V_0}{V} \right)^{\frac{1}{n}}$$


$$\frac{c}{C_0} = \left( \frac{V_0}{V} \right)^{\frac{1}{n}} - 1$$

$$c = C_0 \left[ \left( \frac{V_0}{V} \right)^{\frac{1}{n}} - 1 \right]$$

Ans. b


(Q.12) What charges will flow after the shorting of the switch  $S_w$  in the circuit illustrated in Fig. through section 1 and 2 in the directions indicated by the arrows? Given  $C_1 = C_2 = 2 \mu F$  and  $E = 1 V$ .

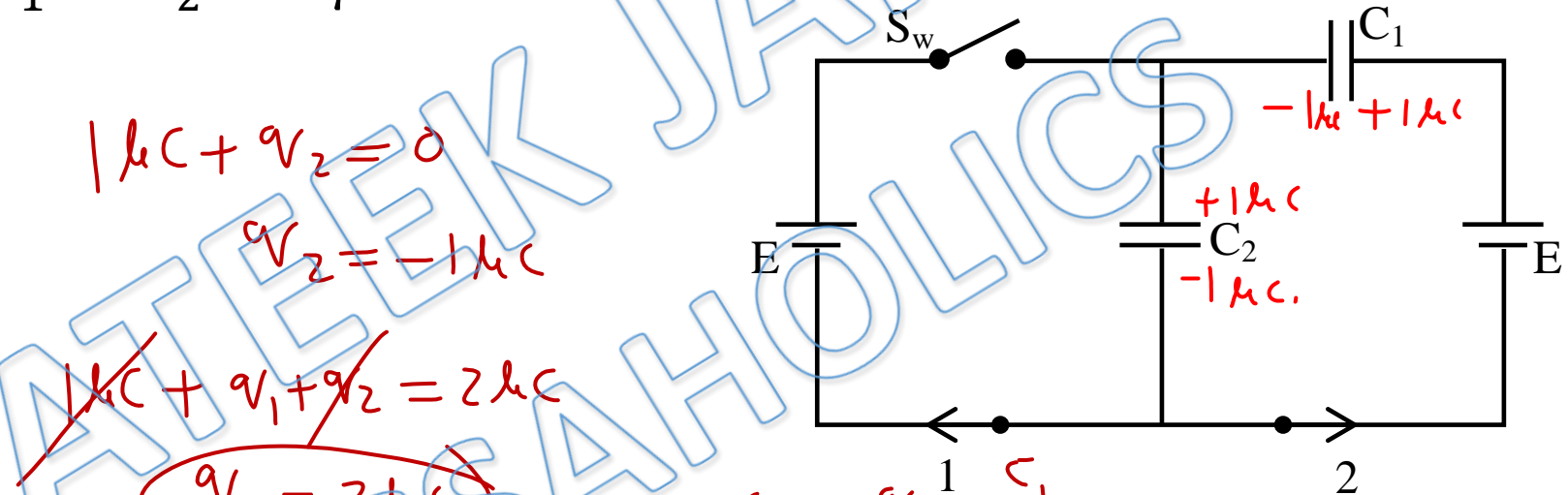- (a)  $2 \mu C, 1 \mu C$
- (b)  $2 \mu C, 2 \mu C$
- (c)  $-2 \mu C, 2 \mu C$
- (d)  $2 \mu C, -1 \mu C$



Handwritten equations in red:

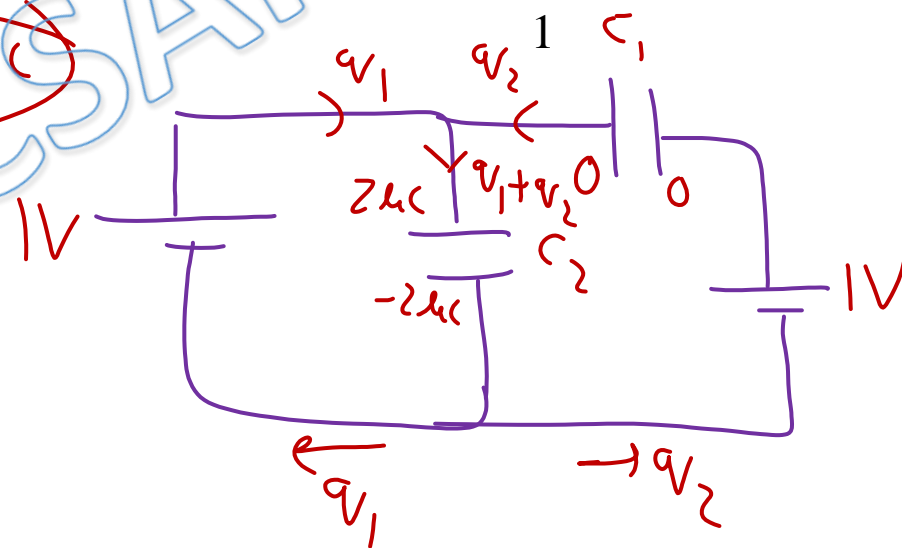- $1 \mu C + q_2 = 0$
- $q_2 = -1 \mu C$
- $1 \mu C + q_1 + q_2 = 2 \mu C$
- $q_1 = 2 \mu C$  (circled)



**For Video Solution of this DPP, Click on below link**

Video Solution  
on Website:-

<https://physicsaholics.com/home/courseDetails/103>

Video Solution  
on YouTube:-

[https://youtu.be/jrt2B\\_rC\\_fA](https://youtu.be/jrt2B_rC_fA)

Written Solution  
on Website:-

<https://physicsaholics.com/note/notesDetails/63>

 **SUBSCRIBE**



[@Physicsaholics](#)

[@Physicsaholics\\_prateek](#)

[@NEET\\_Physics](#)

[@IITJEE-Physics](#)

[physicsaholics.com](#)

[Unacademy](#)



**CLICK**

Chalo Niklo