


## DPP – 4 (Capacitor)

Video Solution on Website :- <https://physicsaholics.com/home/courseDetails/103>

Video Solution on YouTube:- <https://youtu.be/cq4Z-W7mCC8>


Written Solution on Website:- <https://physicsaholics.com/note/notesDetalis/63>

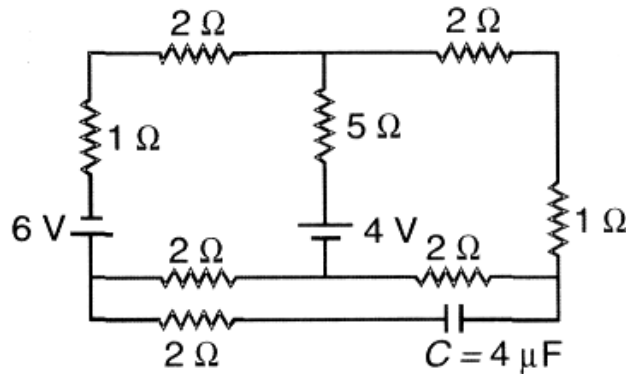Q 1. Find charge on capacitor in steady state of given circuit





- (a)  $9.6 \mu\text{C}$  (b)  $7.2 \mu\text{C}$   
 (c)  $4.8 \mu\text{C}$  (d)  $2.4 \mu\text{C}$

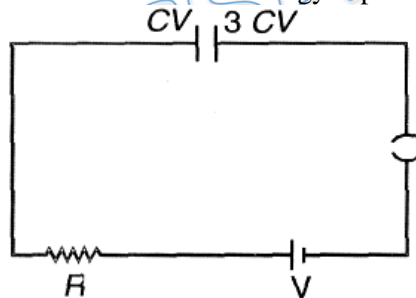Q 2. Plates of a parallel plate capacitor C have charges  $CV$  and  $3CV$  on its plate. If switch is closed at  $t = 0$ . Then initial rate at which heat energy is produced in resistance R is




- (a)  $\frac{V^2}{R}$   
 (b)  $4 \frac{V^2}{R}$   
 (c)  $9 \frac{V^2}{R}$   
 (d)  $16 \frac{V^2}{R}$

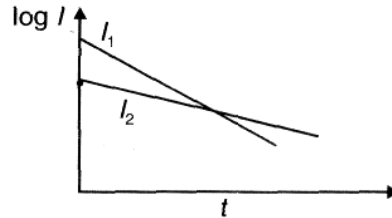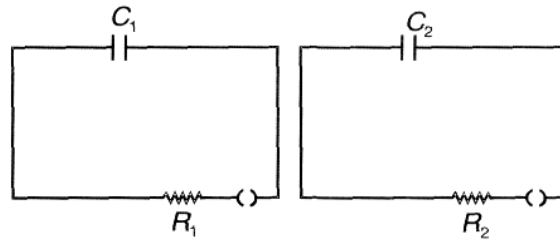Q 3. Two capacitors of capacitance  $C_1$  and  $C_2$  are charged to a potential difference  $V$  and connected in series with resistance  $R_1$  and  $R_2$  at  $t = 0$ . Both keys are closed. Graph of current  $I_1$  &  $I_2$  in two circuits are as shown here. Which of the following must be incorrect?




- (a)  $R_1 > R_2$       (b)  $R_1 < R_2$       (c)  $C_1 > C_2$       (d)  $C_1 < C_2$

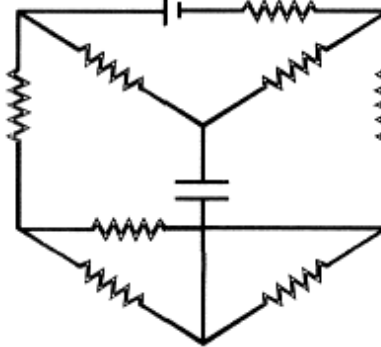Q 4. What is equivalent time constant of following RC circuit?



- (A)  $1.5 RC$   
 (B)  $3RC$   
 (C)  $2RC$   
 (D)  $RC/2$

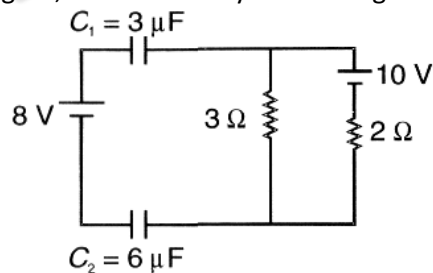
Q 5. In the circuit shown in figure, find the steady state charge on C, capacitor




- (a)  $2\mu C$   
 (b)  $3\mu C$   
 (c)  $4\mu C$   
 (d) Zero



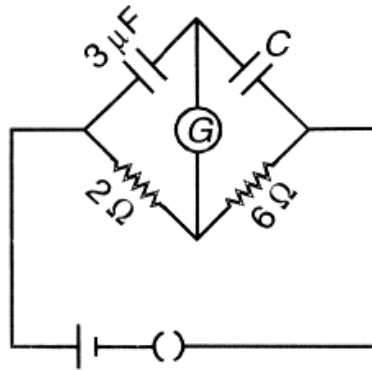
- Q 6. If key K, is closed in circuit shown in figure and galvanometer doesn't give deflection at any time, then value of C is



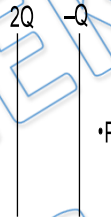
- (a)  $3\mu\text{F}$   
 (b)  $9\mu\text{F}$   
 (c)  $4\mu\text{F}$   
 (d)  $1\mu\text{F}$
- Q 7. In the figure shown the plates of a parallel plate capacitor have unequal charges. Its capacitance is 'C'. P is a point outside the capacitor and close to the plate of charge  $-Q$ . The distance between the plates is 'd'.



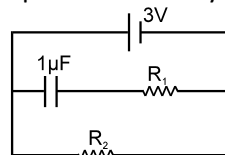- (A) A point charge at point 'P' will experience electric force due to capacitor  
 (B) The potential difference between the plates will be  $\frac{3Q}{2C}$   
 (C) The energy stored in the electric field in the region between the plates is  $\frac{9Q^2}{8C}$   
 (D) The force on one plate due to the other plate is  $\frac{Q^2}{2\pi\epsilon_0 d^2}$
- Q 8. A  $1\mu\text{F}$  capacitor is connected in the circuit shown below. The e.m.f. of the cell is 3 volts and internal resistance is 0.5 ohms. The resistors  $R_1$  and  $R_2$  have values 4 ohms and 1 ohm respectively. The charge on the capacitor in steady state must be :




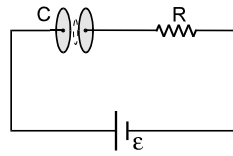- (A)  $2\mu\text{C}$   
 (B)  $1\mu\text{C}$   
 (C)  $1.33\mu\text{C}$   
 (D) zero
- Q 9. In the circuit shown the capacitor of capacitance C is initially uncharged. Now the capacitor is connected in the circuit as shown. The charge passed through an imaginary circular loop parallel to the plates (also circular) and having the area equal to half of the area of the plates, in one time constant is:




- (A)  $C\epsilon \left(1 - \frac{1}{e}\right)$   
 (B)  $\frac{C\epsilon}{2} \left(1 - \frac{1}{e}\right)$   
 (C)  $\frac{C\epsilon}{4}$   
 (D) zero

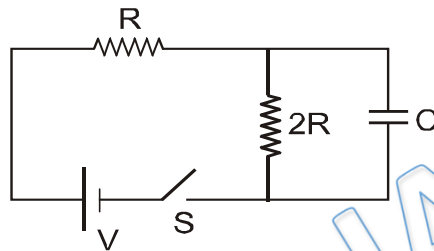Q 10. Consider the circuit shown, capacitor is uncharged initially. Switch is closed at  $t = 0$ , then select correct alternative/s :



- (A) charge on the capacitor as function of time is  $q = \frac{2CV}{3} \left(1 - e^{-\frac{3t}{2RC}}\right)$   
 (B) current in the resistance  $2R$  on function of time will be  $i = \frac{V}{3R} \left(1 - e^{-\frac{3t}{2RC}}\right)$   
 (C) current in the resistance  $2R$  on function of time will be  $i = \frac{V}{3R} \left(1 - e^{-\frac{3t}{2RC}}\right)$   
 (D) charge on the capacitor on function of time will be  $q = \frac{2CV}{3} \left(1 - e^{-\frac{t}{2RC}}\right)$

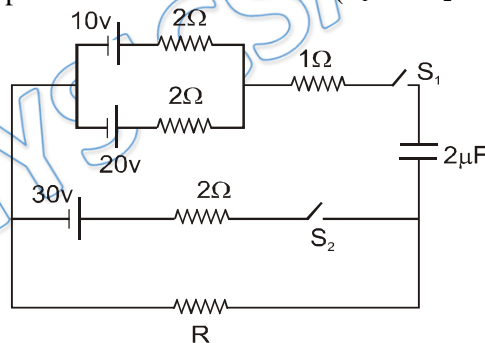
Q 11. Some ideal batteries and an unknown resistance are connected as shown in the circuit. At  $t = 0$ , current in  $R$  is 1 amp towards left. Calculate  $R$ . ( $S_1$  and  $S_2$  are closed at  $t = 0$ )



- (A)  $20.5 \Omega$       (B)  $21.5 \Omega$       (C)  $20 \Omega$       (D) None of these
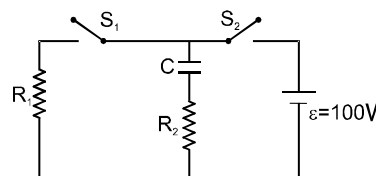
### Comprehension (Q.12 TO Q.14)

In the circuit shown in the figure the capacitor is initially uncharged





- Q 12.  $S_1$  and  $S_2$  are simultaneously closed at  $t = 0$ . Power dissipated in the resistor  $R_1$  is  $0.2 \text{ W}$  and initial current through  $R_2$  is  $10 \text{ mA}$ . Choose the correct option :
- (A)  $R_1 = 50 \text{ k}\Omega$  ,  $R_2 = 10 \text{ M}\Omega$  (B)  $R_1 = 50 \text{ k}\Omega$  ,  $R_2 = 10 \text{ k}\Omega$   
(C)  $R_1 = R_2 = 50 \text{ k}\Omega$  (D)  $R_1 = 10 \text{ k}\Omega$  ,  $R_2 = 50 \text{ k}\Omega$
- Q 13. When the capacitor gets fully charging switch  $S_2$  is opened. It is observed that after  $5 \text{ sec}$ , the current in  $R_1$  is  $0.74 \text{ mA}$ . [ $\ln(2.25) = 0.812$ ]. Choose the correct option :
- (A)  $C = 100 \text{ mF}$  approximately  
(B)  $C = 50 \text{ mF}$  approximately  
(C) The charge on the capacitor at the instant mentioned in the question is approximately equal to  $2 \text{ mC}$   
(D) Both (A) and (C) are correct
- Q 14. At the instant mentioned in the previous question  $S_1$  is opened and  $S_2$  is closed simultaneously. Taking this instant is  $t = 0$ , the charge on the capacitor as a function of time is best represented by
- (A)  $q = (4.4 e^{-t}) \text{ mC}$  (B)  $q = (10 + 5.6 e^{-t}) \text{ mC}$   
(C)  $q = (10 - 5.6 e^{-t}) \text{ mC}$  (D)  $q = (5.6 e^{-t} - 1.2) \text{ mC}$

PRATEEK JAIN  
PHYSICSAHOLICS

## Answer Key

Q.1 a	Q.2 b	Q.3 a	Q.4 a	Q.5 c
Q.6 d	Q.7 a, b, c	Q.8 a	Q.9 d	Q.10 a, b
Q.11 b	Q.12 b	Q.13 a	Q.14 c	

PLUS

ICONIC \*\*

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- × Personal Coach
- × Study Planner

24 months ₹2,333/mo >  
No cost EMI ₹56,000

18 months ₹2,625/mo >  
No cost EMI ₹47,250

12 months ₹3,208/mo >  
No cost EMI ₹38,500

6 months ₹4,667/mo >  
No cost EMI ₹28,000

To be paid as a one-time payment

View all plans



Add a referral code

APPLY

# PHYSICSLIVE

PLUS

ICONIC \*\*

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- × Personal Coach
- × Study Planner

24 months ₹2,100/mo >  
No cost EMI +10% OFF ₹50,400

18 months ₹2,363/mo >  
No cost EMI +10% OFF ₹42,525

12 months ₹2,888/mo >  
No cost EMI +10% OFF ₹34,650

6 months ₹4,200/mo >  
No cost EMI +10% OFF ₹25,200

To be paid as a one-time payment

View all plans



Awesome! PHYSICSLIVE code applied




Use code **PHYSICSLIVE** to get 10% OFF on Unacademy PLUS.

# Written Solution


**DPP-4 Capacitor- Energy in Capacitor, R-C Circuit,  
Energy stored in Electric Field & Electrostatic  
Pressure**

**By Physicsaholics Team**

1)

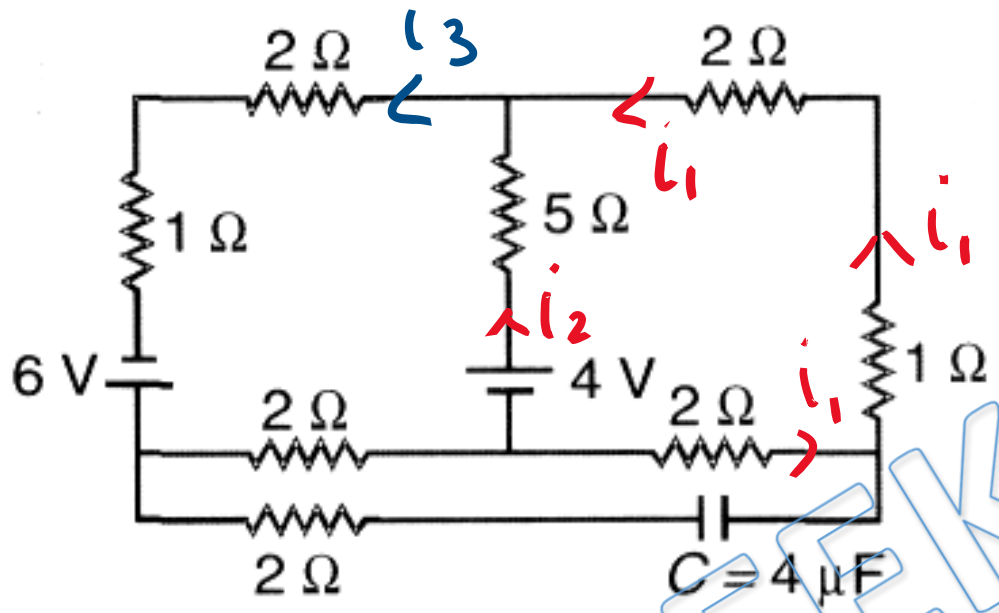

Steady state current in capacitor = 0

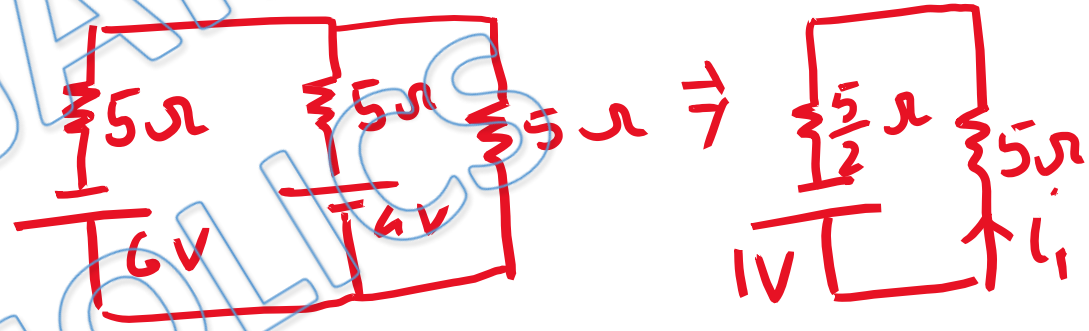

$$i_1 = \frac{1}{7.5} = \frac{2}{15} \text{ A}$$

by using KVL  $\rightarrow 4 - 5i_2 + 5 \times \frac{2}{15} = 0$

$$\Rightarrow 5i_2 = 4 + \frac{2}{3} = \frac{14}{3} \Rightarrow i_2 = \frac{14}{15}$$

$$\Rightarrow i_3 = i_1 + i_2 = \frac{2}{15} + \frac{14}{15} = \frac{16}{15} \text{ A}$$




$$\begin{aligned}\text{Voltage across capacitor} &= 2i_1 + 2i_3 \\ &= 2 \left( \frac{2}{15} + \frac{16}{15} \right) = \frac{36}{15} = \frac{12}{5} = 2.4 \text{ V}\end{aligned}$$

$$\begin{aligned}\text{Charge on Capacitor} &= CV \\ &= 4 \mu \text{F} \times 2.4 \\ &= 9.6 \mu \text{C}\end{aligned}$$

Ans(a)

2)

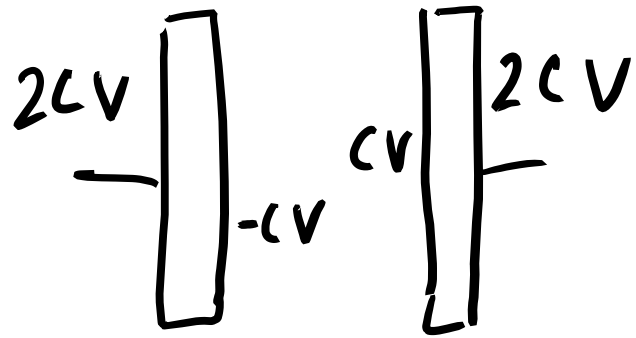


Potential difference

across capacitor =  $\frac{CV}{V} = V$

Potential difference across resistance

=  $V + V = 2V$

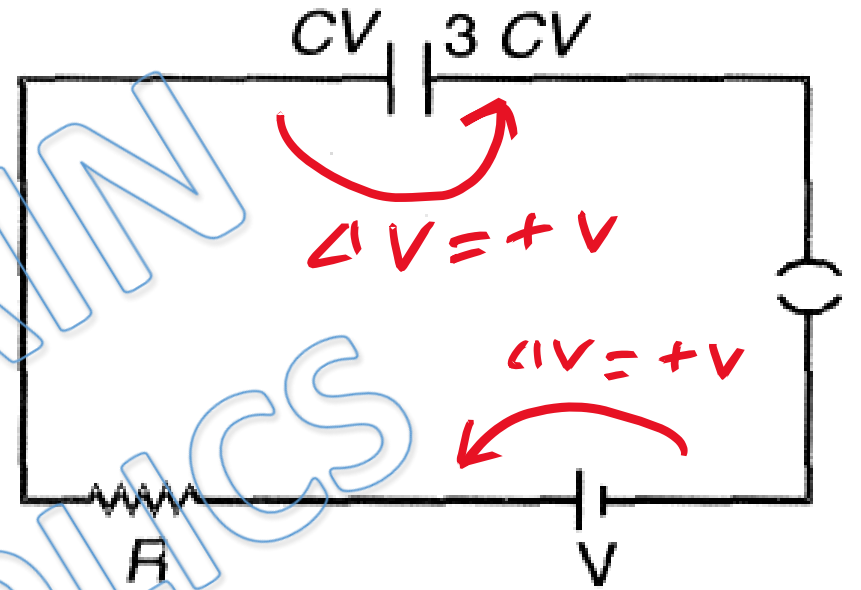Power of resistance =  $\frac{(2V)^2}{R} = \frac{4V^2}{R}$



Ans (b)

3) for Discharging RC circuit  $\rightarrow$

$$i = i_0 e^{-t/RC} \Rightarrow i = \frac{V}{R} e^{-t/RC}$$

$$\Rightarrow \ln i = -\frac{t}{RC} + \ln(V/R)$$



$$\Rightarrow |\text{Slope}| = \frac{1}{RC}, \text{intercept} = \ln(V/R)$$

$$\Rightarrow \ln(V/R_1) > \ln(V/R_2)$$

$\Rightarrow R_1 < R_2 \rightarrow$  option (a) is not possible.




$$\frac{1}{R_1 C_1} > \frac{1}{R_2 C_2} \Rightarrow \frac{C_1}{C_2} < \frac{R_2}{R_1} > 1$$

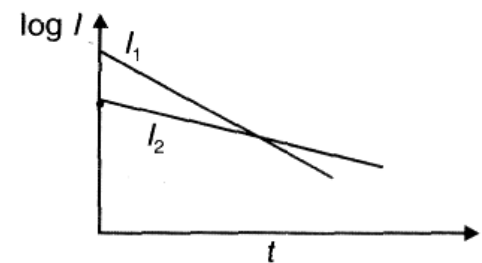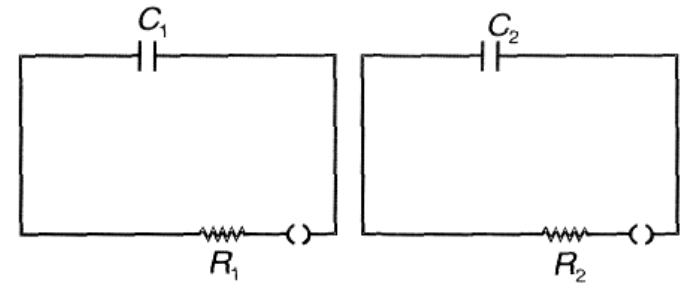$\Rightarrow C_1$  may be greater & may be smaller than  $C_2$ .



ANS(a)

4)

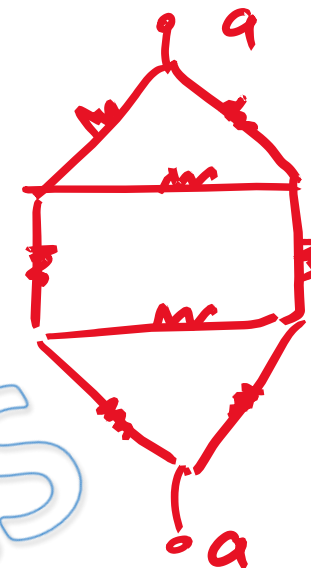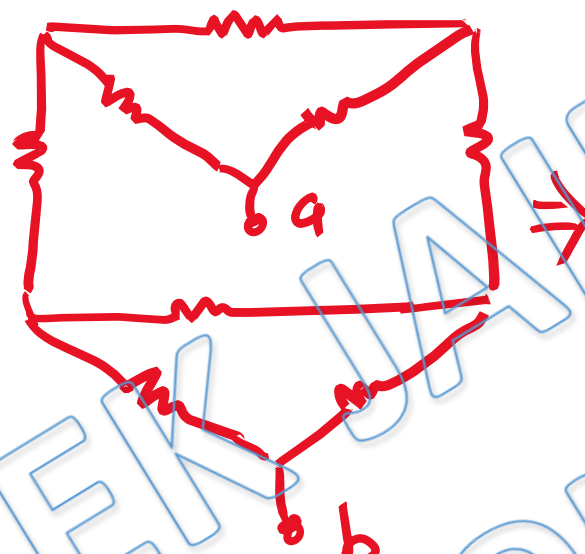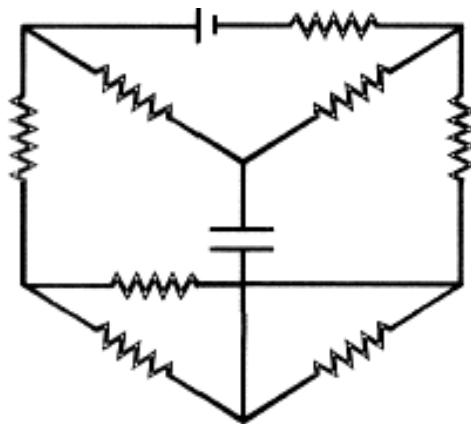


$$R_{ab} = \frac{3R}{2}$$

$T = R_{\text{eff}} C$  where  $R_{\text{eff}}$  is effective resistance between  
 $a$  &  $b$ .  
 $= \frac{3RC}{2}$

Ans(a)

5)

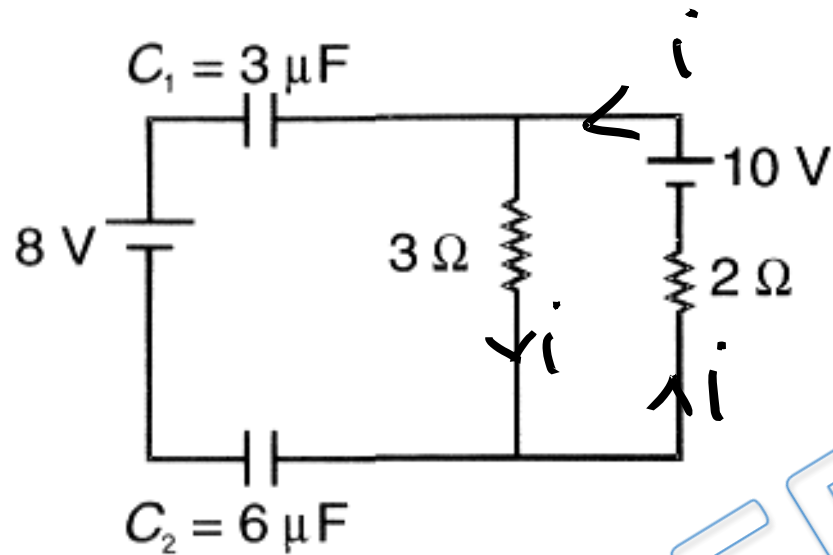

in steady state current

in capacitor = 0

$$\Rightarrow \text{Current in } 3\Omega \text{ resistance} = \frac{10}{3+2} = 2 \text{ A.}$$

$$\text{Voltage across } 3\Omega = 3i = 6 \text{ V}$$

$$\text{Voltage across combination of } C_1 \text{ \& } C_2 = 8 - 6 = 2 \text{ V}$$


$$\text{effective capacitance of } C_1 \text{ \& } C_2 = \frac{3\mu \times 6\mu}{9\mu} = 2\mu \text{ F}$$

$$\text{Charge on } C_1 = \text{Charge on effective} = 2 \times 2\mu = 4\mu \text{ C}$$

(ANS(c))

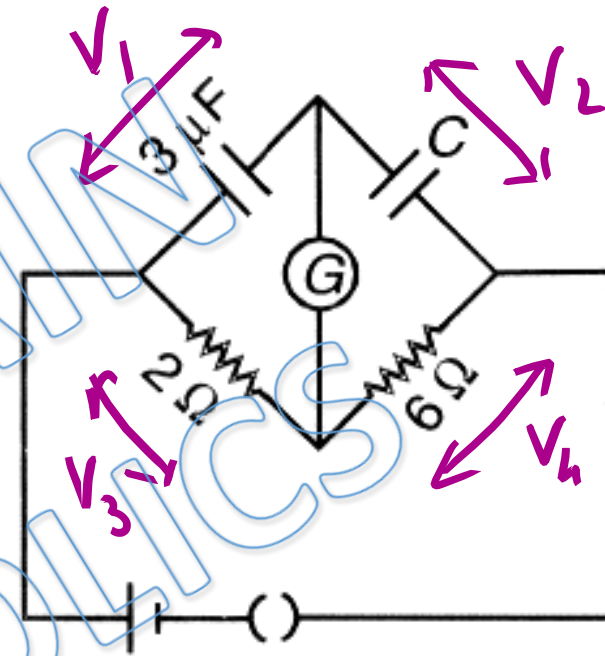6) Since reading of galvanometer is zero.

$3\mu\text{F}$  &  $C$  are in series  
and  $2\Omega$  and  $6\Omega$  are in series.



$$\Rightarrow \frac{V_1}{V_2} = \frac{V_3}{V_4} \Rightarrow \frac{C}{3\mu} = \frac{2}{6} \Rightarrow C = 1\mu\text{F}$$

Ans(d)

7) Electric field at P =  $\frac{(Q/2)}{A\epsilon_0}$


⇒ charge at P will experience force.

P.D. b/w plates =  $\frac{(3Q/2)}{C} = \frac{3Q}{2C}$

Energy stored b/w plates =  $\frac{(3Q/2)^2}{2C} = \frac{9Q^2}{8C}$

field of 2Q on -ve plate =  $\frac{2Q}{2A\epsilon_0} = \frac{Q}{A\epsilon_0}$

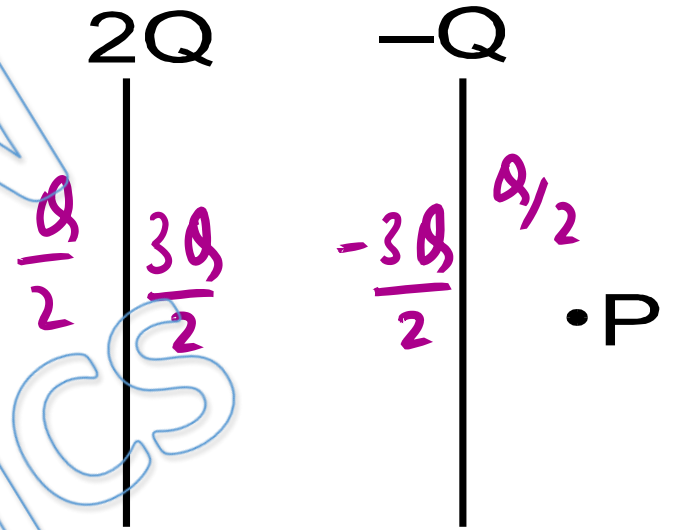force on -ve plate =  $QE = \frac{Q^2}{A\epsilon_0}$



Ans (a, b, c)


$$8) \quad i = \frac{3}{1+0.5} = 2 \text{ A.}$$

Voltage across capacitor

= ' ' '  $R_2$

$$= 2 \times 1 = 2 \text{ V}$$

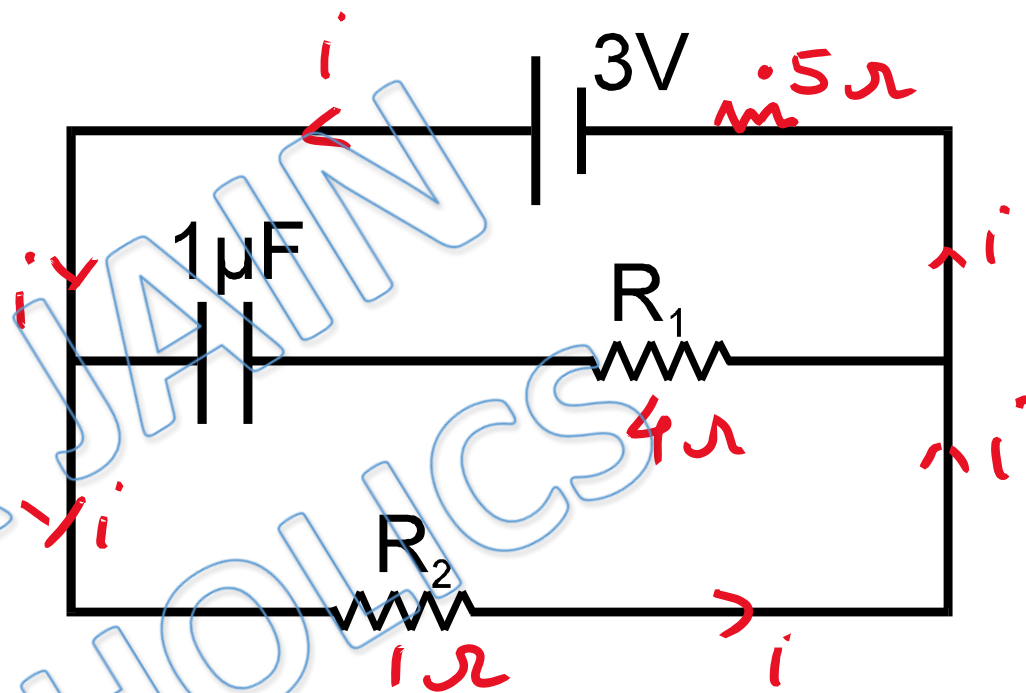
$$\text{Charge on capacitor} = 1 \mu \times 2 = 2 \mu \text{ C}$$



Ans(a)




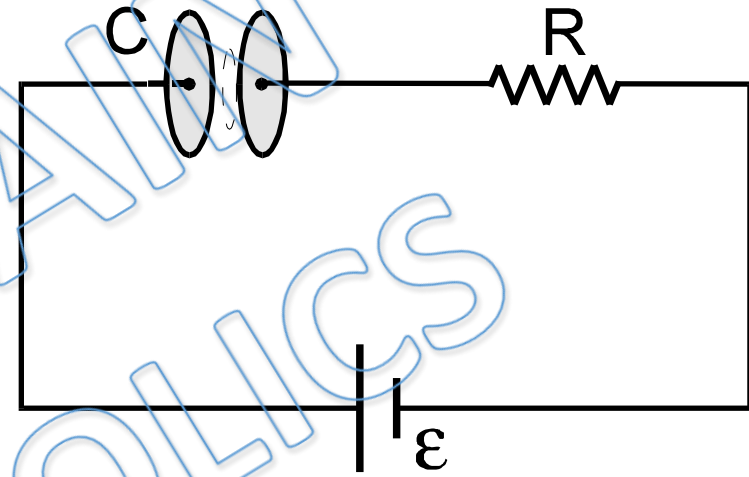9) During charging of Capacitor no current flows in space between plates.



Ans(d)

10)

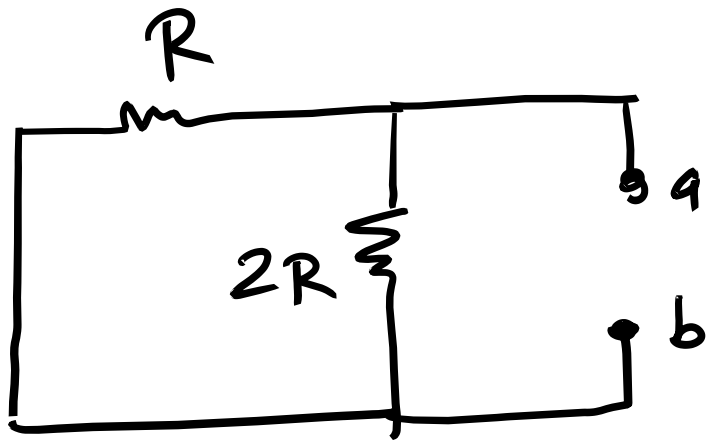


$$R_{\text{eff}} = \frac{2R \times R}{2R + R} = \frac{2R}{3}$$

$$\tau = R_{\text{eff}} C = \frac{2RC}{3}$$

Steady state voltage across  $C$

= , , , , ,  $2R = \frac{2V}{3}$

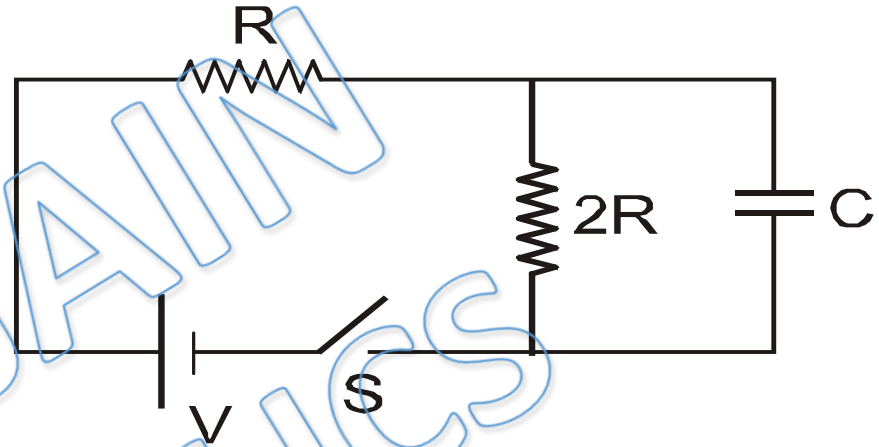Steady state charge on  $C = \frac{2CV}{3}$



Charge on capacitor at  $t = t$

$$q = q_0 (1 - e^{-t/\tau}) = \frac{2CV}{3} (1 - e^{-3t/2RC})$$


If  $i$  is current in  $3R$  at  $t = t$ .

$$2iR = q/C \Rightarrow i = \frac{q}{2RC}$$



$$\Rightarrow i = \frac{V}{3R} (1 - e^{-3t/2RC})$$

Ans(a, b)

11)

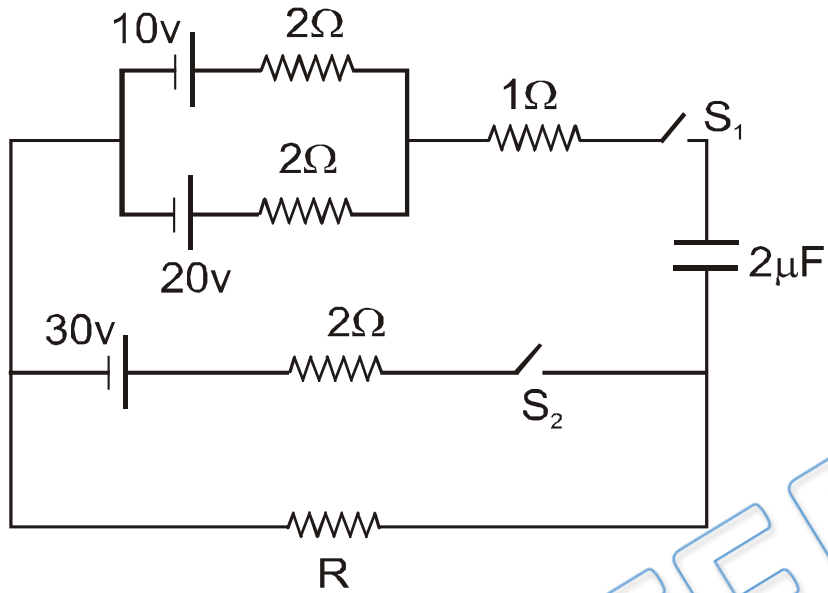

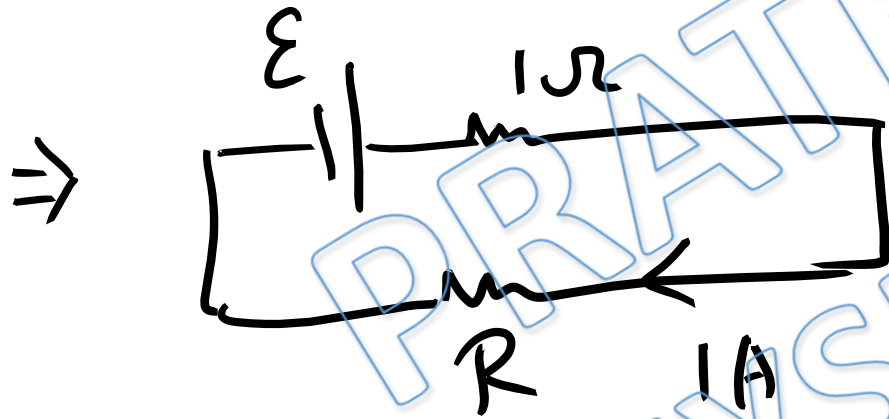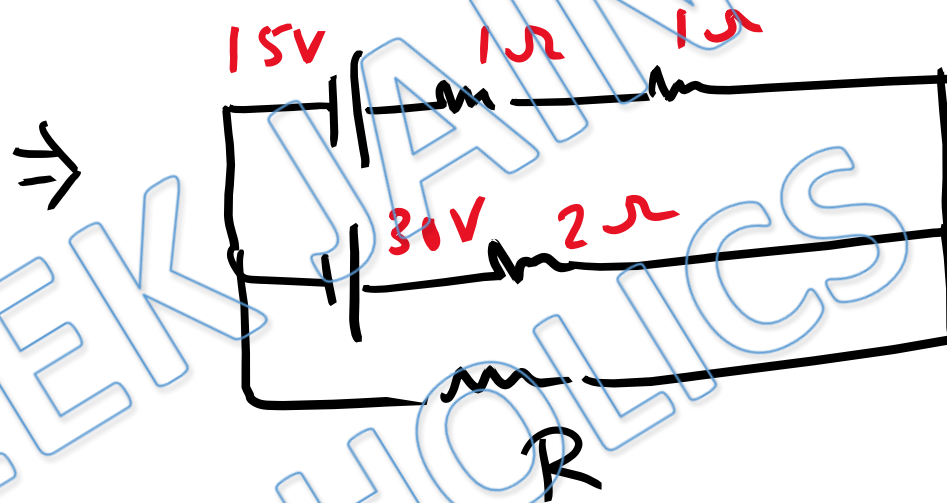at  $t=0$ , Capacitor behaves as simple wire.



$$\mathcal{E} = \frac{30 \times 2 + 15 \times 2}{2 + 2} = \frac{90}{4} = 22.5 \text{ V}$$

$$\mathcal{E} = i(R + r) \Rightarrow 22.5 = 1(R + 1)$$

$$\Rightarrow R = 21.5 \Omega$$

Ans(b)

12)

$$\text{Power of } R_1 = 2 \text{ W}$$


$$\frac{(100)^2}{R_1} = 2$$

$$\Rightarrow R_1 = 50 \text{ k}\Omega$$

$$\text{Current in } R_2 = 10 \text{ mA}$$

$$\frac{100}{R_2} = 10 \text{ mA}$$

$$R_2 = 10 \text{ k}\Omega$$

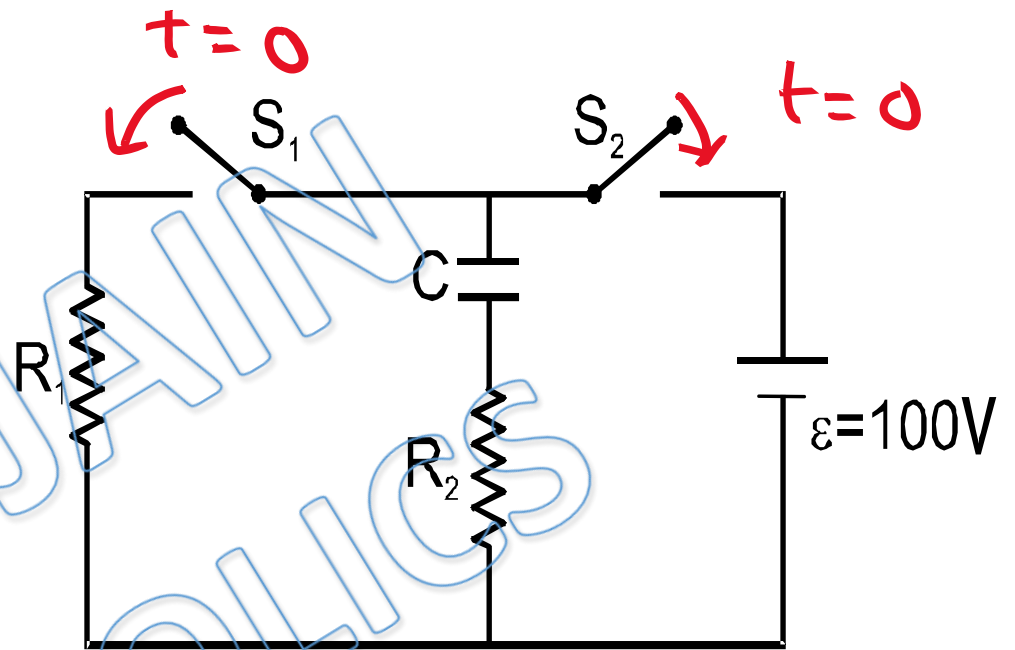

Ans (b)

(3) At the instant of opening  $S_2$

Voltage across  $C = 100V$

Voltage across  $C$  after 5 Sec


$$= 100 e^{-t/60kC}$$

Current in  $R_1$  after 5 Sec

$$= 74 \text{ mA} = \frac{100 e^{-t/60kC}}{60k}$$

$$e^{-t/60kC} = 0.444$$

$$e^{t/60kC} = \frac{1}{0.444} = 2.25$$

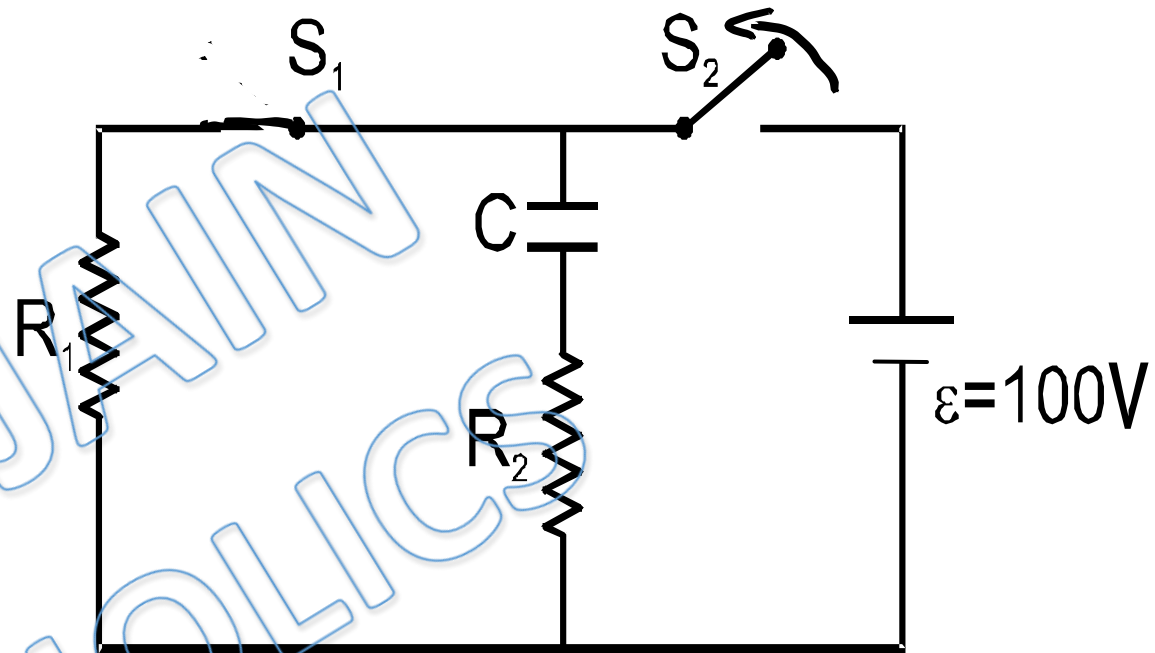

$$\frac{5}{60 \text{ K}\Omega} = \ln(2.25) = .812$$

$$C = \frac{1}{12 \times .812 \text{ K}} \approx 100 \mu\text{F}$$

Charge on capacitor at this instant

$$= C V = 100 \mu \text{ (Voltage across } R_1 \text{ \& } R_2)$$

$$= 100 \mu \times .74 \text{ m} \times 60 \text{ K}$$

$$= 4.44 \mu\text{C}$$

(Ans(a))

14) Charge on Capacitor

at  $t=0$


$$Q_0 = 4.4 \mu\text{C}$$

Charge on Capacitor at  $t=t$

$$Q = \frac{100}{10\text{K}} (1 - e^{-t}) + 4.4 \mu\text{C} e^{-t}$$

$$= (10 - 5.6 e^{-t}) \mu\text{C}$$

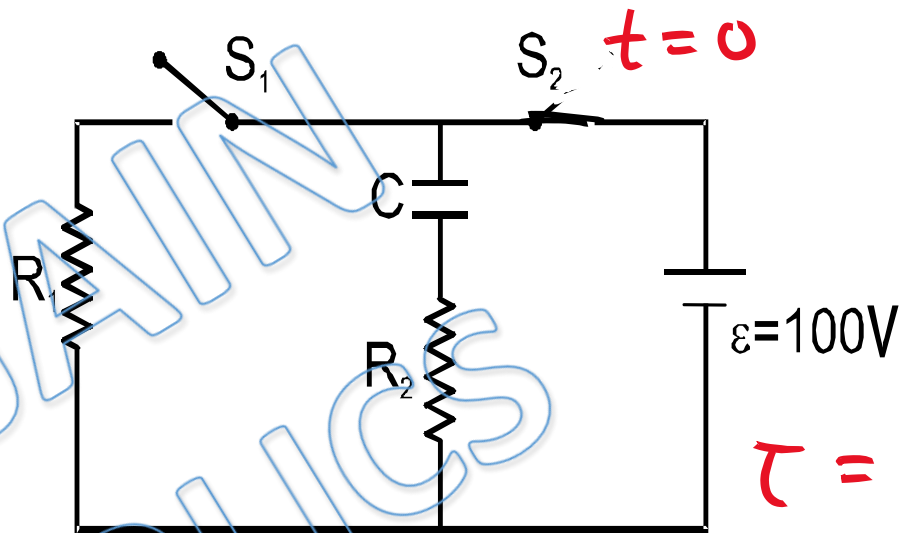Charge if there was no initial charge on capacitor



$$\tau = R_2 C = 1$$

Charge if there was no battery.



**For Video Solution of this DPP, Click on below link**

Video Solution  
on Website:-

<https://physicsaholics.com/home/courseDetails/103>

Video Solution  
on YouTube:-

<https://youtu.be/cq4Z-W7mCC8>

Written Solution  
on Website:-

<https://physicsaholics.com/note/notesDetails/63>

 **SUBSCRIBE**



[@Physicsaholics](#)

[@Physicsaholics\\_prateek](#)

[@NEET\\_Physics](#)

[@IITJEE-Physics](#)

[physicsaholics.com](#)

[Unacademy](#)



**CLICK**

Chalo Niklo