



Video Solution on Website :-

<https://physicsaholics.com/home/courseDetails/104>


Video Solution on YouTube:-

<https://youtu.be/xAhvcTRPmxg>


Written Solution on Website:-

<https://physicsaholics.com/note/notesDetails/65>

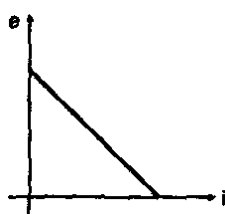
- Q 1. In an L-R circuit connected to a battery of constant emf  $E$  switch  $s$  is closed at time  $t = 0$ . If  $e$  denotes the induced emf across inductor and  $i$  the current in the circuit at any time  $t$ . Then which of the following graphs shows the variation of  $e$  with  $i$ ?




(a)

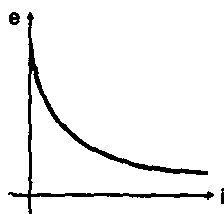

(b)

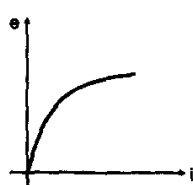


(c)

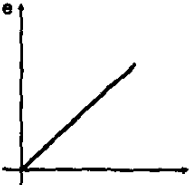


(d)

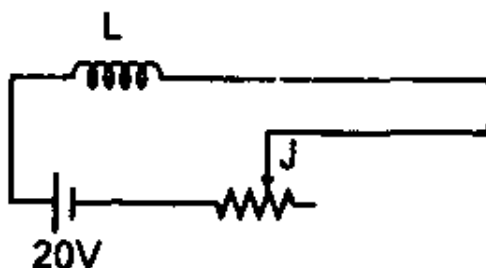
- Q 2. In the circuit shown in figure the jockey  $J$  is being pulled towards right so that the resistance in the circuit is increasing. Its value at some instant is  $5\ \Omega$ . The current in the circuit at this instant will be:



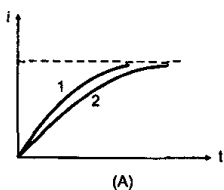
- (a) 4 A  
(b) less than 4 A  
(c) more than 4 A  
(d) may be less than or more than 4 A depending on the value of  $L$
- Q 3. Current growth in two L-R circuits (B) and (C) is as shown in figure (A). Let  $L_1$ ,  $L_2$ ,  $R_1$  and  $R_2$  be the corresponding values in two circuits. Then:



(a)  $R_1 > R_2$

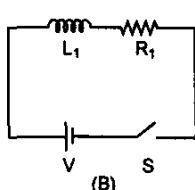


(b)  $R_1 = R_2$

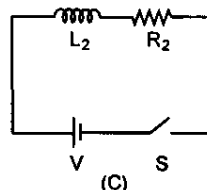


(c)  $L_1 > L_2$

(d)  $L_1 < L_2$

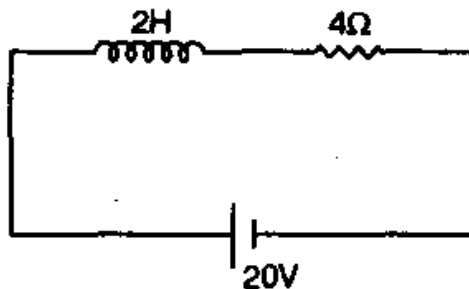
- Q 4. In the L-R circuit shown in figure, potential difference across the resistance at some instant is 4 V. Then:



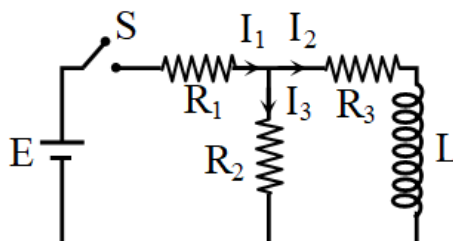- (a) current is increasing at a rate of 8 A/s at this instant  
 (b) power supplied by the battery at this instant is 20 W  
 (c) power stored in the magnetic field at this instant is 16 W  
 (d) current in the circuit at this instant is 1 A
- Q 5. In the figure circuit, if  $E = 10V$ ,  $R_1 = 2 \text{ ohm}$ ,  $R_2 = 3 \text{ ohm}$ ,  $R_3 = 6 \text{ ohm}$  and  $L = 5 \text{ henry}$ . The current  $I_1$  just after pressing the switch S is




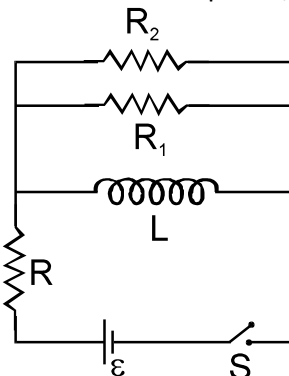- (a)  $(10/4)$  ampere  
 (b)  $(10/5)$  ampere  
 (c)  $(10/12)$  ampere  
 (d)  $(10/6)$  ampere
- Q 6. Switch S is closed for a long time. at  $t = 0$  It is opened, then:



- (a) total heat produced in resistor R after opening the switch is  $\frac{1}{2} \frac{L\epsilon^2}{R^2}$   
 (b) total heat produced in resistor  $R_2$  after opening the switch is  $\frac{1}{2} \frac{L\epsilon^2}{R^2} \left( \frac{R_1}{R_1+R_2} \right)$   
 (c) heat produced in resistor  $R_1$  after opening the switch is  $\frac{1}{2} \frac{R_2 L \epsilon^2}{(R_1+R_2) R^2}$   
 (d) Current through  $R_1$  just after opening the switch is  $\frac{\epsilon}{R} \cdot \left( \frac{R_1}{R_1+R_2} \right)$

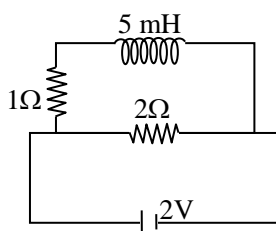
Q 7. When induced emf in inductor coil is 50% of its maximum value then stored energy in inductor coil in the given circuit will be-




- (a) 2.5 mJ  
 (b) 5 mJ  
 (c) 15 mJ  
 (d) 20 mJ
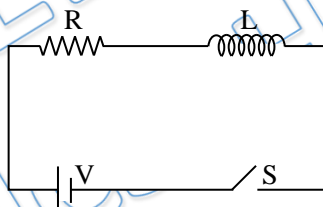
### Passage (Q.8 to Q.10)

A resistor and inductor are connected in series through a battery. The switch S is closed at time  $t = 0$ .







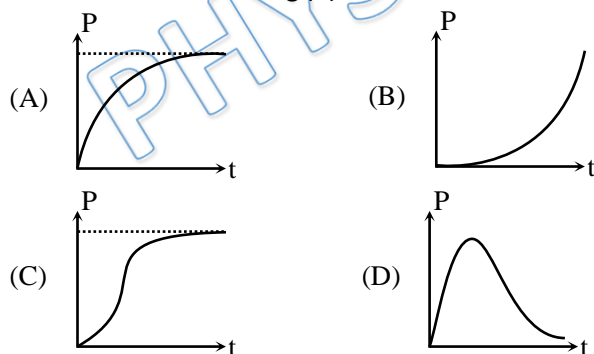Q 8. The rate of Joule heating (P) in resistor varies with the time 't' is best represented by the graph.




- Q 9. What is the magnitude of current flowing when the rate of increase of magnetic energy in the inductor is maximum –  
 (a)  $I = V/R$   
 (b)  $I = V/2R$   
 (c)  $I = V/4R$   
 (d)  $I = (V/R) \ln 2$

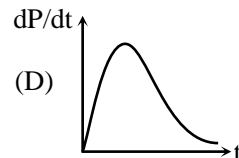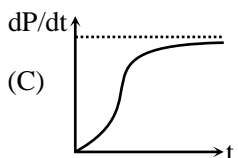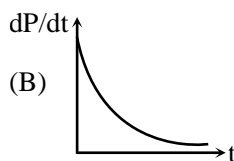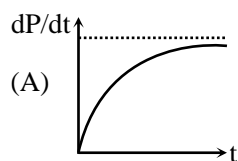- Q 10. Which of the following graph best represent rate of change of power dissipated in resistor as a function of time -




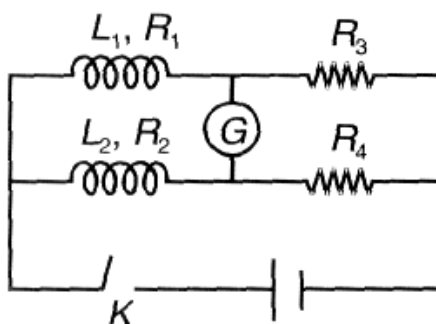- Q 11. After the key  $k$  is closed, galvanometer in the shown arrangement shows zero deflection at all the times if ( $R_1$ , and  $R_2$  are resistances of inductors  $L_1$  and  $L_2$ )



- (a)  $\frac{R_1}{R_2} = \frac{R_3}{R_4} = \frac{L_1}{L_2}$   
 (b)  $\frac{R_2}{R_1} = \frac{R_3}{R_4} = \frac{L_1}{L_2}$   
 (c)  $\frac{L_1}{L_2} = \frac{R_1}{R_2} = \frac{R_3}{R_4}$   
 (d)  $\frac{L_1}{L_2} = \frac{R_3}{R_4} = \frac{R_1}{R_2}$

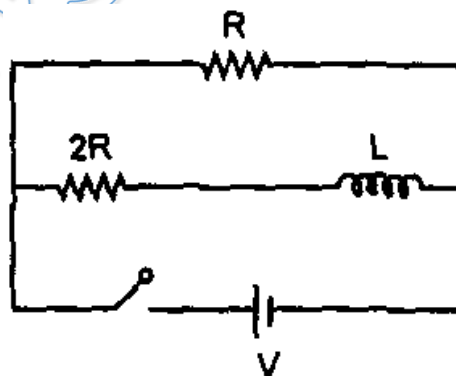- Q 12. The ratio of time constants during current growth and current decay of the circuit shown in figure is:



- (a) 1 : 1      (b) 3 : 2      (c) 2 : 3      (d) 1 : 3



## **Answer Key**

|                 |               |                 |                       |               |
|-----------------|---------------|-----------------|-----------------------|---------------|
| <b>Q.1 a</b>    | <b>Q.2 c</b>  | <b>Q.3 b, d</b> | <b>Q.4 a, b, c, d</b> | <b>Q.5 b</b>  |
| <b>Q.6 b, c</b> | <b>Q.7 a</b>  | <b>Q.8 c</b>    | <b>Q.9 b</b>          | <b>Q.10 d</b> |
| <b>Q.11 a</b>   | <b>Q.12 b</b> |                 |                       |               |

# PHYSICSLIVE

PLUS

ICONIC \*

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

24 months ₹2,333/mo >  
No cost EMI ₹56,000

18 months ₹2,625/mo >  
No cost EMI ₹47,250

12 months ₹3,208/mo >  
No cost EMI ₹38,500

6 months ₹4,667/mo >  
No cost EMI ₹28,000

To be paid as a one-time payment

[View all plans](#)



Add a referral code

APPLY

PLUS

ICONIC \*

- ✓ India's Best Educators
- ✓ Interactive Live Classes
- ✓ Structured Courses & PDFs
- ✓ Live Tests & Quizzes
- ✗ Personal Coach
- ✗ Study Planner

24 months ₹2,100/mo >  
No cost EMI +10% OFF ₹50,400

18 months ₹2,363/mo >  
No cost EMI +10% OFF ₹42,525

12 months ₹2,888/mo >  
No cost EMI +10% OFF ₹34,650

6 months ₹4,200/mo >  
No cost EMI +10% OFF ₹25,200

To be paid as a one-time payment

[View all plans](#)



Awesome! PHYSICSLIVE code applied








Use code **PHYSICSLIVE** to get 10% OFF on Unacademy PLUS.

# **Written Solution**

**DPP- 4 EMI- Self inductance, RL Circuit, Energy  
stored in Inductor**

**By Physicsaholics Team**

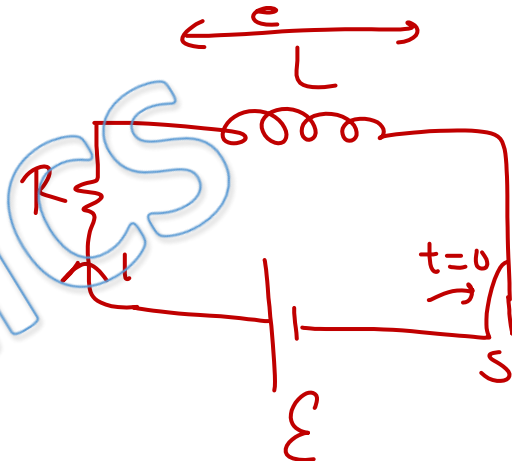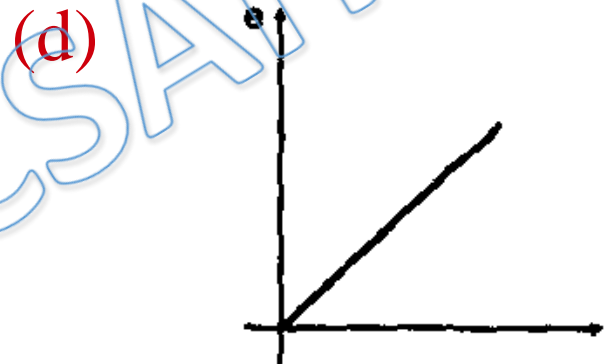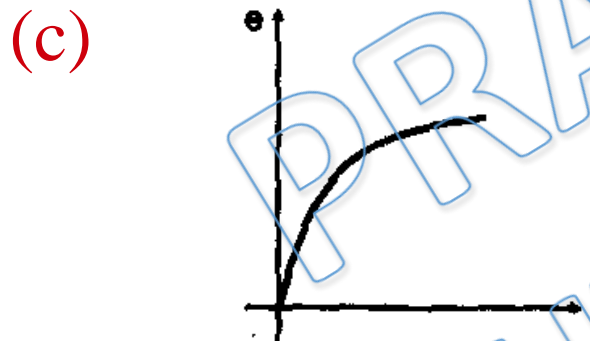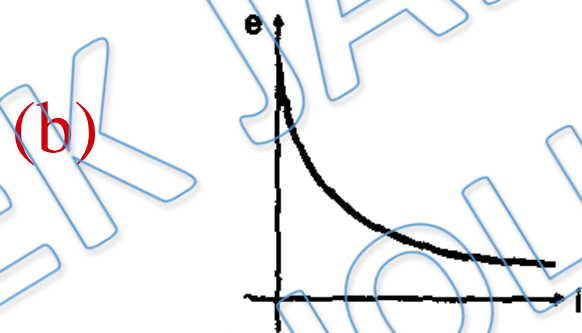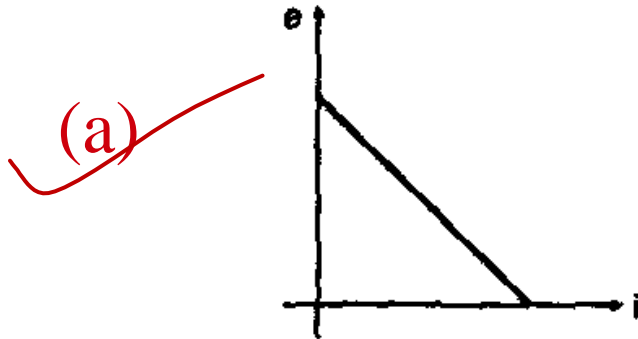Q.1) In an L-R circuit connected to a battery of constant emf  $\mathcal{E}$  switch  $s$  is closed at time  $t = 0$ . If  $e$  denotes the induced emf across inductor and  $i$  the current in the circuit at any time  $t$ . Then which of the following graphs shows the variation of  $e$  with  $i$ ?



$$\mathcal{E} - iR - e = 0$$

$$e = \mathcal{E} - iR$$

$\downarrow$   
 Constant  
 & line graph

Q.2) In the circuit shown in figure the jockey J is being pulled towards right so that the resistance in the circuit is increasing. Its value at some instant is  $5\ \Omega$ . The current in the circuit at this instant will be:


$$I = \frac{20 + \mathcal{E}}{R}$$

$$\text{at } R = 5$$

$$I = \frac{20 + \mathcal{E}}{5}$$

$$= 4 + \frac{\mathcal{E}}{5}$$

$$I > 4\text{ A}$$

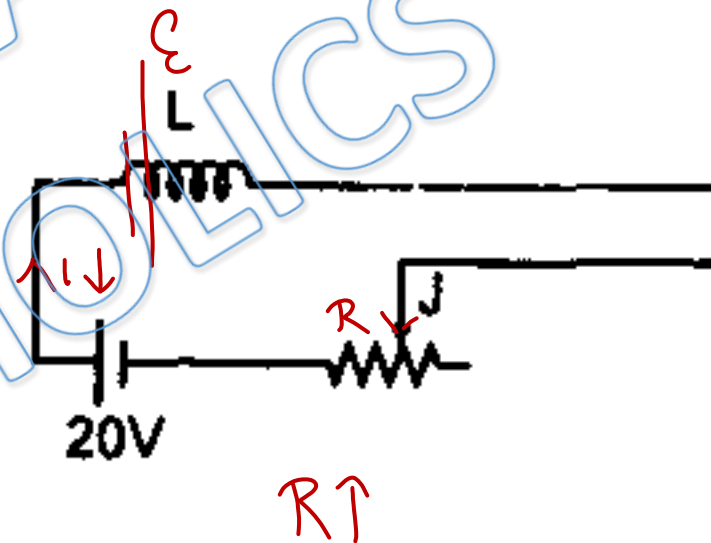


(a) 4 A

(b) less than 4 A

☒ (c) more than 4 A

(d) may be less than or more than 4 A depending on the value of L

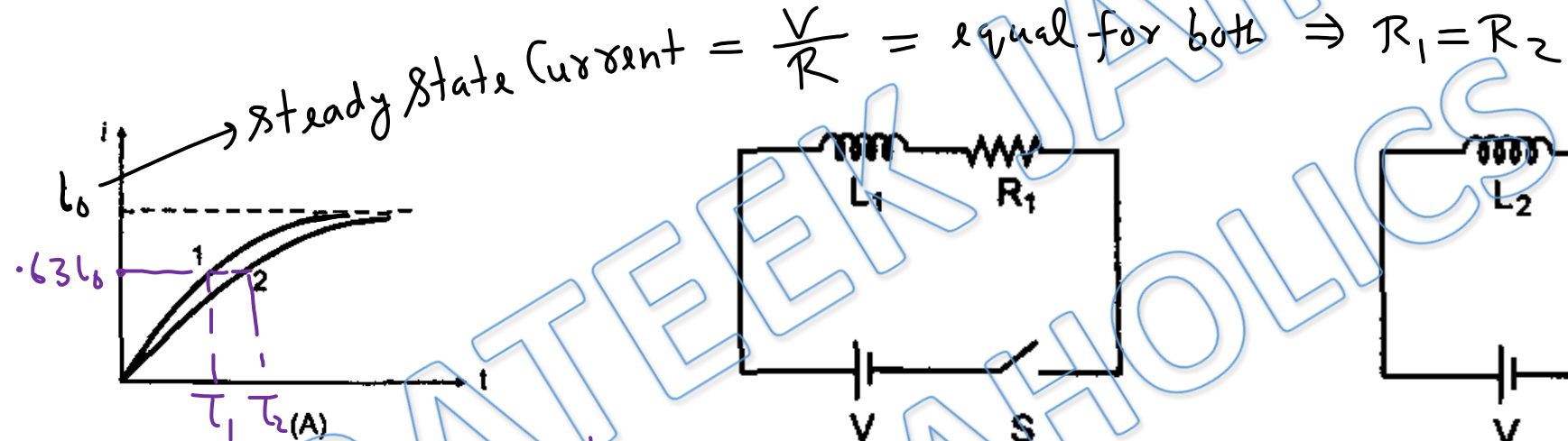Q.3) Current growth in two L-R circuits (B) and (C) is as shown in figure (A). Let  $L_1$ ,  $L_2$ ,  $R_1$  and  $R_2$  be the corresponding values in two circuits. Then:



$$\tau_2 > \tau_1 \Rightarrow \frac{L_2}{R_2} > \frac{L_1}{R_1} \Rightarrow L_2 > L_1$$

(a)  $R_1 > R_2$

(b)  $R_1 = R_2$

(c)  $L_1 > L_2$


(d)  $L_1 < L_2$

Q.4) In the L-R circuit shown in figure, potential difference across the resistance at some instant is 4 V. Then:

$$L \frac{di}{dt} = 16 \Rightarrow \frac{di}{dt} = \frac{16}{2} = 8 \text{ A/s}$$

$$V = iR \Rightarrow 4 = i \times 4 \Rightarrow i = 1 \text{ A}$$
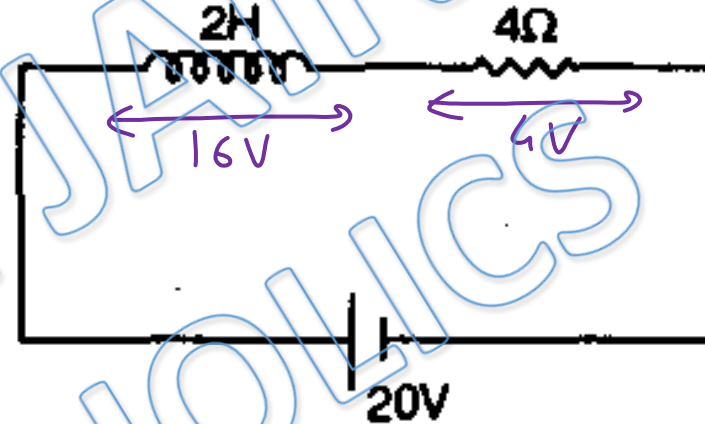
$$P_{\text{batt}} = \mathcal{E} i = 20 \times 1 = 20 \text{ W}$$




- (a) current is increasing at a rate of 8 A/s at this instant
- (b) power supplied by the battery at this instant is 20 W
- (c) power stored in the magnetic field at this instant is 16 W
- (d) current in the circuit at this instant is 1 A

$$P_{\text{Inductor}} = V i = 16 \times 1 = 16 \text{ W}$$


Q.5) In the figure circuit, if  $E = 10\text{V}$ ,  $R_1 = 2\text{ ohm}$ ,  $R_2 = 3\text{ ohm}$ ,  $R_3 = 6\text{ ohm}$  and  $L = 5\text{ henry}$ . The current  $I_1$  just after pressing the switch  $S$  is

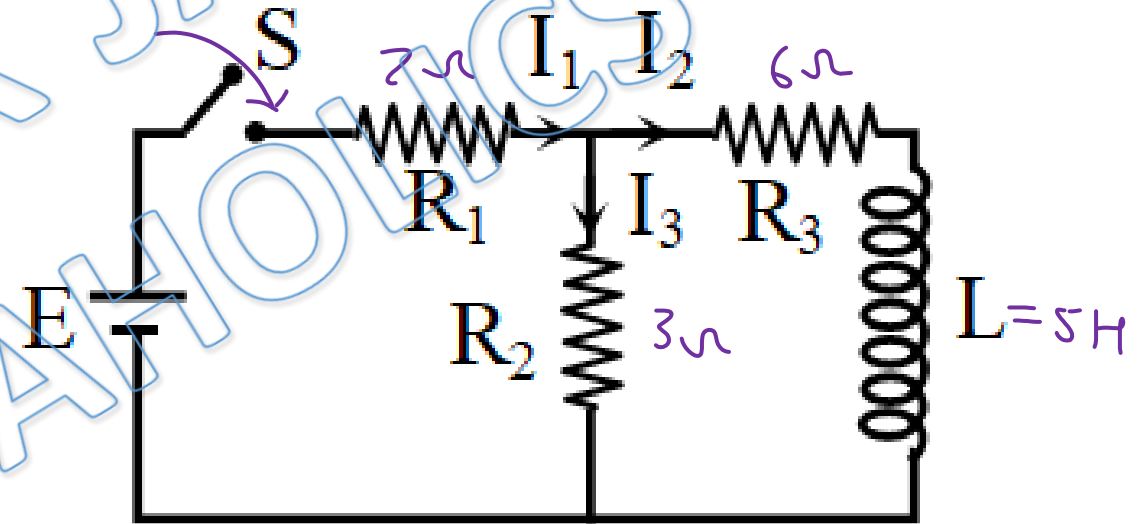- (a)  $(10/4)$  ampere
- ☒ (b)  $(10/5)$  ampere
- (c)  $(10/12)$  ampere
- (d)  $(10/6)$  ampere



At  $t=0$
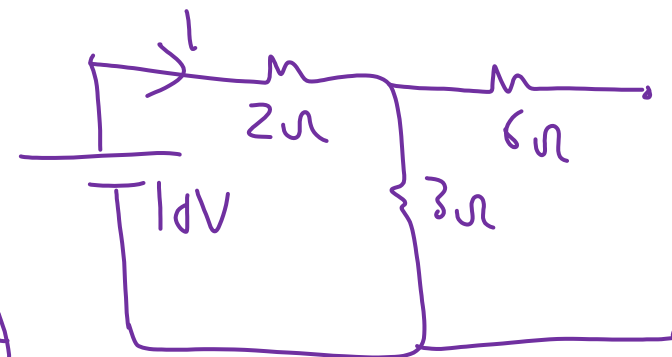
$$I = \frac{10}{2+3} = \frac{10}{5} \text{ A}$$



$$P = \frac{V^2}{R}$$

Q.6) Switch S is closed for a long time. At  $t = 0$  It is opened, then:

(a) total heat produced in resistor R after opening the switch is  $\frac{1}{2} \frac{L \epsilon^2}{R^2}$

just after  $t=0 \rightarrow$

R is out of circuit, no heat will be generated in R

(b) total heat produced in resistor  $R_2$  after opening the switch is  $\frac{1}{2} \frac{L \epsilon^2}{R^2} \left( \frac{R_1}{R_1 + R_2} \right)$

$$\frac{\Delta H_1}{\Delta H_2} = \frac{R_2}{R_1}, \quad \Delta H_1 + \Delta H_2 = \frac{L \epsilon^2}{2 R^2}$$


(c) heat produced in resistor  $R_1$  after opening the switch is  $\frac{1}{2} \frac{R_2 L \epsilon^2}{(R_1 + R_2) R^2}$

$$\Delta H_1 = \frac{R_2}{R_1 + R_2} \left( \frac{L \epsilon^2}{2 R^2} \right)$$

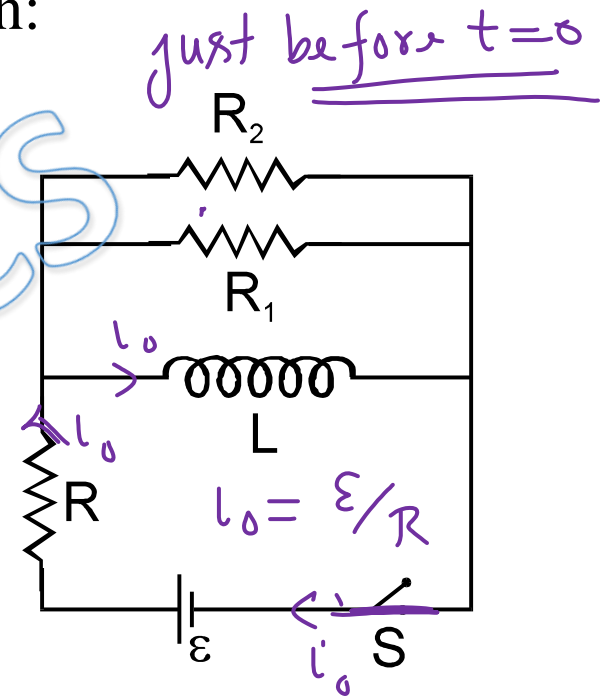(d) Current through  $R_1$  just after opening the switch is  $\frac{\epsilon}{R} \cdot \left( \frac{R_1}{R_1 + R_2} \right)$

$$\Delta H_2 = \frac{R_1}{R_1 + R_2} \left( \frac{L \epsilon^2}{2 R^2} \right)$$

$$i_1 = \frac{R_2}{R_1 + R_2} i_0 = \frac{R_2}{R_1 + R_2} \times \frac{\epsilon}{R}$$



Energy of inductor  
 $= \frac{1}{2} L \frac{\epsilon^2}{R^2}$

Q.7) When induced emf in inductor coil is 50% of its maximum value then stored energy in inductor coil in the given circuit will be-


$$\begin{aligned} U &= \frac{1}{2} L i^2 \\ &= \frac{1}{2} \times 5 \text{ mH} \times 1^2 \\ &= 2.5 \text{ mJ} \end{aligned}$$

☒ (a) 2.5 mJ

(b) 5 mJ


(c) 15 mJ

(d) 20 mJ

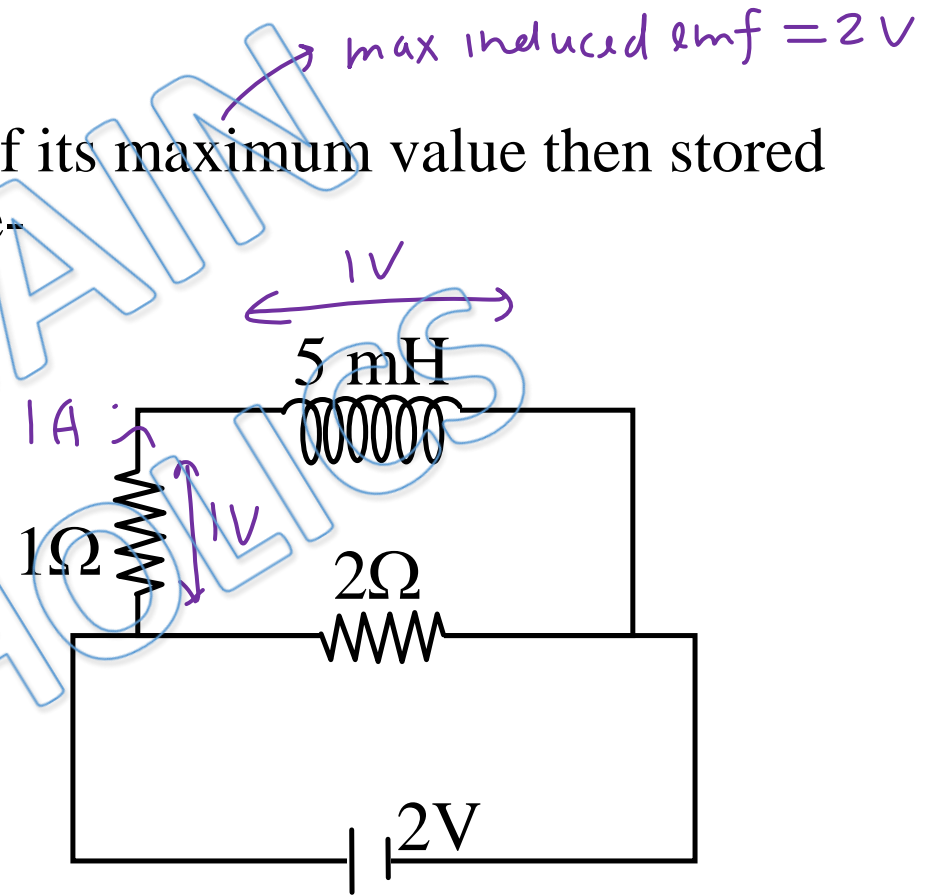


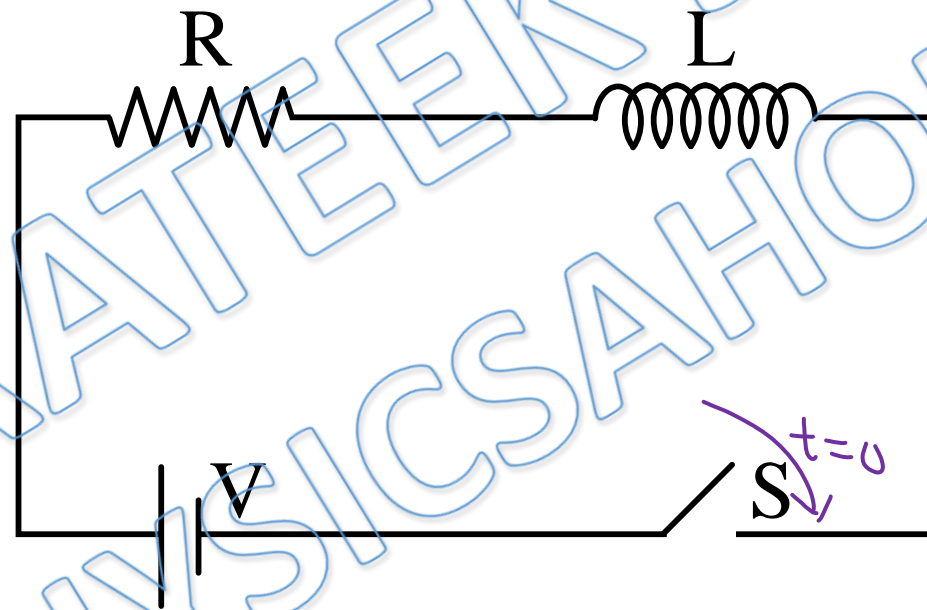
***Passage II (Question 8 to 10)***

A resistor and inductor are connected in series through a battery. The switch  $S$  is closed at time  $t = 0$ .






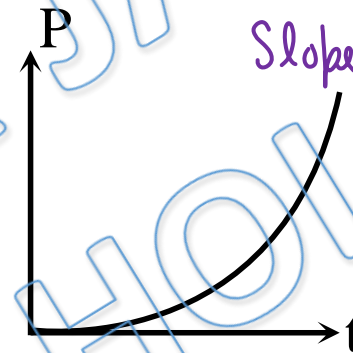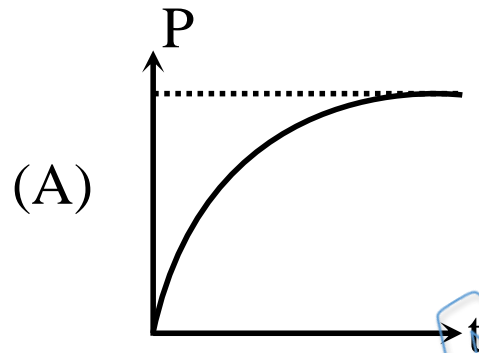Q.8) The rate of Joule heating (P) in resistor varies with the time 't' is best represented by the graph.

$$P = I^2 R = \left[ \frac{\mathcal{E}}{R} (1 - e^{-t/\tau}) \right]^2 R = \frac{\mathcal{E}^2}{R} (1 - e^{-Rt/L})^2$$


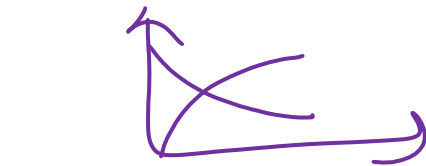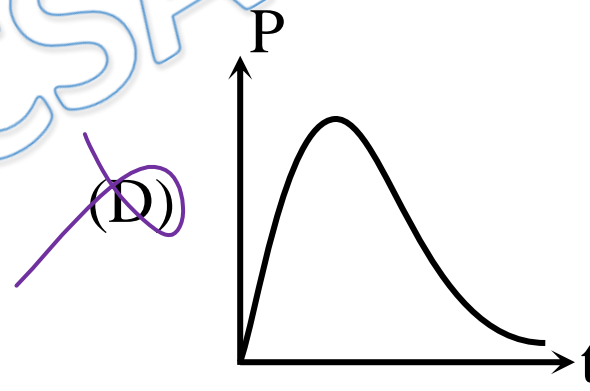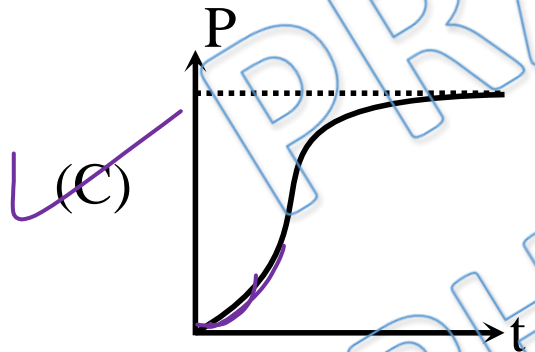
$$\begin{aligned} \text{Slope} = \frac{dP}{dt} &= \frac{\mathcal{E}^2}{R} 2(1 - e^{-Rt/L}) \left( 0 + \frac{L}{R} e^{-Rt/L} \right) \\ &= \frac{2\mathcal{E}^2 L}{R^2} (1 - e^{-Rt/L}) e^{-Rt/L} \\ &= \frac{2\mathcal{E}^2 L}{R^2} (e^{-Rt/L} - e^{-2Rt/L}) \end{aligned}$$



at  $t=0$ , Slope = 0  
at  $t \rightarrow \infty$ , ' ' = 0

Slope first  $\uparrow$  then  $\downarrow$

Q.9) What is the magnitude of current flowing when the rate of increase of magnetic energy in the inductor is maximum –

Power of inductor  $P = V_L = \mathcal{E} e^{-Rt/L} - \frac{\mathcal{E}}{R} (1 - e^{-Rt/L})$

$$P = \frac{\mathcal{E}^2}{R} (e^{-Rt/L} - e^{-2Rt/L})$$

for  $P = P_{\max}$ ,  $\frac{dP}{dt} = 0 \Rightarrow \frac{\mathcal{E}^2}{R} \left[ -\frac{R}{L} e^{-Rt/L} + \frac{2R}{L} e^{-2Rt/L} \right] = 0$

(a)  $I = V/R$

(b)  $I = V/2R$

(c)  $I = V/4R$

(d)  $I = (V/R) \ln 2$



$$\Rightarrow 2 e^{-2Rt/L} = e^{-Rt/L}$$

$$\Rightarrow e^{Rt/L} = 2 \Rightarrow e^{-Rt/L} = \frac{1}{2}$$

$$I = \frac{\mathcal{E}}{R} (1 - e^{-Rt/L})$$

$$= \frac{\mathcal{E}}{2R}$$

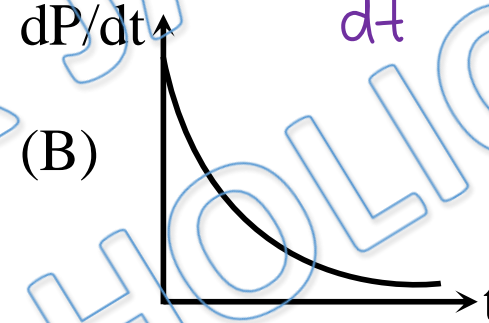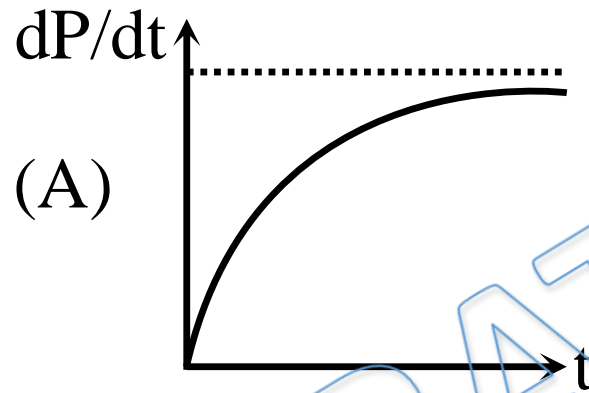Q.10) Which of the following graph best represent rate of change of power dissipated in resistor as a function of time -





$$\frac{dP}{dt} = \text{Slope of } P-t \text{ curve}$$

$$= \frac{2\varepsilon^2 L}{R^2} \left( e^{-\frac{Rt}{L}} - 2e^{-\frac{2Rt}{L}} \right)$$

$$= \frac{2\varepsilon^2 L}{R} \left( 1 - e^{-\frac{Rt}{L}} \right) e^{-\frac{Rt}{L}}$$

$$\text{at } t=0, \frac{dP}{dt} = 0$$
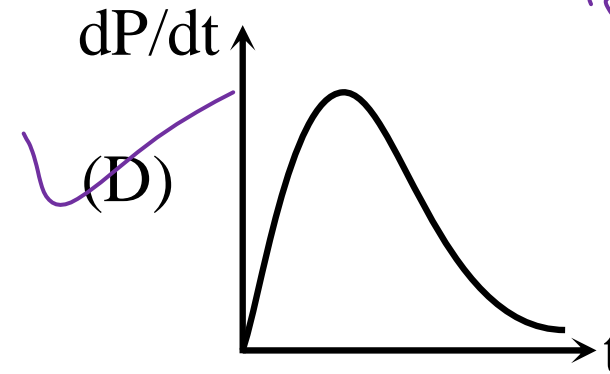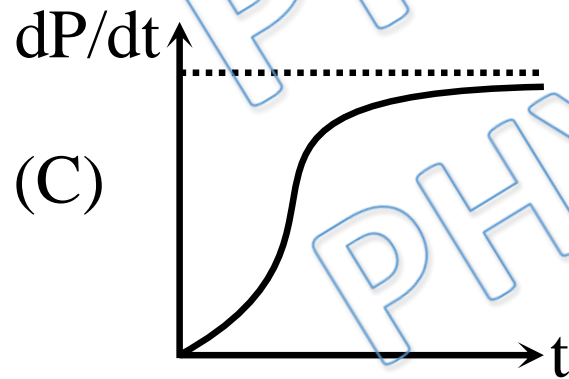
$$\text{at } t \rightarrow \infty, \frac{dP}{dt} = 0$$




Q.11) After the key k is closed, galvanometer in the shown arrangement shows zero deflection at all the times if ( $R_1$ , and  $R_2$  are resistances of inductors  $L_1$  and  $L_2$ )


- (a)  $\frac{R_1}{R_2} = \frac{R_3}{R_4} = \frac{L_1}{L_2}$
- (b)  $\frac{R_2}{R_1} = \frac{R_3}{R_4} = \frac{L_1}{L_2}$
- (c)  $\frac{L_1}{L_2} = \frac{R_1}{R_2}$
- (d)  $\frac{L_1}{L_2} = \frac{R_3}{R_4}$

$$\underline{V_A = V_B}$$

$$L_1 \frac{di_1}{dt} + i_1 R_1 = L_2 \frac{di_2}{dt} + i_2 R_2$$

$$L_1 R_3 = i_2 R_4$$

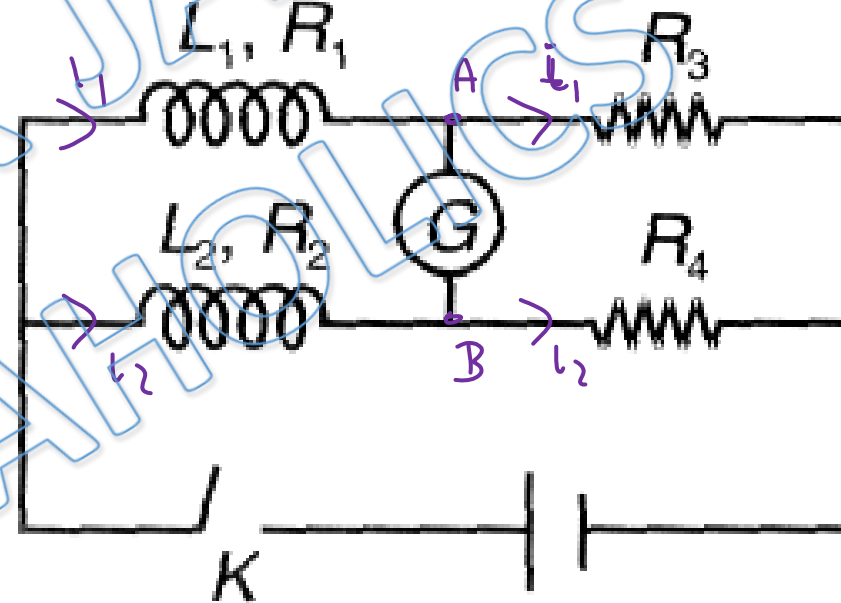

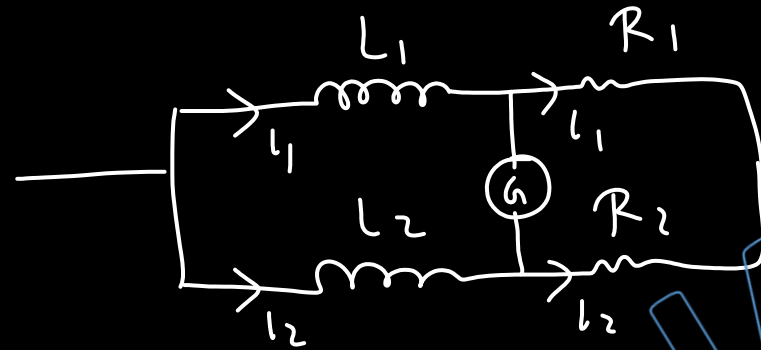


$$L_1 i_1 = L_2 i_2$$

$$\frac{i_1}{i_2} = \frac{L_2}{L_1}$$

$$i_1 R_1 = i_2 R_2$$

$$\frac{i_1}{i_2} = \frac{R_2}{R_1}$$

$$\frac{L_1}{L_2} = \frac{R_1}{R_2}$$

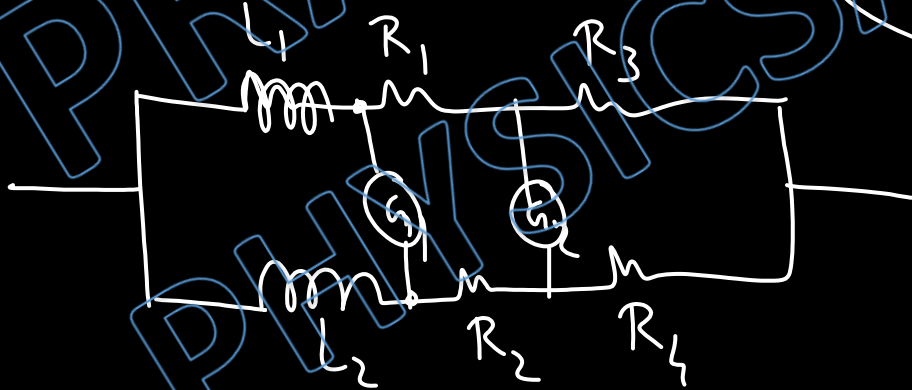


$$\frac{L_1}{L_2} = \frac{R_1}{R_2} = \frac{R_3}{R_4}$$

$$G_1 = G_2 = 0$$

Ans. a


Q.12) The ratio of time constants during current growth and current decay of the circuit shown in figure is:

for  $\tau$  of charging  $\rightarrow$

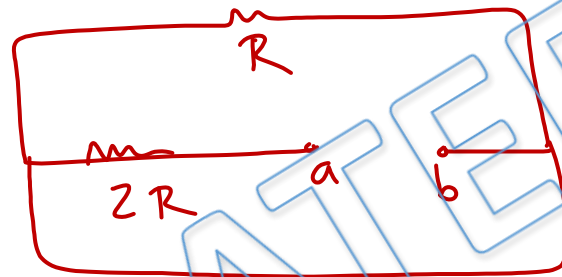

$$R_{\text{eff}} = 2R$$

$$\tau_1 = \frac{L}{2R}$$

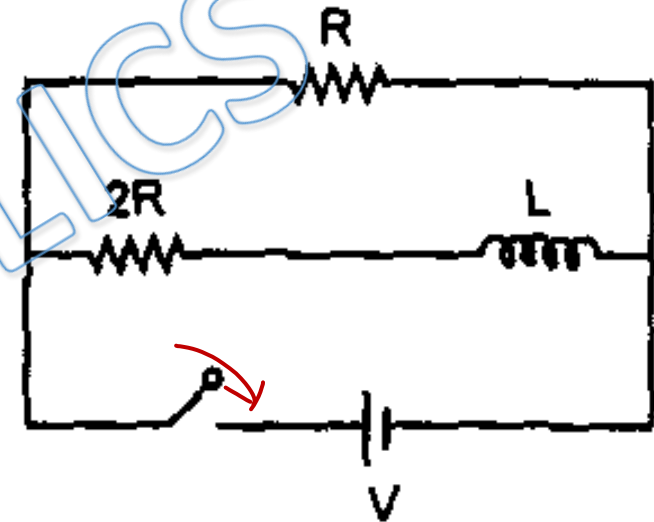

(a) 1 : 1

~~(b) 3 : 2~~

(c) 2 : 3

(d) 1 : 3

for  $\tau$  of discharging



$$R_{\text{eff}} = 3R$$

$$\tau_2 = \frac{L}{3R}$$

$$\frac{\tau_1}{\tau_2} = \frac{3}{2}$$

**For Video Solution of this DPP, Click on below link**

Video Solution  
on Website:-

<https://physicsaholics.com/home/courseDetails/104>

Video Solution  
on YouTube:-

<https://youtu.be/xAhvcTRPmxg>

Written Solution  
on Website:-

<https://physicsaholics.com/note/notesDetails/65>



[@Physicsaholics](#)

[@Physicsaholics\\_prateek](#)

[@NEET\\_Physics](#)  
[@IITJEE\\_Physics](#)

[physicsaholics.com](#)

[Unacademy](#)



**CLICK**

Chalo Niklo